


## Symmetrical system components

Decomposition of unsymmetrical (unbalanced) voltage:

$$\hat{U}_A = \hat{U}_{A1} + \hat{U}_{A2} + \hat{U}_{A0}$$

$$\hat{U}_B = \hat{U}_{B1} + \hat{U}_{B2} + \hat{U}_{B0}$$
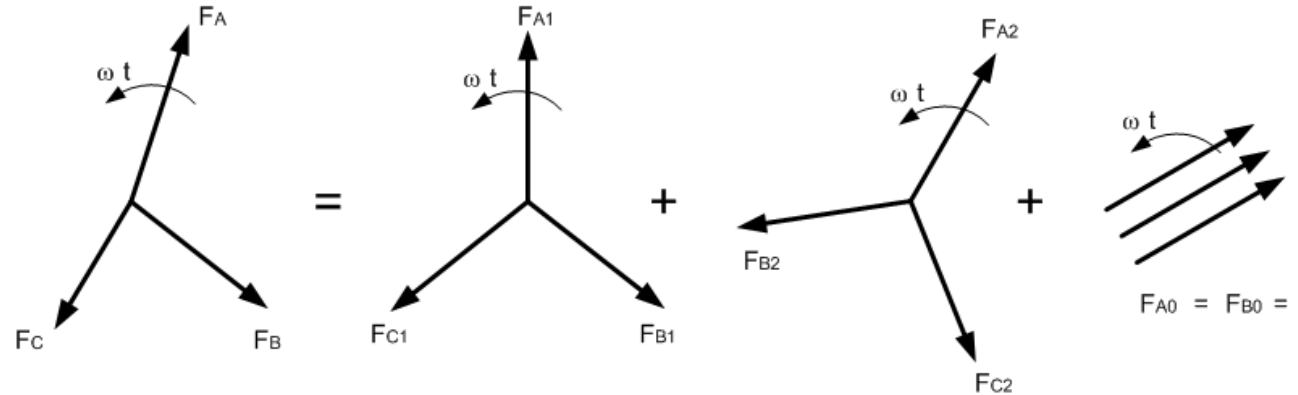
$$\hat{U}_C = \hat{U}_{C1} + \hat{U}_{C2} + \hat{U}_{C0}$$



Positive sequence (1), negative (2) and zero (0) sequence.

Hence (reference phase A)

$$\hat{U}_A = \hat{U}_1 + \hat{U}_2 + \hat{U}_0$$

$$\hat{U}_B = \hat{a}^2 \hat{U}_1 + \hat{a} \hat{U}_2 + \hat{U}_0$$

$$\hat{U}_C = \hat{a} \hat{U}_1 + \hat{a}^2 \hat{U}_2 + \hat{U}_0$$

$$\hat{I}_A = \hat{I}_1 + \hat{I}_2 + \hat{I}_0$$

$$\hat{I}_B = \hat{a}^2 \hat{I}_1 + \hat{a} \hat{I}_2 + \hat{I}_0$$

$$\hat{I}_C = \hat{a} \hat{I}_1 + \hat{a}^2 \hat{I}_2 + \hat{I}_0$$

where  $\hat{a} = -\frac{1}{2} + j\frac{\sqrt{3}}{2} = e^{j\frac{2\pi}{3}}$

$$\hat{a}^2 = -\frac{1}{2} - j\frac{\sqrt{3}}{2} = e^{j\frac{4\pi}{3}}$$

## Matrix

$$\begin{pmatrix} \mathbf{U}_{ABC} \end{pmatrix} = \begin{pmatrix} \hat{\mathbf{U}}_A \\ \hat{\mathbf{U}}_B \\ \hat{\mathbf{U}}_C \end{pmatrix} = \begin{pmatrix} 1 & 1 & 1 \\ \hat{a}^2 & \hat{a} & 1 \\ \hat{a} & \hat{a}^2 & 1 \end{pmatrix} \begin{pmatrix} \hat{\mathbf{U}}_1 \\ \hat{\mathbf{U}}_2 \\ \hat{\mathbf{U}}_0 \end{pmatrix} = (\mathbf{T})(\mathbf{U}_{120})$$

---

## Inversely

$$\begin{pmatrix} \mathbf{U}_{120} \end{pmatrix} = \begin{pmatrix} \hat{\mathbf{U}}_1 \\ \hat{\mathbf{U}}_2 \\ \hat{\mathbf{U}}_0 \end{pmatrix} = \frac{1}{3} \begin{pmatrix} 1 & \hat{a} & \hat{a}^2 \\ 1 & \hat{a}^2 & \hat{a} \\ 1 & 1 & 1 \end{pmatrix} \begin{pmatrix} \hat{\mathbf{U}}_A \\ \hat{\mathbf{U}}_B \\ \hat{\mathbf{U}}_C \end{pmatrix} = (\mathbf{T}^{-1})(\mathbf{U}_{ABC})$$

## 3ph power

$$\hat{S} = \hat{U}_A \hat{I}_A^* + \hat{U}_B \hat{I}_B^* + \hat{U}_C \hat{I}_C^* = \begin{pmatrix} \hat{U}_A & \hat{U}_B & \hat{U}_C \end{pmatrix} \begin{pmatrix} \hat{I}_A \\ \hat{I}_B \\ \hat{I}_C \end{pmatrix}^* = (\mathbf{U}_{ABC})^T (\mathbf{I}_{ABC})^*$$

$$\hat{S} = [(\mathbf{T})(\mathbf{U}_{120})]^T [(\mathbf{T})(\mathbf{I}_{120})]^* = (\mathbf{U}_{120})^T (\mathbf{T})^T (\mathbf{T})^* (\mathbf{I}_{120})^*$$


$$(\mathbf{T})^T (\mathbf{T})^* = \begin{pmatrix} 1 & \hat{a}^2 & \hat{a} \\ 1 & \hat{a} & \hat{a}^2 \\ 1 & 1 & 1 \end{pmatrix} \begin{pmatrix} 1 & 1 & 1 \\ \hat{a} & \hat{a}^2 & 1 \\ \hat{a}^2 & \hat{a} & 1 \end{pmatrix} = \begin{pmatrix} 3 & 0 & 0 \\ 0 & 3 & 0 \\ 0 & 0 & 3 \end{pmatrix} = 3(\mathbf{E})$$

$$\hat{S} = 3(\mathbf{U}_{120})^T (\mathbf{I}_{120})^*$$

$$\hat{S} = \underline{3(\hat{U}_1 \hat{I}_1^* + \hat{U}_2 \hat{I}_2^* + \hat{U}_0 \hat{I}_0^*)}$$
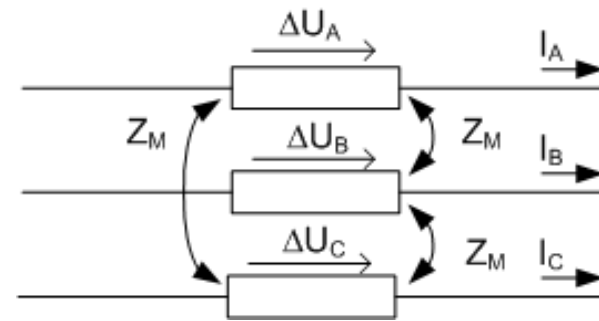
## Series symmetrical segments in ES

$$\begin{pmatrix} \Delta \hat{U}_A \\ \Delta \hat{U}_B \\ \Delta \hat{U}_C \end{pmatrix} = \begin{pmatrix} \hat{Z} & \hat{Z}' & \hat{Z}' \\ \hat{Z}' & \hat{Z} & \hat{Z}' \\ \hat{Z}' & \hat{Z}' & \hat{Z} \end{pmatrix} \begin{pmatrix} \hat{I}_A \\ \hat{I}_B \\ \hat{I}_C \end{pmatrix}$$



$$(\Delta U_{ABC}) = (Z_{ABC})(I_{ABC})$$

$$(T)(\Delta U_{120}) = (Z_{ABC})(T)(I_{120})$$

$$(\Delta U_{120}) = (T)^{-1}(Z_{ABC})(T)(I_{120}) = (Z_{120})(I_{120})$$

$$(Z_{120}) = (T)^{-1}(Z_{ABC})(T)$$

$$(Z_{120}) = \begin{pmatrix} \hat{Z}_1 & 0 & 0 \\ 0 & \hat{Z}_2 & 0 \\ 0 & 0 & \hat{Z}_0 \end{pmatrix} = \begin{pmatrix} \hat{Z} - \hat{Z}' & 0 & 0 \\ 0 & \hat{Z} - \hat{Z}' & 0 \\ 0 & 0 & \hat{Z} + 2\hat{Z}' \end{pmatrix}$$

## Multiple lines

$$\begin{pmatrix} (\Delta U_{V1}) \\ (\Delta U_{V2}) \\ \dots \end{pmatrix}_{ABC} = (Z_{ABC}) \begin{pmatrix} (I_{V1}) \\ (I_{V2}) \\ \dots \end{pmatrix}_{ABC}$$

$$\begin{pmatrix} (T) & 0 & 0 \\ 0 & (T) & 0 \\ 0 & 0 & \dots \end{pmatrix} \begin{pmatrix} (\Delta U_{V1}) \\ (\Delta U_{V2}) \\ \dots \end{pmatrix}_{120} = (Z_{ABC}) \begin{pmatrix} (T) & 0 & 0 \\ 0 & (T) & 0 \\ 0 & 0 & \dots \end{pmatrix} \begin{pmatrix} (I_{V1}) \\ (I_{V2}) \\ \dots \end{pmatrix}_{120}$$

$$\begin{pmatrix} (\Delta U_{V1}) \\ (\Delta U_{V2}) \\ \dots \end{pmatrix}_{120} = \begin{pmatrix} (T) & 0 & 0 \\ 0 & (T) & 0 \\ 0 & 0 & \dots \end{pmatrix}^{-1} (Z_{ABC}) \begin{pmatrix} (T) & 0 & 0 \\ 0 & (T) & 0 \\ 0 & 0 & \dots \end{pmatrix} \begin{pmatrix} (I_{V1}) \\ (I_{V2}) \\ \dots \end{pmatrix}_{120}$$

$$\begin{pmatrix} (\Delta U_{V1}) \\ (\Delta U_{V2}) \\ \dots \end{pmatrix}_{120} = \begin{pmatrix} (T)^{-1} & 0 & 0 \\ 0 & (T)^{-1} & 0 \\ 0 & 0 & \dots \end{pmatrix} (Z_{ABC}) \begin{pmatrix} (T) & 0 & 0 \\ 0 & (T) & 0 \\ 0 & 0 & \dots \end{pmatrix} \begin{pmatrix} (I_{V1}) \\ (I_{V2}) \\ \dots \end{pmatrix}_{120}$$

## Shunt symmetrical segments in ES


$$(\mathbf{U}_{ABC}) = (\mathbf{Z}_{ABC})(\mathbf{I}_{ABC}) + (\mathbf{Z}_N)(\mathbf{I}_{ABC})$$

$$(\mathbf{Z}_N) = \begin{pmatrix} \hat{Z}_N & \hat{Z}_N & \hat{Z}_N \\ \hat{Z}_N & \hat{Z}_N & \hat{Z}_N \\ \hat{Z}_N & \hat{Z}_N & \hat{Z}_N \end{pmatrix}$$

$$(\mathbf{U}_{120}) = (\mathbf{T})^{-1}(\mathbf{Z}_{ABC})(\mathbf{T})(\mathbf{I}_{120}) + (\mathbf{T})^{-1}(\mathbf{Z}_N)(\mathbf{T})(\mathbf{I}_{120})$$

$$(\mathbf{Z}_{120}) = (\mathbf{T})^{-1}[(\mathbf{Z}_{ABC}) + (\mathbf{Z}_N)](\mathbf{T})$$
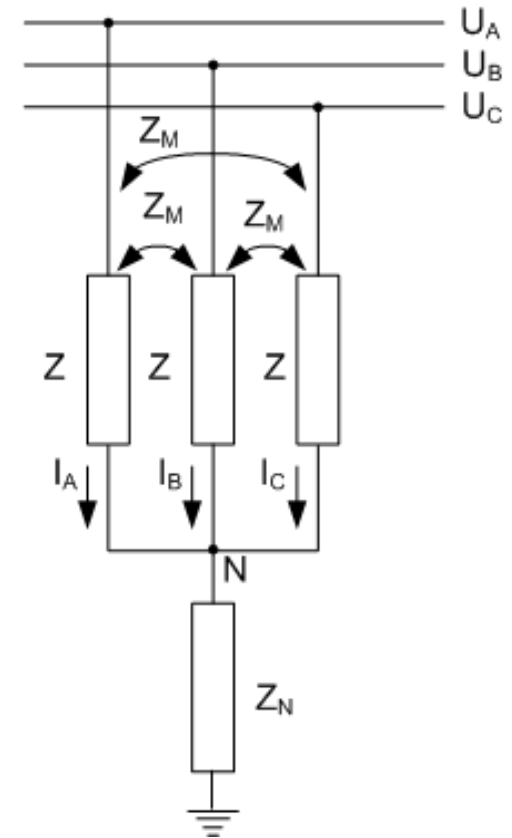
$$(\mathbf{Z}_{120}) = \begin{pmatrix} \hat{Z} - \hat{Z}' & 0 & 0 \\ 0 & \hat{Z} - \hat{Z}' & 0 \\ 0 & 0 & \hat{Z} + 2\hat{Z}' + 3Z_N \end{pmatrix}$$



Symmetrical components voltages in the symmetrical segments depend only on the corresponding component current and component impedance.

## Inductors and capacitors in ES

### a) Series inductors


- reactors are used to limit short-circuit currents
- used in grids up to 35 kV, single-phase ( $I_n > 200\text{A}$ ) or three-phase ( $I_n < 200\text{A}$ ), usually air-cooled (small L)
- the same design in LC filters for harmonics suppression







$$R_{tl} \ll X_{tl}$$

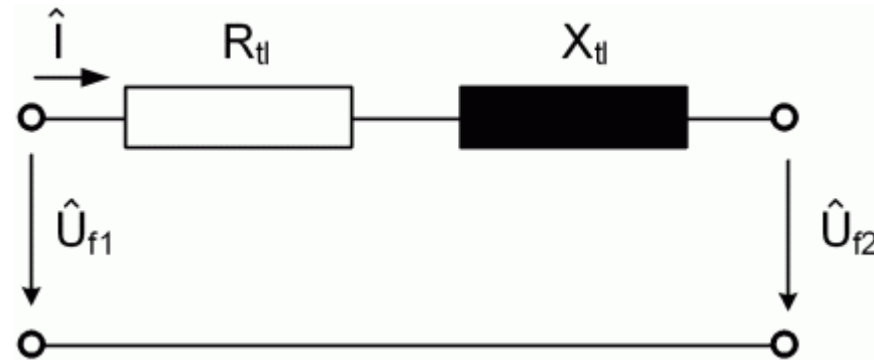

Input:  $X_{tl\%}$ ,  $S_{tl}$ ,  $U_n$ ,  $I_n$

Calculation:  $S_{tl} = \sqrt{3} \cdot U_n \cdot I_n$

$$X_{tl} = \frac{X_{t\%} \cdot U_n}{100 \cdot \sqrt{3} \cdot I_n} = \frac{X_{t\%} \cdot U_n^2}{100 \cdot S_{tl}}$$

$$\Delta \hat{U}_f = \hat{U}_{f1} - \hat{U}_{f2} = (R_t + jX_t) \hat{I} = \hat{Z}_t \hat{I}$$

$$\begin{bmatrix} \hat{Z}_{tabc} \end{bmatrix} = \begin{bmatrix} \hat{Z}_{t012} \end{bmatrix} = \hat{Z}_t \cdot [E] \text{ - 3ph inductor}$$

→ self-impedance  $\hat{Z}_t$ , mutual impedances 0

In fault-free state the inductor can be bypassed by a fuse to reduce a voltage drop.

## b) Shunt (parallel) inductors

- in the systems  $U_N > 220$  kV, oil cooling, Fe core
- used to compensate capacitive (charging) currents of overhead lines for no-load or small loads  $\rightarrow$  U control:

$$X_{tl} = \frac{U_{tl n}}{\sqrt{3} \cdot I_{tl n}} = \frac{U_{tl n}^2}{Q_{tl n}}$$

$$\hat{Z}_{tl} = \hat{Z}_{tl1} = \hat{Z}_{t2}, Z_{tl0} \rightarrow \infty$$



Connection in the system:

### a) galvanic connection to the line

- Y winding, neutral point connected to the ground through V only during auto-reclosing (disturbances)
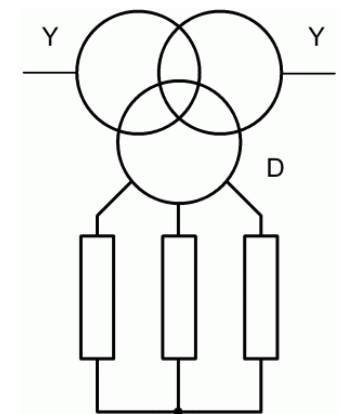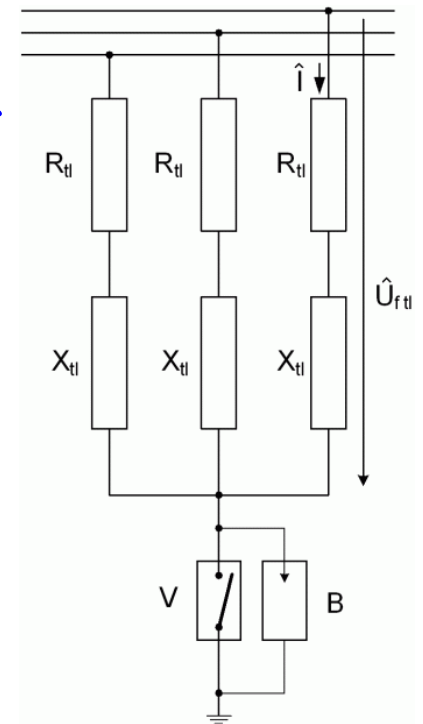
### b) inductor connection to transformer tertiary winding

- lower voltage  $U_n \approx 10 \div 35$  kV
- problem with switch-off (purely inductive load)




# Kočín 400 kV


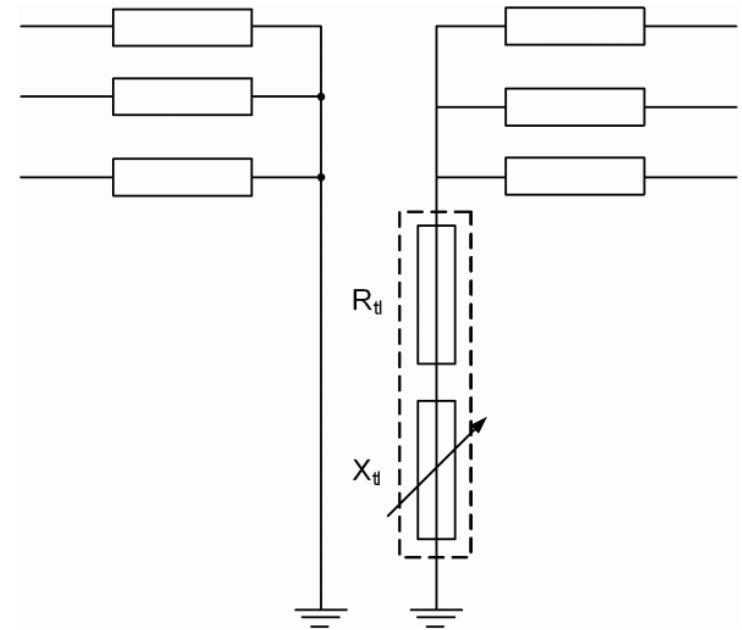
### c) Neutral point inductors

- used in networks with indirectly earthed neutral point to compensate currents during ground fault
- value of the fault current does not depend on the ground fault position and the current is capacitive
- inductor reactance  $X_{tl}$  should assure that the value of the inductive current is equal to the value of capacitive current  $\rightarrow$  arc extinction
- for voltage 6 to 35 kV (rated at  $U_{fn}$ ), reactor is single-phased!, oil cooling
- capacitive current change (network reconfiguration)  $\rightarrow$  change in inductance (air gap correction in the magnetic circuit)  
= arc-suppression coil (Peterson coil)
- it doesn't occur in positive and negative sequence component,  $X_0 = 3X_{tl}$




## 6 MVar, 13 kV, Sokolnice



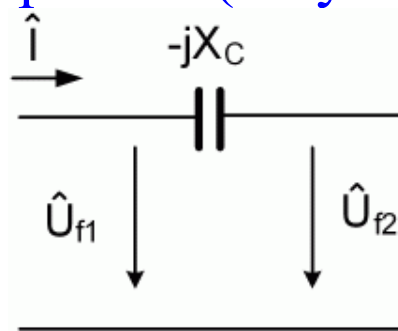
## d) Series capacitors

- capacitors in ES = capacitor banks = series and parallel connection
- to improve voltage conditions (MV lines) or adjusting parameters (long HV lines)
- voltage and power of the capacitor varies with the load
- during short-circuits and overcurrents there appears overvoltage on the capacitor (very fast protections are used)


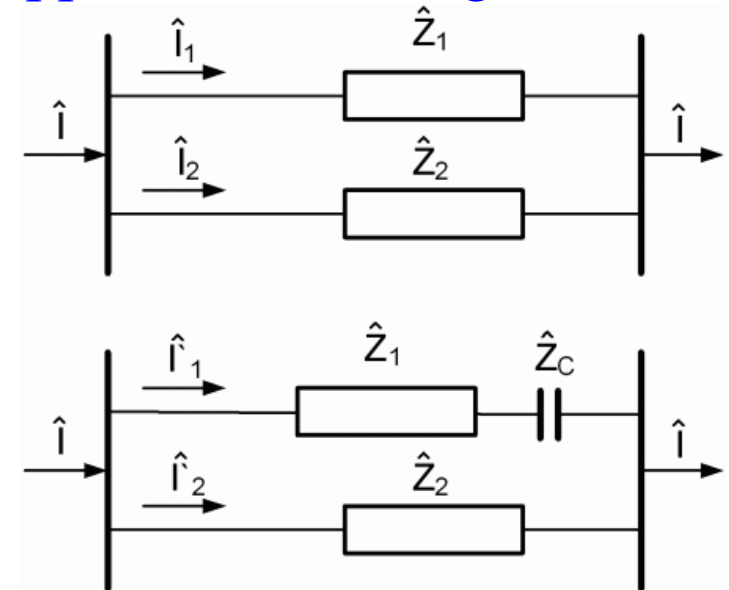
$$\hat{U}_C = -j \frac{1}{\omega C} \hat{I}$$




- C must be insulated against the ground (insulated platforms) – C under voltage
- drawback – allows harmonic currents flow
- current distribution among parallel transmission lines could be achieved

## Canada 750 kV


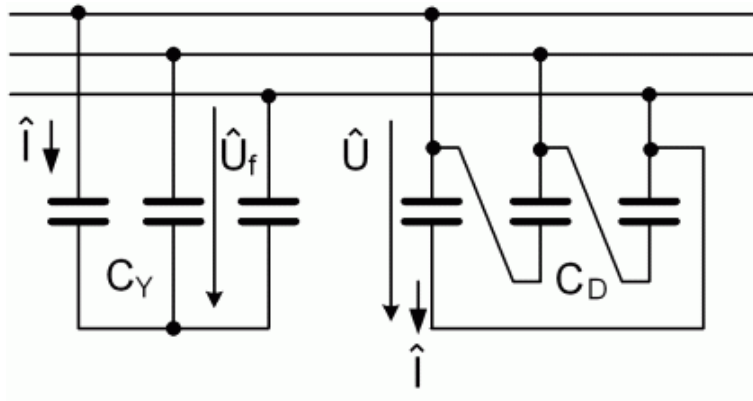
## e) Shunt capacitors


- used in industrial networks up to 1 kV
- connection:
  - a) wye - Y
  - b) delta -  $\Delta$  (D)



$$Q_f = U_f \cdot I_C = U_f^2 \omega C_Y \quad Q_f = U \cdot I_C = U^2 \omega C_\Delta$$
$$Q = 3U_f^2 \omega C_Y = U^2 \omega C_Y \quad Q = 3U^2 \omega C_\Delta$$

- with the same reactive power
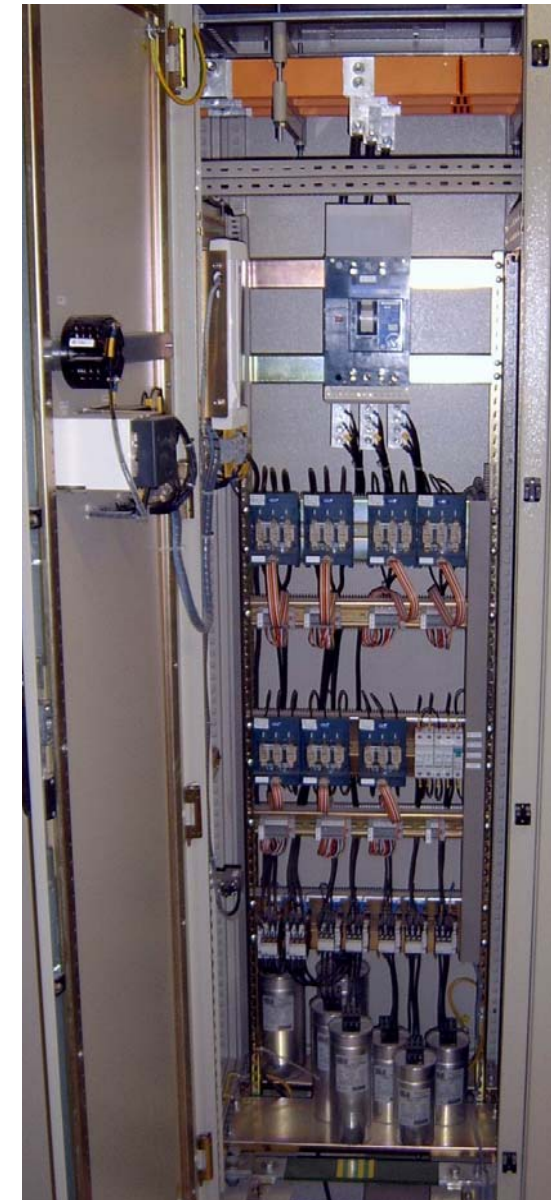
$$U^2 \omega C_Y = 3U^2 \omega C_\Delta \rightarrow C_Y = 3C_\Delta \rightarrow \text{rather delta}$$






- reactive power compensation
  - a)  $Q_C < Q$  under-compensated
  - b)  $Q_C = Q$  exact compensation
  - c)  $Q_C > Q$  over-compensated

→ power factor improvement, lower power losses, voltage drops


- individual or group compensation could be used

## Transformer parameters



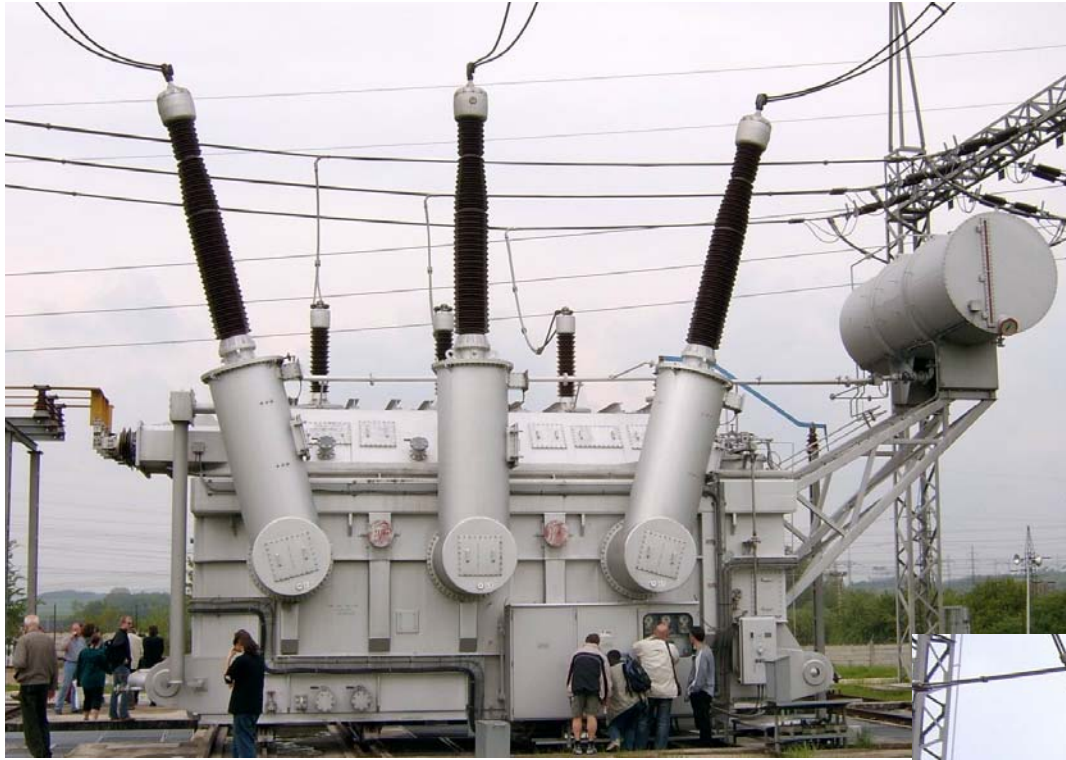

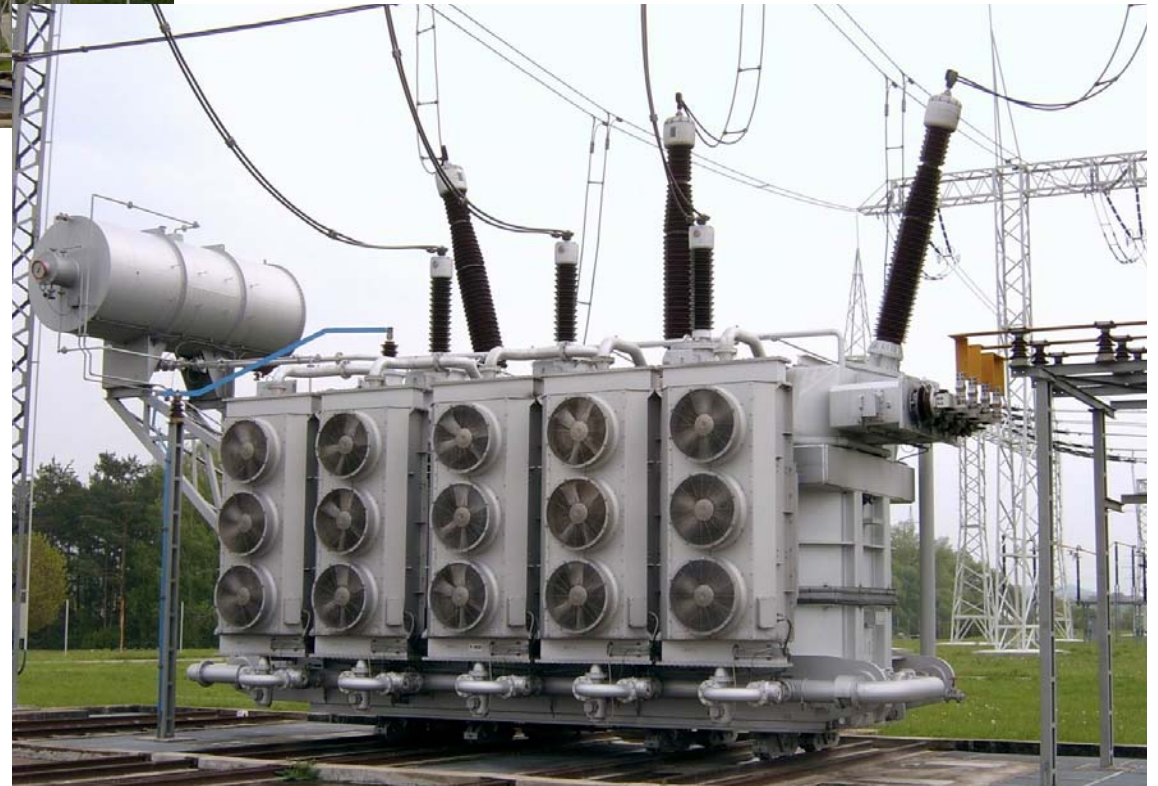350 MVA, 400/110 kV  
YNauto - d1, Sokolnice



## a) Two-winding transformers

- winding connection Y, Yn, D, Z, Zn, V

Yzn – distribution TRF MV/LV up to 250 kVA, for unbalanced load

Dyn – distribution TRF MV/LV from 400 kVA


Yd – block TRF in power plants, the 3<sup>rd</sup> harmonic suppression

Yna-d, YNynd – power grid transformer (400, 220, 110 kV)

YNyd – power grid transformer (e.g. 110/23/6,3 kV)

- equivalent circuit: T – network
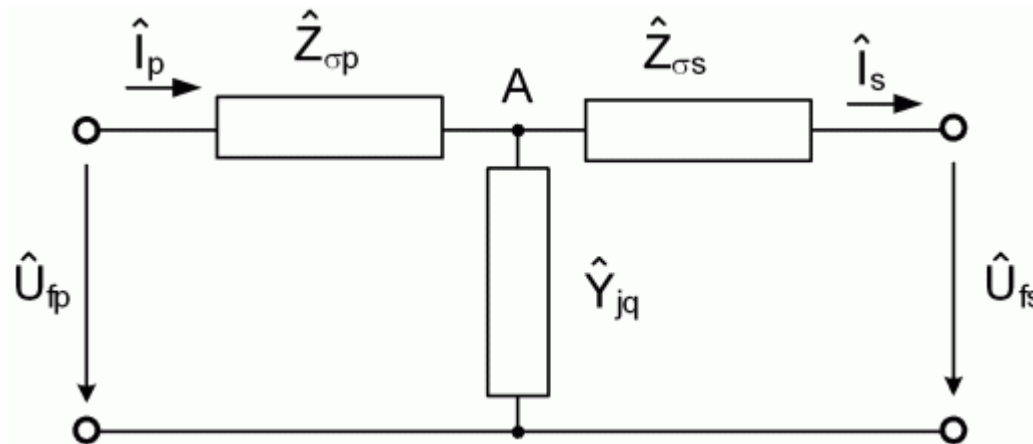
$$\hat{Z}_{\sigma p} = R_p + jX_{\sigma p} \quad \hat{Z}_{\sigma s} = R_s + jX_{\sigma s} \quad \hat{Y}_{jq} = G_q - jB_q$$



- each phase can be considered separately (unbalance is neglected), i.e. operational impedance (positive sequence) is used
- values of the parameters are calculated, then verified by no-load and short-circuit tests
  - *no-load test* – secondary winding open, primary w. supplied by rated voltage, no-load current flows (lower than rated one)
  - *short-circuit test* – secondary winding short-circuit, primary w. supplied by short-circuit voltage (lower than rated one) so that rated current flows

$\Delta P_0$  (W),  $i_0$  (%),  $\Delta P_k$  (W),  $z_k = u_k$  (%),  $S_n$  (VA),  $U_n$  (V)

$u_k \approx 4 \div 14$  % (increases with TRF power)

$p_k \approx 0,1 \div 1$  % (decreases with TRF power)

$p_0 \approx 0,01 \div 0,1$  % (decreases with TRF power)

- shunt branch:

$$g_q = \frac{\Delta P_0}{S_n} \quad y_q = \frac{i_{0\%}}{100} \quad b_q = \sqrt{y_q^2 - g_q^2}$$

$$\hat{y}_q = \frac{\Delta P_0}{S_n} - j \sqrt{\left(\frac{i_{0\%}}{100}\right)^2 - \left(\frac{\Delta P_0}{S_n}\right)^2} = g_q - j \cdot b_q$$

$$\hat{Y}_q = \hat{y}_q \frac{S_n}{U_n^2} = \frac{S_n}{U_n^2} \left[ \frac{\Delta P_0}{S_n} - j \sqrt{\left(\frac{i_{0\%}}{100}\right)^2 - \left(\frac{\Delta P_0}{S_n}\right)^2} \right] = G_q - j \cdot B_q$$

- series branch:

$$r_k = \frac{\Delta P_k}{S_n} \quad z_k = \frac{u_{k\%}}{100} \quad x_k = \sqrt{z_k^2 - r_k^2}$$

$$\hat{z}_k = \frac{\Delta P_k}{S_n} + j \sqrt{\left(\frac{u_{k\%}}{100}\right)^2 - \left(\frac{\Delta P_k}{S_n}\right)^2} = r_k + j \cdot x_k$$


$$\hat{Z}_k = \hat{z}_k \frac{U_n^2}{S_n} = \frac{U_n^2}{S_n} \left[ \frac{\Delta P_k}{S_n} + j \sqrt{\left(\frac{u_{k\%}}{100}\right)^2 - \left(\frac{\Delta P_k}{S_n}\right)^2} \right] = R_k + j \cdot X_k$$

$$\hat{Z}_{\sigma ps} = \hat{Z}_k = (R_p + R_s) + j(X_{\sigma p} + X_{\sigma s})$$

- we choose  $\hat{Z}_{\sigma p} = 0,5 \hat{Z}_{\sigma ps} = \hat{Z}_{\sigma s}$

- this division is not physically correct (different leakage flows, different resistances)

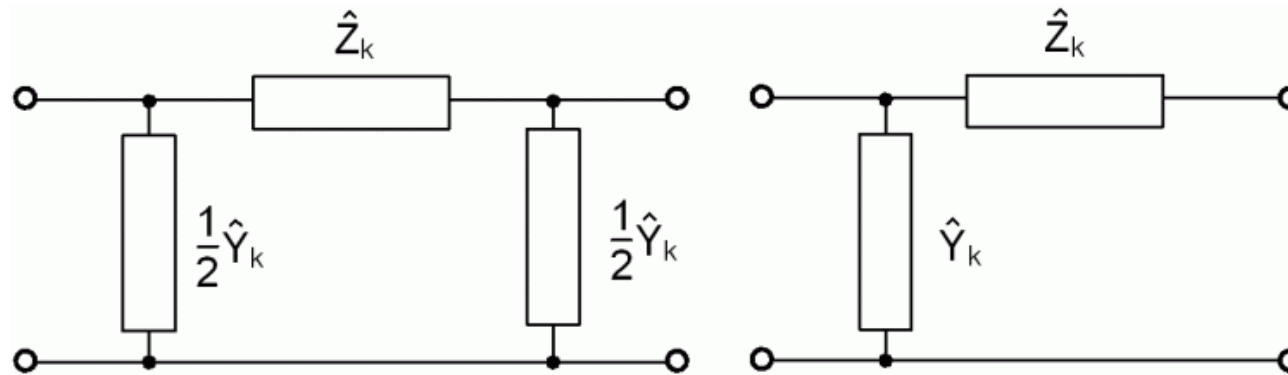- usage of T-network to calculate meshed systems is not appropriate sometimes (it adds another node)
- therefore calculation using  $\pi$ -network,  $\Gamma$ -network






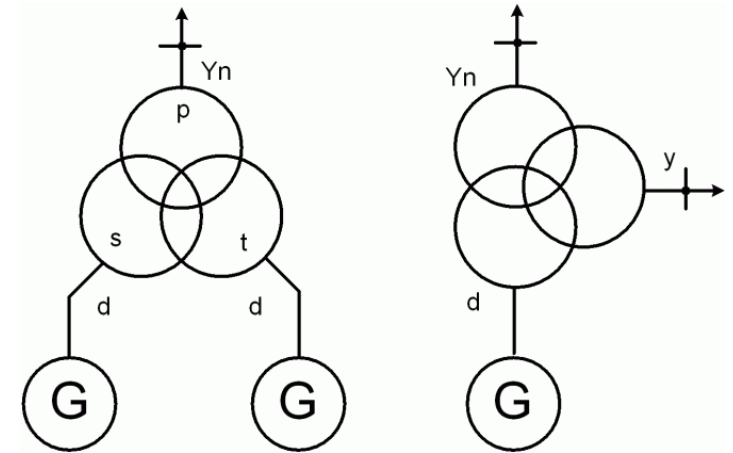
## b) Three-winding transformers

- parameters are calculated, then verified by no-load and short-circuit measurements (3 short-circuit tests: 1 winding no-load, 1 short-circuit and 1 supplied):

$\Delta P_0$  (W),  $i_0$  (%),  $\Delta P_k$  (W),  $z_K = u_K$  (%),  
 $S_n$  (VA),  $U_n$  (V)



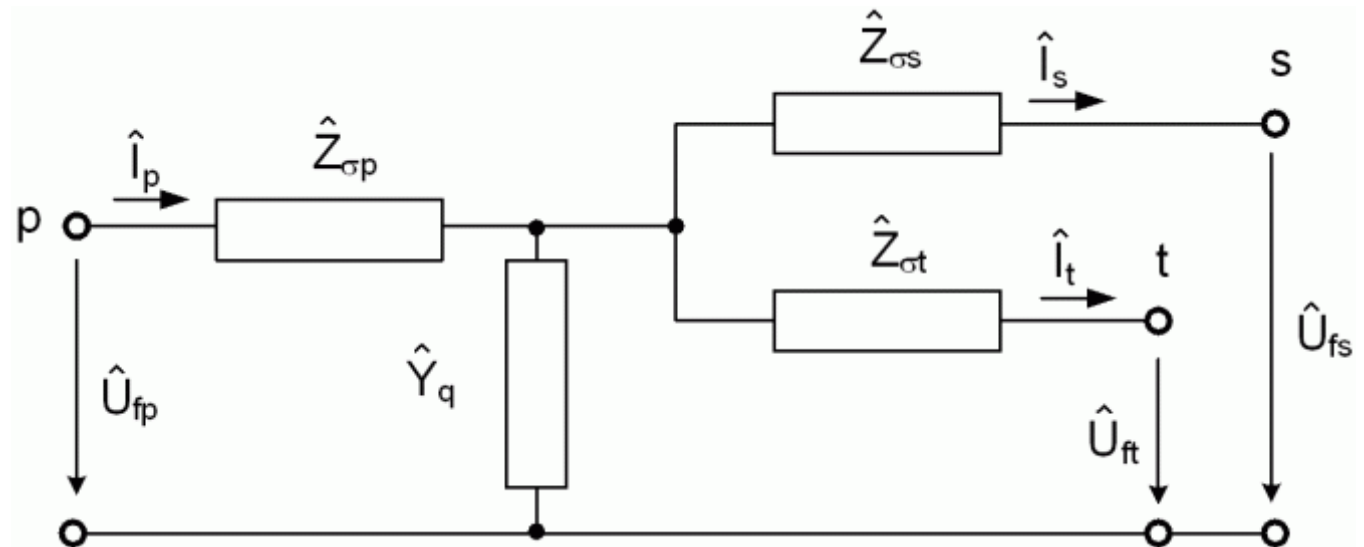- powers needn't be the same: e.g.  $S_{Sn} = S_{Tn} = 0,5 \cdot S_{Pn}$
- equivalent circuit:



- no-load measurement:

related to the primary rated power and rated voltage  $S_{Pn}$  a  $U_{PN}$  (supplied)

$$\hat{y}_q = g_q - j \cdot b_q = \frac{\Delta P_0}{S_{Pn}} - j \sqrt{\left(\frac{i_{0\%}}{100}\right)^2 - \left(\frac{\Delta P_0}{S_{Pn}}\right)^2}$$

denominated value (S) – related to  $U_{PN}$

$$\hat{Y}_q = \hat{y}_q \frac{S_{Pn}}{U_{Pn}^2} = G_q - j \cdot B_q = \frac{S_{Pn}}{U_{Pn}^2} \left[ \frac{\Delta P_0}{S_{Pn}} - j \sqrt{\left(\frac{i_{0\%}}{100}\right)^2 - \left(\frac{\Delta P_0}{S_{Pn}}\right)^2} \right]$$

- short-circuit measurement: (3x, supply – short-circuit – no-load)

provided:  $S_{Pn} \neq S_{Sn} \neq S_{Tn}$

measurement between	P - S	P - T	S - T
short-circuit losses (W)	$\Delta P_{kPS}$	$\Delta P_{kPT}$	$\Delta P_{kST}$
short-circuit voltage (%)	$u_{kPS}$	$u_{kPT}$	$u_{kST}$
measurement corresponds to power (VA)	$S_{Sn}$	$S_{Tn}$	$S_{Tn}$

short-circuit tests S – T:

parameter to be found:

$$\hat{Z}_{ST} = \hat{Z}_{\sigma S} + \hat{Z}_{\sigma T} \left( \hat{Z}_{\sigma S} = R_S + j \cdot X_{\sigma S} \right) - \text{recalculated to } U_{PN}$$

$$\hat{Z}_{ST} = \hat{Z}_{\sigma S} + \hat{Z}_{\sigma T} - \text{recalculated to } U_{PN}, S_{PN}$$

$$\Delta P_k \text{ for } I_{Tn} \rightarrow \Delta P_{kST} = 3 \cdot R_{ST}^+ \cdot I_{Tn}^2, \quad I_{Tn} = \frac{S_{Tn}}{\sqrt{3} \cdot U_{Tn}}$$

$R_{ST}^+$ ....resistance of secondary and tertiary windings (related to  $U_{Tn}$ )

$$R_{ST}^+ = \frac{\Delta P_{kST}}{S_{Tn}^2} \cdot U_{Tn}^2$$

$$R_{ST} = R_{ST}^+ \cdot \frac{U_{Pn}^2}{U_{Tn}^2} \rightarrow R_{ST} = R_S + R_T = \frac{\Delta P_{kST}}{S_{Tn}^2} \cdot U_{Pn}^2$$

$r_S$  ( $r_T$ )...resistance of sec. and ter. windings recalculated to primary

$$r_{ST} = R_{ST} \cdot \frac{S_{Pn}}{U_{Pn}^2} = \frac{\Delta P_{kST}}{S_{Tn}^2} \cdot S_{Pn}$$

- impedance:

$$Z_{ST} = \frac{u_{kST\%}}{100} \cdot \frac{S_{Pn}}{S_{Tn}}, \quad Z_{ST} = z_{ST} \cdot \frac{U_{Pn}^2}{S_{Pn}} = \frac{u_{kST\%}}{100} \cdot \frac{U_{Pn}^2}{S_{Tn}}$$

$$\hat{Z}_{ST} = r_{ST} + j \cdot X_{ST}, \quad X_{ST} = \sqrt{Z_{ST}^2 - r_{ST}^2}, \quad X_{ST} = X_{\sigma S} + X_{\sigma T}$$

- based on the derived relations we can write:

P - S:

$$\hat{Z}_{PS} = r_{PS} + j \cdot X_{PS} = \frac{\Delta P_{kPS}}{S_{Sn}^2} \cdot S_{Pn} + j \cdot \sqrt{\left( \frac{u_{kPS\%}}{100} \cdot \frac{S_{Pn}}{S_{Sn}} \right)^2 - \left( \frac{\Delta P_{kPS}}{S_{Sn}^2} \cdot S_{Pn} \right)^2}$$

$$\hat{Z}_{PS} = R_{PS} + j \cdot X_{PS} = \frac{\Delta P_{kPS}}{S_{Sn}^2} \cdot U_{Pn}^2 + j \cdot \sqrt{\left( \frac{u_{kPS\%}}{100} \cdot \frac{U_{Pn}^2}{S_{Sn}} \right)^2 - \left( \frac{\Delta P_{kPS}}{S_{Sn}^2} \cdot U_{Pn}^2 \right)^2}$$

- analogous for P – T and S – T

- leakage reactances for P, S, T:


$$\hat{Z}_{\sigma P} = R_P + j \cdot X_{\sigma P} = 0,5 \cdot (\hat{Z}_{PS} + \hat{Z}_{PT} - \hat{Z}_{ST})$$

$$\hat{Z}_{\sigma S} = R_S + j \cdot X_{\sigma S} = 0,5 \cdot (\hat{Z}_{PS} + \hat{Z}_{ST} - \hat{Z}_{PT})$$

$$\hat{Z}_{\sigma T} = R_T + j \cdot X_{\sigma T} = 0,5 \cdot (\hat{Z}_{PT} + \hat{Z}_{ST} - \hat{Z}_{PS})$$

- knowledge of the series impedances and shunt admittances allows to study voltage and power conditions of 3-winding transformers
- mentioned impedances are valid for positive and negative sequences

## Transformers zero sequence impedances

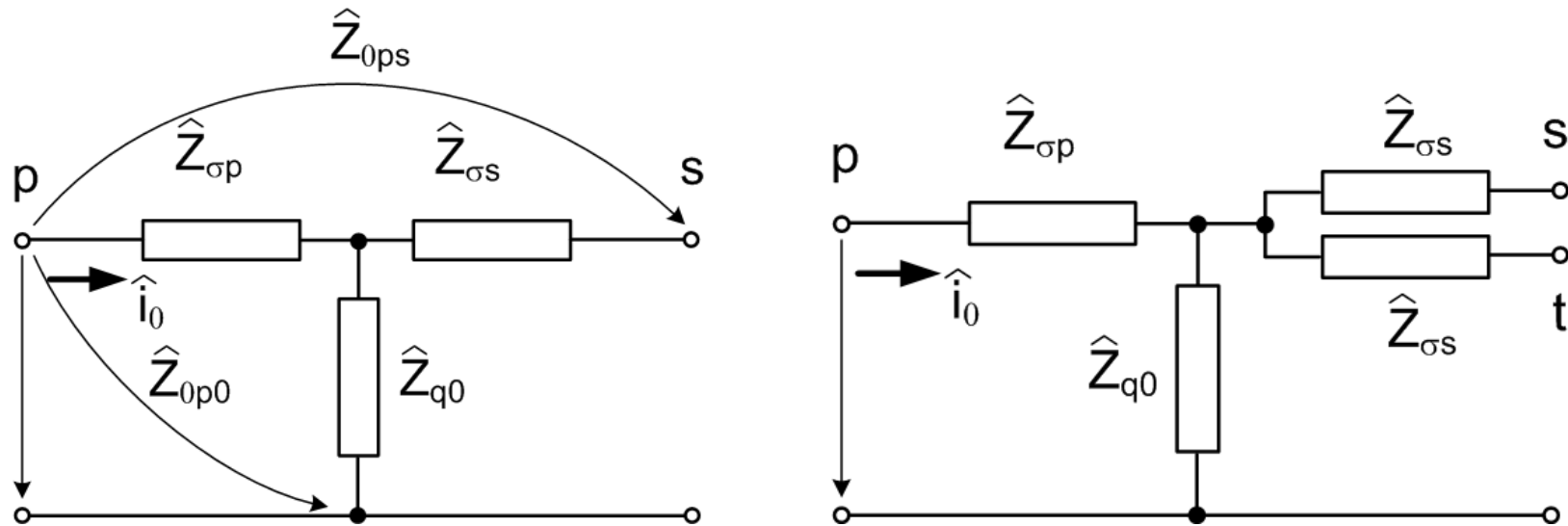

Series parameters are the same as for the positive sequence, the shunt always need to be determined.

Assumptions:

- Zero sequence voltage supplies the primary winding.
- The relative values are related to  $U_{Pn}$  and  $S_{Pn}$ .
- We distinguish free and tied magnetic flows (core x shell TRF).

$Z_0$  depends on the winding connection.

note: reluctance, inductance

magnetic resistance (reluctance)

$$R_m = \frac{1}{\mu} \frac{l}{S} \quad \text{analogy} \quad R_e = \frac{1}{\gamma} \frac{l}{S} = \rho \frac{l}{S}$$

magnetic flux (Hopkinson's law)

$$\Phi = \frac{N \cdot I}{R_m} \quad \text{analogy (Ohm's law)} \quad I = \frac{U}{R_e}$$

$$L = \frac{\Phi_c}{I} = \frac{N \cdot \Phi}{I} = \frac{N^2}{R_m}$$

$$\mu_{Fe} \gg \mu_0 \Rightarrow R_{mFe} \ll R_{m0} \Rightarrow L_{Fe} \gg L_{\sigma}$$

TRF magnetic circuit

$$\Phi = \Phi_h + \Phi_{\sigma} = \frac{N \cdot I}{R_{mFe}} + \frac{N \cdot I}{R_{m0}} = \frac{L_{Fe} \cdot I}{N} + \frac{L_{\sigma} \cdot I}{N} = \frac{I}{N} (L_{Fe} + L_{\sigma})$$



## a) Y / any connection

$$3i_0 = 0$$

$$Z_0 = \frac{u_0}{i_0} \rightarrow \infty$$

$$Z_{0p0} \rightarrow \infty$$

$$Z_{0ps} \rightarrow \infty$$

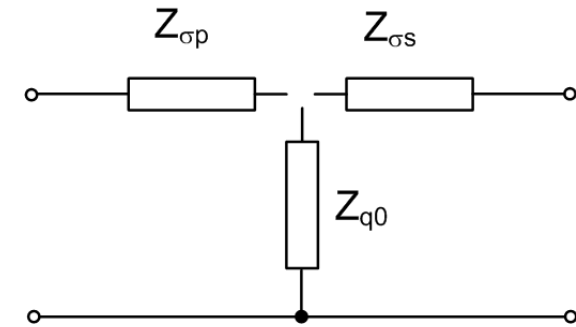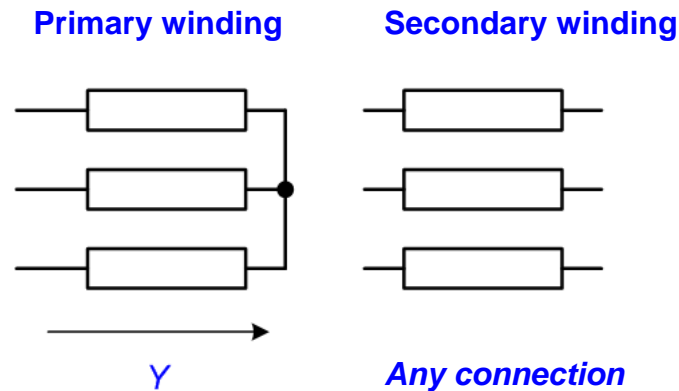

## b) D / any connection



Zero sequence voltage is attached to D  $\rightarrow$  voltage at each phase

$$u_0 - u_0 = 0 \rightarrow i_a = i_b = i_c = 0 \rightarrow i_0 = 0$$

$$Z_0 = \frac{u_0}{i_0} \rightarrow \infty$$

$$Z_{0p0} \rightarrow \infty$$

$$Z_{0ps} \rightarrow \infty$$

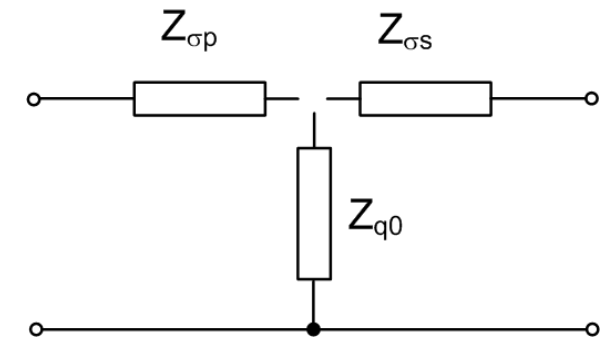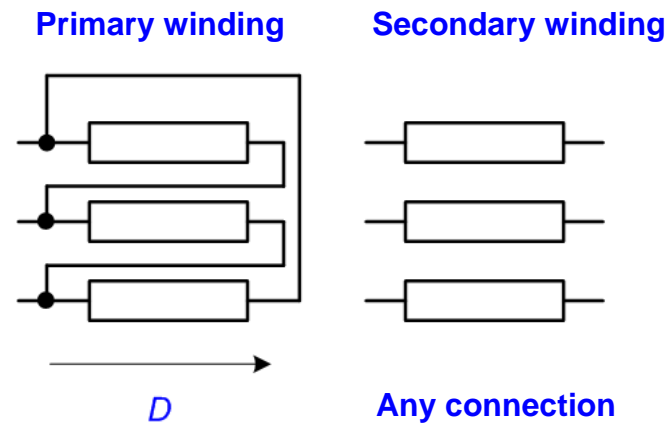



### c) **YN / D**

Currents in the primary winding  $i_0$  induce currents  $i_0'$  in the secondary winding to achieve magnetic balance.

Currents  $i_0'$  in the secondary winding are short-closed and do not flow further into the grid.

$$\hat{Z}_{0p0} = \hat{Z}_{\sigma p} + \hat{Z}_{q0}$$


$$\hat{Z}_0 = \frac{\hat{u}_0}{\hat{i}_0} = \hat{Z}_{\sigma p} + \frac{\hat{Z}_{\sigma s} \cdot \hat{Z}_{q0}}{\hat{Z}_{\sigma s} + \hat{Z}_{q0}}$$

shell

$$\hat{Z}_{q0} = \hat{y}_q^{-1} \gg \hat{Z}_{\sigma s} \rightarrow \hat{Z}_0 \approx \hat{Z}_{\sigma ps} = \hat{Z}_{1k}$$

3-core

$$|\hat{Z}_{q0}| < |\hat{y}_q^{-1}| \rightarrow |\hat{Z}_0| \approx (0,7 \div 0,9) |\hat{Z}_{\sigma ps}|$$

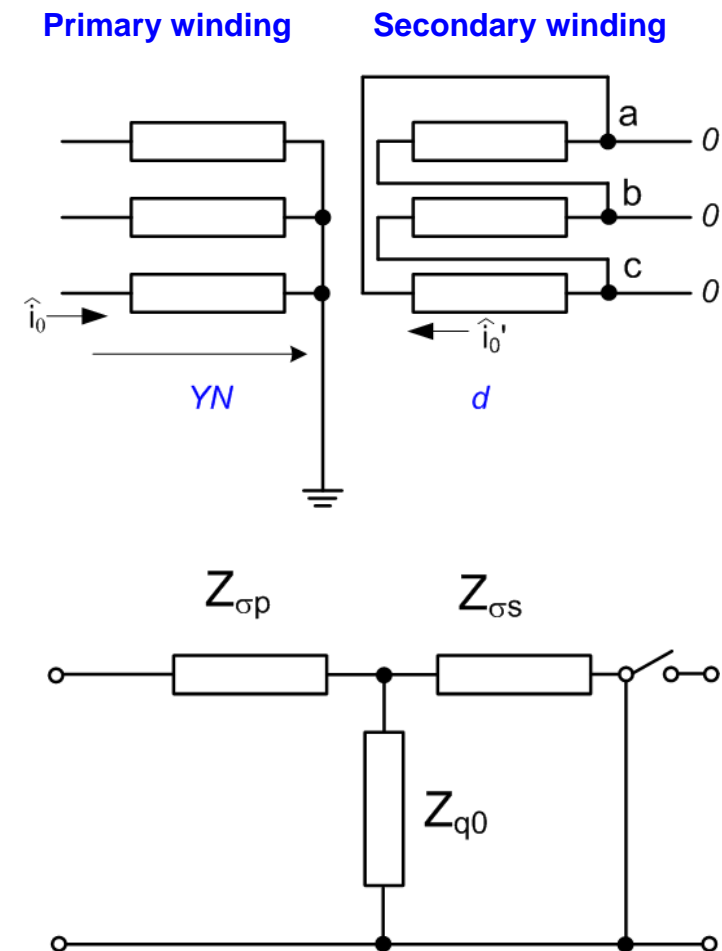

## d) YN / Y

Zero sequence current can't flow through the secondary winding.  
Current  $i_0$  corresponds to the magnetization current.

$$Z_{0ps} \rightarrow \infty$$



$$\hat{Z}_0 = \hat{Z}_{0p0} = \hat{Z}_{\sigma p} + \hat{Z}_{q0}$$

shell

$$\hat{Z}_{q0} = \hat{y}_q^{-1} \rightarrow Z_0 \rightarrow \infty$$

3-core



$$|\hat{Z}_{q0}| < |\hat{y}_q^{-1}| \rightarrow |\hat{Z}_0| \approx (0,3 \div 1)$$

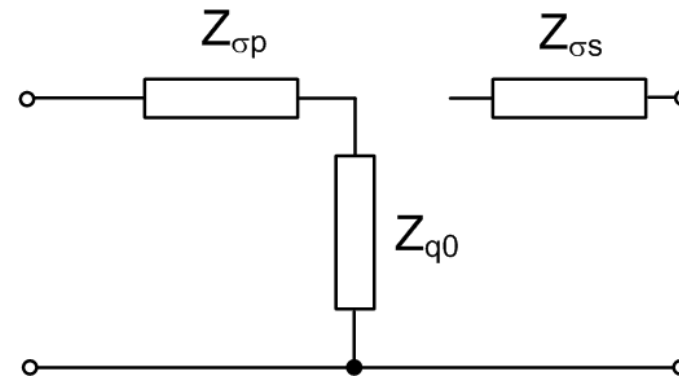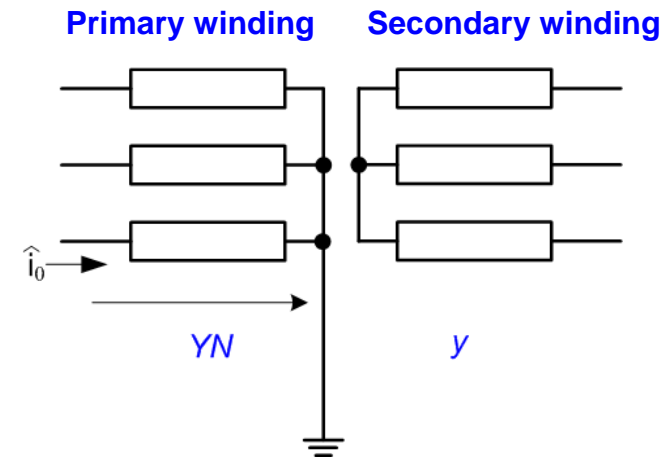

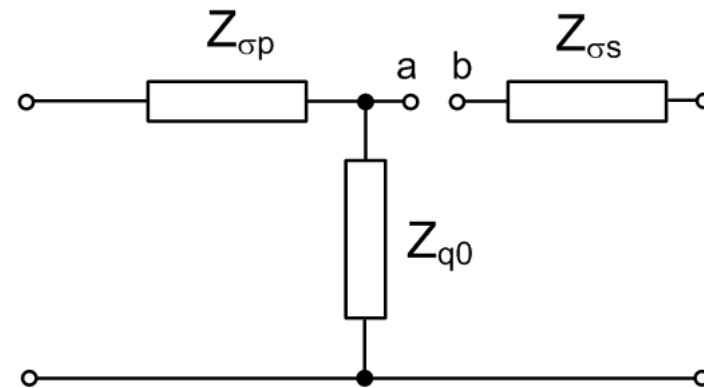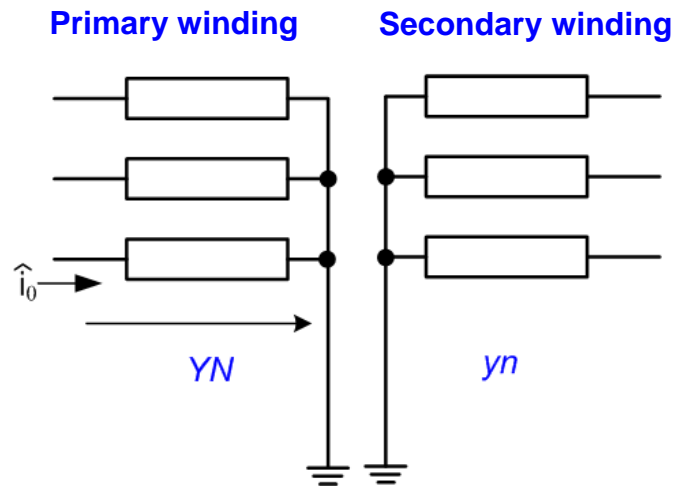e) **YN / YN**

If element with YN or ZN behind TRF → points a-b are connected → as the positive sequence.

If element with Y, Z or D behind TRF → a-b are disconnected → as YN / Y.





**f) ZN / any connection**

Currents  $i_0$  induce mag. balance on the core themselves  $\rightarrow$  only leakages between the halves of the windings.

$$Z_{0ps} \rightarrow \infty$$

$$\hat{Z}_0 = \hat{Z}_{0p0} \approx (0,1 \div 0,3) \hat{Z}_{\sigma ps}$$

$$r_0 = r_p$$

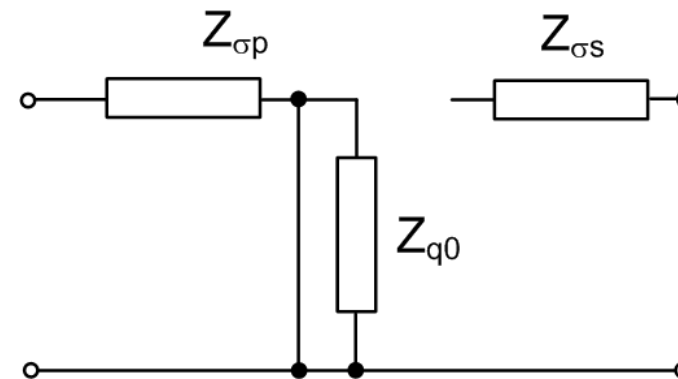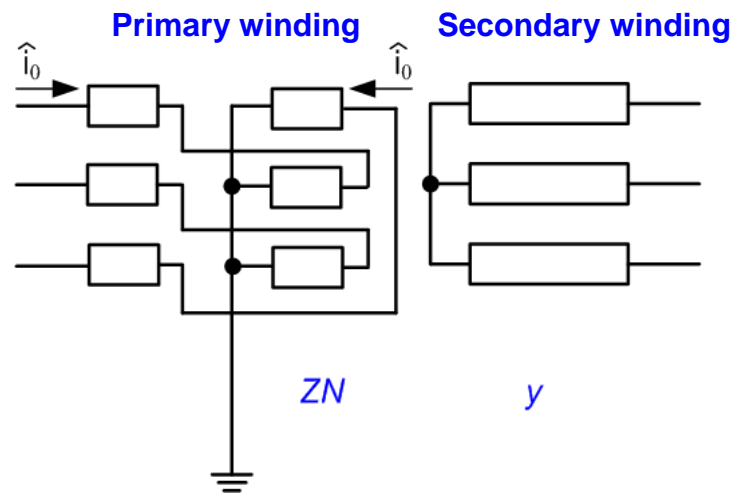



### g) impedance in the neutral point

Current flowing through the neutral point is  $3i_0$ .

Voltage drop: 
$$\Delta \hat{u}_{uz} = \hat{Z}_u \cdot 3\hat{i}_0 = 3\hat{Z}_u \cdot \hat{i}_0$$

→ in the model  $3\hat{Z}_u$  in series with the leakage reactance

### h) three-winding TRF

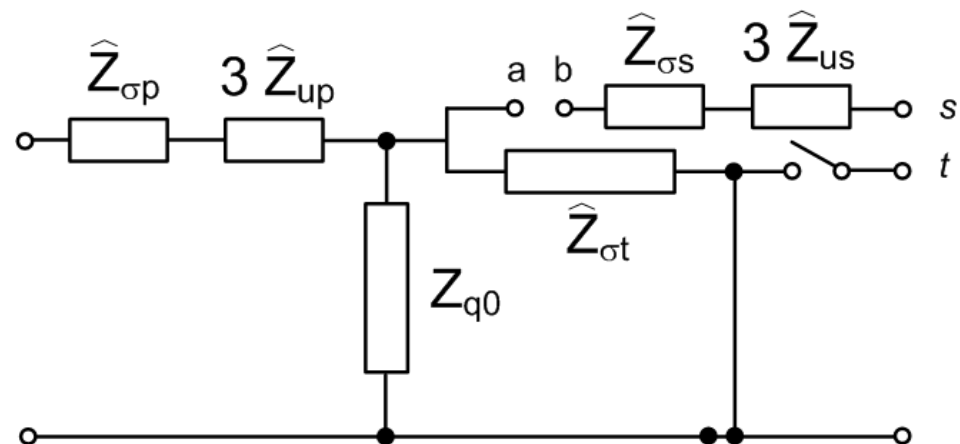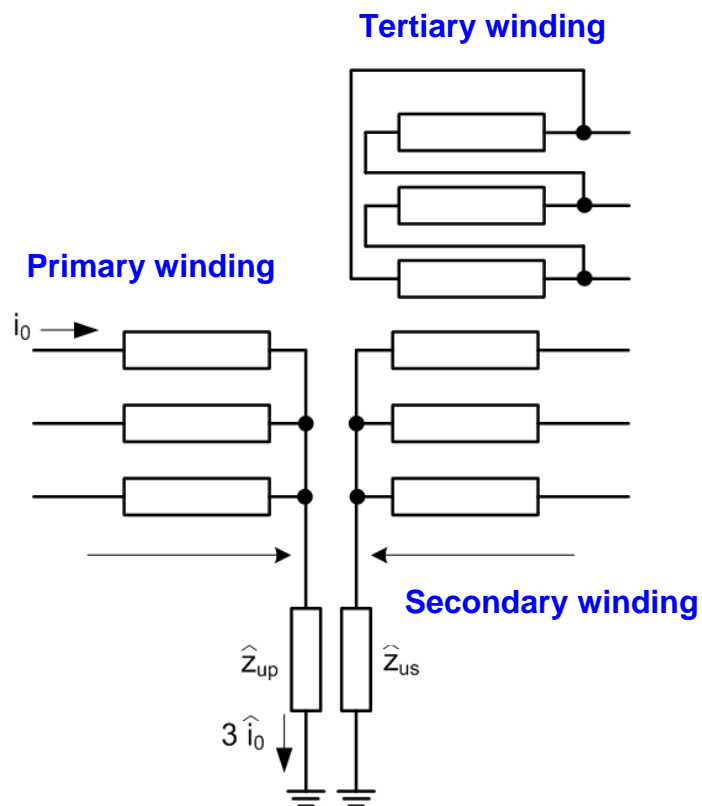

## System equivalent

Impedance (positive sequence) is given by the nominal voltage and short-circuit current (power).

Three-phase (symmetrical) short-circuit:  $S_k''$  (MVA),  $I_k''$  (kA)

$$S_k'' = \sqrt{3} U_n I_k''$$

$$Z_s = \frac{U_n^2}{S_k''} = \frac{U_n}{\sqrt{3} \cdot I_k''}$$

CR:	400 kV	$S_k'' \approx (6000 \div 30000) \text{ MVA}$	$I_k'' \approx (9 \div 45) \text{ kA}$
	220 kV	$S_k'' \approx (2000 \div 12000) \text{ MVA}$	$I_k'' \approx (2 \div 30) \text{ kA}$
	110 kV	$S_k'' \approx (100x \div 3000) \text{ MVA}$	$I_k'' \approx (x \div 15) \text{ kA}$