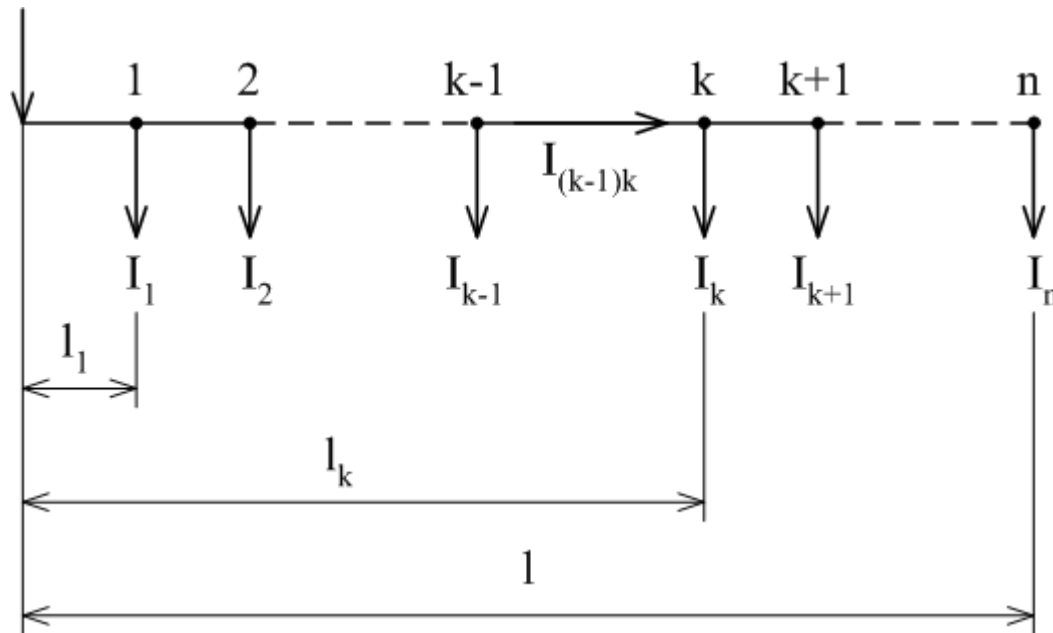


# VOLTAGE DROPS IN POWER SYSTEM

## Simple DC line (LV, MV)

Double-wire circuit. Assumption: constant cross-section and resistivity.  
El. traction, electrochemistry, light sources, long-distance transmission,  
power electronics.

### Single loads supplied from one side



## a) addition method

It adds voltage drops along the power line sections.

(Voltage drops are always in both conductors in the section.)

$k^{\text{th}}$  section

$$U_{(k-1)} - U_k = \Delta U_{(k-1)k} = 2 \frac{\rho}{S} (l_k - l_{(k-1)}) \cdot I_{(k-1)k} \quad (\text{V}; \Omega\text{m}, \text{m}^2, \text{m}, \text{A})$$

Current in  $k^{\text{th}}$  section

$$I_{(k-1)k} = \sum_{y=k}^n I_y$$

Maximum voltage drop

$$\Delta U_n = \sum_{k=1}^n \Delta U_{(k-1)k} = 2 \frac{\rho}{S} \sum_{k=1}^n (l_k - l_{(k-1)}) \cdot \sum_{y=k}^n I_y$$

## b) superposition method

It adds voltage drops for individual discrete loads:

$$\Delta U_n = 2 \frac{\rho}{S} \sum_{k=1}^n l_k I_k$$

$l_k I_k$  ... current moments to the feeder

Relative voltage drop:


$$\varepsilon = \frac{\Delta U}{U_n} \quad (-; V, V)$$

Note. Losses must be calculated only by means of the addition method!

$$\Delta P_{(k-1)k} = 2 \frac{\rho}{S} (l_k - l_{(k-1)}) \cdot I_{(k-1)k}^2 \quad (W; \Omega m, m^2, m, A)$$

$$\Delta P = \sum_{k=1}^n \Delta P_{(k-1)k}$$
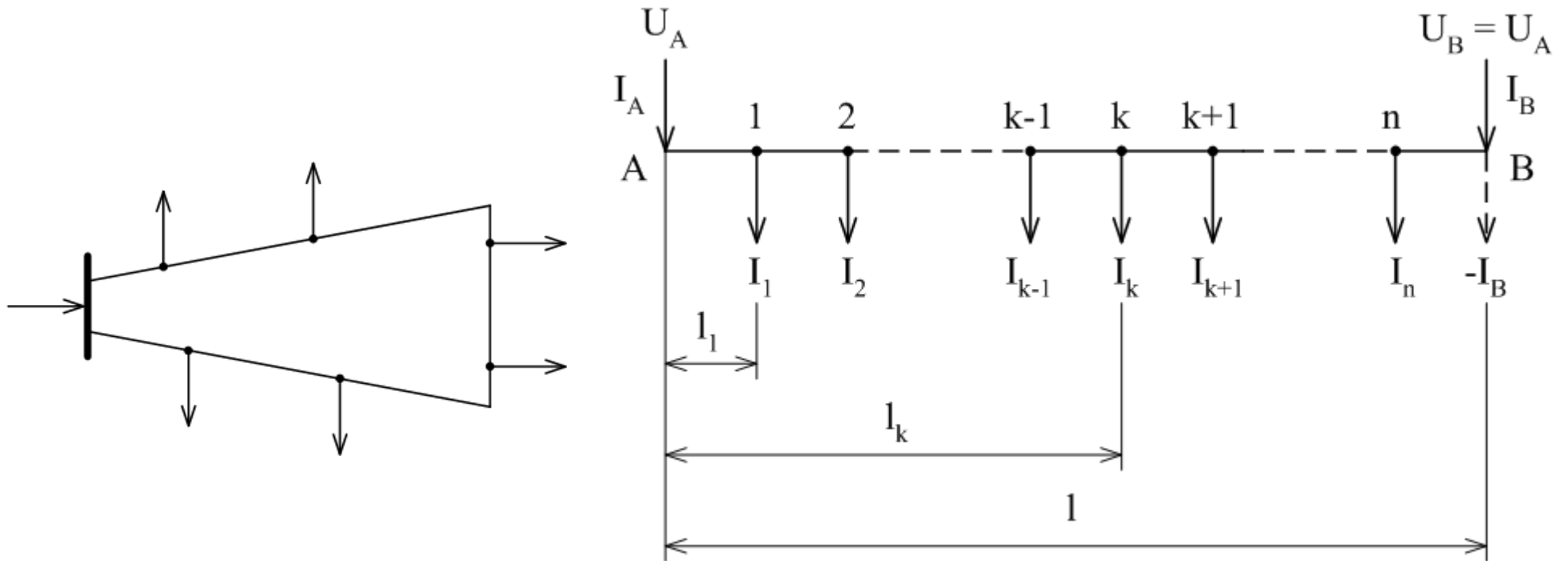
## Single loads supplied from both sides – the same feeders voltages



- Ring grid, higher reliability of supply.
- Two one-feeder lines after a fault.
- Calculation of current distribution and voltage drops.

Consider  $I_B$  as a negative load:

$$\Delta U_{AB} = U_A - U_B = 0 = 2 \frac{\rho}{S} \sum_{k=1}^n l_k I_k - 2 \frac{\rho}{S} l I_B$$

Hence (moment theorem)

$$I_B = \frac{\sum_{k=1}^n l_k I_k}{l}$$


Analogous (current moments to other feeder)

$$I_A = \frac{\sum_{k=1}^n (l - l_k) I_k}{l}$$

Of course


$$I_A + I_B = \sum_{y=1}^n I_y$$

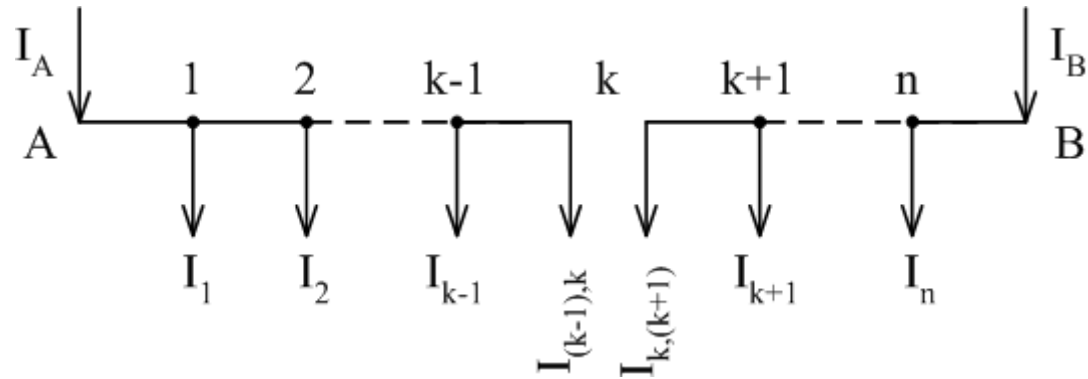Current distribution identifies the place with the biggest voltage drop = the place with feeder division → split-up into two one-feeder lines.



Single loads supplied from both sides – different feeders voltages

Two different sources, meshed grid.

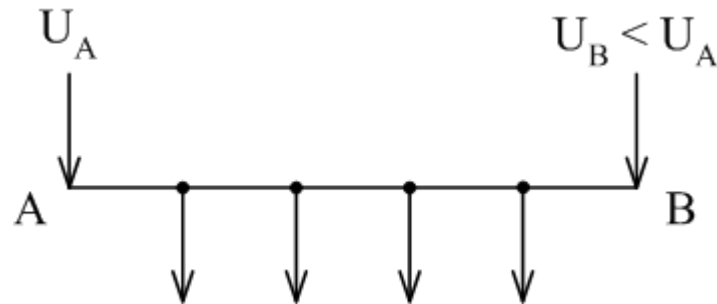

## Superposition:

- 1) Current distribution with the same voltages.
- 2) Different voltages and zero loads  $\rightarrow$  balancing current

$$I_v = \frac{U_A - U_B}{2 \frac{\rho}{S} l}$$




- 3) Sum of the solutions 1+2

Further calculation is the same.

Or directly:

$$U_A - U_B = 2 \frac{\rho}{S} \sum_{k=1}^n l_k I_k - 2 \frac{\rho}{S} l I_B$$
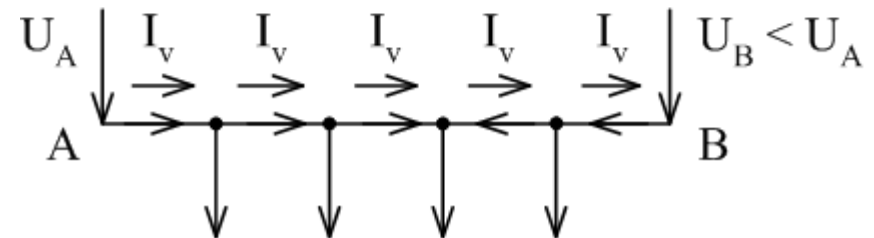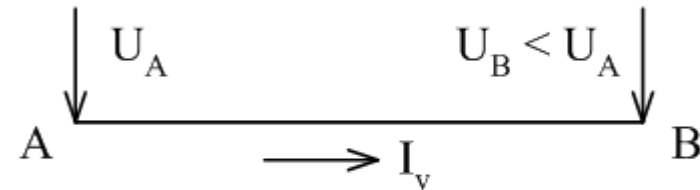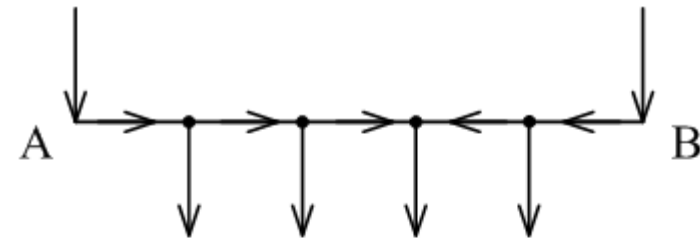
$$I_B = \frac{2 \frac{\rho}{S} \sum_{k=1}^n l_k I_k}{2 \frac{\rho}{S} l} - \frac{U_A - U_B}{2 \frac{\rho}{S} l}$$



## Direct current transmission HV


Long distance transmission or local stations (AC-DC-AC).

Reasons: transmission stability, short-circuit conditions, parameters compensation, power losses, economic aspects, power systems connection.

Possibility of smaller insulation distances and higher transmission capacity than for AC systems.


Control by DC voltage.

Principle

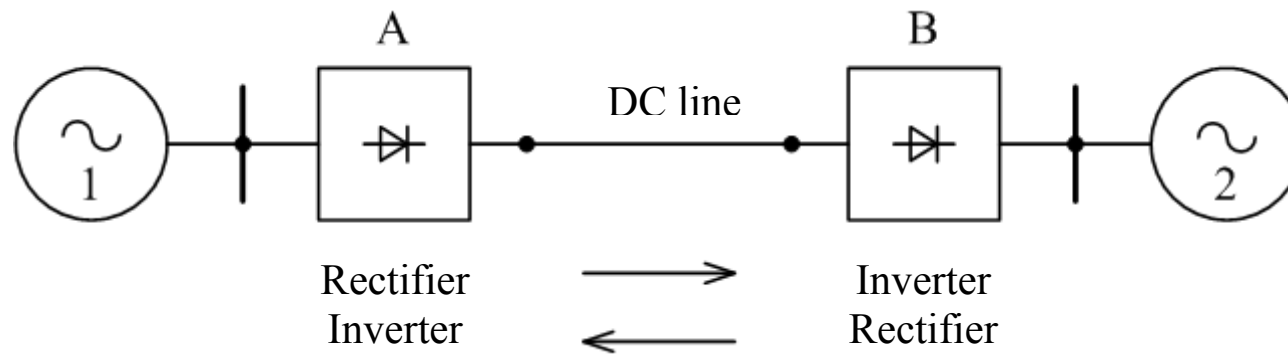



## Configurations:

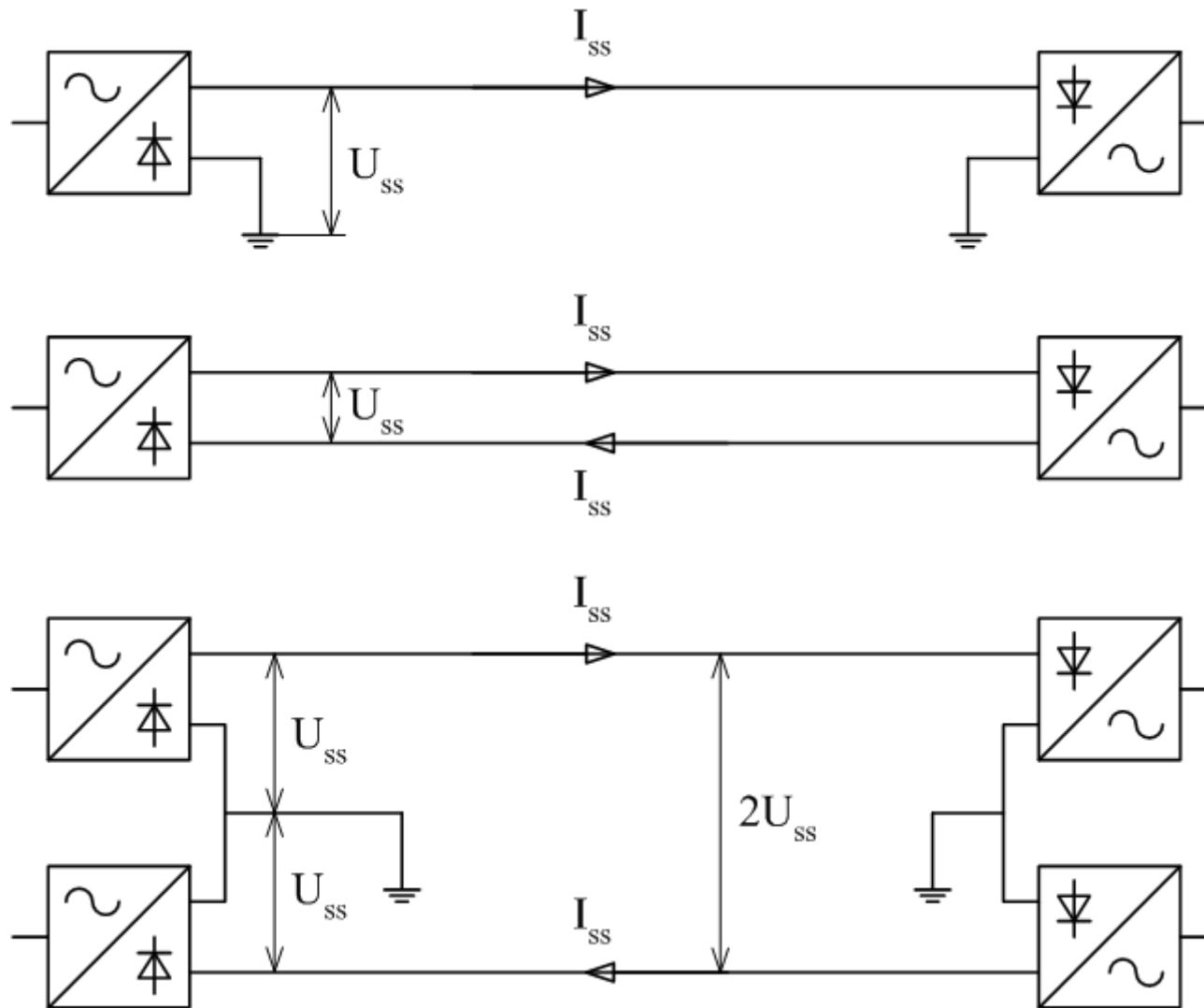

- a) Ground as return conductor. Ground resistance does not depend on line length but on ground connection. Suitable for unoccupied regions (corrosion, EMC).
- b) Two wires line. Compared to 3ph less material, lighter towers.
- c) Two convertors in series. Low balancing ground current caused by unbalance. During a fault it transforms to a), half power.

## 450 kV DC Canada



## Complex power in AC grids

3 phase

$$P = 3U_f I \cos \varphi = \sqrt{3}UI \cos \varphi \quad (\text{W})$$

$$Q = 3U_f I \sin \varphi = \sqrt{3}UI \sin \varphi \quad (\text{VAr})$$

$$S = 3U_f I = \sqrt{3}UI = \sqrt{P^2 + Q^2} \quad (\text{VA})$$

### Complex (1 phase)

$$\hat{S}_f = P_f \pm jQ_f = U_f I (\cos \varphi \pm j \sin \varphi) = S_f e^{\pm j\varphi}$$

Sign according a convention.


### Inductive load

$$\hat{U}_f = U_f e^{j\varphi_u}, \quad \hat{I}_f = I e^{j\varphi_i}$$
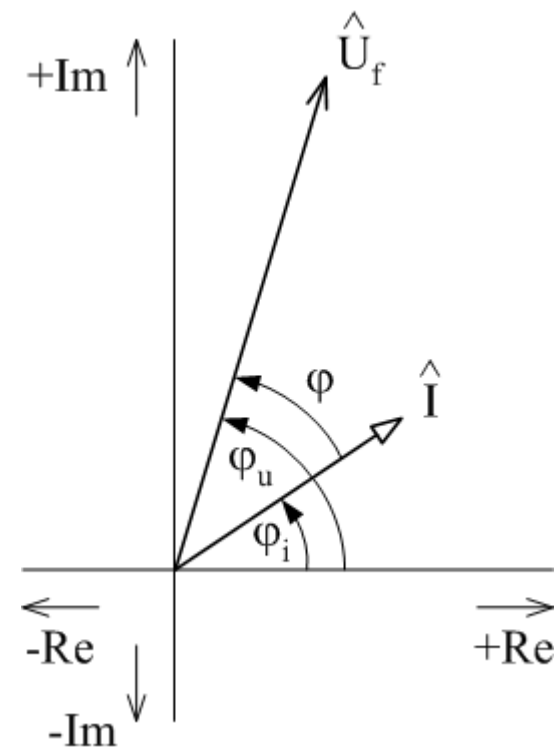
### Complex conjugated current

$$\hat{S}_f = \hat{U}_f \hat{I}^* = U_f I e^{j(\varphi_u - \varphi_i)} = U_f I e^{j\varphi}$$

$$\hat{S}_f = \hat{U}_f \hat{I}^* = P_f \pm jQ_f \begin{array}{l} \text{IND} \\ \text{CAP} \end{array}$$




## 3 phase power lines LV, MV

Series parameters are applied, for LV  $X \rightarrow 0$ .
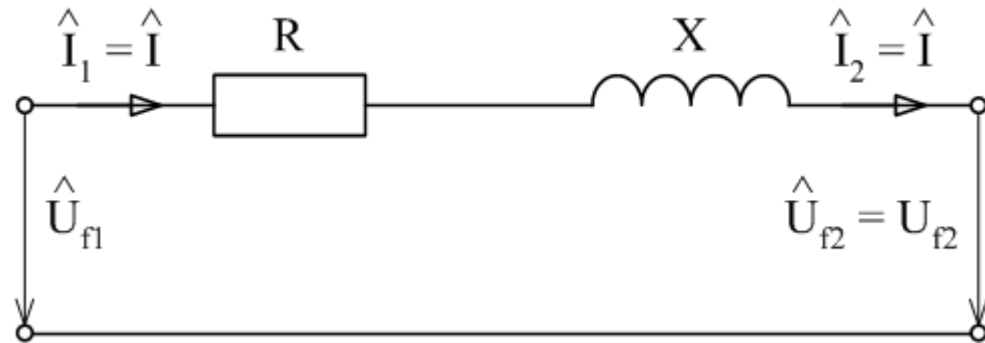
### 3 phase power line MV, 1 load at the end

Symmetrical load  $\rightarrow$  1 phase diagram, operational parameters.



Complex voltage drop

$$\Delta \hat{U}_f = \hat{Z}_1 \hat{I} = (R + jX) \left( I_c \mp j I_j \right) \begin{matrix} \text{IND} \\ \text{CAP} \end{matrix}$$

$$\Delta \hat{U}_f = R I_c \pm X I_j + j \left( X I_c \mp R I_j \right) \begin{matrix} \text{IND} \\ \text{CAP} \end{matrix}$$

magnitude      phase

Phasor diagram (input  $U_{f2}$ ,  $I$ ,  $\varphi_2$ )  
 (angle  $\upsilon$  usually small, up to  $3^\circ$ )

Imagin. part neglecting and modifications


$$\Delta U_f = \frac{R3U_f I_{\check{c}} \pm X3U_f I_j}{3U_f} = \frac{RP \pm XQ}{3U_f}$$

Percentage voltage drop

$$\varepsilon = \frac{\Delta U_f}{U_f} = \frac{RP \pm XQ}{3U_f^2} = \frac{RP \pm XQ}{U^2}$$

3 phase active power losses
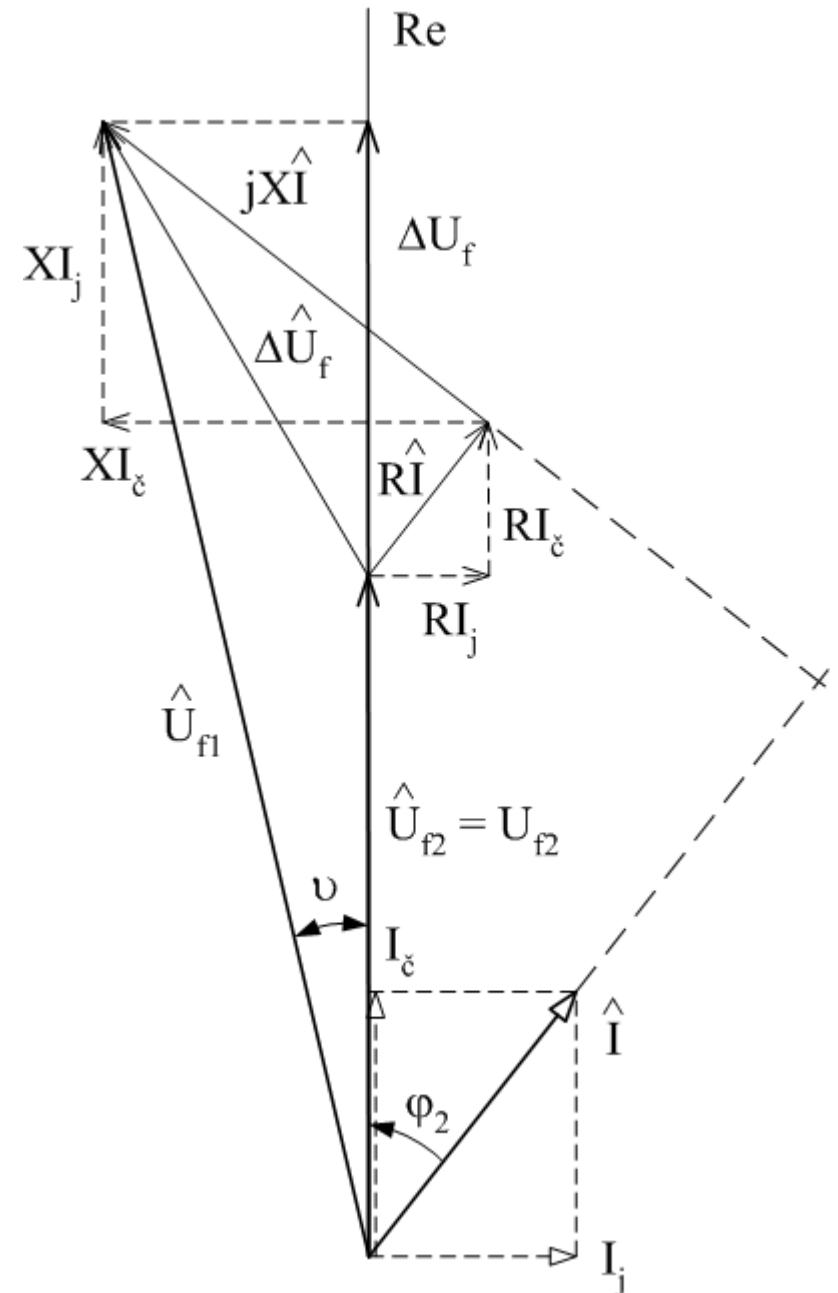
$$\begin{aligned} \Delta \hat{S} &= 3\Delta \hat{U}_f \hat{I}^* = 3\hat{Z}_1 \hat{I} \cdot \hat{I}^* = 3\hat{Z}_1 I^2 = \\ &= 3(R + jX)I^2 = 3RI^2 + j3XI^2 \\ \Delta P &= 3RI^2 = 3R(I_{\check{c}}^2 + I_j^2) \quad (\text{W}; \Omega, \text{A}) \end{aligned}$$




! Even the reactive current causes active power losses!

→ reactive power compensation
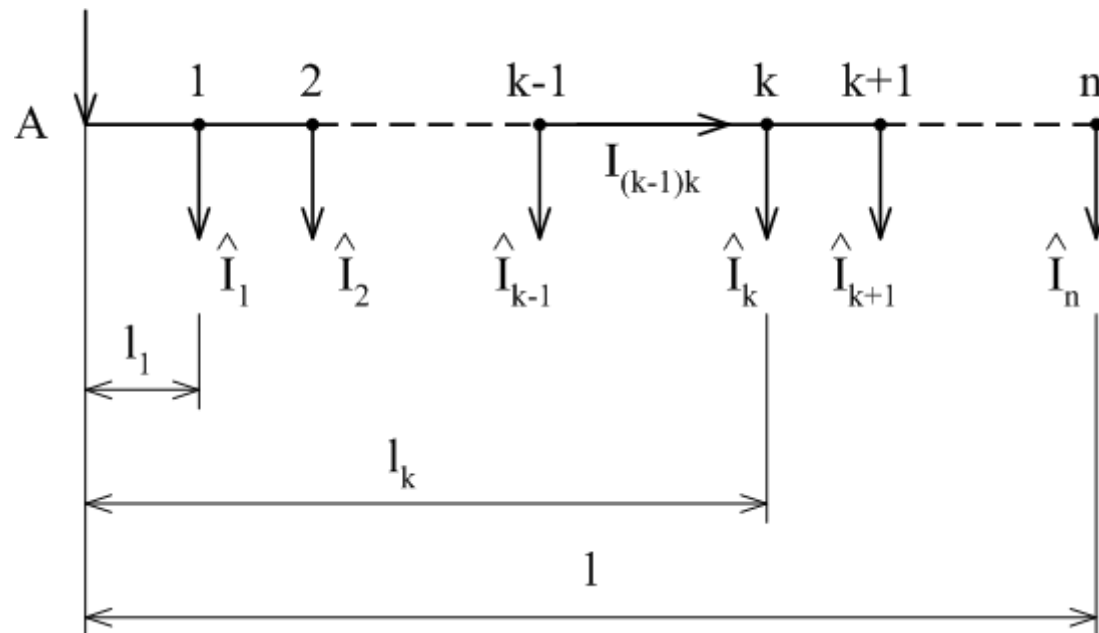
### 3 phase MV power line supplied from one side

Constant series impedance

$$\hat{Z}_{l_1} = R_1 + jX_1 \quad (\Omega / \text{km})$$



Voltage drop at the end (needn't be the highest one, it depends on load character)

$$\Delta \hat{U}_{fAn} = \hat{Z}_{l_1} \sum_{k=1}^n l_k \hat{I}_k$$

After imaginary part neglecting


$$\Delta U_{fAn} \doteq R_1 \sum_{k=1}^n l_k I_{ck} \pm X_1 \sum_{k=1}^n l_k I_{jk} \quad \begin{array}{l} \text{IND} \\ \text{CAP} \end{array}$$

$$\Delta U_{fAn} \doteq \frac{R_1 \sum_{k=1}^n l_k P_k \pm X_1 \sum_{k=1}^n l_k Q_k}{3U_f} \quad \begin{array}{l} \text{IND} \\ \text{CAP} \end{array}$$

Voltage drop up to the point X (superposition)

$$\Delta \hat{U}_{fAX} = \hat{Z}_{l_1} \sum_{k=1}^X l_k \hat{I}_k + \hat{Z}_{l_1} l_{AX} \sum_{k=X+1}^n \hat{I}_k$$
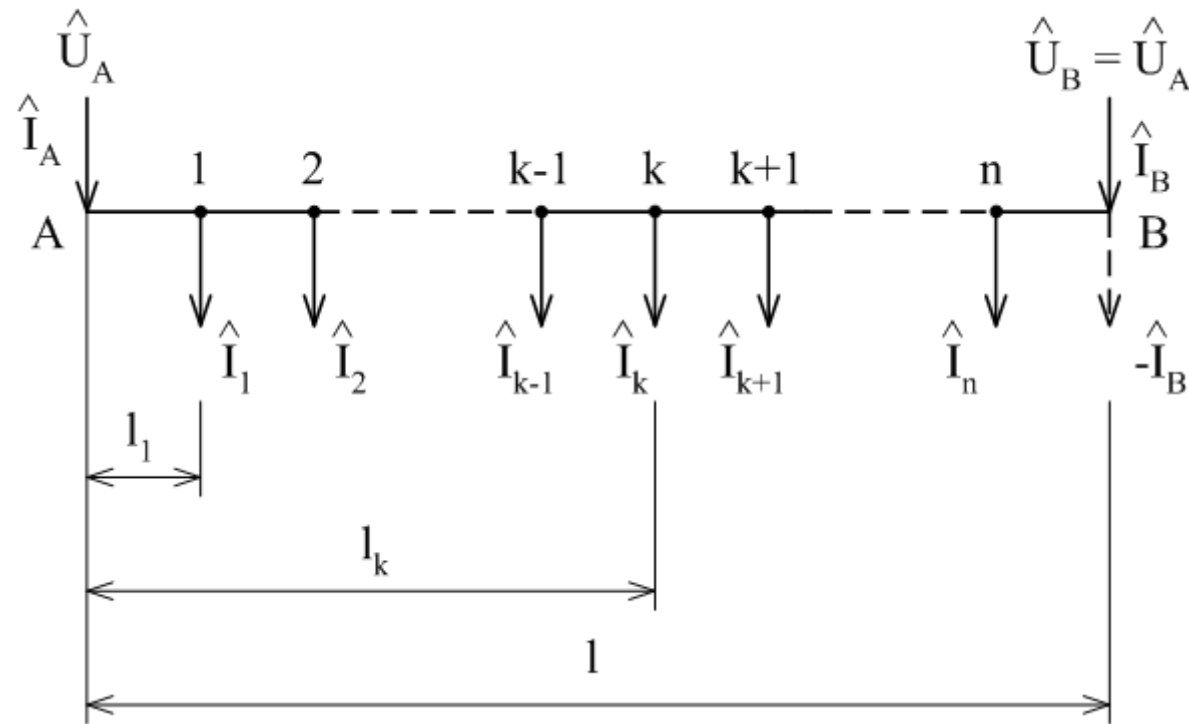
### 3 phase MV power line supplied from both sides



Calculation as for DC line (feeder is a negative load, zero voltage drop).

$$\Delta \hat{U}_{AB} = 0 = \hat{Z}_{l_1} \sum_{k=1}^n l_k \hat{I}_k - \hat{Z}_{l_1} l \cdot \hat{I}_B$$



## Moment theorems

$$\hat{I}_B = \frac{\sum_{k=1}^n l_k \hat{I}_k}{1} \quad \hat{I}_A = \frac{\sum_{k=1}^n (1-l_k) \hat{I}_k}{1} \quad \hat{I}_A + \hat{I}_B = \sum_{y=1}^n \hat{I}_y$$

(In principle it is the current divider for each load.)


Active and reactive current sign change could be in different nodes → maximum voltage drop should be checked in all grid points.

## Meshed grids MV



NO!




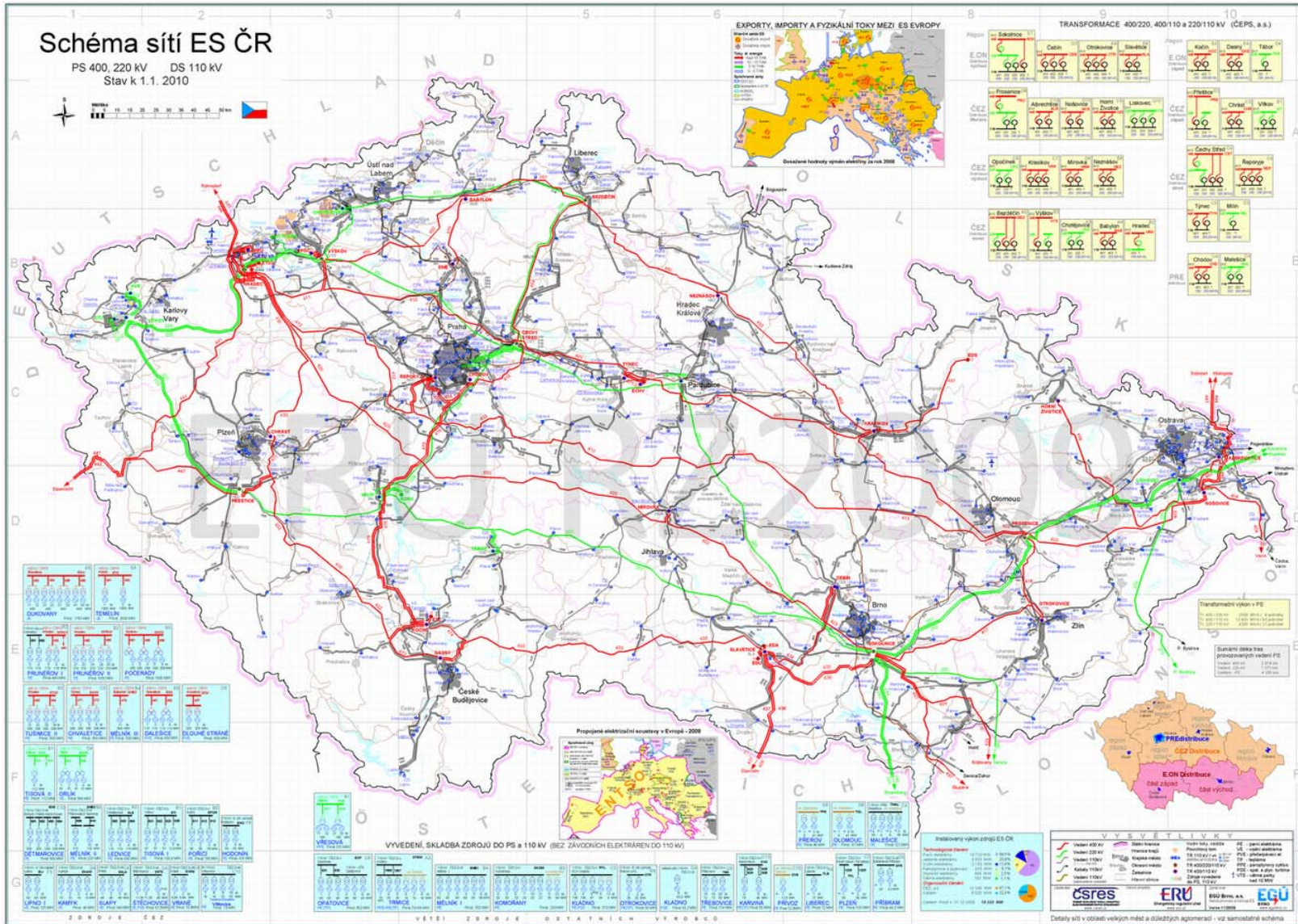

YES!
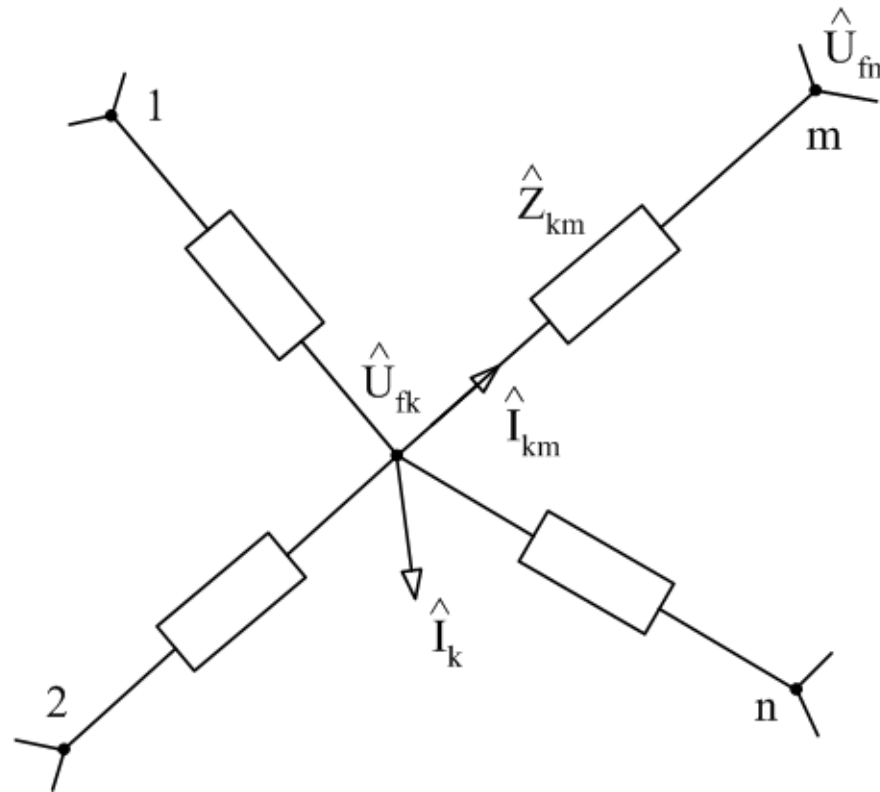
## Node voltage method

Grid with  $n$  nodes. Set series branch parameters  $\hat{Z}_{km}$ , load currents (nodal currents)  $\hat{I}_k$ , min. 1 node voltage  $\hat{U}_{fk}$  (between the node and the ground).



## Calculation with series admittances

$$\hat{Y}_{km} = \hat{Z}_{km}^{-1} = \frac{1}{R_{km} + jX_{km}}$$

### Node $k$

$$\hat{I}_k + \sum_{\substack{m=1 \\ m \neq k}}^n \hat{I}_{km} + \hat{I}_{k0} = 0$$


$$\hat{I}_{k0} = \hat{U}_{fk} \hat{Y}_{k0}$$

### Branches $k, m$

$$\hat{I}_{km} = (\hat{U}_{fk} - \hat{U}_{fm}) \hat{Y}_{km}$$
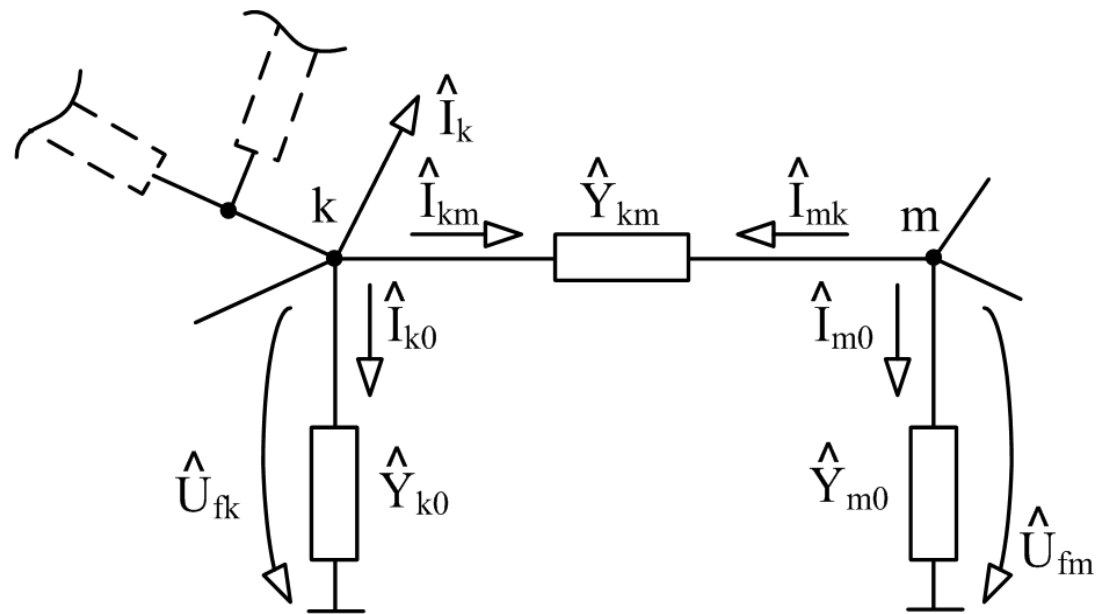
### After modifications:

$$\hat{I}_k = - \sum_{\substack{m=1 \\ m \neq k}}^n (\hat{U}_{fk} - \hat{U}_{fm}) \hat{Y}_{km} - \hat{U}_{fk} \hat{Y}_{k0}$$



$$\hat{\mathbf{I}}_k = -\hat{\mathbf{U}}_{fk} \left( \sum_{\substack{m=1 \\ m \neq k}}^n \hat{\mathbf{Y}}_{km} + \hat{\mathbf{Y}}_{k0} \right) + \sum_{\substack{m=1 \\ m \neq k}}^n \hat{\mathbf{U}}_{fm} \hat{\mathbf{Y}}_{km}$$

Admittance matrix parameters definition:  
Nodal self-admittance (diagonal element)

$$\hat{\mathbf{Y}}_{(k,k)} = -\sum_{\substack{m=1 \\ m \neq k}}^n \hat{\mathbf{Y}}_{km} - \hat{\mathbf{Y}}_{k0}$$

Between nodes admittance (non-diagonal element)

$$\hat{\mathbf{Y}}_{(k,m)} = \hat{\mathbf{Y}}_{(m,k)} = \hat{\mathbf{Y}}_{km} \quad \text{for } m \neq k$$

(for non-connected nodes  $\hat{\mathbf{Y}}_{(k,m)} = 0$ )

Hence

$$\hat{\mathbf{I}}_k = \sum_{m=1}^n \hat{\mathbf{Y}}_{(k,m)} \hat{\mathbf{U}}_{fm}$$

Matrix form

$$\begin{pmatrix} \hat{\mathbf{I}} \end{pmatrix} = \begin{pmatrix} \hat{\mathbf{Y}} \end{pmatrix} \begin{pmatrix} \hat{\mathbf{U}}_f \end{pmatrix}$$

Set voltages at nodes 1 to  $k$  ( $\mathbf{x}$ ), currents at nodes  $k+1$  to  $n$  ( $\mathbf{y}$ )

$$\begin{pmatrix} \begin{pmatrix} \hat{\mathbf{I}}_x \end{pmatrix} \\ \begin{pmatrix} \hat{\mathbf{I}}_y \end{pmatrix} \end{pmatrix} = \begin{pmatrix} \begin{pmatrix} \hat{\mathbf{Y}}_{xx} \end{pmatrix} & \begin{pmatrix} \hat{\mathbf{Y}}_{xy} \end{pmatrix} \\ \begin{pmatrix} \hat{\mathbf{Y}}_{xy} \end{pmatrix}^T & \begin{pmatrix} \hat{\mathbf{Y}}_{yy} \end{pmatrix} \end{pmatrix} \begin{pmatrix} \begin{pmatrix} \hat{\mathbf{U}}_{fx} \end{pmatrix} \\ \begin{pmatrix} \hat{\mathbf{U}}_{fy} \end{pmatrix} \end{pmatrix}$$

Hence

$$\begin{pmatrix} \hat{\mathbf{I}}_x \end{pmatrix} = \begin{pmatrix} \hat{\mathbf{Y}}_{xx} \end{pmatrix} \begin{pmatrix} \hat{\mathbf{U}}_{fx} \end{pmatrix} + \begin{pmatrix} \hat{\mathbf{Y}}_{xy} \end{pmatrix} \begin{pmatrix} \hat{\mathbf{U}}_{fy} \end{pmatrix}$$

$$\begin{pmatrix} \hat{\mathbf{I}}_y \end{pmatrix} = \begin{pmatrix} \hat{\mathbf{Y}}_{xy} \end{pmatrix}^T \begin{pmatrix} \hat{\mathbf{U}}_{fx} \end{pmatrix} + \begin{pmatrix} \hat{\mathbf{Y}}_{yy} \end{pmatrix} \begin{pmatrix} \hat{\mathbf{U}}_{fy} \end{pmatrix}$$

Calculate  $\begin{pmatrix} \hat{\mathbf{I}}_x \end{pmatrix}$ ,  $\begin{pmatrix} \hat{\mathbf{U}}_{fy} \end{pmatrix}$

$$\begin{pmatrix} \hat{\mathbf{U}}_{fy} \end{pmatrix} = \begin{pmatrix} \hat{\mathbf{Y}}_{yy} \end{pmatrix}^{-1} \begin{pmatrix} \hat{\mathbf{I}}_y \end{pmatrix} - \begin{pmatrix} \hat{\mathbf{Y}}_{yy} \end{pmatrix}^{-1} \begin{pmatrix} \hat{\mathbf{Y}}_{xy} \end{pmatrix}^T \begin{pmatrix} \hat{\mathbf{U}}_{fx} \end{pmatrix}$$

If some nodes are connected to the ground (through an admittance), then the admittance matrix is regular  $\rightarrow$  to set all nodal current is enough.

$$\left(\hat{U}_f\right) = \left(\hat{Y}\right)^{-1} \left(\hat{I}\right)$$

Note 1: Similar for DC grid.

$$(I) = (G)(U)$$

Note 2: For power engineering – powers are set, currents are calculated from the powers.

$$\hat{I} = \left( \frac{\hat{S}}{\sqrt{3}\hat{U}} \right)^*$$

Results are not precise if nominal voltages are used  $\rightarrow$  iteration methods.