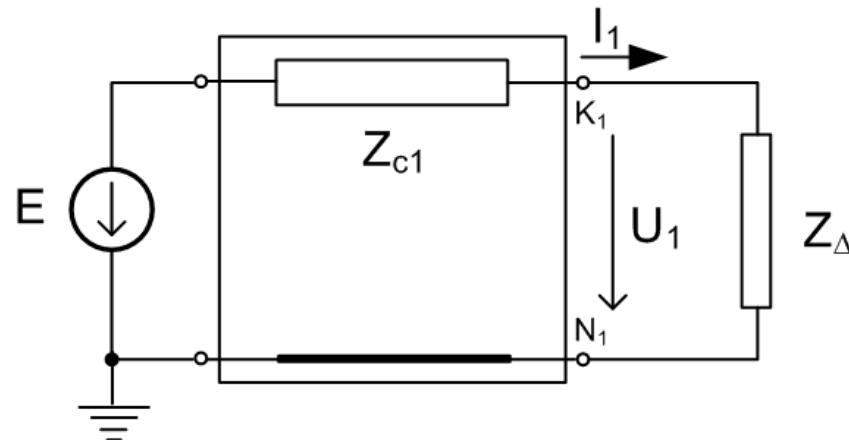


Short-circuits in ES (2nd part)

Unbalanced short-circuits equivalence with three-phase short-circuit

Positive-sequence current component calculation by means of an additional impedance (in the short-circuit place according to short-circuit type)



Generalized relation

$$\hat{I}_1 = \frac{\hat{E}}{\hat{Z}_1 + \hat{Z}_\Delta}$$

Short-cir. type	3ph	1ph	2ph	2ph to ground
\hat{Z}_Δ	0	$\hat{Z}_2 + \hat{Z}_0$	\hat{Z}_2	$\frac{\hat{Z}_2 \cdot \hat{Z}_0}{\hat{Z}_2 + \hat{Z}_0}$
Current components	\hat{I}_1	$\hat{I}_1 = \hat{I}_2 = \hat{I}_0$	$\hat{I}_2 = -\hat{I}_1$	$\hat{I}_1 = -(\hat{I}_2 + \hat{I}_0)$
$m (I_k = m \cdot I_1)$	1	3	$\sqrt{3}$	$\sqrt{3} \sqrt{1 - \frac{X_2 \cdot X_0}{(X_2 + X_0)^2}}$
Substitution diagram				

Individual short-circuit types comparison

For: $t = 0$ (I''), $R = 0$, $X_1 = X_2$
ratio X_0/X_1 can be changed from 0 to ∞
reference 3ph short-circuit

Three-phase short-circuit

$$I_k''^{(3)} = I_1 = \frac{E''}{X_1}$$

Single-phase-to-ground short-circuit

$$I_k''^{(1)} = 3I_1 = \frac{3E''}{X_1 + X_2 + X_0} = \frac{3X_1}{2X_1 + X_0} I_k''^{(3)} = \frac{3}{2 + \frac{X_0}{X_1}} I_k''^{(3)}$$

$$I_k''^{(1)} = (0 \div 1,5) I_k''^{(3)}$$


Phase-to-phase short-circuit

$$I_k''^{(2)} = \sqrt{3} I_1 = \frac{\sqrt{3} E''}{X_1 + X_2} = \frac{\sqrt{3} X_1}{2 X_1} I_k''^{(3)} = \frac{\sqrt{3}}{2} I_k''^{(3)} \cong 0,866 I_k''^{(3)}$$

Double-phase-to-ground short-circuit

$$I_k''^{(2z)} = \sqrt{3} \sqrt{1 - \frac{X_2 \cdot X_0}{(X_2 + X_0)^2}} \frac{E''}{X_1 + \frac{X_2 \cdot X_0}{X_2 + X_0}} = \sqrt{3} \sqrt{1 - \frac{\frac{X_0}{X_1}}{\left(1 + \frac{X_0}{X_1}\right)^2} \frac{I_k''^{(3)}}{1 + \frac{X_0}{X_1}}}$$

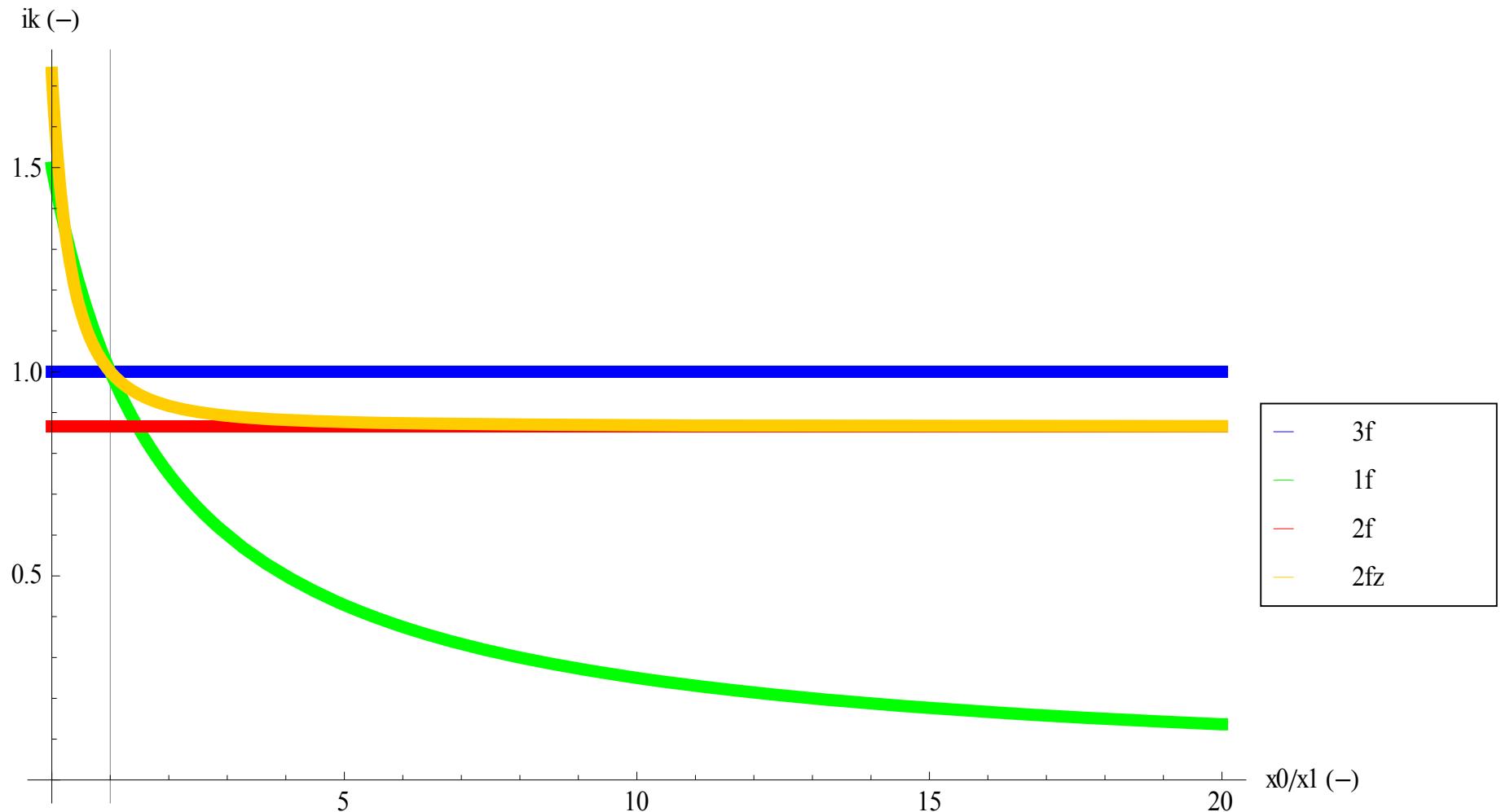
$$I_k''^{(2z)} = \left(\frac{\sqrt{3}}{2} \div \sqrt{3} \right) I_k''^{(3)}$$



Arc influence during short-circuit


Single-phase-to-ground s.-c.
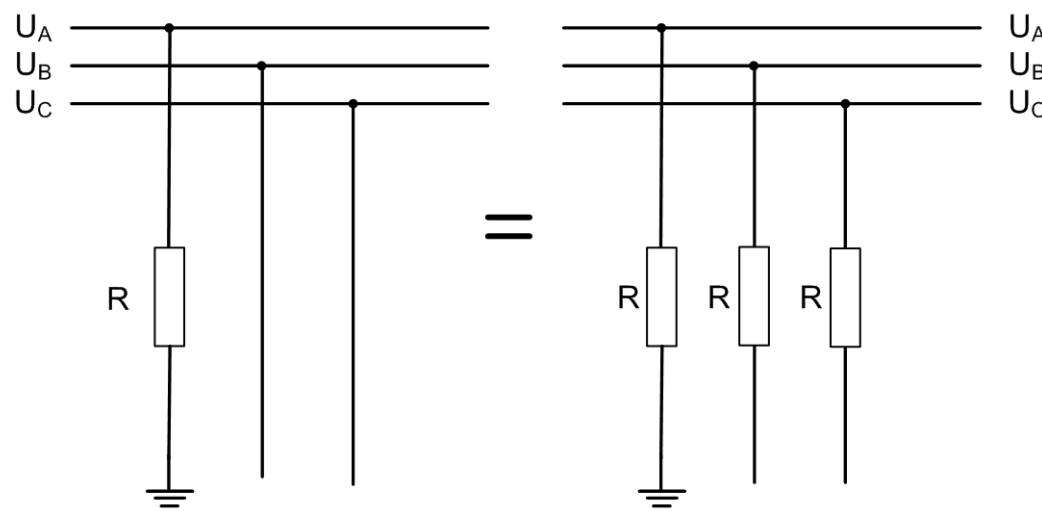
$$\hat{I}_1 = \frac{\hat{E}}{\hat{Z}_1 + \hat{Z}_2 + \hat{Z}_0 + 3R}$$





Three-phase s.-c.
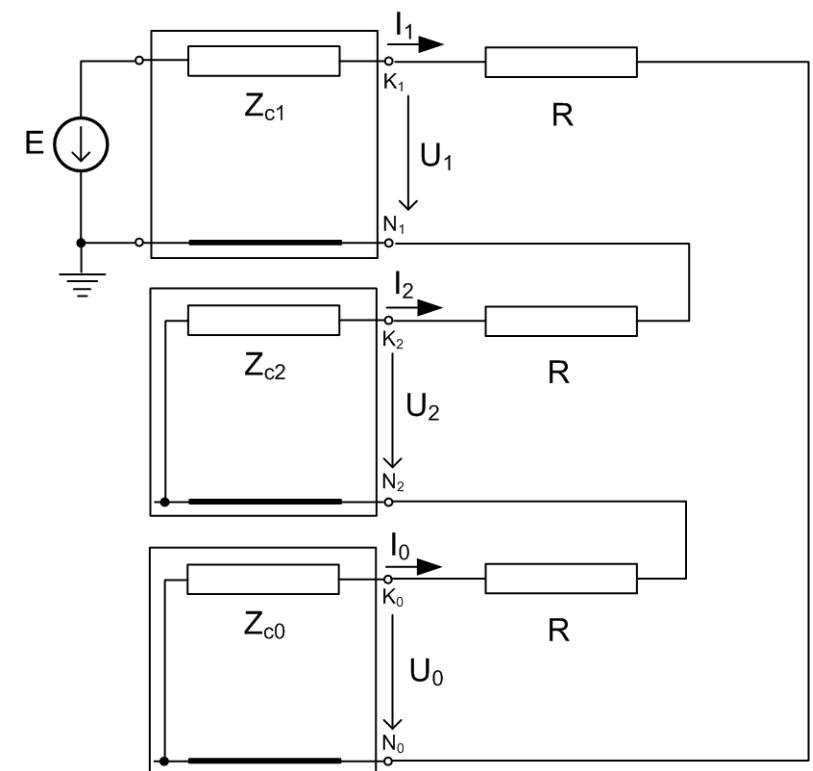
$$\hat{I}_1 = \frac{\hat{E}}{\hat{Z}_1 + R}$$




Phase-to-phase s.-c.
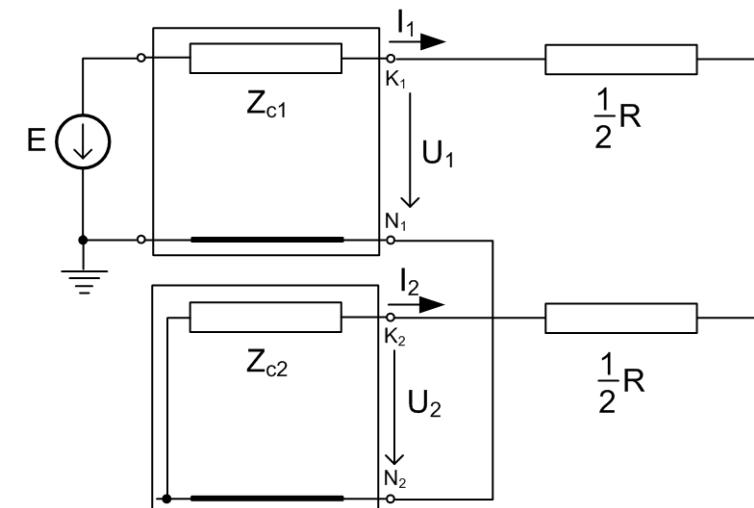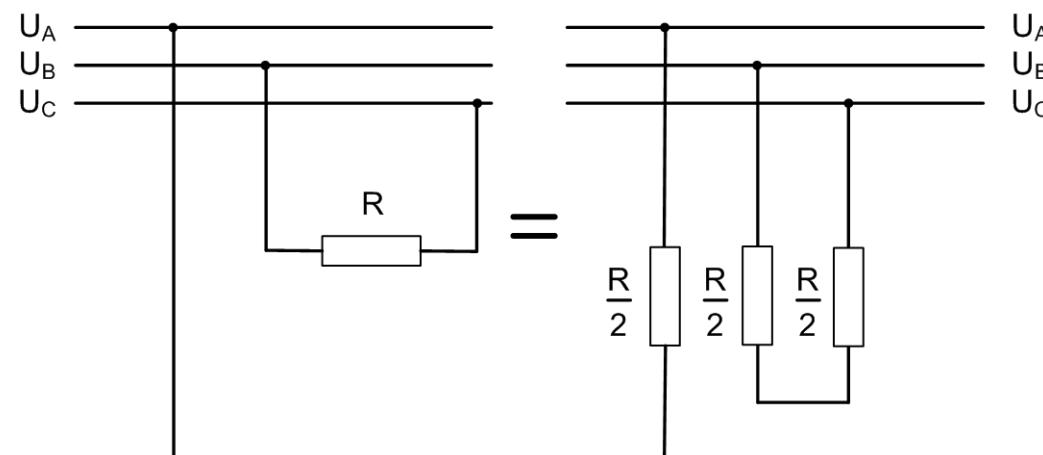
$$\hat{I}_1 = \frac{\hat{E}}{\hat{Z}_1 + \hat{Z}_2 + R}$$




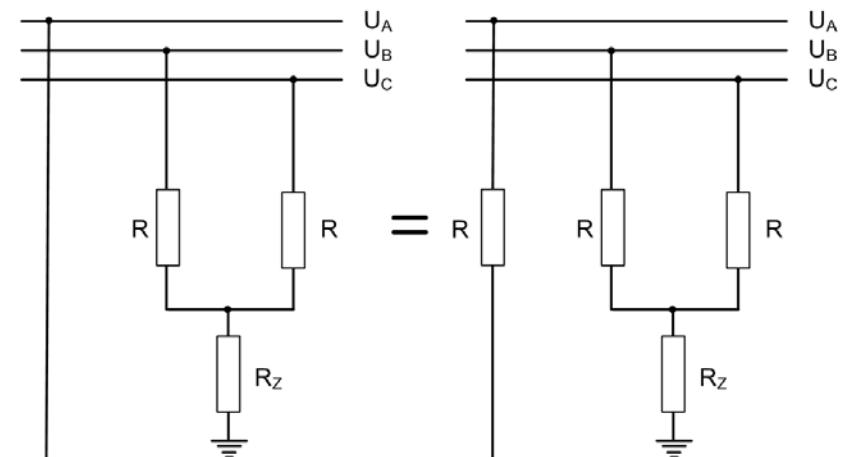Note: Double-phase-to-ground s.-c.
doesn't have a symmetrical resistance segment.



Phase interruption

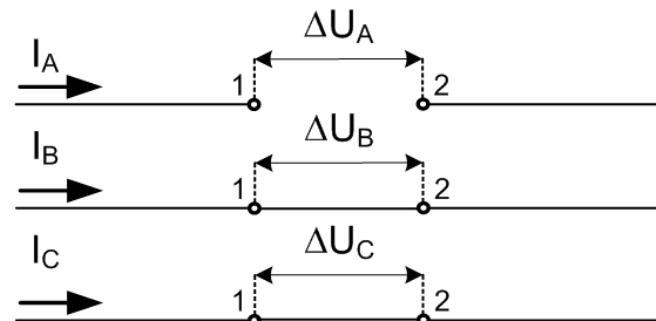Single-phase interruption (analogy with double-phase-to-ground s.-c.)




$$\hat{\Delta U}_B = \hat{\Delta U}_C = 0; \quad \hat{I}_A = 0$$


Components

$$\hat{\Delta U}_1 = \hat{\Delta U}_2 = \hat{\Delta U}_0 = \frac{1}{3} \hat{\Delta U}_A$$

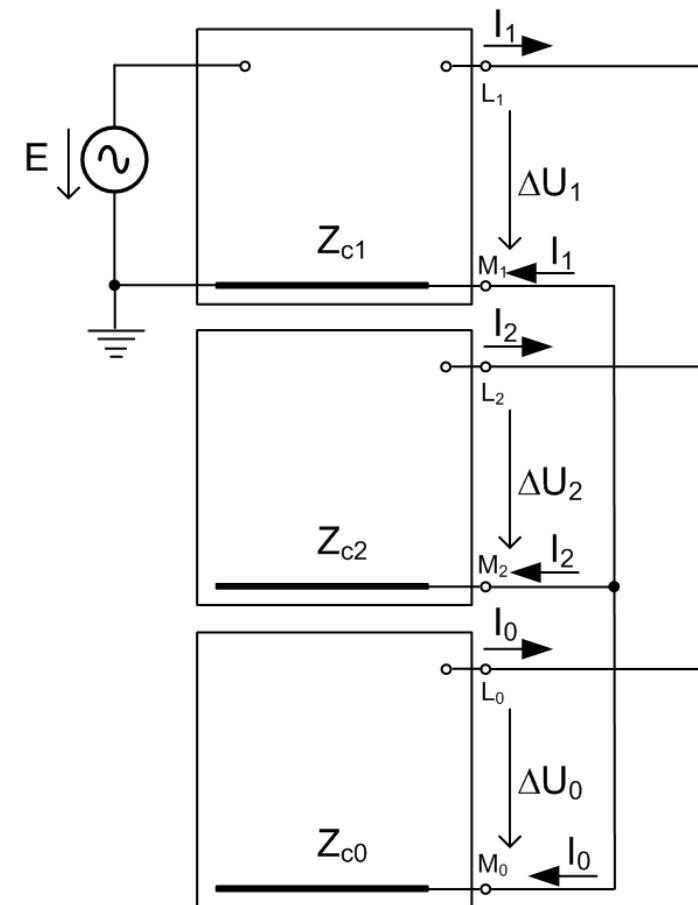
$$\hat{I}_1 = \frac{\hat{E}}{\hat{Z}_1 + \frac{\hat{Z}_0 \hat{Z}_2}{\hat{Z}_0 + \hat{Z}_2}} = \frac{\hat{E}}{\hat{Z}_1 + \hat{Z}_\Delta}$$



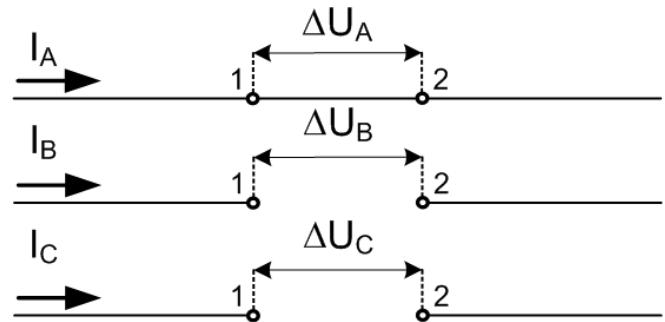Double-phase interruption (analogy with single-phase-to-ground s.-c.)


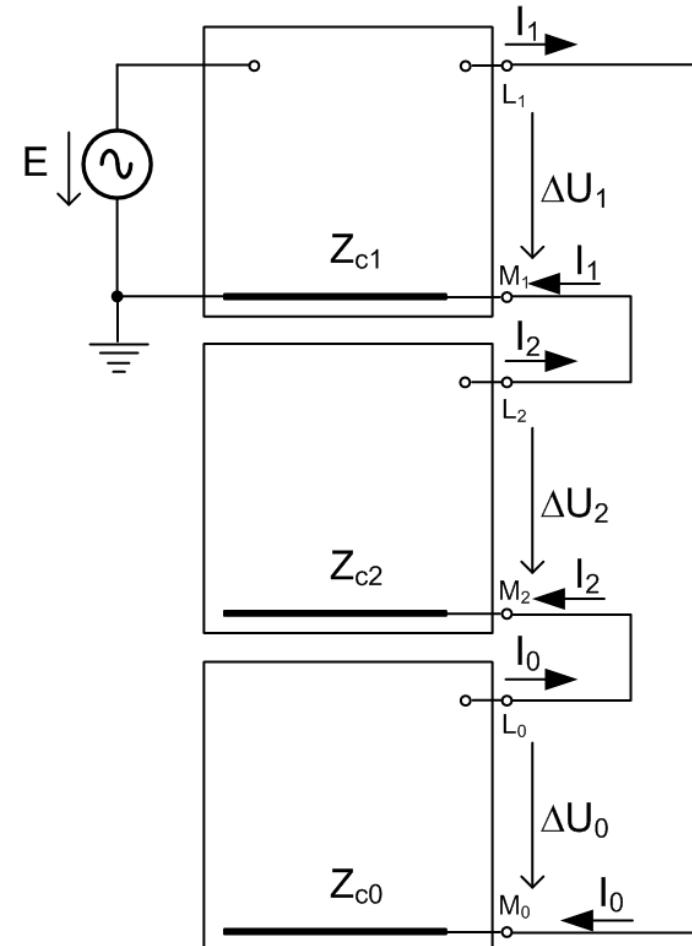
$$\hat{\Delta U}_A = 0; \quad \hat{I}_B = \hat{I}_C = 0$$



Components

$$\hat{I}_1 = \hat{I}_2 = \hat{I}_0 = \frac{\hat{E}}{\hat{Z}_1 + \hat{Z}_2 + \hat{Z}_0} = \frac{1}{3} \hat{I}_A$$





Analogy between interruptions and short-circuits

Sequence impedances

- short-circuits – between s.-c. place and the ground
- interruption – between places on both sides of the interruption

Similarly for the additional impedance.

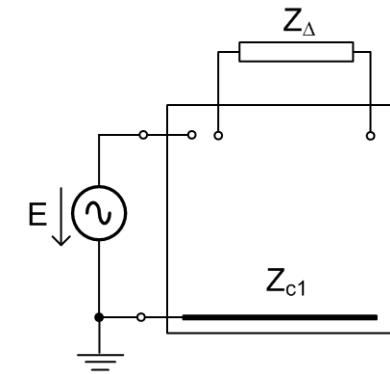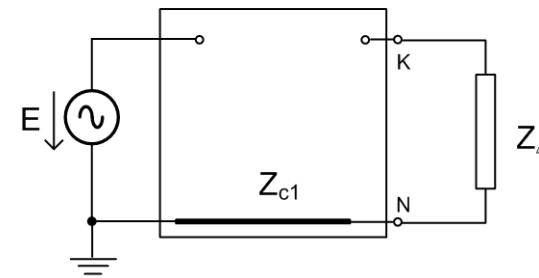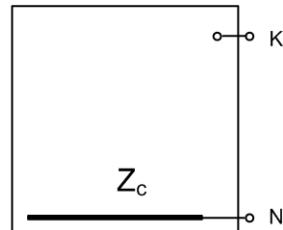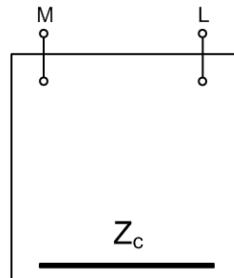Sources always by means of impedances to the ground.



Multiple unbalances in ES

Single-phase-to-ground short-circuit in phase B, reference phase A


$$(I_{120}) = (T^{-1})(I_{ABC}) = \frac{1}{3} \begin{pmatrix} 1 & \hat{a} & \hat{a}^2 \\ 1 & \hat{a}^2 & \hat{a} \\ 1 & 1 & 1 \end{pmatrix} \begin{pmatrix} 0 \\ \hat{I}_B \\ 0 \end{pmatrix} = \frac{1}{3} \begin{pmatrix} \hat{a}\hat{I}_B \\ \hat{a}^2\hat{I}_B \\ \hat{I}_B \end{pmatrix}$$

$$\hat{I}_1 = \hat{a}\hat{I}_0; \hat{I}_2 = \hat{a}^2\hat{I}_0; \hat{I}_0 = \frac{1}{3}\hat{I}_B$$

$$\hat{p}_0 = 1$$

$$\hat{p}_1 = \frac{\hat{I}_0}{\hat{I}_1} = \frac{1}{\hat{a}} = \hat{a}^2$$
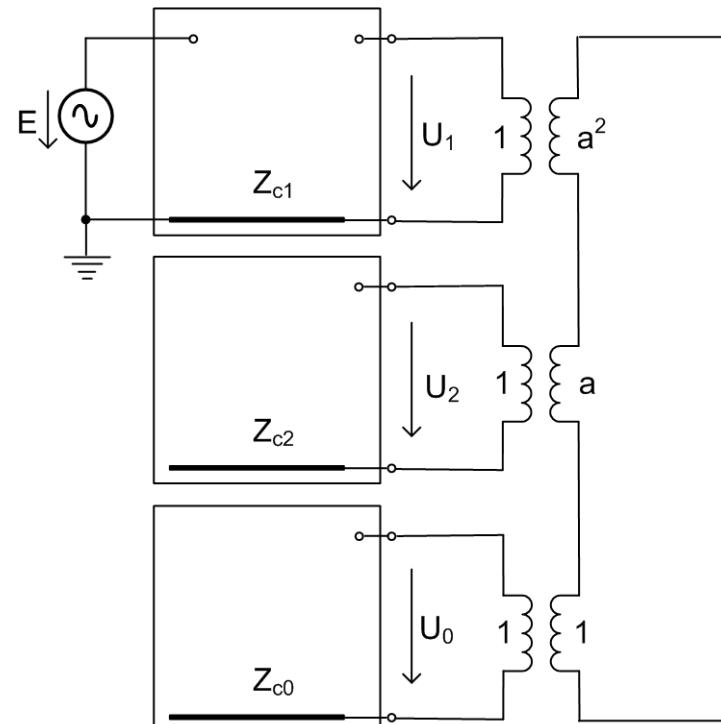
$$\hat{p}_2 = \frac{\hat{I}_0}{\hat{I}_2} = \frac{1}{\hat{a}^2} = \hat{a}$$



Note: TRF ratio (1ph)

$$\hat{u}_s = \hat{p}_u \hat{u}_p$$

$$\hat{i}_s = \hat{p}_i \hat{i}_p$$

power invariance

$$\hat{u}_s \cdot \hat{i}_s^* = \hat{p}_u \hat{u}_p \cdot \hat{p}_i^* \hat{i}_p^* = \hat{u}_p \cdot \hat{i}_p^*$$

$$\hat{p}_u = \frac{1}{\hat{p}_i^*}$$

If $\hat{p}_u = \hat{a}$ then $\hat{p}_i = \frac{1}{\hat{a}^*} = \frac{1}{\hat{a}^2} = \hat{a} = \hat{p}_u$.

It is valid for reference phase B

$$\hat{U}_1 = \hat{U}_{B1}, \hat{U}_2 = \hat{U}_{B2}, \hat{U}_0 = \hat{U}_{B0}$$

$$\hat{U}_A = \hat{a}\hat{U}_1 + \hat{a}^2\hat{U}_2 + \hat{U}_0$$



$$\hat{U}_B = \hat{U}_1 + \hat{U}_2 + \hat{U}_0$$

$$\hat{U}_C = \hat{a}^2\hat{U}_1 + \hat{a}\hat{U}_2 + \hat{U}_0$$

$$(T) = \begin{pmatrix} \hat{a} & \hat{a}^2 & 1 \\ 1 & 1 & 1 \\ \hat{a}^2 & \hat{a} & 1 \end{pmatrix} \quad (T^{-1}) = \frac{1}{3} \begin{pmatrix} \hat{a}^2 & 1 & \hat{a} \\ \hat{a} & 1 & \hat{a}^2 \\ 1 & 1 & 1 \end{pmatrix}$$

$$(I_{120}) = (T^{-1})(I_{ABC}) = \frac{1}{3} \begin{pmatrix} \hat{a}^2 & 1 & \hat{a} \\ \hat{a} & 1 & \hat{a}^2 \\ 1 & 1 & 1 \end{pmatrix} \begin{pmatrix} 0 \\ \hat{I}_B \\ 0 \end{pmatrix} = \frac{1}{3} \begin{pmatrix} \hat{I}_B \\ \hat{I}_B \\ \hat{I}_B \end{pmatrix}$$

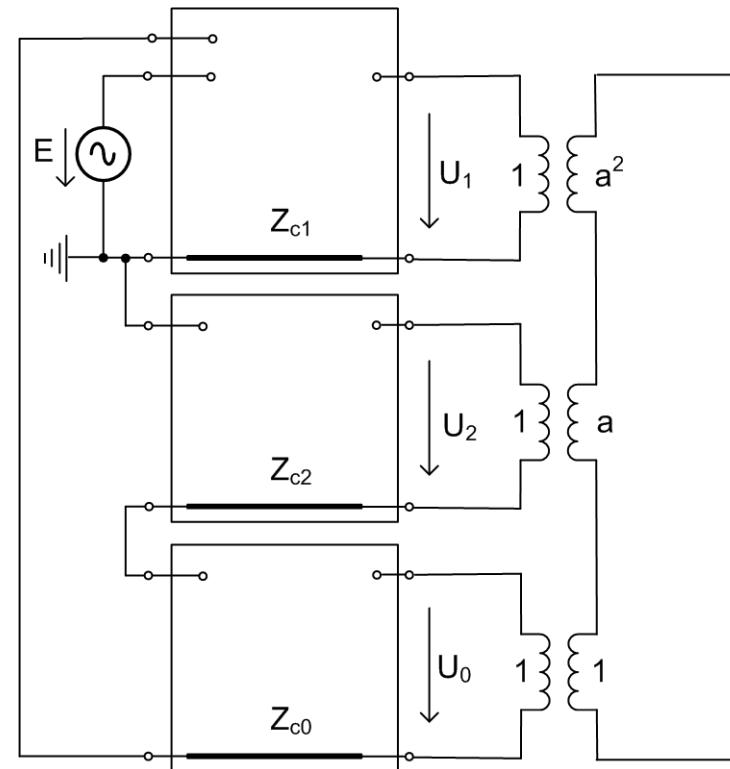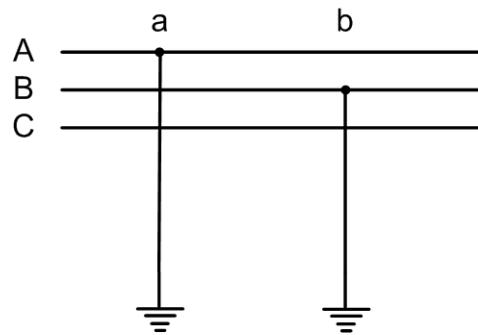
Two simultaneous single-phase-to-ground short-circuits in different ES places



More than 2 faults \rightarrow sequence diagrams interconnection is complicated \rightarrow rather calculation in phases.

Short-circuit impedance matrix

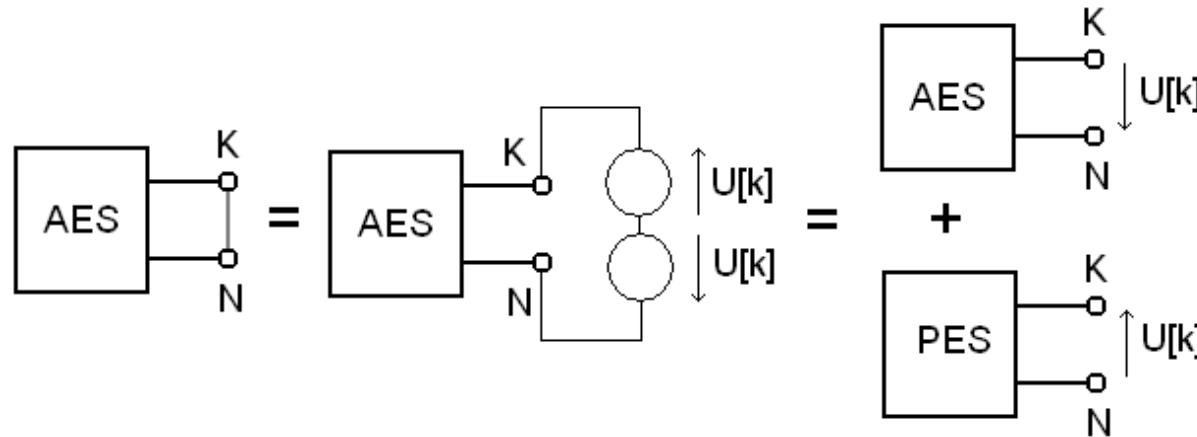- short-circuit is replaced by two sources with $U[k]$ voltage and the opposite orientation
- $U[k]$ voltage size equals to voltage value in the node k just before the fault
- superposition principle





- AES (active ES) => ES steady-state just before the short-circuit, sources modelled by an ideal voltage source and generator reactance
- PES (passive ES) => without sources: fault state, generators replaced only by sub-transient reactance against the ground

$$(I) = (Y)(U)$$

$$\hat{Y}_{(k,k)} = \sum_{m \in M_i} \hat{Y}_{km} \quad \hat{Y}_{(k,m)} = -\hat{Y}_{km}$$

ES simplified diagram

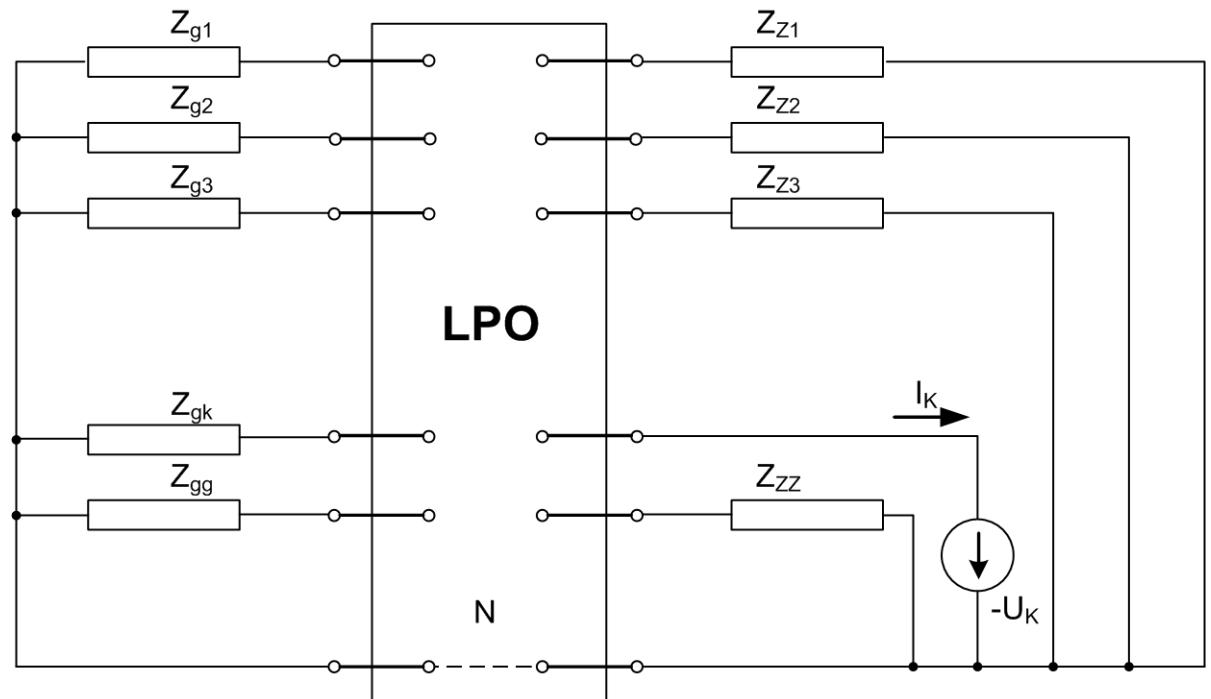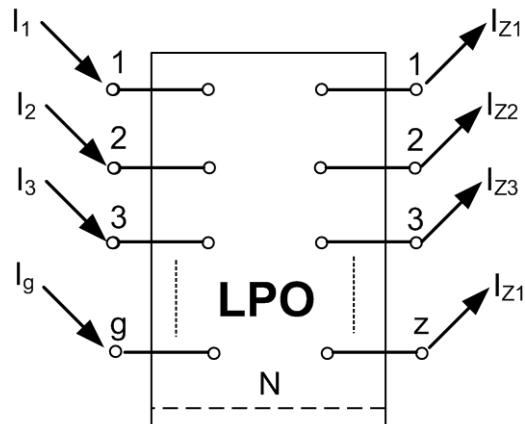- a) corresponding with node admittance matrix
- b) corresponding with short-circuit admittance matrix



All node currents are zero except the short-circuit place, here an ideal voltage source → short-circuit admittance matrix.

$$(I) = (Y_k)(U)$$

$$\begin{pmatrix} 0 \\ \vdots \\ -\hat{I}_k \\ \vdots \\ 0 \end{pmatrix} = (Y_k) \begin{pmatrix} \hat{U}_1 \\ \vdots \\ -\hat{U}_k \\ \vdots \\ \hat{U}_n \end{pmatrix}$$

Conversion to short-circuit impedance matrix

$$(U) = (Y_k)^{-1}(I) = (Z_k)(I)$$

$$\begin{pmatrix} \hat{U}_1 \\ \vdots \\ -\hat{U}_k \\ \vdots \\ \hat{U}_n \end{pmatrix} = \begin{pmatrix} \hat{Z}_{(1,1)} & & & & \hat{Z}_{(1,n)} \\ \vdots & \ddots & & & \vdots \\ & & \hat{Z}_{(k,k)} & & \vdots \\ & & & \ddots & \hat{Z}_{(n,n)} \\ \hat{Z}_{(n,1)} & & \cdots & & 0 \end{pmatrix} \begin{pmatrix} 0 \\ \vdots \\ -\hat{I}_k \\ \vdots \\ 0 \end{pmatrix}$$

Short-circuit current

$$\hat{I}_k = \frac{\hat{U}_k}{\hat{Z}_{(k,k)}}$$

$\hat{Z}_{(k,k)}$ short-circuit impedance in the node k

Voltage in any node

$$\hat{U}_j = -\hat{Z}_{(j,k)}\hat{I}_k$$

Current in a branch

$$\hat{I}_{ij} = \frac{\hat{U}_i - \hat{U}_j}{\hat{Z}_{ij}} = \frac{\hat{Z}_{(j,k)} - \hat{Z}_{(i,k)}}{\hat{Z}_{ij}} \hat{I}_k$$

\hat{Z}_{ij} impedance of the branch between the nodes i and j

Real node voltages and real branch currents during short-circuits are:

$$\text{fault} = \text{AES} + \text{PES}$$

$$I_{ij}^k = I_{(ij)} + I_{ij} \quad U_j^k = U_{(j)} + U_j$$

where: current in the branch between the nodes i and j , node j voltage

I_{ij}^k, U_j^k during short-circuit

$I_{(ij)}, U_{(j)}$ just before the short-circuit origin

I_{ij}, U_j self fault state

Short-circuit currents impacts

Mechanical impacts

Influence mainly at tightly placed stiff conductors, supporting insulators, disconnectors, construction elements,...

Forces frequency $2f$ at AC → dynamic strain.

Force on the conductor in magnetic field

$$F = B \cdot I \cdot l \cdot \sin \alpha \quad (\text{N})$$

$$B = \mu \cdot H \quad (\text{T})$$

$$\mu_0 = 4\pi \cdot 10^{-7} \quad (\text{H/m})$$

α – angle between mag. induction vector and the conductor axis
(current direction)

Magnetic field intensity in the distance a from the conductor

$$H = \frac{I}{2\pi a} \quad (\text{A/m})$$

2 parallel conductors → force perpendicular to the conductor axis
($\sin \alpha = 1$) → it is the biggest

$$F = 4\pi \cdot 10^{-7} \frac{I}{2\pi a} Il = 2 \cdot 10^{-7} \frac{I^2}{a} l \quad (\text{N})$$

The highest force corresponds to the highest immediate current value
→ peak short-circuit current I_{km} (1^{st} magnitude after s.-c. origin)

$$I_{km} = \sqrt{2} I''_{k0} \left(1 + e^{-0,01/T_k} \right) = \kappa \sqrt{2} I''_{k0} \quad (\text{A})$$

κ – peak coefficient according to grid type ($\kappa_{LV} = 1,8$; $\kappa_{HV} = 1,7$)
theoretical range $\kappa = 1 \div 2$

T_k – time constant of equivalent short-circuit loop (L_e/R_e)
i.e. for DC component of short-circuit current

I''_{k0} - initial sub-transient short-circuit current

Real value differs according to the short-circuit origin moment.
AC component decreasing slower than for DC therefore neglected.


Max. instantaneous force on the conductor length unit

$$f = 2 \cdot k_1 \cdot k_2 \cdot 10^{-7} \frac{I_{km}^2}{a} \text{ (N/m)}$$

k_1 – conductor shape coefficient

k_2 – conductors configuration and currents phase shift coefficient

a – conductors distance

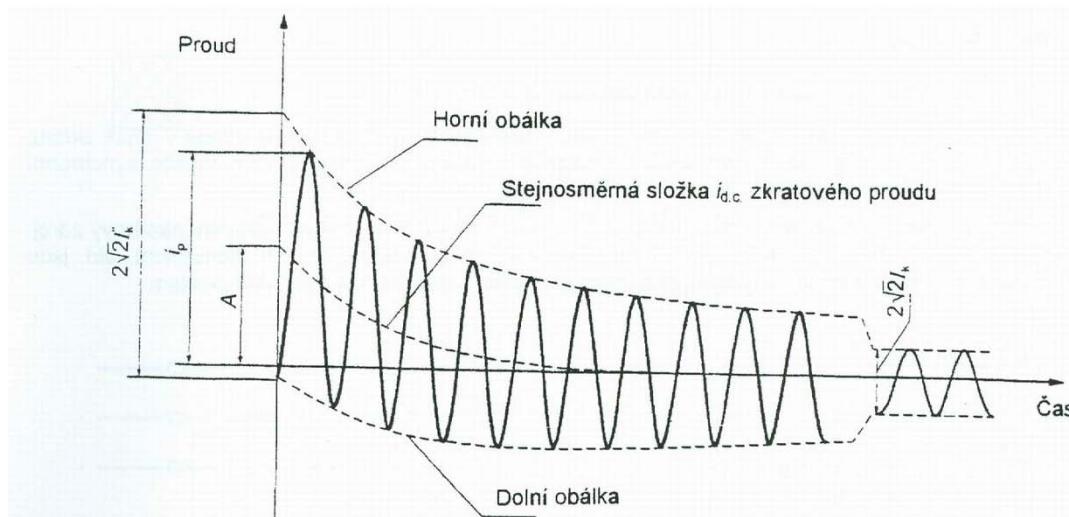

I_k'' je počáteční souměrný rázový zkratový proud

i_p nárazový zkratový proud

I_k ustálený zkratový proud

$i_{d.c.}$ stejnosměrná složka zkratového proudu

A počáteční hodnota stejnosměrné složky $i_{d.c.}$

Heat impacts

Key for dimensioning mainly at freely placed conductors.

They are given by heat accumulation influenced by time-changing current during short-circuit time t_k (adiabatic phenomenon).

Heat produced in conductors

$$Q = \int_0^{t_k} R(\vartheta) \cdot i_k^2(t) dt \quad (J)$$

Thermal equivalent current – current RMS value which has the same heating effect in the short-circuit duration time as the real short-circuit current

$$I_{ke}^2 t_k = \int_0^{t_k} i_k^2(t) dt$$

$$I_{ke} = \sqrt{\frac{1}{t_k} \int_0^{t_k} i_k^2(t) dt} \quad (A)$$

Calculation according to k_e coefficient as I''_k multiple

$$I_{ke} = k_e I''_k$$

Short-circuit duration time t_k (s)	Coefficient k_e		
	S.-c. on generator terminals	S.-c. in ES	
		HV, MV	LV
pod 0,05	1,70	1,60	1,50
0,05 – 0,1	1,60	1,50	1,20
0,1 – 0,2	1,55	1,40	1,10
0,2 – 1,0	1,50	1,30	1,05
1,0 – 3,0	1,30	1,10	1,00
nad 3,0	1,15	1,00	1,00