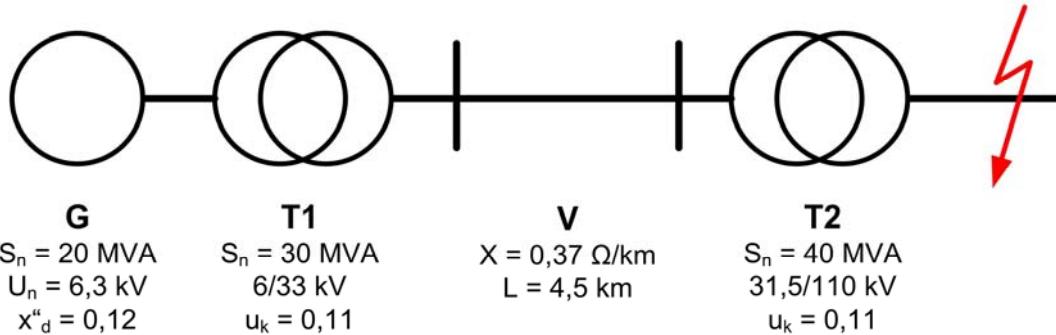


## Example 1

Three phase short-circuit is in the figure in the marked place.

- Calculate:
- Initial sub-transient short-circuit current
  - Initial sub-transient short-circuit power
  - Peak short-circuit current



### Solution:

- We choose a base power  $S_v = 110 \text{ MVA}$  and a base voltage  $U_v = 110 \text{ kV}$  (any value).
- We recalculate all reactances to the chosen base power  $S_v$  and the voltage in the short-circuit place  $U_v$ . This example doesn't have continuing voltage levels therefore we must respect transformer ratios.

Generator:

$$x_g = x_d'' \cdot \frac{S_v}{S_{ng}} \cdot \left( \frac{U_{ng}}{U_v} \right)^2 \cdot p_{T1}^2 \cdot p_{T2}^2 = 0,12 \cdot \frac{110}{20} \cdot \left( \frac{6,3}{110} \right)^2 \cdot \left( \frac{33}{6} \right)^2 \cdot \left( \frac{110}{31,5} \right)^2 = 0,799$$

Transformer T1

$$x_{T1} = x_k \cdot \frac{S_v}{S_{nT1}} \cdot \left( \frac{U_{nT1}}{U_v} \right)^2 \cdot p_{T2}^2 = 0,11 \cdot \frac{110}{30} \cdot \left( \frac{33}{110} \right)^2 \cdot \left( \frac{110}{31,5} \right)^2 = 0,443$$


Transformer T2

$$x_{T2} = x_k \cdot \frac{S_v}{S_{nT2}} \cdot \left( \frac{U_{nT2}}{U_v} \right)^2 = 0,11 \cdot \frac{110}{40} \cdot \left( \frac{110}{110} \right)^2 = 0,303$$


Power line V: (the denominated value recalculation to a relative value and then to  $S_v$  and  $U_v$ )

$$x_v = x \cdot l \cdot \frac{S_v}{U_v^2} \cdot p_{T2}^2 = 0,37 \cdot 4,5 \cdot \frac{110}{110^2} \cdot \left( \frac{110}{31,5} \right)^2 = 0,185$$

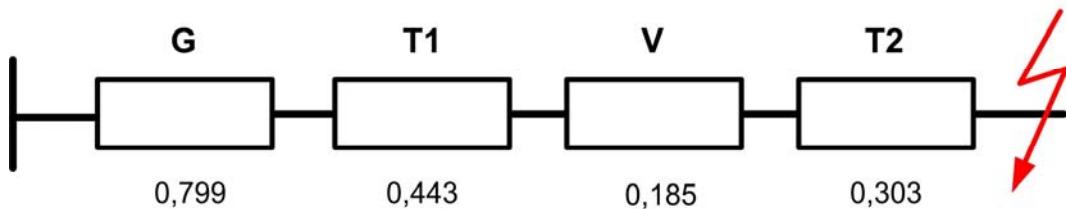3) We draw the equivalent circuit (only positive sequence for 3ph short-circuit)



4) After simplification:

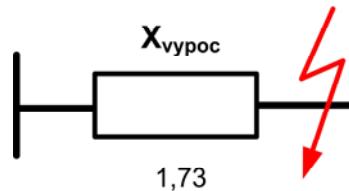

5) We calculate a base current

$$I_v = \frac{S_v}{\sqrt{3} \cdot U_v} = \frac{110}{\sqrt{3} \cdot 110} = 0,577 \text{ kA}$$

6) Initial sub-transient short-circuit current

$$I''_{k0} = k \cdot \frac{I_v}{X_{vypoc}} = 1,1 \cdot \frac{0,577}{1,73} = 0,367 \text{ kA}$$

7) Initial sub-transient short-circuit power

$$S''_{k0} = \sqrt{3} \cdot U_v \cdot I''_{k0} = \sqrt{3} \cdot 110 \cdot 0,367 = 69,9 \text{ MVA}$$

Or:

$$S''_{k0} = k \cdot \frac{S_v}{X_{vypoc}} = 1,1 \cdot \frac{110}{1,73} = 69,9 \text{ MVA}$$

6a) Initial sub-transient short-circuit current

$$I''_{k0} = \frac{S''_{k0}}{\sqrt{3} \cdot U_{sv}} = \frac{69,9}{\sqrt{3} \cdot 110} = 0,367 \text{ kA}$$

8) Peak short-circuit current

$$I_{km} = k \cdot \sqrt{2} \cdot I''_{k0} = 1,7 \cdot \sqrt{2} \cdot 0,367 = 0,882 \text{ kA}$$


factor  $k = 1,7$  for HV systems

## Example 2

Calculate initial sub-transient short-circuit power during three-phase short-circuit behind a transformer  $S_{nT} = 15 \text{ MVA}$ ,  $u_k = 10\%$ ,  $115/10,5 \text{ kV}$ . Transformer is connected to the power grid with initial sub-transient short-circuit power  $S''_{ks} = 3500 \text{ MVA}$ . If short-circuit occurs on the grid terminals, the grid contribution to the initial sub-transient short-circuit power is:


$$S''_{ks} = \frac{S_v}{x_s} = 3500 \text{ MVA}$$

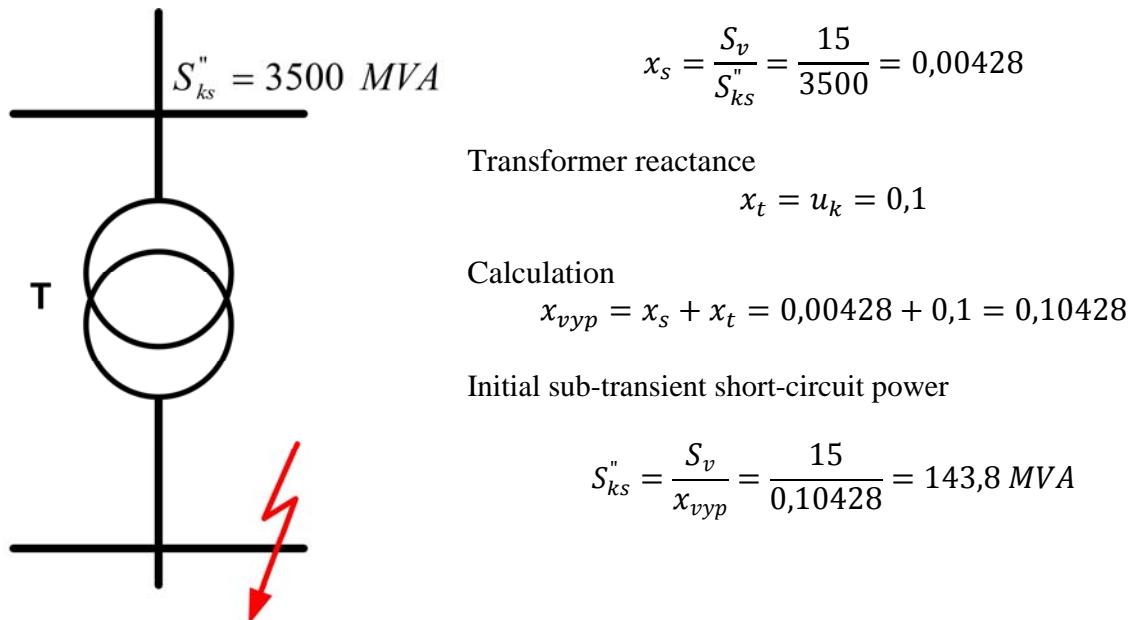We choose the base power  $S_v = S_{nT}$ . Power grid reactance is:


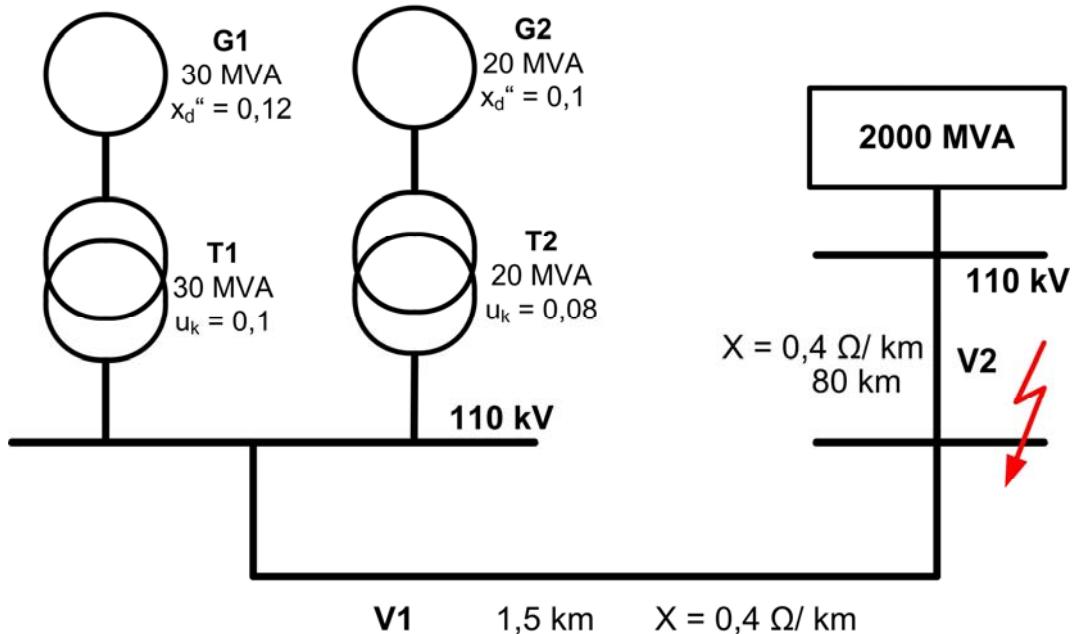
### Example 3

Calculate initial sub-transient short-circuit current and power in case of three phase short-circuit.



1) Base power and voltage:

$$S_v = 30 \text{ MVA}, U_v = 110 \text{ kV}$$

2) Reactances recalculation to the base power and voltage in the short-circuit place

$$\text{generator G1: } x_{G1} = 0,12$$

$$\text{generator G2: } x_{G2} = x_d'' \cdot \frac{S_v}{S_{nG2}} = 0,1 \cdot \frac{30}{20} = 0,15$$

$$\text{transformer T1: } x_{T1} = 0,1$$


$$\text{transformer T2: } x_{T2} = u_k \cdot \frac{S_v}{S_{nT2}} = 0,08 \cdot \frac{30}{20} = 0,12$$

$$\text{power line V1: } x_{V1} = x \cdot l \cdot \frac{S_v}{U_v^2} = 0,4 \cdot 1,5 \cdot \frac{30}{110^2} = 0,0015$$

$$\text{power line V2: } x_{V2} = X \cdot l \cdot \frac{S_v}{U_v^2} = 0,4 \cdot 80 \cdot \frac{30}{110^2} = 0,0793$$

$$\text{power grid: } x_S = 1,1 \cdot \frac{S_v}{S_{k0S}} = 1,1 \cdot \frac{30}{2000} = 0,0165$$

## 3) equivalent circuit

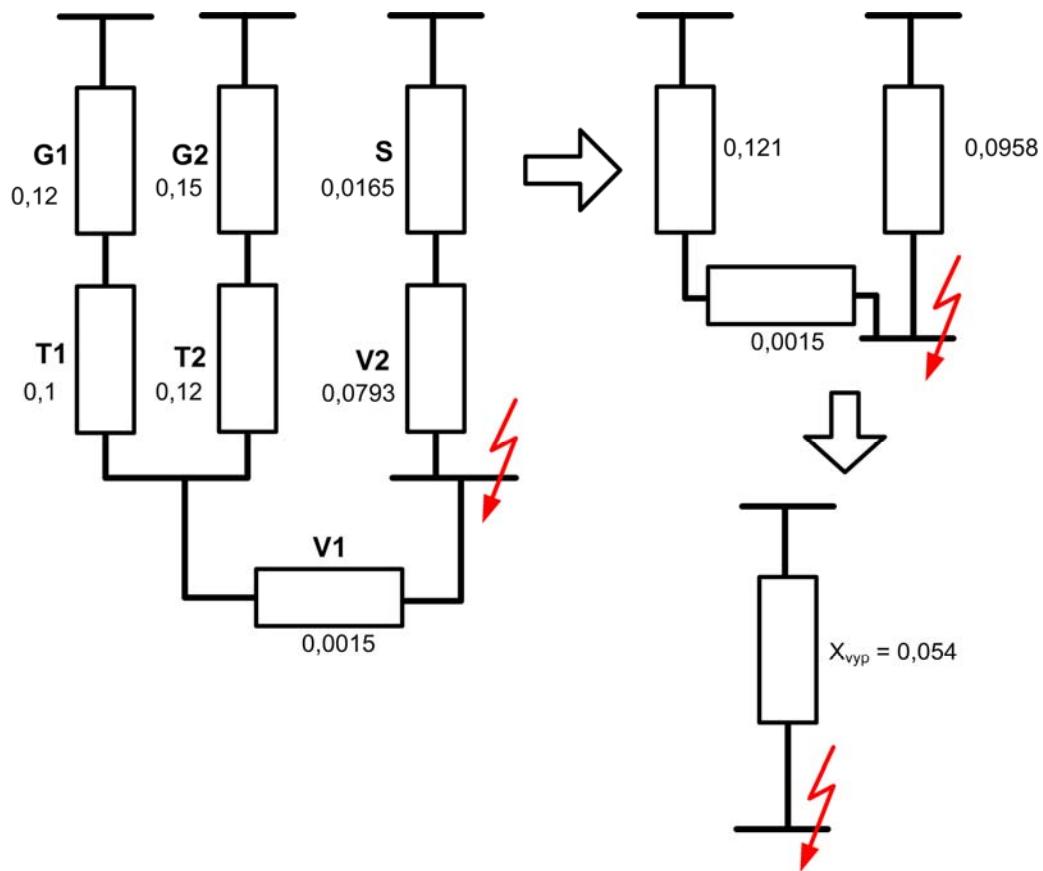

## 4) initial sub-transient short-circuit power

$$S''_{k0} = k \cdot \frac{S_v}{x_{vyp}} = 1,1 \cdot \frac{30}{0,054} = 611,1 \text{ MVA}$$

## 5) initial sub-transient short-circuit current

$$I''_{k0} = \frac{S''_{k0}}{\sqrt{3} \cdot 110} = 3,207 \text{ kA}$$