

## CONSEQUENCES OF REACTIVE POWER 1


- lower use of existing electrical distribution equipment (smaller transmitted active power),

$$P = S \cdot \cos \varphi = U \cdot I \cdot \cos \varphi \quad (\text{W}; \text{VA}, \text{V}, \text{A})$$


- higher costs of all equipment dimensioned according to the size of apparent power (transformers, circuit breakers, protections, measurement equipment)
- higher losses in electrical power distribution (the power losses depend on the square of apparent power)

$$P_{\text{ztr}} = 3R \cdot I^2 = 3R \cdot \left( \frac{S}{\sqrt{3}U} \right)^2 = \frac{R}{U^2} \cdot S^2 = \frac{R}{U^2} \cdot (P^2 + Q^2) \quad (\text{W})$$
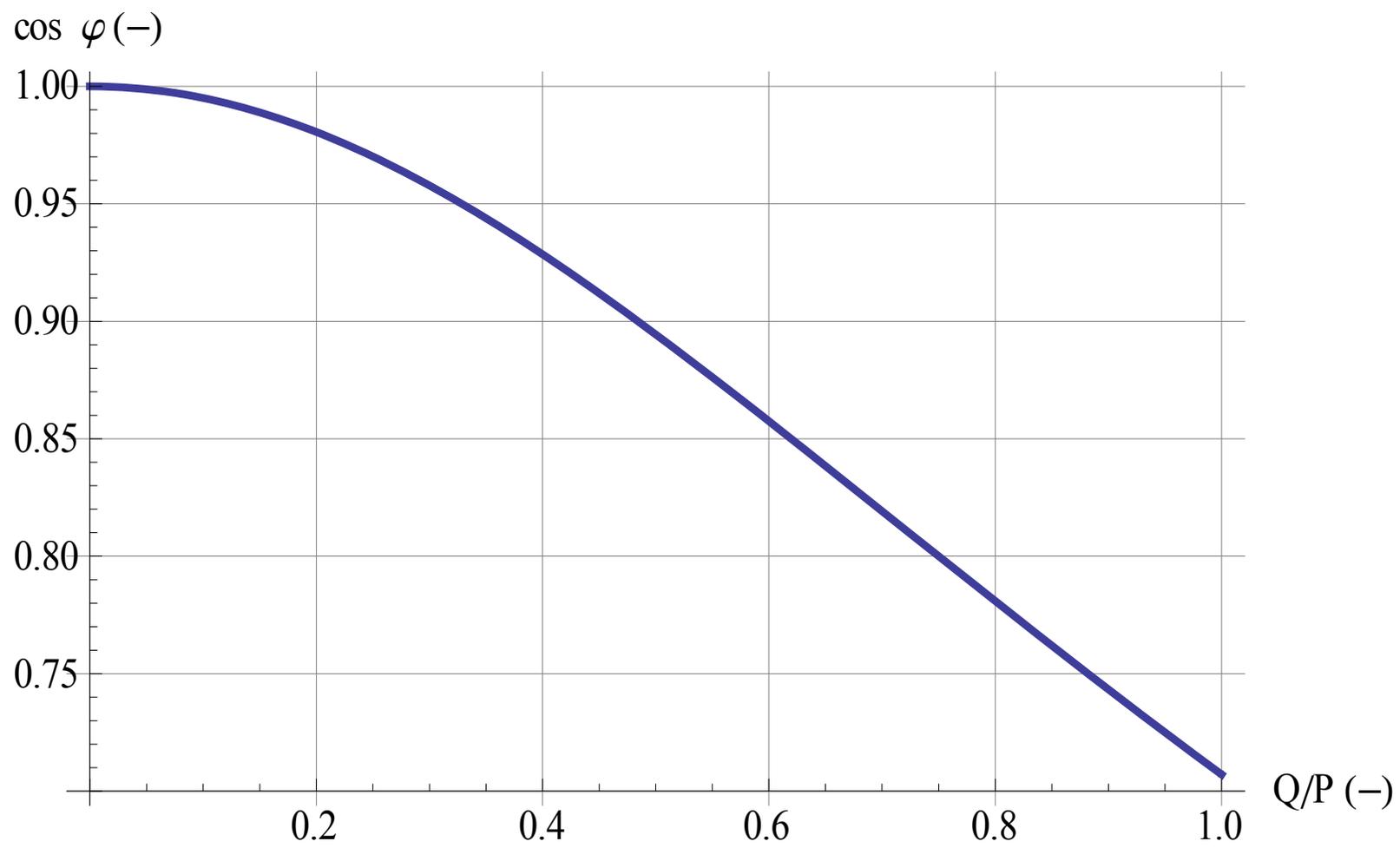
$$Q = P \cdot \text{tg} \varphi \rightarrow P_{\text{ztr}} = k \cdot (1 + \text{tg}^2 \varphi)$$


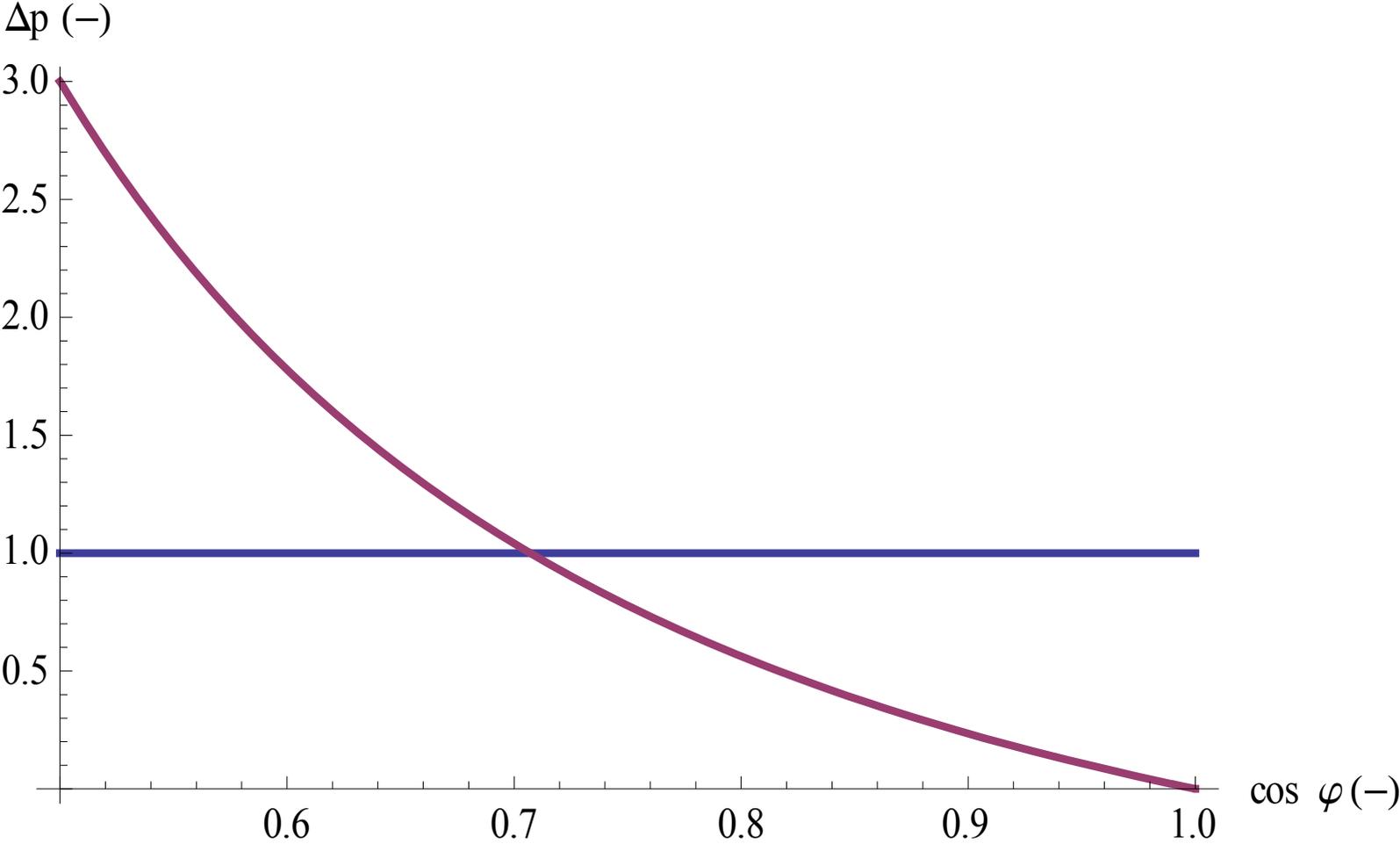
# The losses due to the active and reactive current component



## CONSEQUENCES OF REACTIVE POWER 2

- increase of voltage drops in the distribution system  
(increase of voltage fluctuation in the electricity grid)

$$\Delta U_f = R \cdot I_c \pm X \cdot I_j \quad (\text{V})$$

- the consequences also affect the size of the rate for the consumed electric energy payment. The distribution companies penalties large consumers with bad power factor.

## COMPENSATION AT CONSTANT ACTIVE POWER

Before compensation  $Q = \sqrt{3} \cdot U \cdot I \cdot \sin \varphi$

After compensation  $Q_k = \sqrt{3} \cdot U \cdot I_k \cdot \sin \varphi_k$  (VAr; V, A)

Compensation power

$$Q_c = Q - Q_k = \sqrt{3} \cdot U \cdot (I \cdot \sin \varphi - I_k \cdot \sin \varphi_k) \quad (\text{VAr; V, A})$$


$$I_{\xi} = I \cdot \cos \varphi = I_k \cdot \cos \varphi_k$$

Capacity value

$$I_{\text{kap}} = \frac{U}{X_{\text{kap}}} = U \cdot \omega \cdot C \quad (\text{A; V, } \Omega)$$

$$Q_c = Q_{\text{kap}} = \omega \cdot C \cdot U^2$$
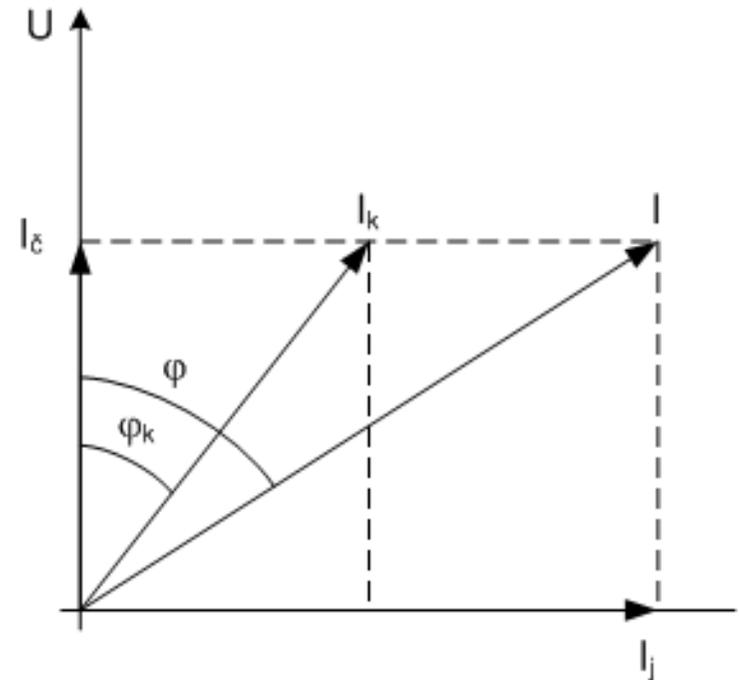
$$C = \frac{Q_c}{\omega \cdot U^2} \quad (\text{F; VAr, s}^{-1}, \text{V})$$



## COMPENSATION AT CONSTANT APPARENT POWER

Before compensation  $Q = \sqrt{3} \cdot U \cdot I \cdot \sin \varphi$

After compensation  $Q_k = \sqrt{3} \cdot U \cdot I \cdot \sin \varphi_k$  (VAr; V, A)

Compensation power

$$Q_c = Q - Q_k = \sqrt{3} \cdot U \cdot I \cdot (\sin \varphi - \sin \varphi_k)$$

$$I_{\check{c}k} = I_k \cdot \cos \varphi_k$$

Increase of active power

$$P = \sqrt{3} \cdot U \cdot I \cdot \cos \varphi$$

$$P_k = \sqrt{3} \cdot U \cdot I \cdot \cos \varphi_k$$

$$\begin{aligned} \Delta P &= P_k - P = \sqrt{3} \cdot U \cdot I \cdot (\cos \varphi_k - \cos \varphi) = \\ &= S \cdot (\cos \varphi_k - \cos \varphi) \quad (\text{W}; \text{V}, \text{A}) \end{aligned}$$

