


## Inductors and capacitors in ES

### a) Series inductors


- reactors are used to limit short-circuit currents → current limiting reactors
- used in grids up to 35 kV, single-phase ( $I_n > 200A$ ) or three-phase ( $I_n < 200A$ )
- usually air-cooled (small L, no mag. saturation x leakage, mag. field induced current nearby metal objects)
- L optimization (small – lower voltage drop, higher – SC reduction)
- In fault-free state the inductor can be bypassed by a fuse to reduce a voltage drop.
- the same design in LC filters for harmonics suppression, SVC (TCR)




## SVC (Static VAr Compensation)

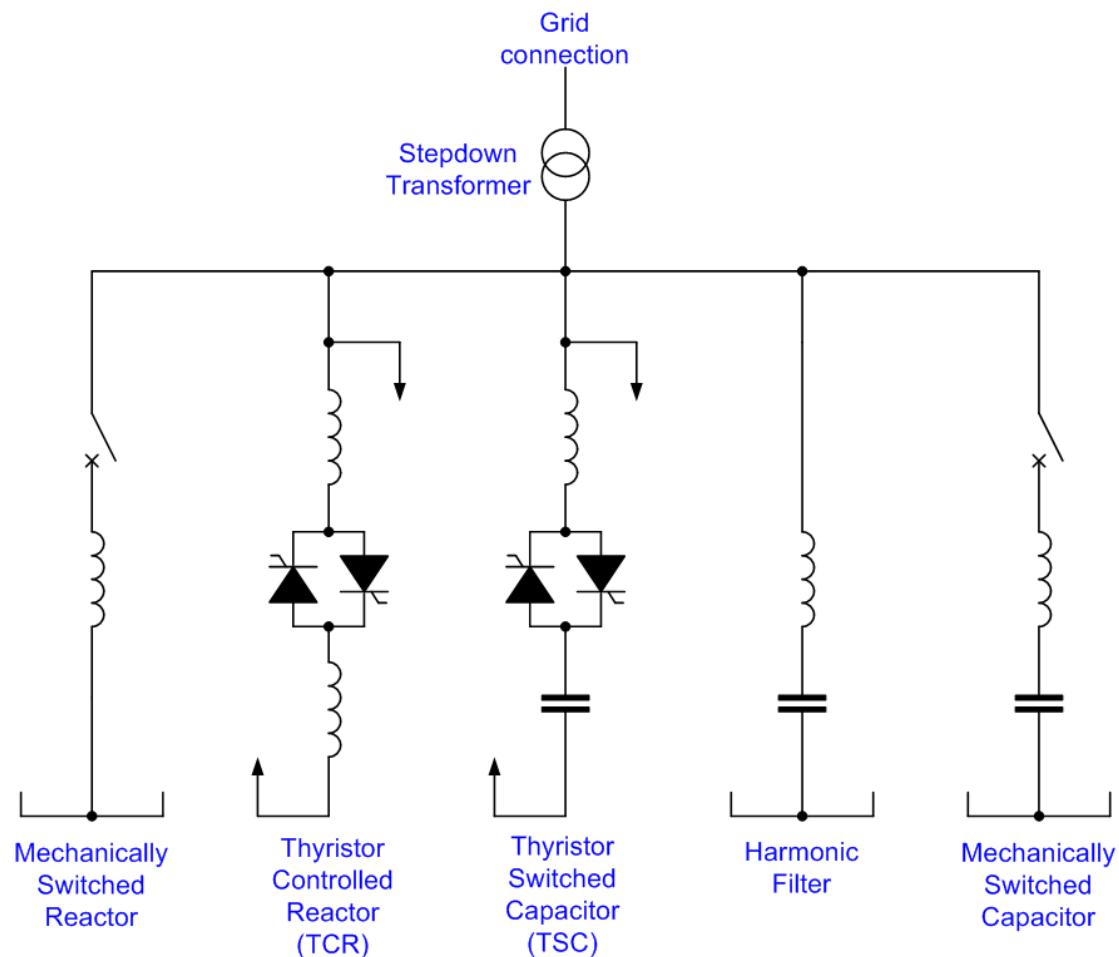

## TCR (Thyristor Controlled Reactor)

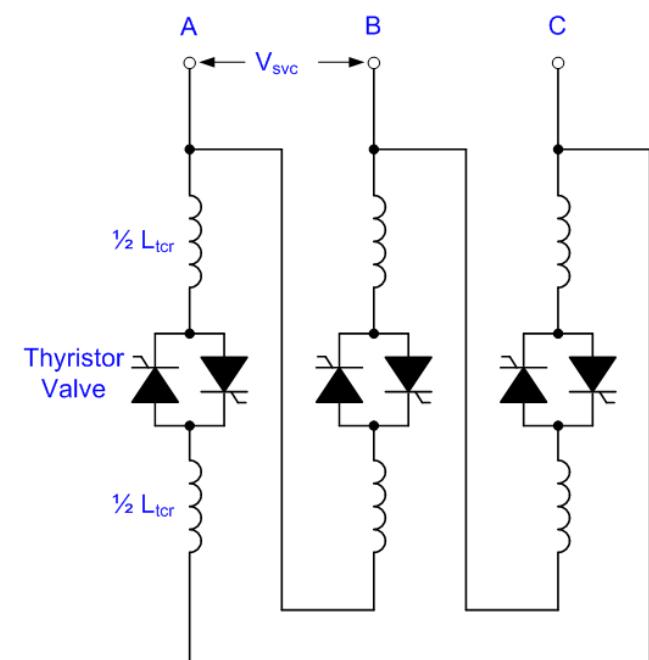



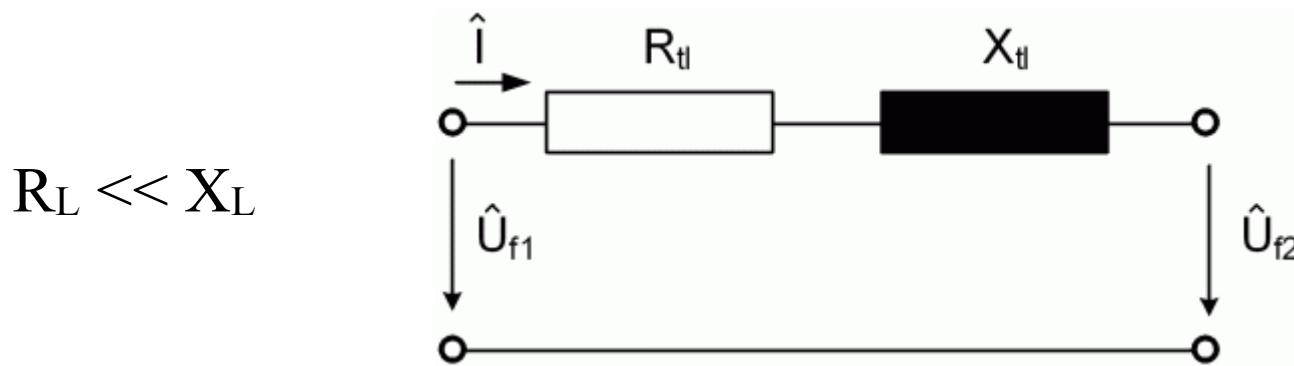

$$R_L \ll X_L$$

Input:  $X_{L\%}$ ,  $S_L$ ,  $U_n$ ,  $I_n$

Calculation:  $S_L = \sqrt{3} \cdot U_n \cdot I_n$

$$X_L = \frac{X_{L\%} \cdot U_n}{100 \cdot \sqrt{3} \cdot I_n} = \frac{X_{L\%} \cdot U_n^2}{100 \cdot S_L}$$

$$\Delta \hat{U}_f = \hat{U}_{f1} - \hat{U}_{f2} = (R_L + jX_L) \hat{I} = \hat{Z}_L \hat{I}$$

$\left[ \hat{Z}_{Labc} \right] = \hat{Z}_L \cdot [E]$  - 3ph inductor

→ self-impedance  $\hat{Z}_L$ , mutual impedances 0

## b) Shunt (parallel) inductors


- in the transmission systems (usually  $U_N > 220$  kV)
- oil cooling, Fe core
- used to compensate capacitive (charging) currents of long OHL for no-load or small loads → U control:

$$X_L = \frac{U_{L_n}}{\sqrt{3} \cdot I_{L_n}} = \frac{U_{L_n}^2}{Q_{L_n}}$$

$$[\hat{Z}_{Labc}] = \hat{Z}_L \cdot [E]$$

- Q: 15, 30, 55 MVA

Connection in the system:

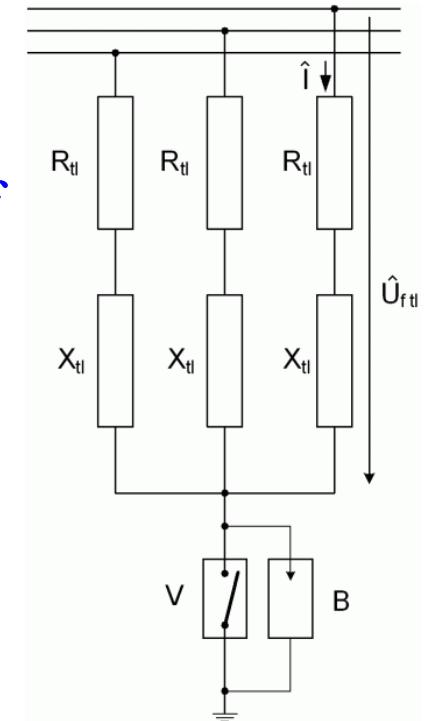


### a) galvanic connection to the line

- Y winding
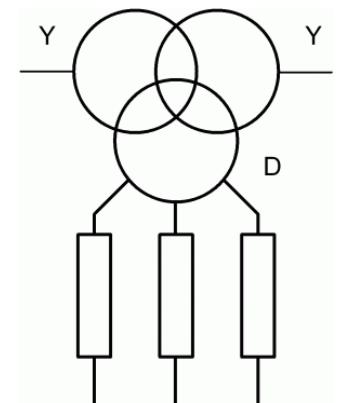
### b) inductor connection to transformer tertiary winding

- lower voltage  $U_n \approx 10 \div 35$  kV




## Kočín 400 kV



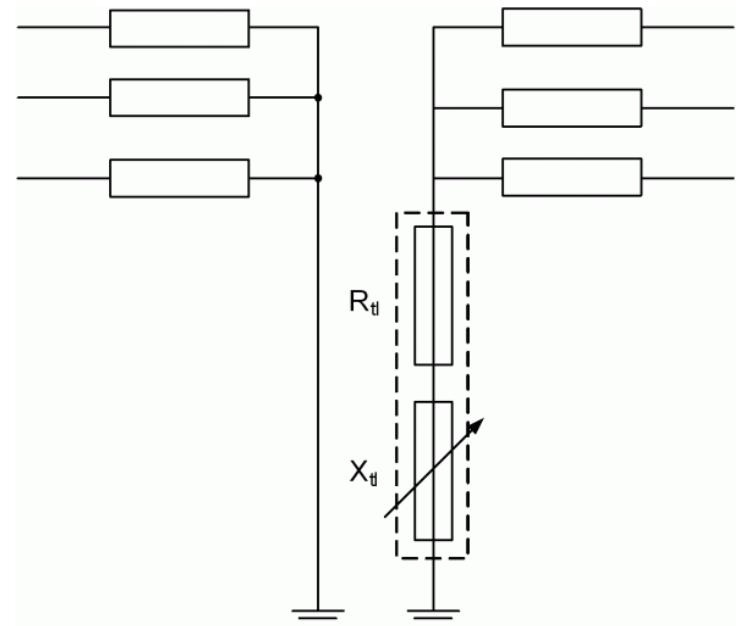
### c) Neutral point inductors

- used in networks with indirectly earthed neutral point to compensate currents during ground fault (capacitive currents)
- resonance compensation
- for distribution systems (6 to 35 kV)
- reactor is single-phased!, oil cooling
- capacitive current change (network reconfiguration) → change in inductance (air gap correction in the magnetic circuit)  
= arc-suppression coil (Peterson coil)

$$X_L = \frac{U_{\text{ph n}}}{I_{\text{Lset}}}$$






# 4 MVAr, 13 kV, Ostrava – Kunčice

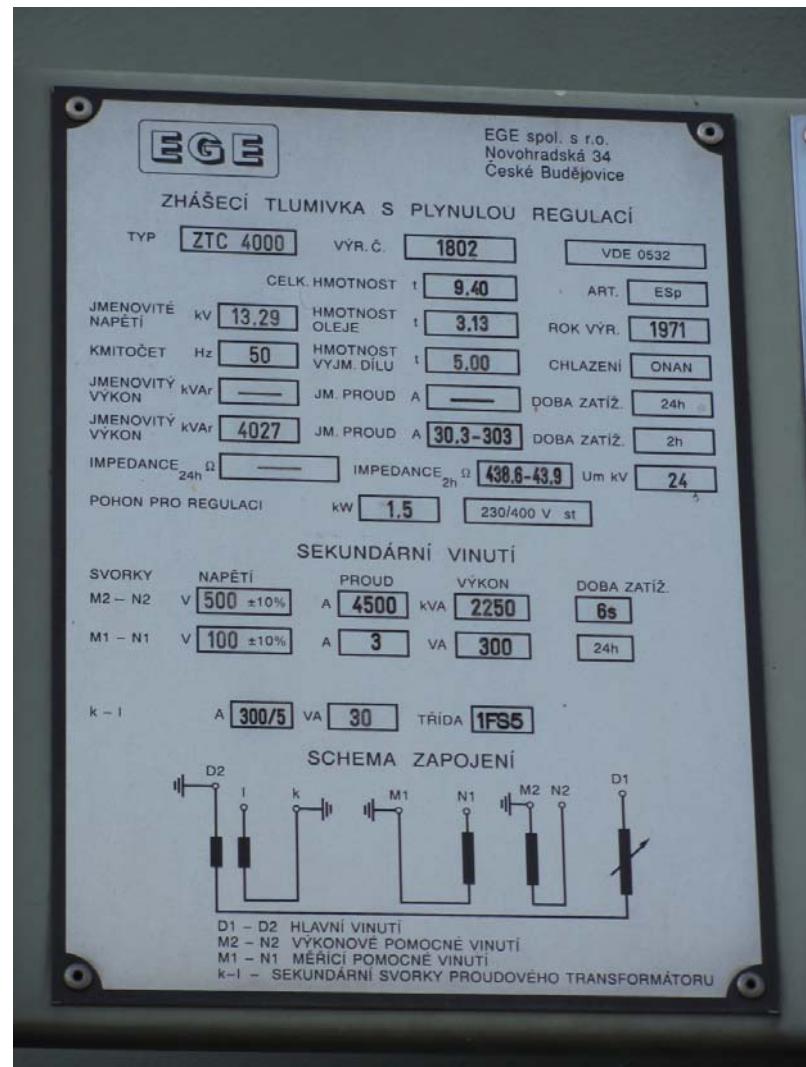
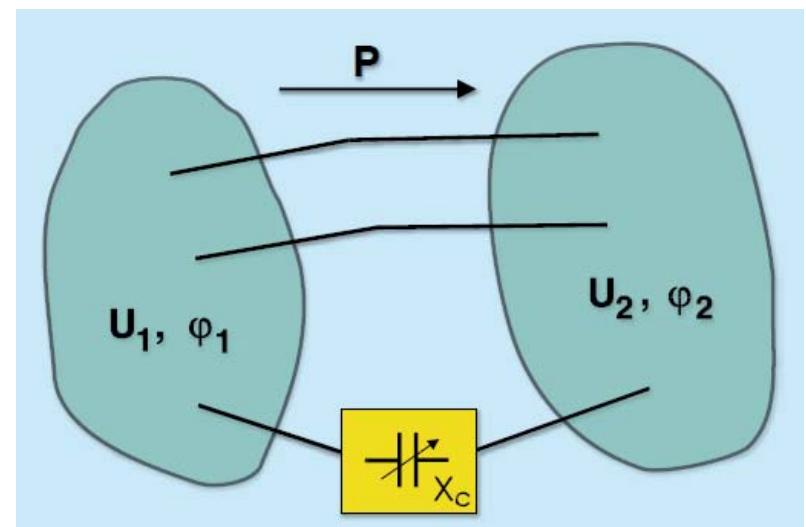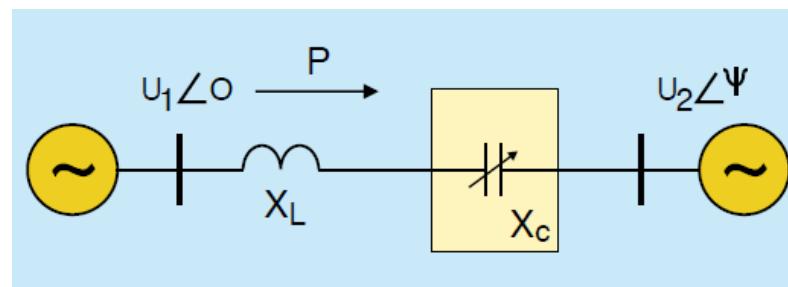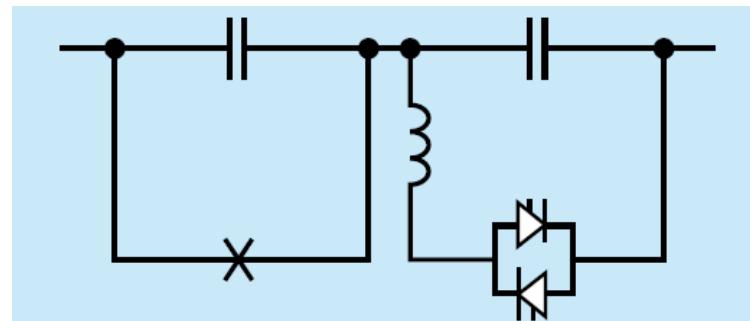
## d) Series capacitors

- capacitors in ES = capacitor banks
- in series → reduce TS line series inductance
- power flow control, voltage drop reduction, dynamic oscillation mitigation
- TCSR (Thyristor Controlled Series Capacitor)



$$\hat{U}_C = -j \frac{1}{\omega C} \hat{I}$$


- device installed on insulated platforms – C under voltage
- during short-circuits and overcurrents there appears overvoltage on the capacitor (very fast protections are used)

Canada 750 kV


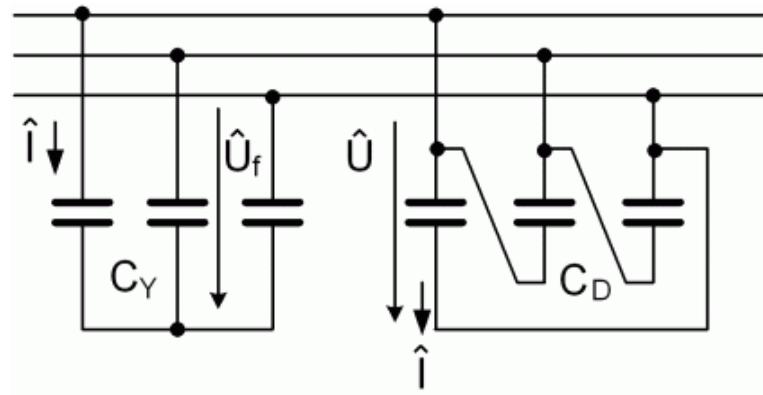
## e) Shunt capacitors

- used in LV industrial networks (up to 1 kV)
- connection:
  - a) wye - Y
  - b) delta -  $\Delta$  (D)



$$Q_f = U_f \cdot I_C = U_f^2 \omega C_Y \quad Q_f = U \cdot I_C = U^2 \omega C_\Delta$$

$$Q = 3U_f^2 \omega C_Y = U^2 \omega C_Y \quad Q = 3U^2 \omega C_\Delta$$


- with the same reactive power

$$U^2 \omega C_Y = 3U^2 \omega C_\Delta \rightarrow C_Y = 3C_\Delta \rightarrow \text{rather delta}$$



- power factor improvement, lower power losses, voltage drops
- individual or group compensation could be used
- shunt – also in harmonic filter (mainly MV, or SVC to HV via transformer)


## Transformer Concept in CR

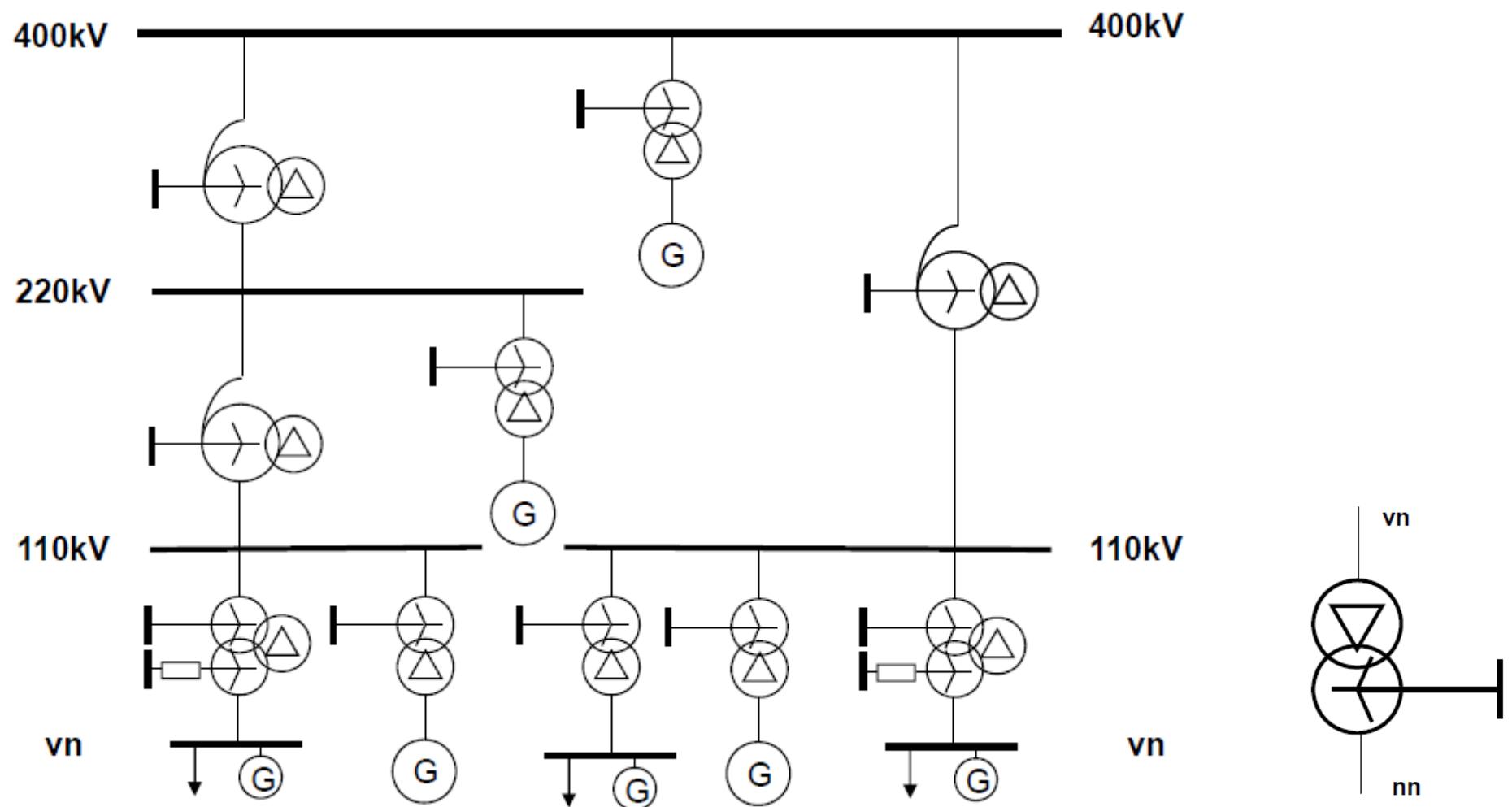

- voltages, neutral point grounding, winding connection + D winding

## Transformers in ES

DTS 22/0,4 kV (35/0,4 kV)

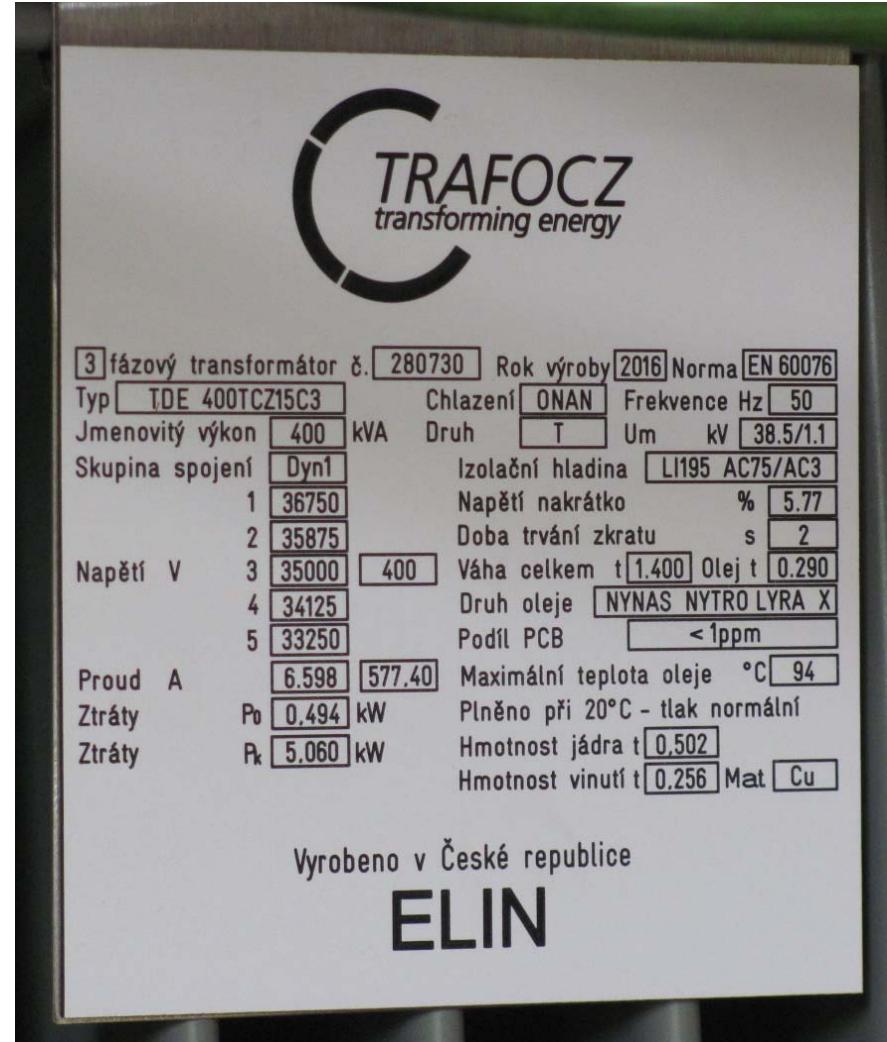



## Industrial (22/6 kV)




110/22 kV





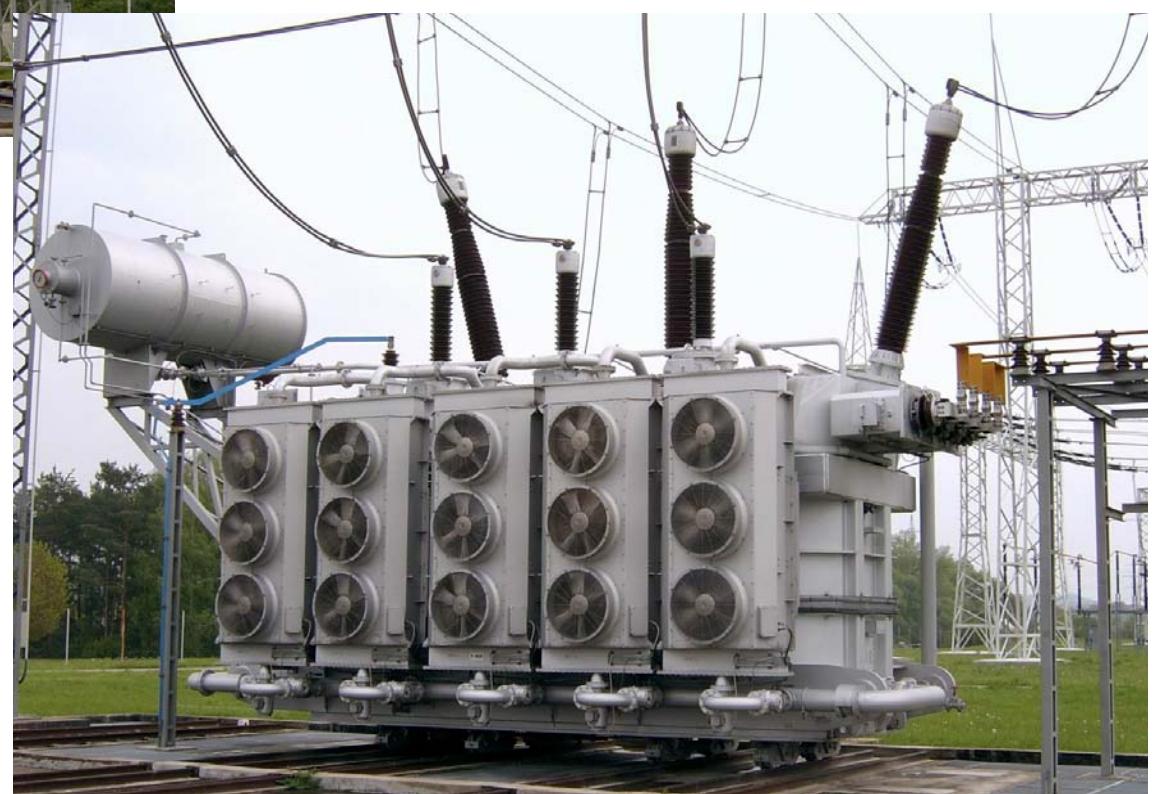350 MVA, 400/110 kV  
YNauto - d1, Sokolnice



## Construction Issues

- winding material (Al, Cu)
- winding connection (D, Y, Z)
- clock hour number (phasor group) (1-11)
- core material (standard, amorphous) → no load losses
- tank (oil, dry)
- cooling (oil, air) – e.g. ONAN, OFAF
- noise
- weight
- voltage levels, ratio
- power
  - DTS: **50, 63, 100, 160, 250, 400, 500, 630, 800, 1000, 1250, 1600, 2000, 2500, 4000 kVA**
  - 110 kV/MV: 10, 16, **25, 40, 50, 63 MVA**
  - HV/MV: 66, 200, **250, 350**
- parameters ...

## a) Two-winding transformers

- winding connection Y, Yn, D, Z, Zn, V

Yzn – distribution TRF MV/LV up to 250 kVA, for unbalanced load









Dyn – distribution TRF MV/LV from 400 kVA

YNyd – power grid transformer (e.g. 110/23/6,3 kV)

Yna-d, YNynd – power grid transformer (400, 220, 110 kV)

Yd – block TRF in power plants, the 3<sup>rd</sup> harmonic suppression

- clock hour number (phasor group)

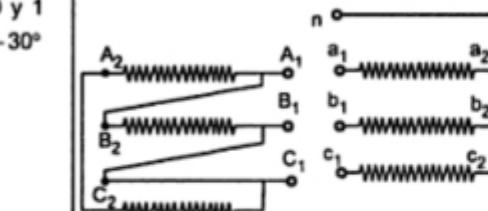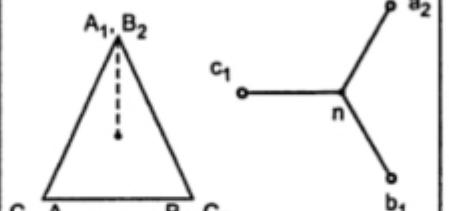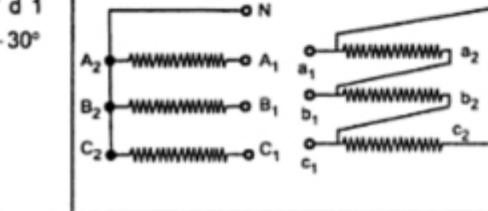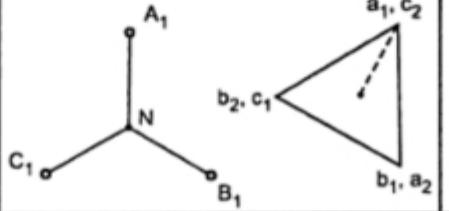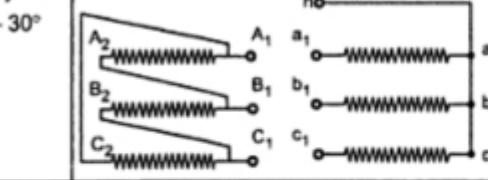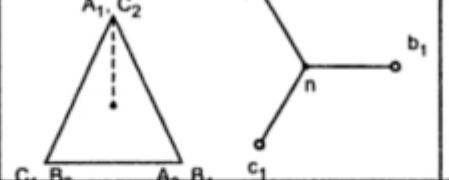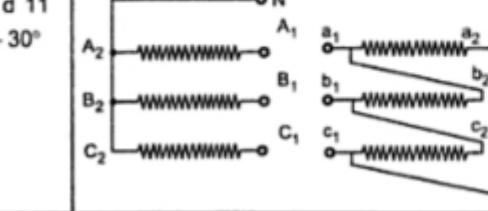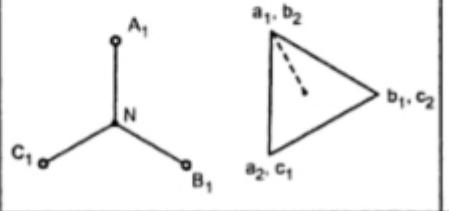
Sr. No.	Symbol	Windings and terminals	EMF vector diagrams	Equivalent clock method representation
5.	D y 1 -30°			
6.	Y d 1 -30°			
7.	D y 11 +30°			
8.	Y d 11 +30°			

- equivalent circuit: T – network

$$\hat{Z}_{\sigma p} = R_p + jX_{\sigma p}$$

$$\hat{Z}_{\sigma s} = R_s + jX_{\sigma s}$$

$$\hat{Y}_q = G_q - jB_q$$

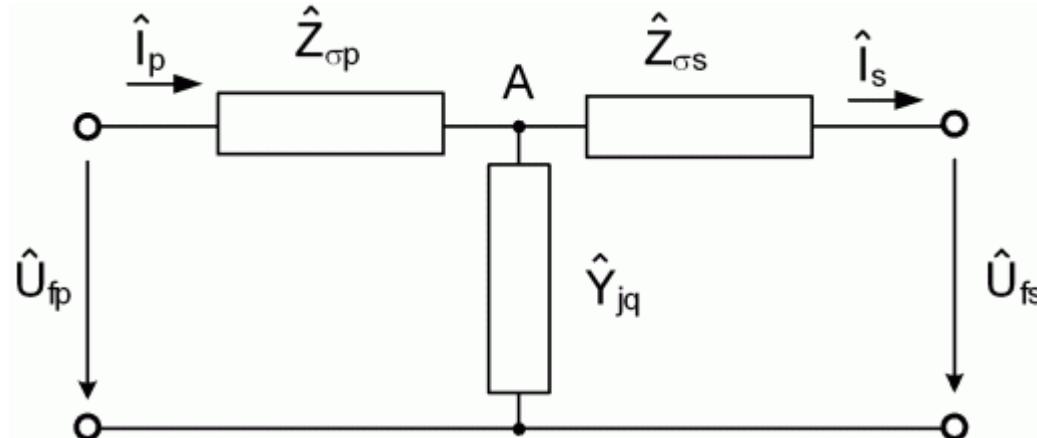

- each phase can be considered separately (unbalance is neglected)
- further operational impedance discussed
- values of the parameters are calculated, then verified by two tests
  - o *no-load test* – secondary winding open, primary winding supplied by rated voltage, no-load current is flowing (lower than rated current)
  - o *short-circuit test* – secondary winding short-circuited, primary winding supplied by short-circuit voltage (lower than rated voltage), so that rated current is flowing

$\Delta P_0$  (W),  $i_0$  (%),  $\Delta P_k$  (W),  $z_k = u_k$  (%),  $S_n$  (VA),  $U_n$  (V)

$u_k \approx 4 \div 17\%$  (increases with TRF power)

$p_k \approx 0,1 \div 1\%$  (decreases with TRF power)

$p_0 \approx 0,01 \div 0,1\%$  (decreases with TRF power)

- shunt branch:

$$g_q = \frac{\Delta P_0}{S_n} \quad y_q = \frac{i_{0\%}}{100} \quad b_q = \sqrt{y_q^2 - g_q^2}$$

$$\hat{y}_q = \frac{\Delta P_0}{S_n} - j \sqrt{\left(\frac{i_{0\%}}{100}\right)^2 - \left(\frac{\Delta P_0}{S_n}\right)^2} = g_q - j \cdot b_q$$

$$\hat{Y}_q = \hat{y}_q \frac{S_n}{U_n^2} = \frac{S_n}{U_n^2} \left[ \frac{\Delta P_0}{S_n} - j \sqrt{\left(\frac{i_{0\%}}{100}\right)^2 - \left(\frac{\Delta P_0}{S_n}\right)^2} \right] = G_q - j \cdot B_q$$

- series branch:

$$r_k = \frac{\Delta P_k}{S_n} \quad z_k = \frac{u_{k\%}}{100} \quad x_k = \sqrt{z_k^2 - r_k^2}$$

$$\hat{z}_k = \frac{\Delta P_k}{S_n} + j \sqrt{\left(\frac{u_{k\%}}{100}\right)^2 - \left(\frac{\Delta P_k}{S_n}\right)^2} = r_k + j \cdot x_k$$

$$\hat{Z}_k = \hat{z}_k \frac{U_n^2}{S_n} = \frac{U_n^2}{S_n} \left[ \frac{\Delta P_k}{S_n} + j \sqrt{\left(\frac{u_{k\%}}{100}\right)^2 - \left(\frac{\Delta P_k}{S_n}\right)^2} \right] = R_k + j \cdot X_k$$

$$\hat{Z}_{\sigma ps} = \hat{Z}_k = (R_p + R_s) + j(X_{\sigma p} + X_{\sigma s})$$

- we choose  $\hat{Z}_{\sigma p} = 0,5 \hat{Z}_{\sigma ps} = \hat{Z}_{\sigma s}$

- this division is not physically correct (different leakage flows, different resistances)



3	fázový transformátor č.	280730	Rok výroby	2016	Norma	EN 60076
Typ	TDE 400TCZ15C3		Chlazení	ONAN	Frekvence Hz	50
Jmenovitý výkon	400	KVA	Druh	T	Um	38.5/1.1
Skupina spojení	Dyn1		Izolační hladina	LI195	AC75/AC3	
	1	36750	Napětí nakrátko	%	5.77	
	2	35875	Doba trvání zkratu	s	2	
Napětí V	3	35000	Váha celkem t	1.400	Olej t	0.290
	4	34125	Druh oleje	NYNAS NYTRO LYRA X		
	5	33250	Podíl PCB	< 1ppm		
Proud A	6.598	577.40	Maximální teplota oleje °C	94		
Ztráty Po	0.494	kW	Plněno při 20°C - tlak normální			
Ztráty Pk	5.060	kW	Hmotnost jádra t	0.502		
			Hmotnost vinutí t	0.256	Mat	Cu

Vyrobeno v České republice

**ELIN**

## Transformer losses and efficiency

$$\Delta P_0 \approx U - \text{constant during operation}$$

$$\Delta P_k \cong R \cdot I^2 \approx I^2 - \text{changing during operation}$$

- efficiency  $\eta = \frac{P_{\text{out}}}{P_{\text{in}}} = 1 - \frac{\Delta P_0 + \Delta P_k}{P_{\text{in}}}$

$$\eta = 1 - \frac{\Delta P_0 + R \cdot I^2}{U_n \cdot I \cdot \cos \varphi} = 1 - \frac{\Delta P_0}{U_n \cdot I \cdot \cos \varphi} - \frac{R \cdot I}{U_n \cdot \cos \varphi}$$

$$\frac{d\eta}{dI} = 0 + \frac{\Delta P_0}{U_n \cdot I^2 \cdot \cos \varphi} - \frac{R}{U_n \cdot \cos \varphi} ! = 0$$

$$\frac{\Delta P_0}{U_n \cdot I^2 \cdot \cos \varphi} ! = \frac{R}{U_n \cdot \cos \varphi}$$



$$\Delta P_0 ! = R I^2 = \Delta P_k$$

## b) Three-winding transformers

- parameters are calculated, then verified by no-load and short-circuit measurements (3 short-circuit tests: 1 winding no-load, 1 short-circuit and 1 supplied):

$$\Delta P_0 \text{ (W)}, i_0 (\%), \Delta P_k \text{ (W)}, z_K = u_K (\%), S_n \text{ (VA)}, U_n \text{ (V)}$$

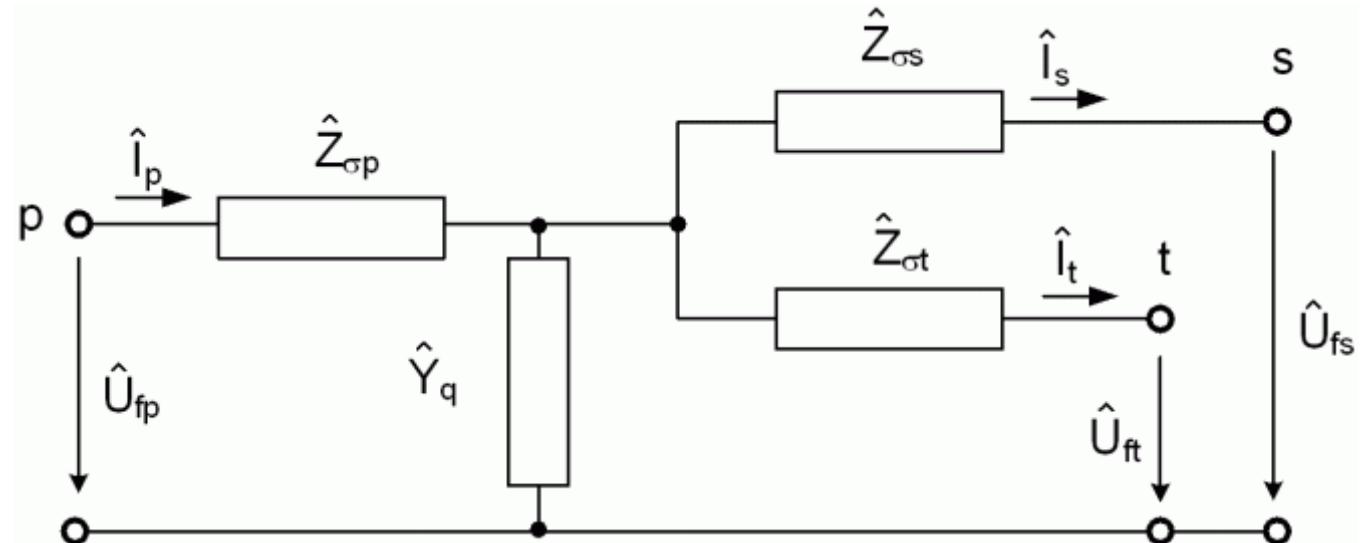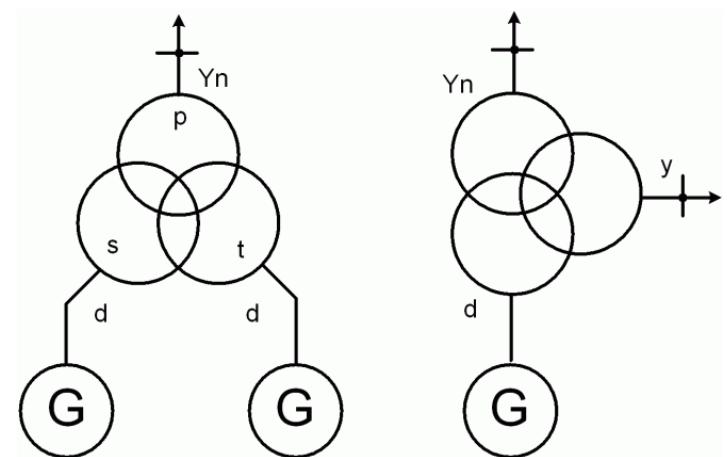- powers needn't be the same:  $S_{Sn} = S_{Tn} = 0,5 \cdot S_{Pn}$
- equivalent circuit:



- no-load measurement:

related to the primary rated power and rated voltage  $S_{Pn}$  a  $U_{PN}$  (supplied)

$$\hat{y}_q = g_q - j \cdot b_q = \frac{\Delta P_0}{S_{Pn}} - j \sqrt{\left(\frac{i_{0\%}}{100}\right)^2 - \left(\frac{\Delta P_0}{S_{Pn}}\right)^2}$$

denominated value ( $S$ ) – related to  $U_{PN}$

$$\hat{Y}_q = \hat{y}_q \frac{S_{Pn}}{U_{Pn}^2} = G_q - j \cdot B_q = \frac{S_{Pn}}{U_{Pn}^2} \left[ \frac{\Delta P_0}{S_{Pn}} - j \sqrt{\left(\frac{i_{0\%}}{100}\right)^2 - \left(\frac{\Delta P_0}{S_{Pn}}\right)^2} \right]$$

- short-circuit measurement: (3x, supply – short-circuit – no-load)  
provided:  $S_{Pn} \neq S_{Sn} \neq S_{Tn}$

measurement between	P - S	P - T	S - T
short-circuit losses (W)	$\Delta P_{kPS}$	$\Delta P_{kPT}$	$\Delta P_{kST}$
short-circuit voltage (%)	$u_{kPS}$	$u_{kPT}$	$u_{kST}$
measurement corresponds to power (VA)	$S_{Sn}$	$S_{Tn}$	$S_{Tn}$

short-circuit tests S – T:

parameter to be found:

$$\hat{Z}_{ST} = \hat{Z}_{oS} + \hat{Z}_{oT} \quad (\hat{Z}_{oS} = R_S + j \cdot X_{oS}) \text{ - recalculated to } U_{PN}$$

$$\hat{z}_{ST} = \hat{z}_{oS} + \hat{z}_{oT} \text{ - recalculated to } U_{PN}, S_{PN}$$

$$\Delta P_k \text{ for } I_{Tn} \rightarrow \Delta P_{kST} = 3 \cdot R^+_{ST} \cdot I_{Tn}^2, \quad I_{Tn} = \frac{S_{Tn}}{\sqrt{3} \cdot U_{Tn}}$$

$R^+_{ST}$ ...resistance of secondary and tertiary windings (related to  $U_{Tn}$ )

$$R^+_{ST} = \frac{\Delta P_{kST}}{S_{Tn}^2} \cdot U_{Tn}^2$$

$$R_{ST} = R^+_{ST} \cdot \frac{U_{Pn}^2}{U_{Tn}^2} \rightarrow R_{ST} = R_S + R_T = \frac{\Delta P_{kST}}{S_{Tn}^2} \cdot U_{Pn}^2$$

$R_S$  ( $R_T$ )...resistance of sec. and ter. windings recalculated to primary

$$r_{ST} = R_{ST} \cdot \frac{S_{PN}}{U_{Pn}^2} = \frac{\Delta P_{kST}}{S_{Tn}^2} \cdot S_{Pn}$$

- impedance:

$$z_{ST} = \frac{u_{kST\%}}{100} \cdot \frac{S_{Pn}}{S_{Tn}}, \quad Z_{ST} = z_{ST} \cdot \frac{U_{Pn}^2}{S_{Pn}} = \frac{u_{kST\%}}{100} \cdot \frac{U_{Pn}^2}{S_{Tn}}$$

$$\hat{Z}_{ST} = r_{ST} + j \cdot x_{ST}, \quad x_{ST} = \sqrt{Z_{ST}^2 - r_{ST}^2}, \quad x_{ST} = x_{\sigma S} + x_{\sigma T}$$

- based on the derived relations we can write:

P - S:

$$\hat{Z}_{PS} = r_{PS} + j \cdot x_{PS} = \frac{\Delta P_{kPS}}{S_{Sn}^2} \cdot S_{Pn} + j \cdot \sqrt{\left( \frac{u_{kPS\%}}{100} \cdot \frac{S_{Pn}}{S_{Sn}} \right)^2 - \left( \frac{\Delta P_{kPS}}{S_{Sn}^2} \cdot S_{Pn} \right)^2}$$

$$\hat{Z}_{PS} = R_{PS} + j \cdot X_{PS} = \frac{\Delta P_{kPS}}{S_{Sn}^2} \cdot U_{Pn}^2 + j \cdot \sqrt{\left( \frac{u_{kPS\%}}{100} \cdot \frac{U_{Pn}^2}{S_{Sn}} \right)^2 - \left( \frac{\Delta P_{kPS}}{S_{Sn}^2} \cdot U_{Pn}^2 \right)^2}$$

- analogous for P – T and S – T

- leakage reactances for P, S, T:

$$\hat{Z}_{\sigma P} = R_P + j \cdot X_{\sigma P} = 0,5 \cdot (\hat{Z}_{PS} + \hat{Z}_{PT} - \hat{Z}_{ST})$$

$$\hat{Z}_{\sigma S} = R_S + j \cdot X_{\sigma S} = 0,5 \cdot (\hat{Z}_{PS} + \hat{Z}_{ST} - \hat{Z}_{PT})$$

$$\hat{Z}_{\sigma T} = R_T + j \cdot X_{\sigma T} = 0,5 \cdot (\hat{Z}_{PT} + \hat{Z}_{ST} - \hat{Z}_{PS})$$

- knowledge of the series impedances and shunt admittances allows to study voltage and power conditions of 3-winding transformers


## Symmetrical system components

Decomposition of unsymmetrical (unbalanced) voltage:

$$\hat{U}_A = \hat{U}_{A1} + \hat{U}_{A2} + \hat{U}_{A0}$$

$$\hat{U}_B = \hat{U}_{B1} + \hat{U}_{B2} + \hat{U}_{B0}$$
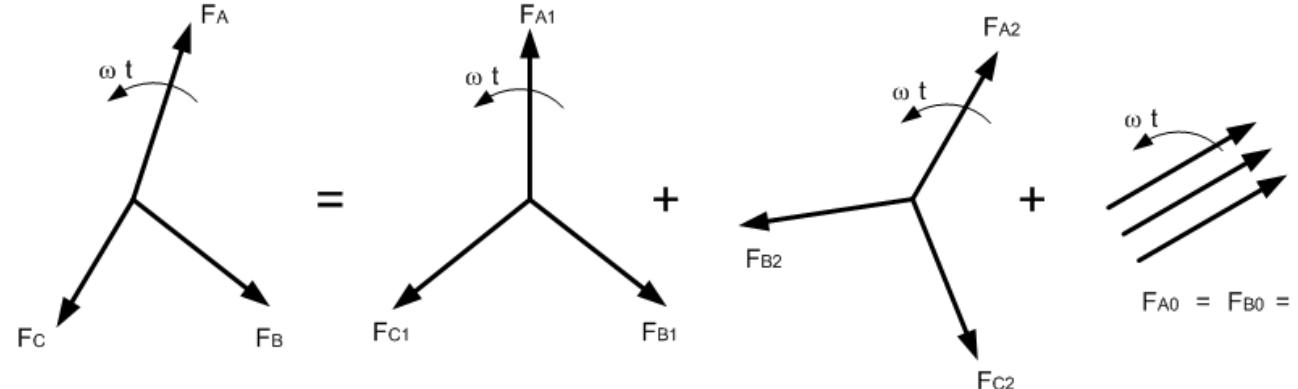
$$\hat{U}_C = \hat{U}_{C1} + \hat{U}_{C2} + \hat{U}_{C0}$$



Positive sequence (1), negative (2) and zero (0) sequence.

Hence (reference phase A)

$$\hat{U}_A = \hat{U}_1 + \hat{U}_2 + \hat{U}_0$$

$$\hat{I}_A = \hat{I}_1 + \hat{I}_2 + \hat{I}_0$$

$$\hat{U}_B = \hat{a}^2 \hat{U}_1 + \hat{a} \hat{U}_2 + \hat{U}_0$$

$$\hat{I}_B = \hat{a}^2 \hat{I}_1 + \hat{a} \hat{I}_2 + \hat{I}_0$$

$$\hat{U}_C = \hat{a} \hat{U}_1 + \hat{a}^2 \hat{U}_2 + \hat{U}_0$$

$$\hat{I}_C = \hat{a} \hat{I}_1 + \hat{a}^2 \hat{I}_2 + \hat{I}_0$$

where  $\hat{a} = -\frac{1}{2} + j\frac{\sqrt{3}}{2} = e^{j\frac{2\pi}{3}}$

$$\hat{a}^2 = -\frac{1}{2} - j\frac{\sqrt{3}}{2} = e^{j\frac{4\pi}{3}}$$

## Matrix

$$(U_{ABC}) = \begin{pmatrix} \hat{U}_A \\ \hat{U}_B \\ \hat{U}_C \end{pmatrix} = \begin{pmatrix} 1 & 1 & 1 \\ \hat{a}^2 & \hat{a} & 1 \\ \hat{a} & \hat{a}^2 & 1 \end{pmatrix} \begin{pmatrix} \hat{U}_1 \\ \hat{U}_2 \\ \hat{U}_0 \end{pmatrix} = (T)(U_{120})$$


---

Inversely

$$(U_{120}) = \begin{pmatrix} \hat{U}_1 \\ \hat{U}_2 \\ \hat{U}_0 \end{pmatrix} = \frac{1}{3} \begin{pmatrix} 1 & \hat{a} & \hat{a}^2 \\ 1 & \hat{a}^2 & \hat{a} \\ 1 & 1 & 1 \end{pmatrix} \begin{pmatrix} \hat{U}_A \\ \hat{U}_B \\ \hat{U}_C \end{pmatrix} = (T^{-1})(U_{ABC})$$
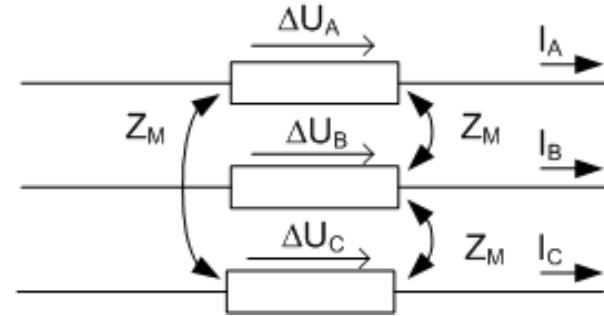
## Series symmetrical segments in ES

$$\begin{pmatrix} \Delta \hat{U}_A \\ \Delta \hat{U}_B \\ \Delta \hat{U}_C \end{pmatrix} = \begin{pmatrix} \hat{Z} & \hat{Z}' & \hat{Z}' \\ \hat{Z}' & \hat{Z} & \hat{Z}' \\ \hat{Z}' & \hat{Z}' & \hat{Z} \end{pmatrix} \begin{pmatrix} \hat{I}_A \\ \hat{I}_B \\ \hat{I}_C \end{pmatrix}$$



$$(\Delta U_{ABC}) = (Z_{ABC})(I_{ABC})$$

$$(T)(\Delta U_{120}) = (Z_{ABC})(T)(I_{120})$$

$$(\Delta U_{120}) = (T)^{-1}(Z_{ABC})(T)(I_{120}) = (Z_{120})(I_{120})$$

$$(Z_{120}) = (T)^{-1}(Z_{ABC})(T)$$

---


$$(Z_{120}) = \begin{pmatrix} \hat{Z}_1 & 0 & 0 \\ 0 & \hat{Z}_2 & 0 \\ 0 & 0 & \hat{Z}_0 \end{pmatrix} = \begin{pmatrix} \hat{Z} - \hat{Z}' & 0 & 0 \\ 0 & \hat{Z} - \hat{Z}' & 0 \\ 0 & 0 & \hat{Z} + 2\hat{Z}' \end{pmatrix}$$


---

## Shunt symmetrical segments in ES

$$(U_{ABC}) = (Z_{ABC})(I_{ABC}) + (Z_N)(I_{ABC})$$


$$(Z_N) = \begin{pmatrix} \hat{Z}_N & \hat{Z}_N & \hat{Z}_N \\ \hat{Z}_N & \hat{Z}_N & \hat{Z}_N \\ \hat{Z}_N & \hat{Z}_N & \hat{Z}_N \end{pmatrix}$$

$$(U_{120}) = (T)^{-1}(Z_{ABC})(T)(I_{120}) + (T)^{-1}(Z_N)(T)(I_{120})$$

$$(Z_{120}) = (T)^{-1}[(Z_{ABC}) + (Z_N)](T)$$


---

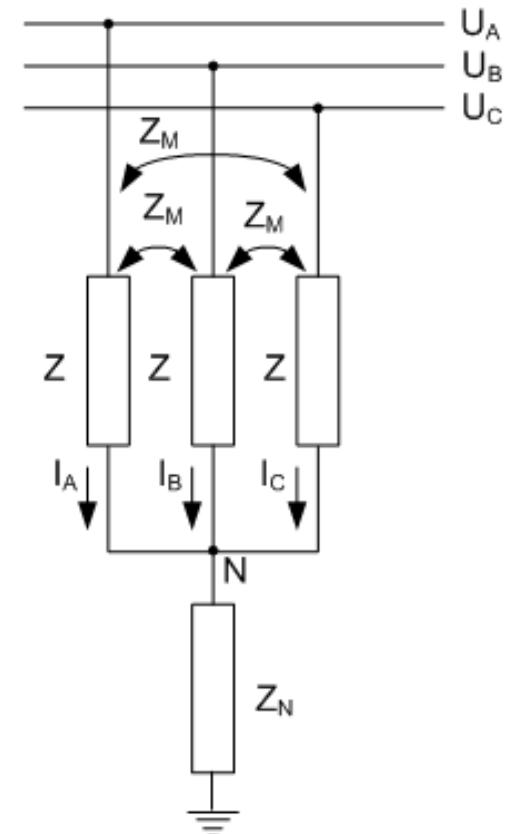
$$(Z_{120}) = \begin{pmatrix} \hat{Z} - \hat{Z}' & 0 & 0 \\ 0 & \hat{Z} - \hat{Z}' & 0 \\ 0 & 0 & \hat{Z} + 2\hat{Z}' + 3Z_N \end{pmatrix}$$



Symmetrical components voltages in the symmetrical segments depend only on the corresponding component current and component impedance.

## Transformers zero sequence impedances

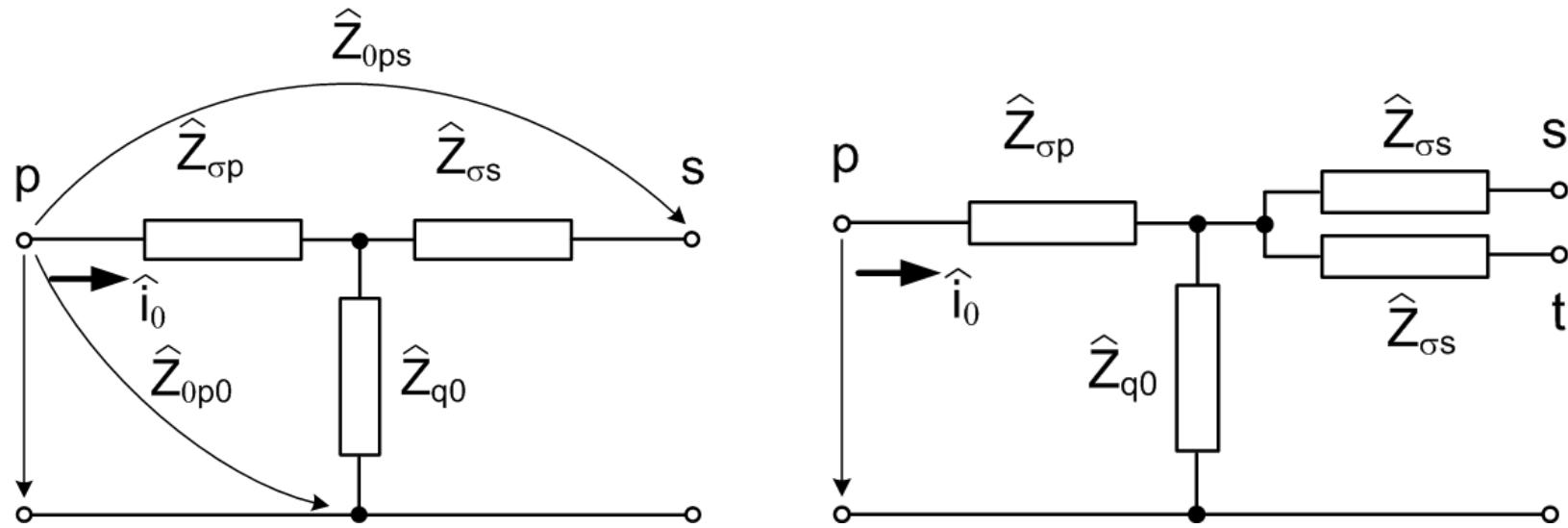

Series parameters are the same as for the positive sequence, the shunt always need to be determined.

Assumptions:

- Zero sequence voltage supplies the primary winding.
- The relative values are related to  $U_{PN}$  and  $S_{PN}$ .
- We distinguish free and tied magnetic flows (core x shell TRF).

$Z_0$  depends on the winding connection.



## a) Y / any connection

$$3i_0 = 0$$

$$Z_0 = \frac{u_0}{i_0} \rightarrow \infty$$

$$Z_{0p0} \rightarrow \infty$$

$$Z_{0ps} \rightarrow \infty$$

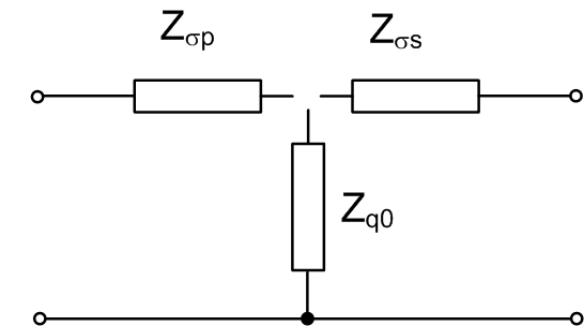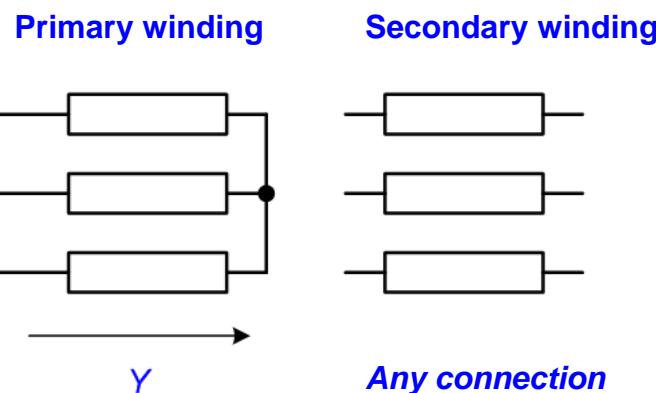

## b) D / any connection



Zero sequence voltage is attached to D  $\rightarrow$  voltage at each phase

$$u_0 - u_0 = 0 \rightarrow i_a = i_b = i_c = 0 \rightarrow i_0 = 0$$

$$Z_0 = \frac{u_0}{i_0} \rightarrow \infty$$

$$Z_{0p0} \rightarrow \infty$$

$$Z_{0ps} \rightarrow \infty$$

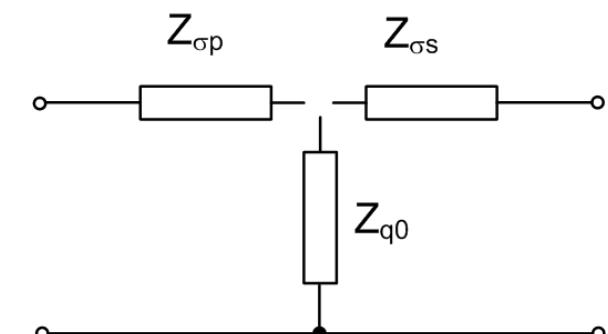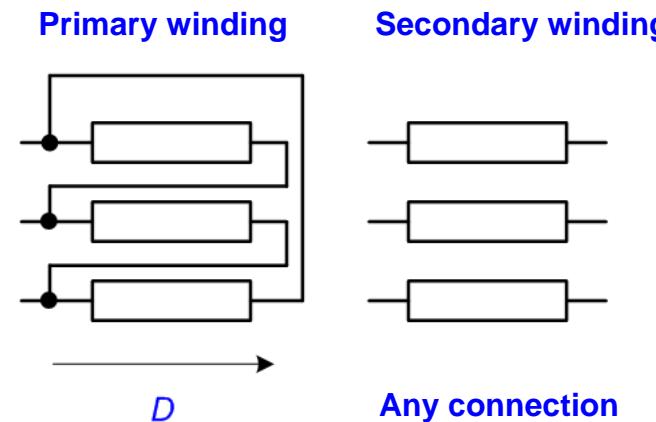

### c) YN / D

Currents in the primary winding  $i_0$  induce currents  $i_0'$  in the secondary winding to achieve magnetic balance.

Currents  $i_0'$  in the secondary winding are short-closed and do not flow further into the grid.

$$\hat{z}_{0p0} = \hat{z}_{\sigma p} + \hat{z}_{q0}$$



$$\hat{z}_0 = \frac{\hat{u}_0}{\hat{i}_0} = \hat{z}_{\sigma p} + \frac{\hat{z}_{\sigma s} \cdot \hat{z}_{q0}}{\hat{z}_{\sigma s} + \hat{z}_{q0}}$$

shell

$$\hat{z}_{q0} = \hat{y}_q^{-1} \gg \hat{z}_{\sigma s} \rightarrow \hat{z}_0 \approx \hat{z}_{\sigma ps} = \hat{z}_{1k}$$

3-core

$$|\hat{z}_{q0}| < |\hat{y}_q^{-1}| \rightarrow |\hat{z}_0| \approx (0,7 \div 0,9) |\hat{z}_{\sigma ps}|$$

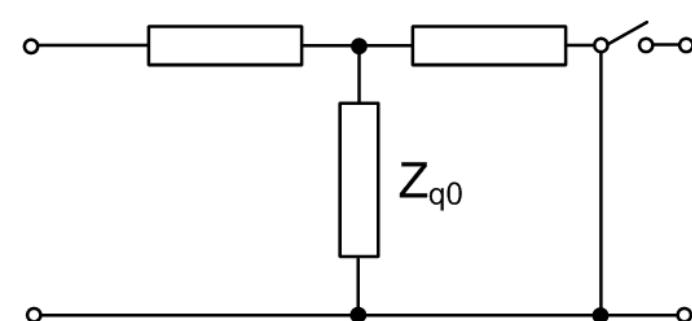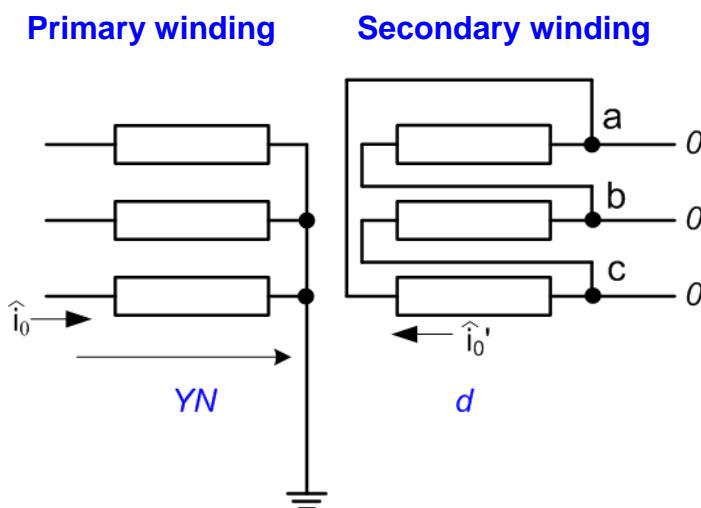

## d) YN / Y

Zero sequence current can't flow through the secondary winding.  
Current  $i_0$  corresponds to the magnetization current.

$$Z_{0ps} \rightarrow \infty$$


$$\hat{z}_0 = \hat{z}_{0p0} + \hat{z}_{q0}$$

shell


$$\hat{z}_{q0} = \hat{y}_q^{-1} \rightarrow z_0 \rightarrow \infty$$

3-core

$$|\hat{z}_{q0}| < |\hat{y}_q^{-1}| \rightarrow |\hat{z}_0| \approx (0,3 \div 1)$$

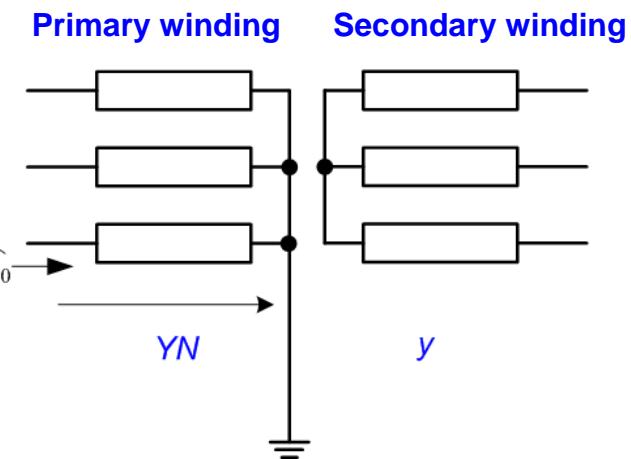


## e)

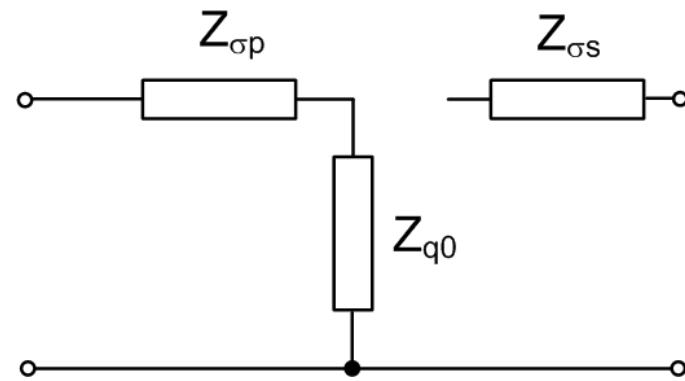
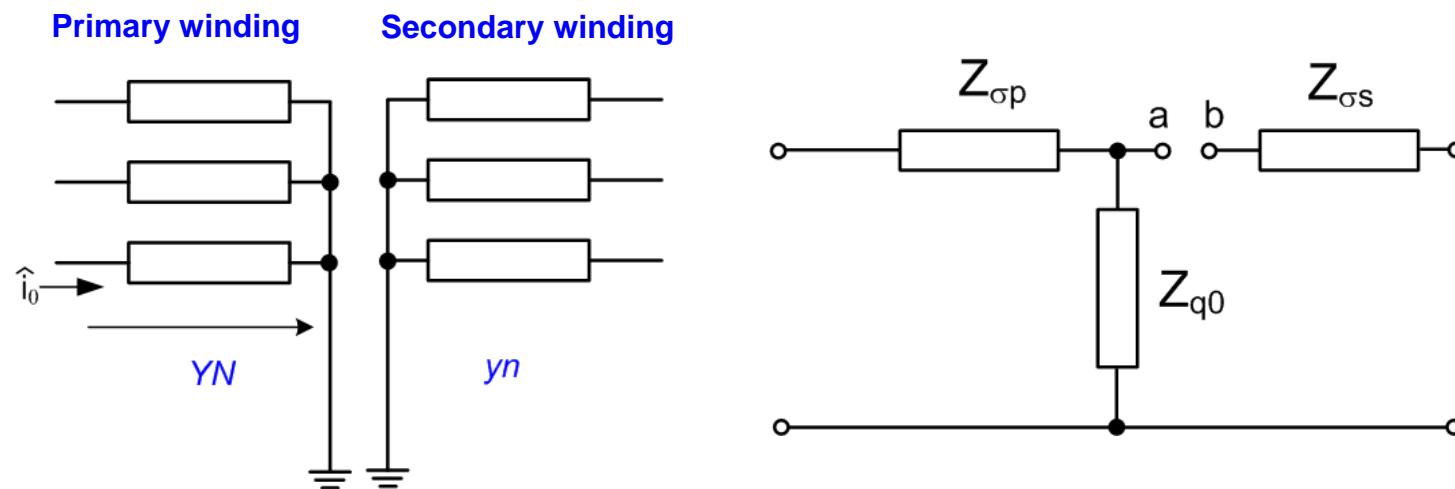
### e) YN / YN

If element with YN or ZN behind TRF → points a-b are connected → as the positive sequence.

If element with Y, Z or D behind TRF → a-b are disconnected → as YN / Y.





## f) ZN / any connection

Currents  $i_0$  induce mag. balance on the core themselves → only leakages between the halves of the windings.

$$Z_{0ps} \rightarrow \infty$$

$$\hat{z}_0 = \hat{z}_{0p0} \approx (0,1 \div 0,3) \hat{z}_{\sigma ps}$$

$$r_0 = r_p$$

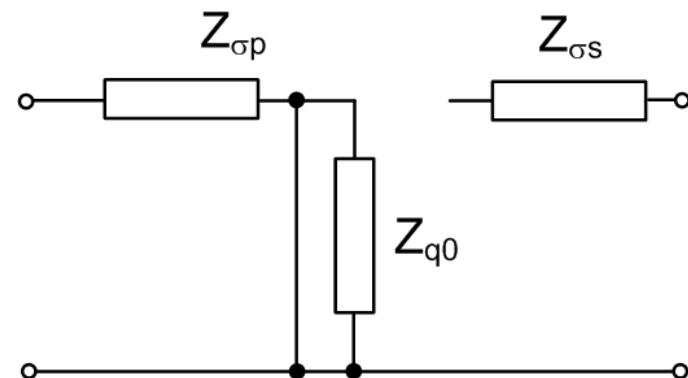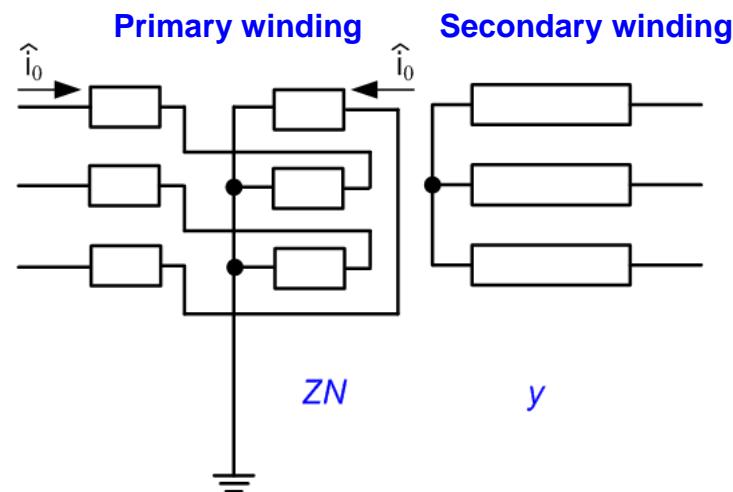


## g) impedance in the neutral point

Current flowing through the neutral point is  $3\hat{i}_0$ .

Voltage drop:  $\Delta\hat{u}_{uz} = \hat{z}_u \cdot 3\hat{i}_0 = 3\hat{z}_u \cdot \hat{i}_0$

## h) three-winding TRF

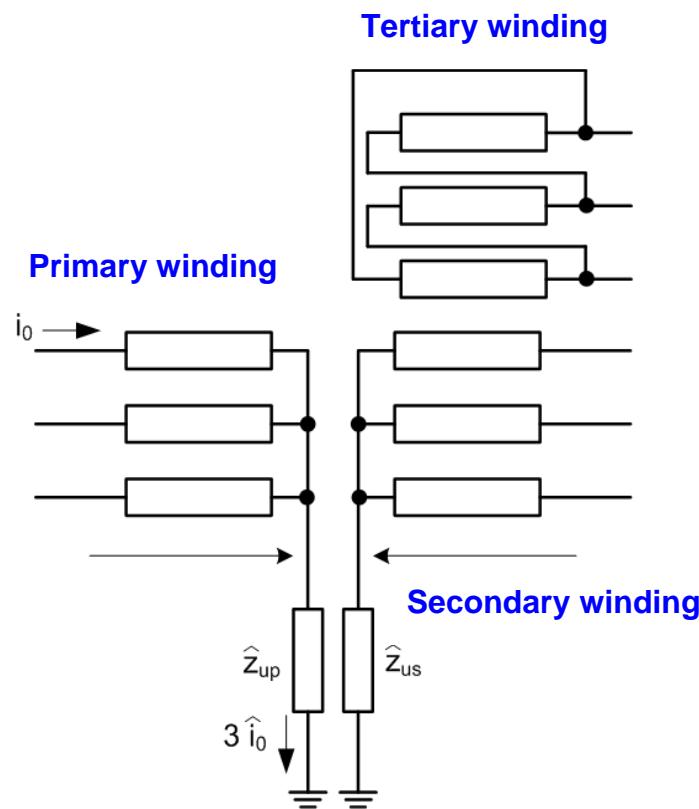

## System equivalent

Impedance (positive sequence) is given by the nominal voltage and short-circuit current (power).

Three-phase (symmetrical) short-circuit:  $S''_k$  (MVA),  $I''_k$  (kA)

$$S''_k = \sqrt{3} U_n I''_k$$

$$Z_s = \frac{U_n^2}{S''_k} = \frac{U_n}{\sqrt{3} \cdot I''_k}$$

CR:	400 kV	$S''_k \approx (6000 \div 30000) \text{ MVA}$	$I''_k \approx (9 \div 45) \text{ kA}$
	220 kV	$S''_k \approx (2000 \div 12000) \text{ MVA}$	$I''_k \approx (2 \div 30) \text{ kA}$
	110 kV	$S''_k \approx (100x \div 3000) \text{ MVA}$	$I''_k \approx (x \div 15) \text{ kA}$
	22 kV	$S''_k \approx 10x \text{ MVA}$	$I''_k \approx x \text{ kA}$
	0,4 kV	$S''_k \approx 100x \text{ kVA}$	$I''_k \approx x \text{ kA}$