


# STEADY STATES (LOAD FLOW) CALCULATIONS IN POWER SYSTEMS - Current loads

## Simple DC line (LV, MV)

Double-wire circuit. Assumption: constant cross-section and resistivity.

Single loads supplied from one side

Standard distribution lines.

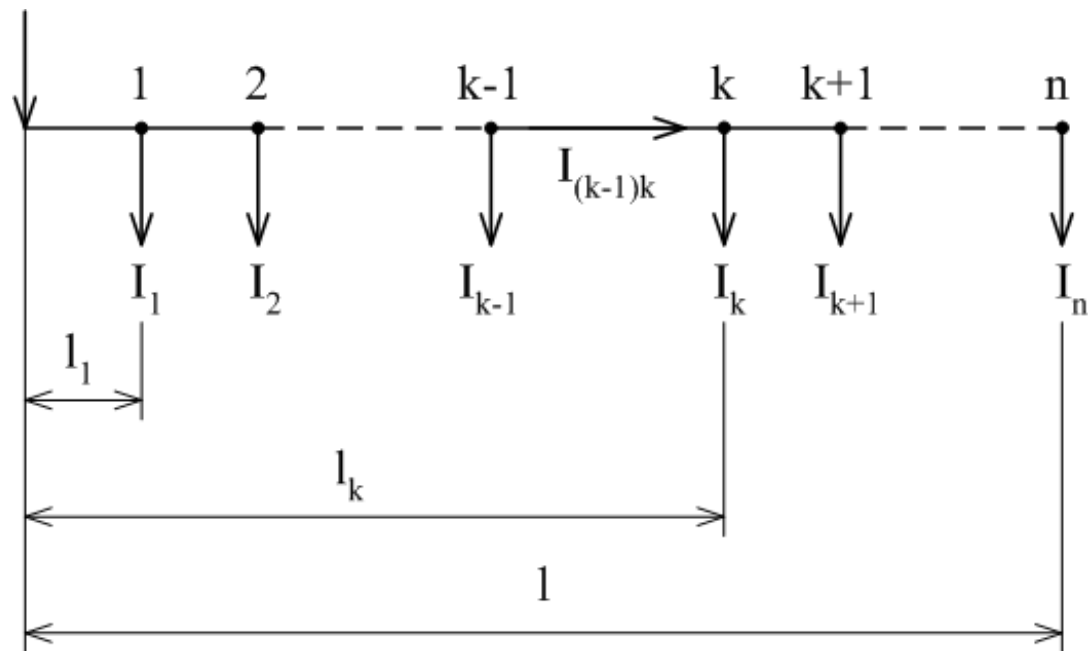

### a) addition method

It adds voltage drops along the power line sections.

(Voltage drops are always in both conductors in the section.)

$k^{\text{th}}$  section

$$U_{(k-1)} - U_k = \Delta U_{(k-1)k} = 2 \frac{\rho}{S} (l_k - l_{(k-1)}) \cdot I_{(k-1)k} \quad (\text{V}; \Omega\text{m}, \text{m}^2, \text{m}, \text{A})$$

Current in  $k^{\text{th}}$  section

$$I_{(k-1)k} = \sum_{y=k}^n I_y$$

Maximum voltage drop

$$\Delta U_n = \sum_{k=1}^n \Delta U_{(k-1)k} = 2 \frac{\rho}{S} \sum_{k=1}^n (l_k - l_{(k-1)}) \cdot \sum_{y=k}^n I_y$$

## b) superposition method

It adds voltage drops for individual discrete loads:

$$\Delta U_n = 2 \frac{\rho}{S} \sum_{k=1}^n l_k I_k$$

$l_k I_k$  ... current moments to the feeder

Relative voltage drop:


$$\varepsilon = \frac{\Delta U}{U_n} \quad (-; V, V)$$

Note. Losses must be calculated only by means of the addition method!

$$\Delta P_{(k-1)k} = 2 \frac{\rho}{S} (l_k - l_{(k-1)}) \cdot I_{(k-1)k}^2 \quad (W; \Omega m, m^2, m, A)$$

$$\Delta P = \sum_{k=1}^n \Delta P_{(k-1)k}$$
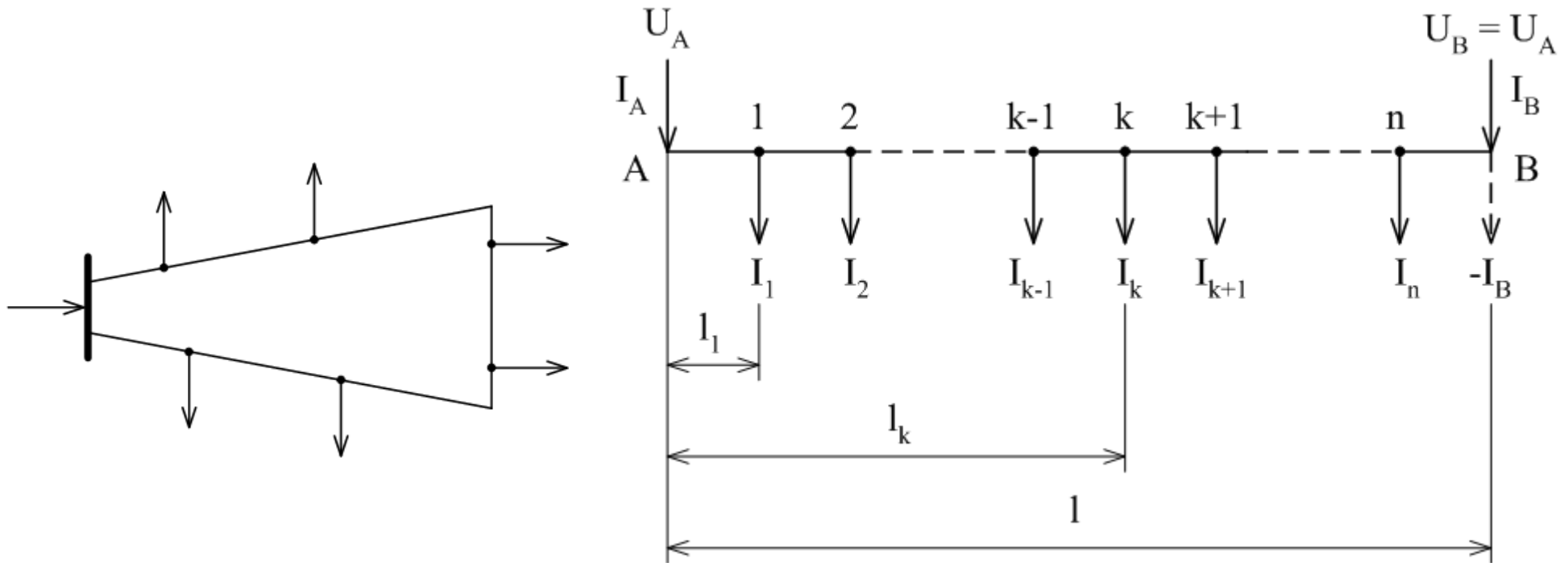
## Single loads supplied from both sides – the same feeders voltages



- Ring grid, higher reliability of supply.
- Two one-feeder lines after a fault. More often also in standard operation mode.
- Calculation of current distribution and voltage drops.

Consider  $I_B$  as a negative load:

$$\Delta U_{AB} = U_A - U_B = 0 = 2 \frac{\rho}{S} \sum_{k=1}^n l_k I_k - 2 \frac{\rho}{S} l I_B$$

Hence (moment theorem)

$$I_B = \frac{\sum_{k=1}^n l_k I_k}{l}$$


Analogous (current moments to other feeder)

$$I_A = \frac{\sum_{k=1}^n (l - l_k) I_k}{l}$$

Of course


$$I_A + I_B = \sum_{y=1}^n I_y$$

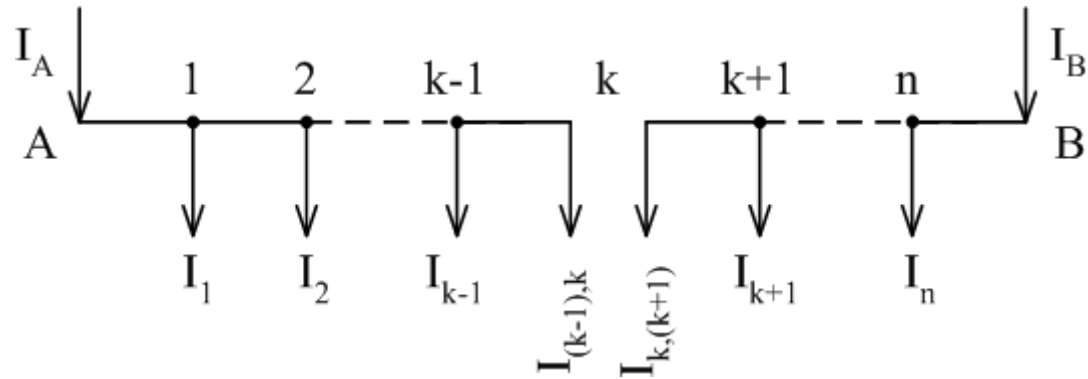Current distribution identifies the place with the biggest voltage drop = the place with feeder division → split-up into two one-feeder lines.



Single loads supplied from both sides – different feeders voltages

Two different sources, meshed grid.

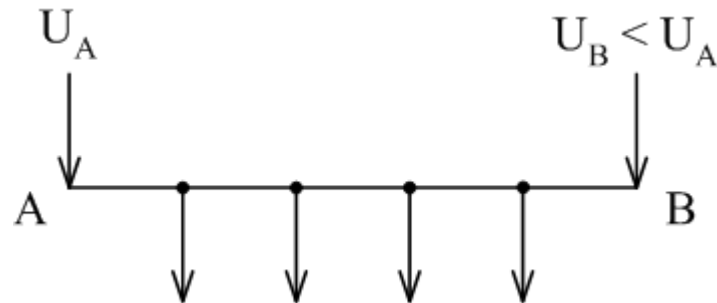

## Superposition:

- 1) Current distribution with the same voltages.
- 2) Different voltages and zero loads  $\rightarrow$  balancing current

$$I_v = \frac{U_A - U_B}{2 \frac{\rho}{S} l}$$




- 3) Sum of the solutions 1+2

Further calculation is the same.

Or directly:

$$U_A - U_B = 2 \frac{\rho}{S} \sum_{k=1}^n l_k I_k - 2 \frac{\rho}{S} l I_B$$
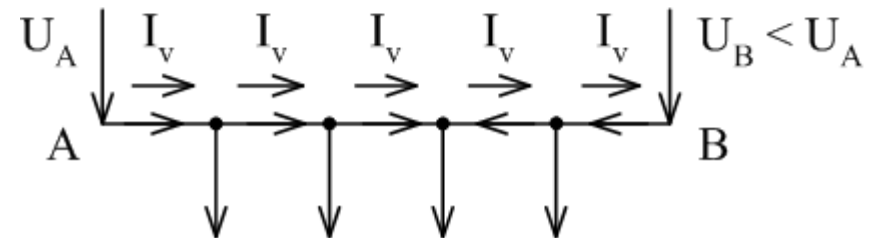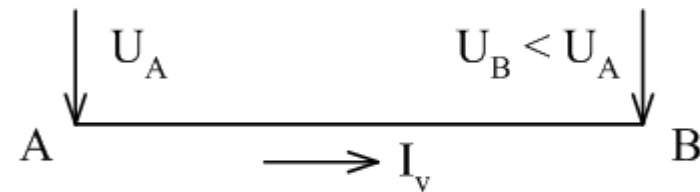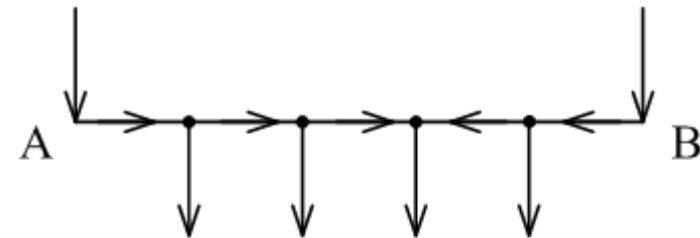
$$I_B = \frac{2 \frac{\rho}{S} \sum_{k=1}^n l_k I_k}{2 \frac{\rho}{S} l} - \frac{U_A - U_B}{2 \frac{\rho}{S} l}$$




## AC - 3 phase power lines LV, MV

Series parameters are applied, for LV  $X \rightarrow 0$ .

3 phase power line MV, 1 load at the end

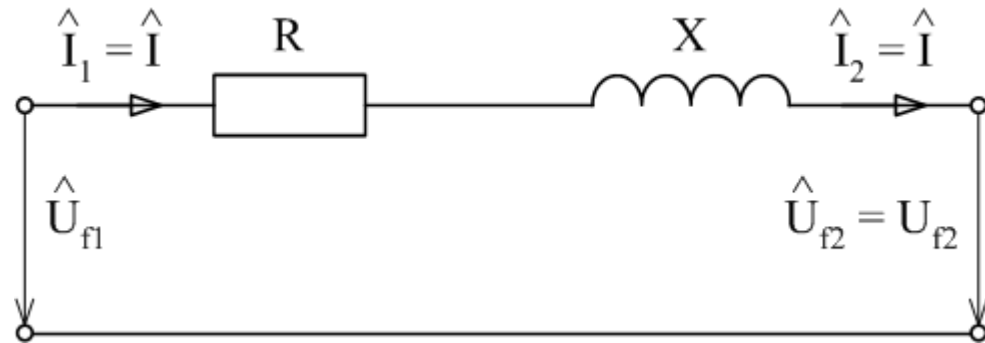Symmetrical load  $\rightarrow$  1 phase diagram, operational parameters.



Complex voltage drop

$$\Delta \hat{U}_{ph} = \hat{Z}_1 \hat{I} = (R + jX)(I_{re} \mp jI_{im}) \begin{matrix} \text{IND} \\ \text{CAP} \end{matrix}$$

$$\Delta \hat{U}_{ph} = RI_{re} \pm XI_{im} + j(XI_{re} \mp RI_{im}) \begin{matrix} \text{IND} \\ \text{CAP} \end{matrix}$$

magnitude      phase



Phasor diagram (input  $U_{ph2}$ ,  $I$ ,  $\varphi_2$ )  
 (angle  $\nu$  usually small, up to  $3^\circ$ )

Imagin. part neglecting and modifications

$$\Delta U_{ph} = \frac{R3U_{ph}I_{re} \pm X3U_{ph}I_{im}}{3U_{ph}} = \frac{RP \pm XQ}{3U_{ph}}$$


Percentage voltage drop

$$\varepsilon = \frac{\Delta U_{ph}}{U_{ph}} = \frac{RP \pm XQ}{3U_{ph}^2} = \frac{RP \pm XQ}{U^2}$$

3 phase active power losses

$$\begin{aligned} \Delta \hat{S} &= 3\Delta \hat{U}_{ph} \hat{I}^* = 3\hat{Z}_1 \hat{I} \cdot \hat{I}^* = 3\hat{Z}_1 I^2 = \\ &= 3(R + jX)I^2 = 3RI^2 + j3XI^2 \\ \Delta P &= 3RI^2 = 3R(I_{re}^2 + I_{im}^2) \quad (W; \Omega, A) \end{aligned}$$

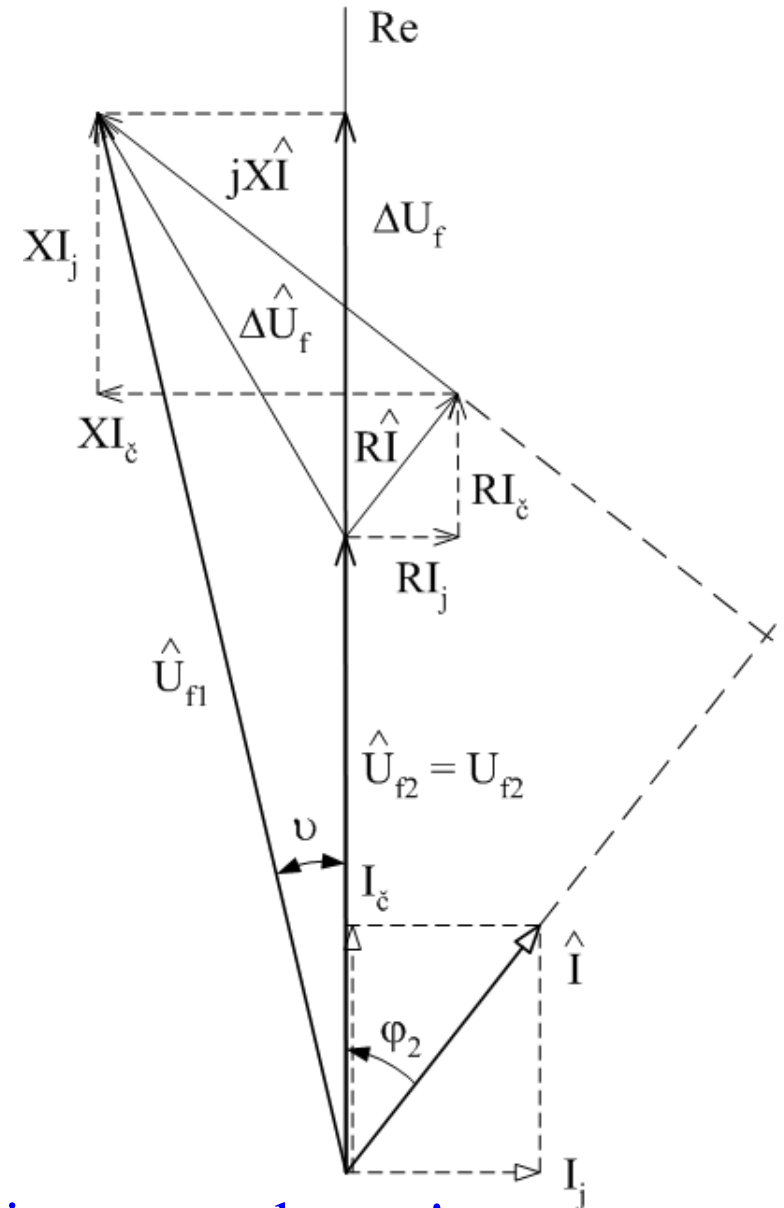
**! Even the reactive current (power) causes active power losses!**


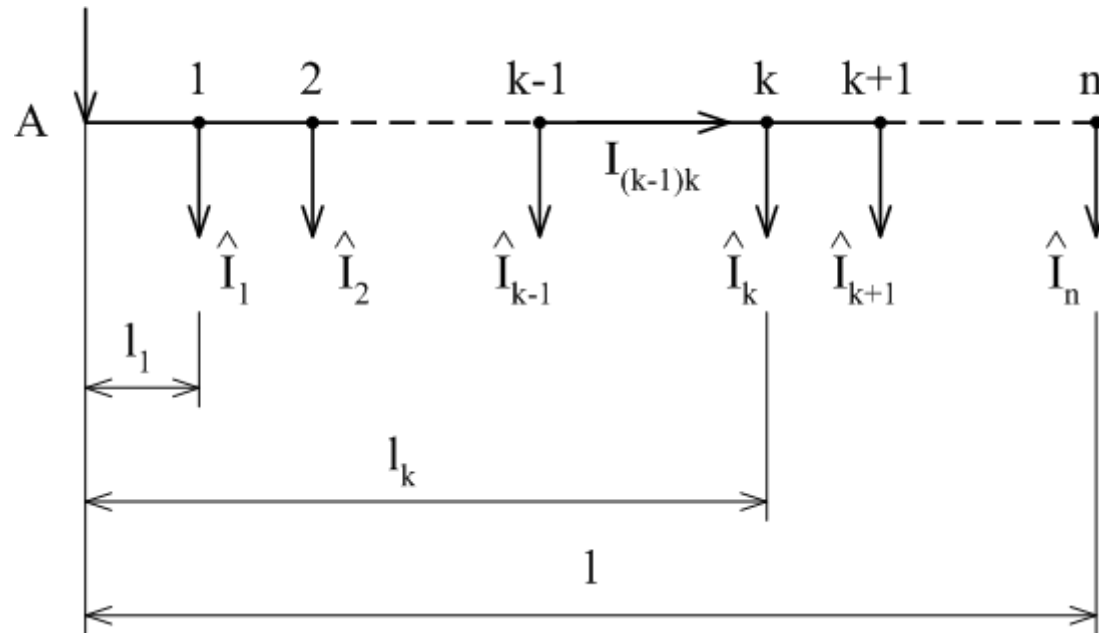
## 3 phase MV power line supplied from one side

Constant series impedance

$$\hat{Z}_{l_1} = R_1 + jX_1 \quad (\Omega / \text{km})$$



Voltage drop at the end (needn't be the highest one, it depends on load character)

- superposition

$$\Delta \hat{U}_{\text{phAn}} = \hat{Z}_{l_1} \sum_{k=1}^n l_k \hat{I}_k$$

- addition

$$\Delta \hat{U}_{\text{phAn}} = \hat{Z}_{l_1} \sum_{k=1}^n (l_k - l_{(k-1)}) \cdot \sum_{y=k}^n \hat{I}_y$$

After imaginary part neglecting (addition)

$$\Delta U_{\text{phAn}} \doteq R_1 \sum_{k=1}^n (l_k - l_{(k-1)}) \cdot \sum_{y=k}^n I_{\text{rek}} \pm X_1 \sum_{k=1}^n (l_k - l_{(k-1)}) \cdot \sum_{y=k}^n I_{\text{imk}} \quad \begin{array}{l} \text{IND} \\ \text{CAP} \end{array}$$

$$\Delta U_{\text{phAn}} \doteq \frac{R_1 \sum_{k=1}^n (l_k - l_{(k-1)}) \cdot \sum_{y=k}^n P_k \pm X_1 \sum_{k=1}^n (l_k - l_{(k-1)}) \cdot \sum_{y=k}^n Q_k}{3U_{\text{ph}}} \quad \begin{array}{l} \text{IND} \\ \text{CAP} \end{array}$$

## Voltage drop up to the point X (not end)


- superposition

$$\Delta \hat{U}_{\text{phAX}} = \hat{Z}_{l_1} \sum_{k=1}^X l_k \hat{I}_k + \hat{Z}_{l_1} l_{AX} \sum_{k=X+1}^n \hat{I}_k$$

- addition

$$\Delta \hat{U}_{\text{phAX}} = \hat{Z}_{l_1} \sum_{k=1}^X (l_k - l_{(k-1)}) \cdot \sum_{y=k}^n \hat{I}_y$$
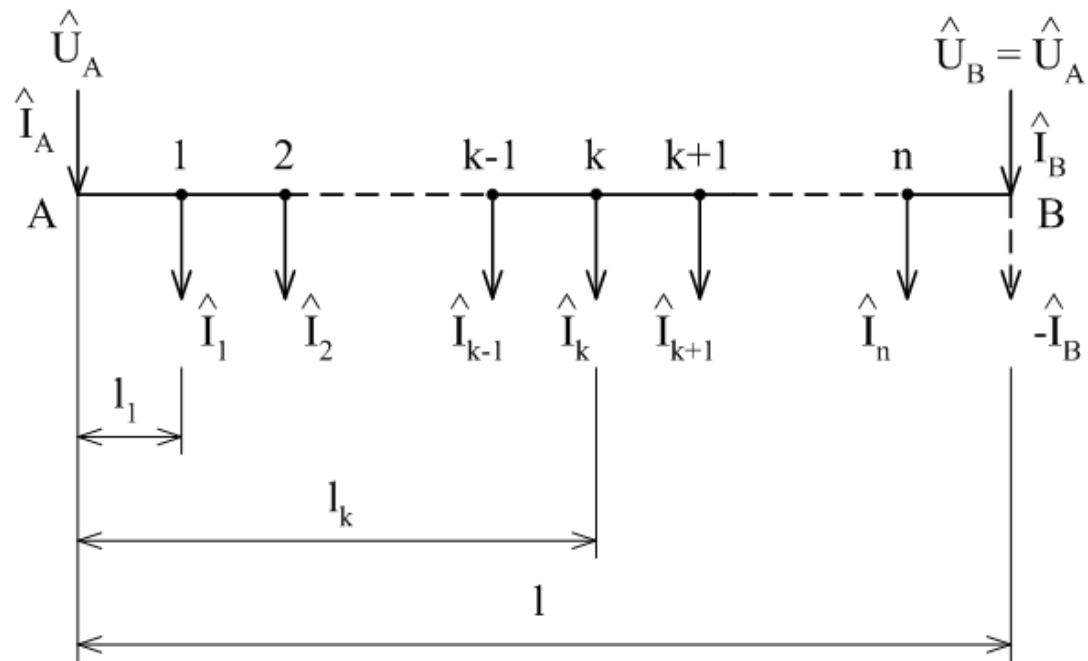
## 3 phase MV power line supplied from both sides



Calculation as for DC line (feeder is a negative load, zero voltage drop).

$$\Delta \hat{U}_{\text{phAB}} = 0 = \hat{Z}_{l_1} \sum_{k=1}^n l_k \hat{I}_k - \hat{Z}_{l_1} l \cdot \hat{I}_B$$

Moment theorems

$$\hat{I}_B = \frac{\sum_{k=1}^n l_k \hat{I}_k}{l} \quad \hat{I}_A = \frac{\sum_{k=1}^n (l - l_k) \hat{I}_k}{l} \quad \hat{I}_A + \hat{I}_B = \sum_{y=1}^n \hat{I}_y$$

(In principle it is the current divider for each load.)


Active and reactive current sign change could be in different nodes → maximum voltage drop should be checked in all grid points.



## Meshed grids MV
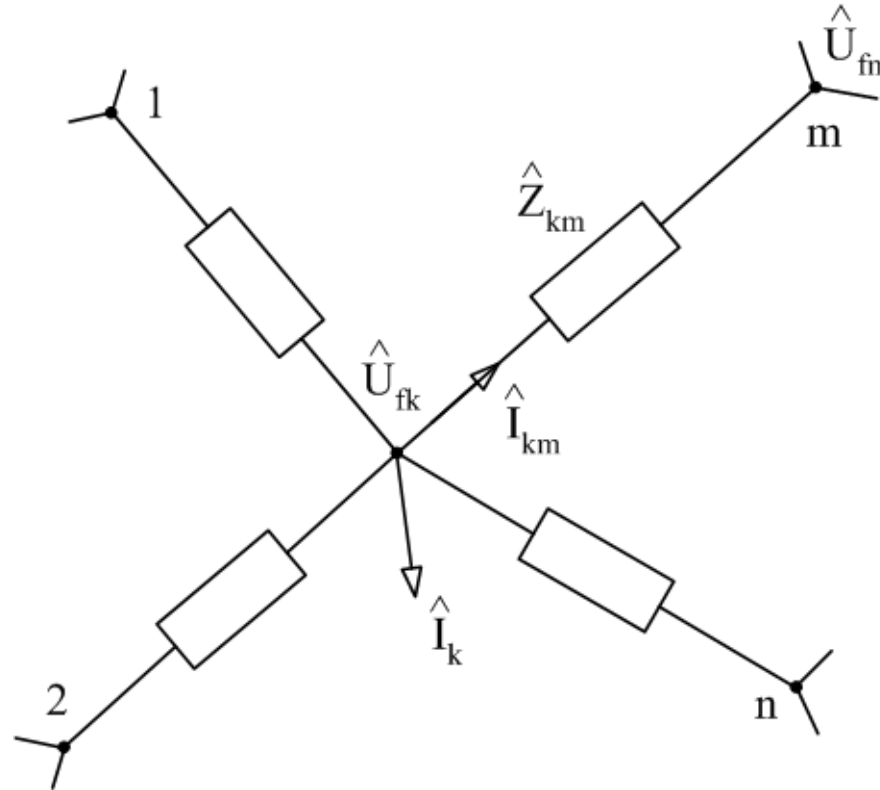
### Bus voltage method

Grid with  $n$  nodes. Set series branch parameters  $\hat{Z}_{km}$ , load currents (bus currents)  $\hat{I}_k$ , min. 1 bus voltage  $\hat{U}_{phk}$  (between the bus and the ground).



## Calculation with series admittances

$$\hat{Y}_{km} = \hat{Z}_{km}^{-1} = \frac{1}{R_{km} + jX_{km}}$$

### Node $k$

$$\hat{I}_k + \sum_{\substack{m=1 \\ m \neq k}}^n \hat{I}_{km} + \hat{I}_{k0} = 0$$


$$\hat{I}_{k0} = \hat{U}_{phk} \hat{Y}_{k0}$$

### Branches $k, m$

$$\hat{I}_{km} = (\hat{U}_{phk} - \hat{U}_{phm}) \hat{Y}_{km}$$
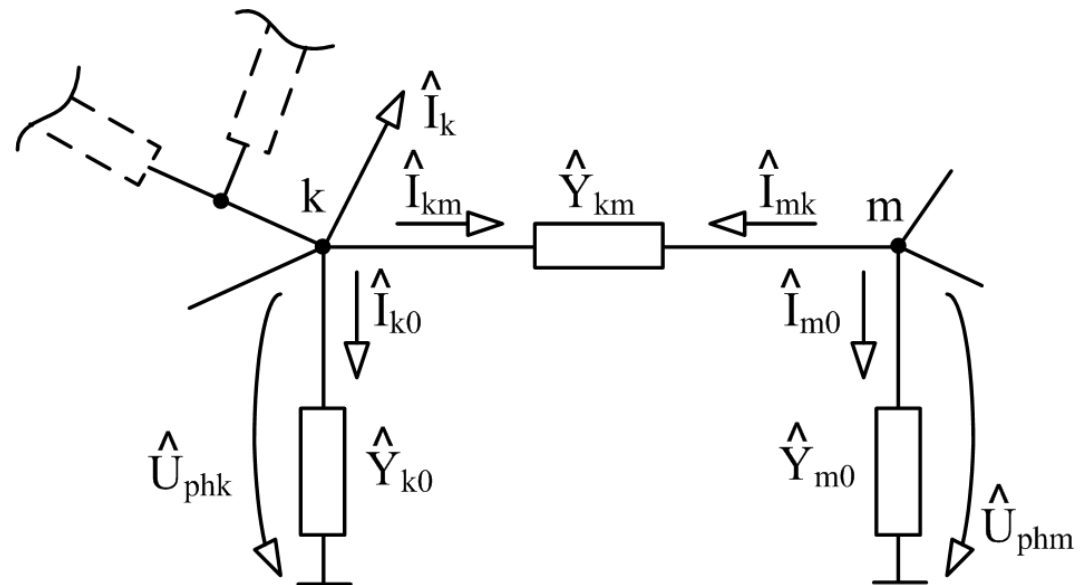
### After modifications:

$$\hat{I}_k = - \sum_{\substack{m=1 \\ m \neq k}}^n (\hat{U}_{phk} - \hat{U}_{phm}) \hat{Y}_{km} - \hat{U}_{phk} \hat{Y}_{k0}$$





$$\hat{I}_k = -\hat{U}_{phk} \left( \sum_{\substack{m=1 \\ m \neq k}}^n \hat{Y}_{km} + \hat{Y}_{k0} \right) + \sum_{\substack{m=1 \\ m \neq k}}^n \hat{U}_{phm} \hat{Y}_{km}$$

Admittance matrix parameters definition:  
 Bus self-admittance (diagonal element)

$$\hat{Y}_{(k,k)} = -\sum_{\substack{m=1 \\ m \neq k}}^n \hat{Y}_{km} - \hat{Y}_{k0}$$

Between buses admittance (non-diagonal element)

$$\hat{Y}_{(k,m)} = \hat{Y}_{(m,k)} = \hat{Y}_{km} \quad \text{for } m \neq k$$

(for non-connected buses  $\hat{Y}_{(k,m)} = 0$ )

Hence

$$\hat{I}_k = \sum_{m=1}^n \hat{Y}_{(k,m)} \hat{U}_{fm}$$

Matrix form

$$\begin{pmatrix} \hat{\mathbf{I}} \end{pmatrix} = \begin{pmatrix} \hat{\mathbf{Y}} \end{pmatrix} \begin{pmatrix} \hat{\mathbf{U}}_{\text{ph}} \end{pmatrix}$$

Set voltages at buses 1 to  $k$  ( $x$ ), currents at buses  $k+1$  to  $n$  ( $y$ )

$$\begin{pmatrix} \begin{pmatrix} \hat{\mathbf{I}}_x \\ \hat{\mathbf{I}}_y \end{pmatrix} \end{pmatrix} = \begin{pmatrix} \begin{pmatrix} \hat{\mathbf{Y}}_{xx} & \hat{\mathbf{Y}}_{xy} \\ \hat{\mathbf{Y}}_{xy}^T & \hat{\mathbf{Y}}_{yy} \end{pmatrix} \end{pmatrix} \begin{pmatrix} \begin{pmatrix} \hat{\mathbf{U}}_{\text{phx}} \\ \hat{\mathbf{U}}_{\text{phy}} \end{pmatrix} \end{pmatrix}$$

Hence

$$\begin{pmatrix} \hat{\mathbf{I}}_x \end{pmatrix} = \begin{pmatrix} \hat{\mathbf{Y}}_{xx} \end{pmatrix} \begin{pmatrix} \hat{\mathbf{U}}_{\text{phx}} \end{pmatrix} + \begin{pmatrix} \hat{\mathbf{Y}}_{xy} \end{pmatrix} \begin{pmatrix} \hat{\mathbf{U}}_{\text{phy}} \end{pmatrix}$$

$$\begin{pmatrix} \hat{\mathbf{I}}_y \end{pmatrix} = \begin{pmatrix} \hat{\mathbf{Y}}_{xy} \end{pmatrix}^T \begin{pmatrix} \hat{\mathbf{U}}_{\text{phx}} \end{pmatrix} + \begin{pmatrix} \hat{\mathbf{Y}}_{yy} \end{pmatrix} \begin{pmatrix} \hat{\mathbf{U}}_{\text{phy}} \end{pmatrix}$$

Calculate  $\begin{pmatrix} \hat{\mathbf{I}}_x \end{pmatrix}$ ,  $\begin{pmatrix} \hat{\mathbf{U}}_{\text{phy}} \end{pmatrix}$

$$\begin{pmatrix} \hat{\mathbf{U}}_{\text{phy}} \end{pmatrix} = \begin{pmatrix} \hat{\mathbf{Y}}_{yy} \end{pmatrix}^{-1} \begin{pmatrix} \hat{\mathbf{I}}_y \end{pmatrix} - \begin{pmatrix} \hat{\mathbf{Y}}_{yy} \end{pmatrix}^{-1} \begin{pmatrix} \hat{\mathbf{Y}}_{xy} \end{pmatrix}^T \begin{pmatrix} \hat{\mathbf{U}}_{\text{phx}} \end{pmatrix}$$

If some nodes are connected to the ground (through an admittance), then the admittance matrix is regular  $\rightarrow$  to set all nodal current is enough.

$$\left(\hat{U}_f\right) = \left(\hat{Y}\right)^{-1} \left(\hat{I}\right)$$

Note 1: Similar for DC grid.

$$(I) = (G)(U)$$

Note 2: For power engineering – powers are set, currents are calculated from the powers.

$$\hat{I} = \left( \frac{\hat{S}}{\sqrt{3}\hat{U}} \right)^*$$

Results are not precise if nominal voltages are used  $\rightarrow$  iteration methods.

## HV lines

No load points.

### Open-circuit

$$\hat{I}_2 = 0$$

$$\hat{U}_{f10} = \hat{U}_{f2} \cosh \hat{\gamma}l$$

$$\hat{I}_{10} = \frac{\hat{U}_{f2}}{\hat{Z}_v} \sinh \hat{\gamma}l$$

For ideal line

$$\hat{U}_{f10} = \hat{U}_{f2} \cos \beta l$$

$$\hat{I}_{10} = j \frac{\hat{U}_{f2}}{Z_v} \sin \beta l$$

It is valid  $U_{f10} \leq U_{f2} \rightarrow$  Ferranti effect  
Line character is like capacity.

## Short-circuit

$$\hat{U}_{f2} = 0$$

$$\hat{U}_{f1} = \hat{Z}_v \hat{I}_2 \sinh \hat{\gamma}l$$

$$\hat{I}_1 = \hat{I}_2 \cosh \hat{\gamma}l$$

For ideal line

$$\hat{U}_{f1} = jZ_v \hat{I}_2 \sin \beta l$$

$$\hat{I}_1 = \hat{I}_2 \cos \beta l$$

Voltage decreases from the beginning to the end.

Line character is like inductance.

Example:


line 1 x 400 kV with two ground wires

phase conductor: 3xACSR 450/52, ground wire: ACSR 185/31,  $l = 300$  km

$R_1 = 0,021 \Omega/\text{km}$ ;  $X_1 = 0,293 \Omega/\text{km}$ ;  $G_1 = 2 \cdot 10^{-8} \text{ S}/\text{km}$ ;  $B_1 = 3,9 \cdot 10^{-6} \text{ S}/\text{km}$


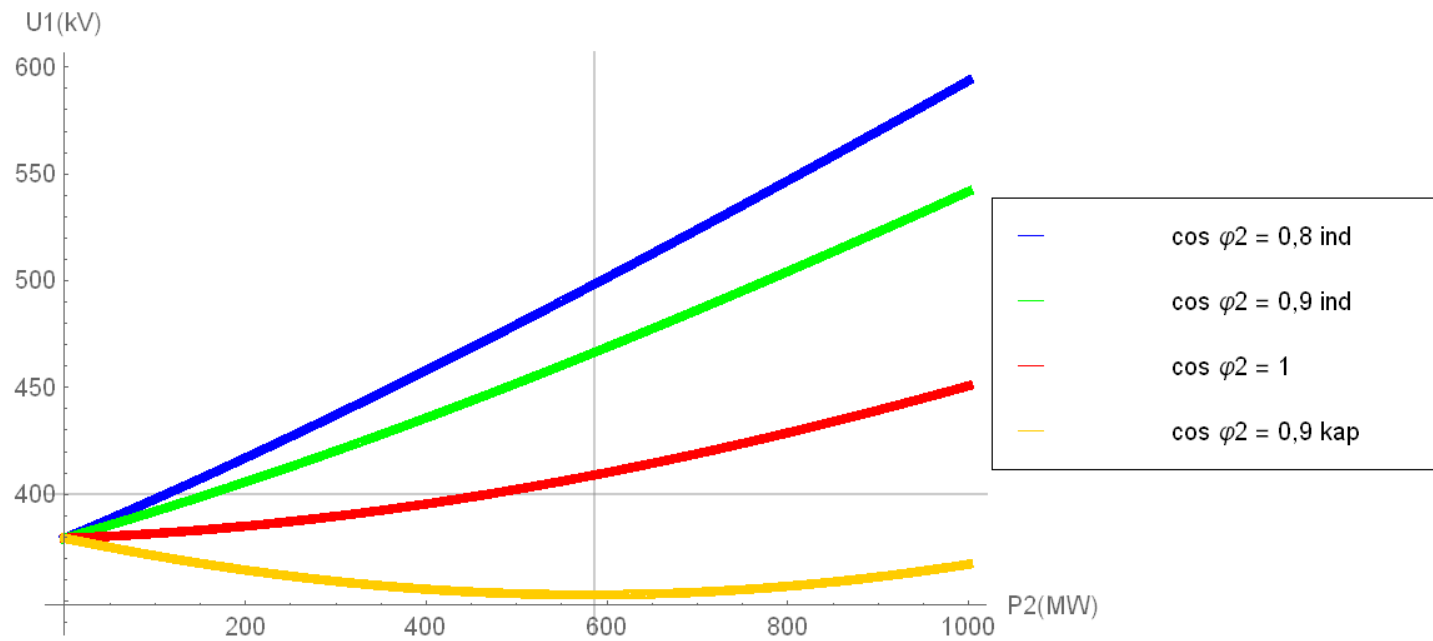
## Voltage level ( $U_2 = 400 \text{ kV}$ )




$U_1 < U_n$ : Ferranti effect

$U_1 \sim U_n$  for  $S_p$  area and  $\cos \varphi = 1$

## Transmission power factor


$$\cos \varphi_1 = \frac{P_1}{S_1}$$

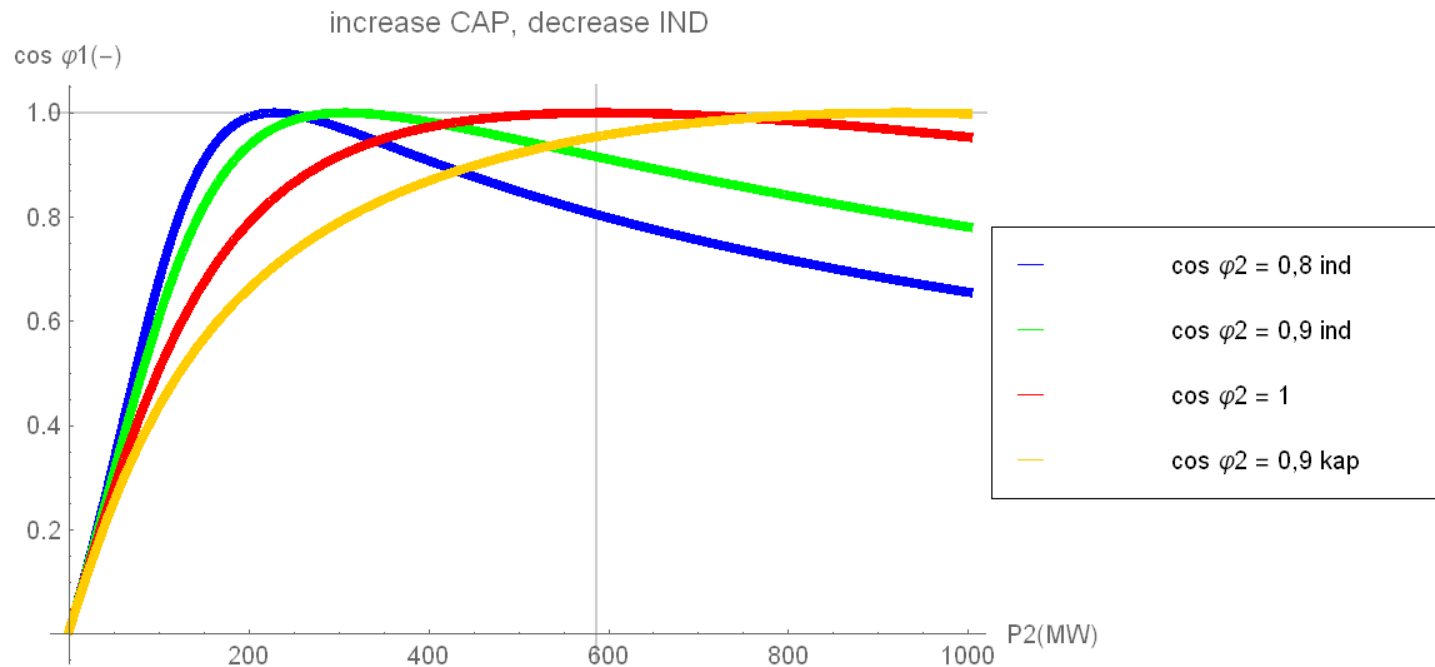

open-circuit → line is like capacitive load  
higher power → line „self-compensation“





## Line reactive power

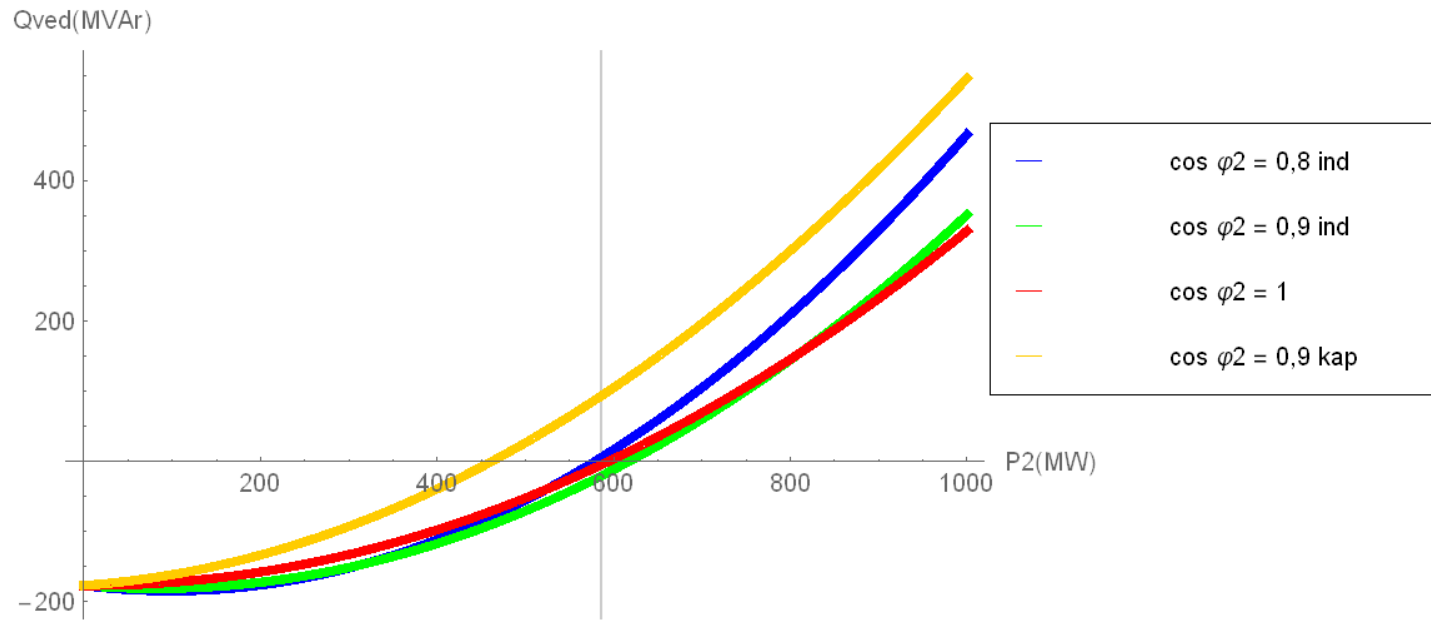
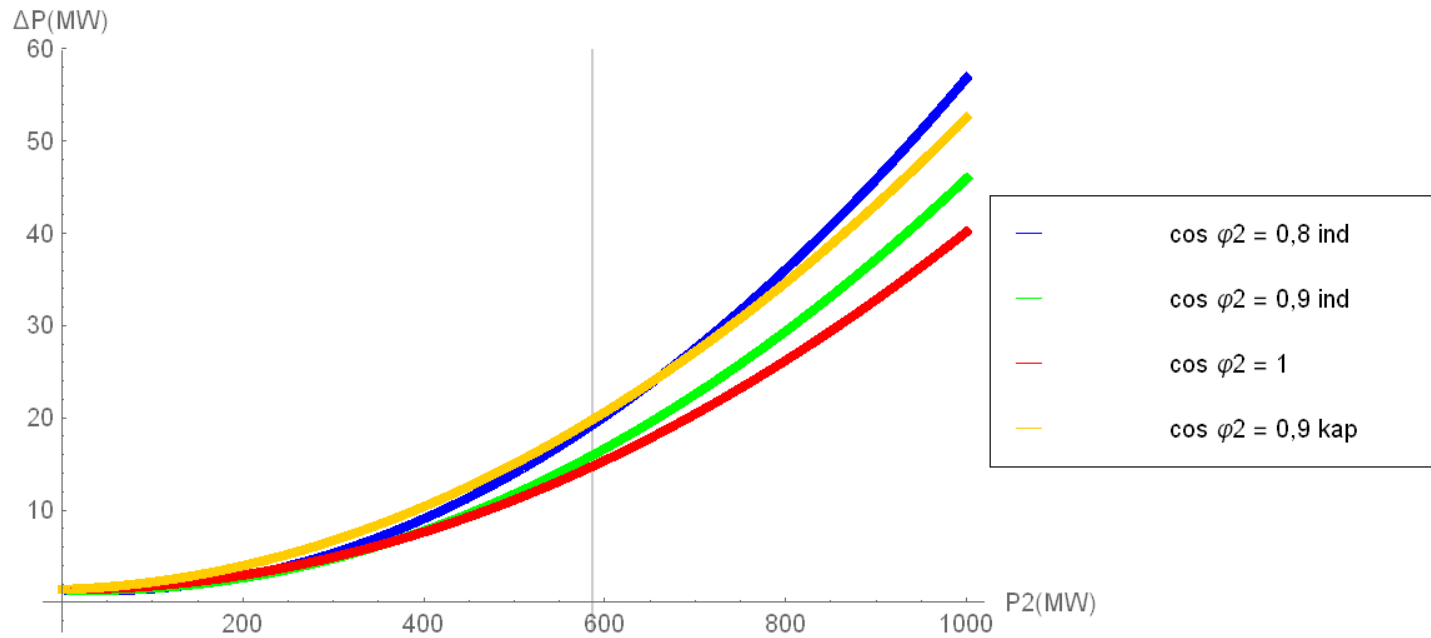
## Line losses


= open-circuit  $\sim U^2$  + load  $\sim I^2$



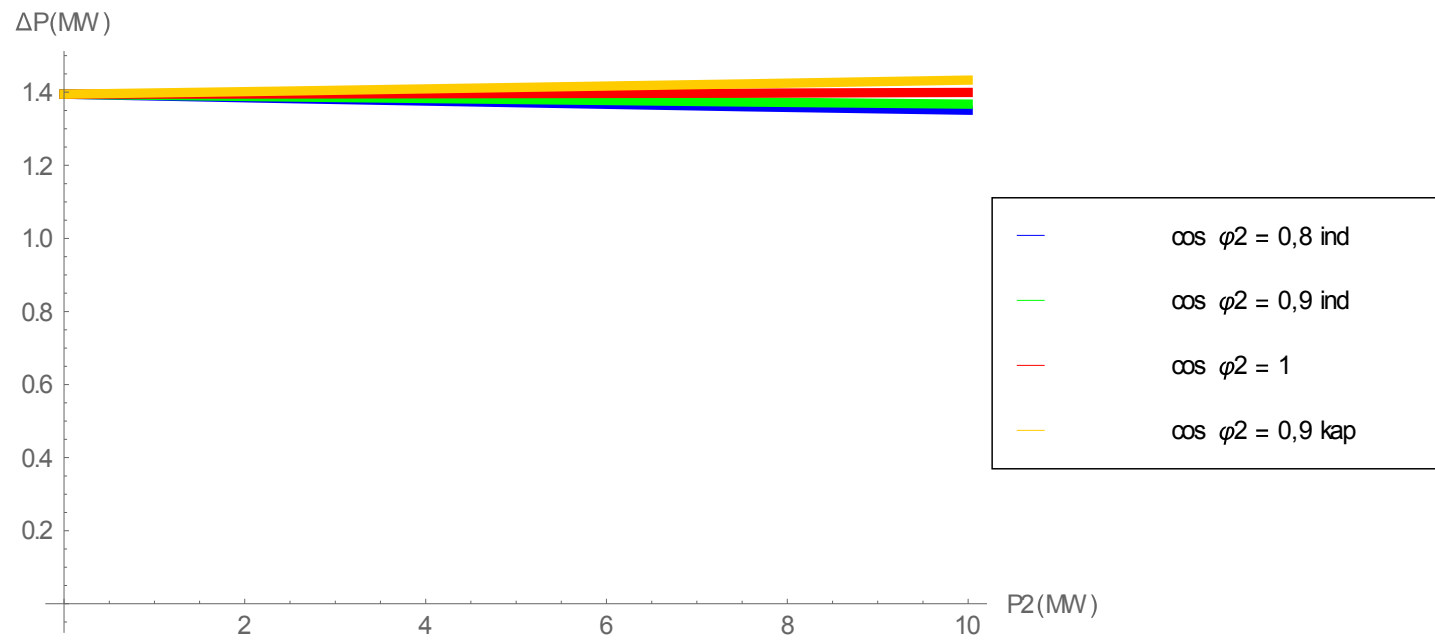

## Transmission efficiency

$$\eta = \frac{P_2}{P_1}$$

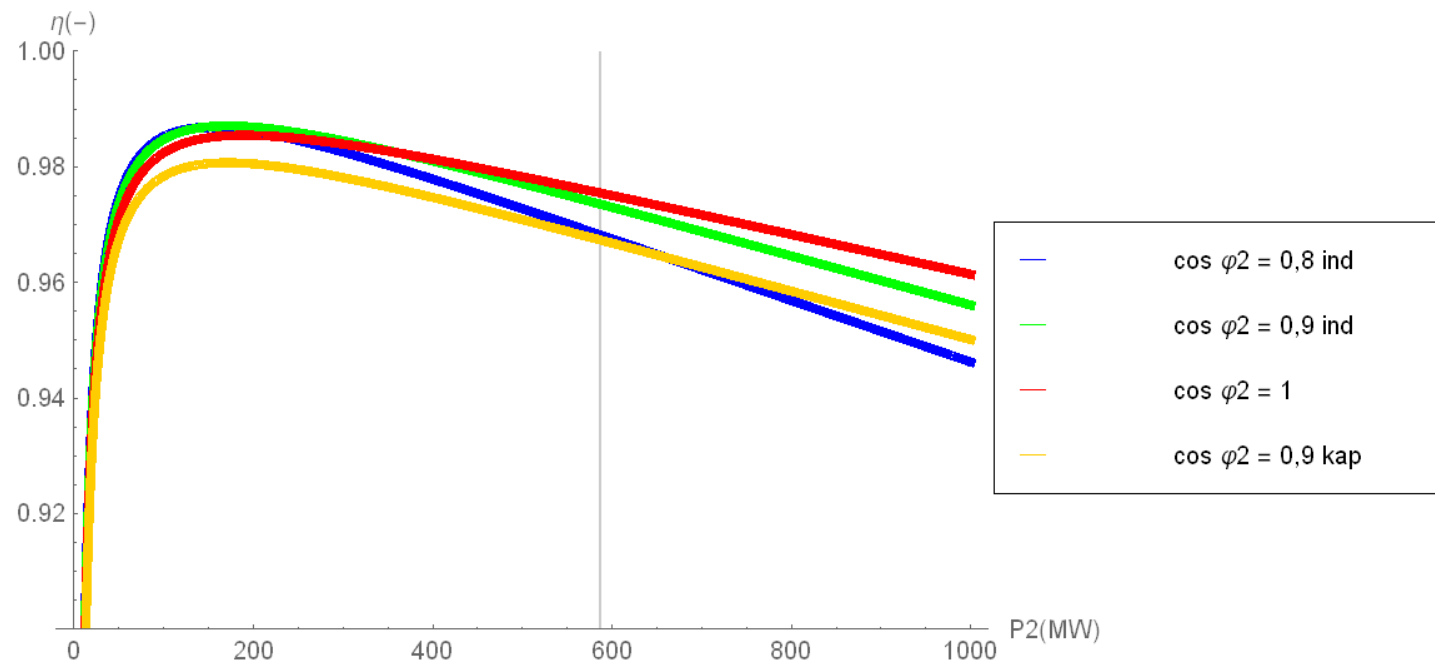

maximum for low powers  
for higher powers a flat curve

## Newton-Raphson method

- the most often method for non-linear equations
- it uses Taylor polynomial
- it converts non-linear equations solution to linear equations solution, gradually higher precision of the estimation

### Basic idea

$$f(x) = c$$

If  $x^{(0)}$  is the initial estimation and  $\Delta x^{(0)}$  is the difference from the right solution, then

$$f(x^{(0)} + \Delta x^{(0)}) = c$$

## Taylor series

$$f(\mathbf{x}) \Big|_{\mathbf{x}_0} = \sum_{k=0}^{\infty} \frac{\left( \frac{df(\mathbf{x}_0)}{d\mathbf{x}} \right)^{(k)}}{k!} (\mathbf{x} - \mathbf{x}_0)^k$$

## Expansion to the Taylor series

$$f(\mathbf{x}^{(0)}) + \left( \frac{df}{d\mathbf{x}} \right)^{(0)} \Delta\mathbf{x}^{(0)} + \frac{1}{2!} \left( \frac{d^2f}{d\mathbf{x}^2} \right)^{(0)} (\Delta\mathbf{x}^{(0)})^2 + \dots = \mathbf{c}$$

## Higher orders neglecting (linearization)

$$\Delta\mathbf{c}^{(0)} \approx \left( \frac{df}{d\mathbf{x}} \right)^{(0)} \Delta\mathbf{x}^{(0)}$$

where

$$\Delta\mathbf{c}^{(0)} = \mathbf{c} - f(\mathbf{x}^{(0)})$$

is called “defect”.

Adding  $\Delta \mathbf{x}^{(0)}$  to the initial estimation gives the second approximation

$$\mathbf{x}^{(1)} = \mathbf{x}^{(0)} + \frac{\Delta \mathbf{c}^{(0)}}{\left(\frac{d\mathbf{f}}{d\mathbf{x}}\right)^{(0)}}$$

(Note: impossible if the derivative equals zero)

The same relations in the next steps give the method algorithm:

$$\Delta \mathbf{c}^{(k)} = \mathbf{c} - \mathbf{f}(\mathbf{x}^{(k)})$$

$$\Delta \mathbf{x}^{(k)} = \frac{\Delta \mathbf{c}^{(k)}}{\left(\frac{d\mathbf{f}}{d\mathbf{x}}\right)^{(k)}}$$

$$\mathbf{x}^{(k+1)} = \mathbf{x}^{(k)} + \Delta \mathbf{x}^{(k)}$$

$$\Delta \mathbf{c}^{(k+1)} = \mathbf{c} - \mathbf{f}(\mathbf{x}^{(k+1)})$$

## The system of n equations with n unknowns

$$f_1(x_1, x_2, \dots, x_n) = c_1$$

$$f_2(x_1, x_2, \dots, x_n) = c_2$$

.....

$$f_n(x_1, x_2, \dots, x_n) = c_n$$

### Expansion to the Taylor series

$$(f_1)^{(0)} + \left(\frac{\partial f_1}{\partial x_1}\right)^{(0)} \Delta x_1^{(0)} + \left(\frac{\partial f_1}{\partial x_2}\right)^{(0)} \Delta x_2^{(0)} + \dots + \left(\frac{\partial f_1}{\partial x_n}\right)^{(0)} \Delta x_n^{(0)} = c_1$$

$$(f_2)^{(0)} + \left(\frac{\partial f_2}{\partial x_1}\right)^{(0)} \Delta x_1^{(0)} + \left(\frac{\partial f_2}{\partial x_2}\right)^{(0)} \Delta x_2^{(0)} + \dots + \left(\frac{\partial f_2}{\partial x_n}\right)^{(0)} \Delta x_n^{(0)} = c_2$$

.....



$$(\mathbf{f}_n)^{(0)} + \left( \frac{\partial \mathbf{f}_n}{\partial \mathbf{x}_1} \right)^{(0)} \Delta \mathbf{x}_1^{(0)} + \left( \frac{\partial \mathbf{f}_n}{\partial \mathbf{x}_2} \right)^{(0)} \Delta \mathbf{x}_2^{(0)} + \dots + \left( \frac{\partial \mathbf{f}_n}{\partial \mathbf{x}_n} \right)^{(0)} \Delta \mathbf{x}_n^{(0)} = \mathbf{c}_n$$

Matrix expression

$$\begin{pmatrix} \mathbf{c}_1 - (\mathbf{f}_1^{(0)}) \\ \mathbf{c}_2 - (\mathbf{f}_2^{(0)}) \\ \vdots \\ \mathbf{c}_n - (\mathbf{f}_n^{(0)}) \end{pmatrix} = \begin{pmatrix} \left( \frac{\partial \mathbf{f}_1}{\partial \mathbf{x}_1} \right)^{(0)} & \left( \frac{\partial \mathbf{f}_1}{\partial \mathbf{x}_2} \right)^{(0)} & \dots & \left( \frac{\partial \mathbf{f}_1}{\partial \mathbf{x}_n} \right)^{(0)} \\ \left( \frac{\partial \mathbf{f}_2}{\partial \mathbf{x}_1} \right)^{(0)} & \left( \frac{\partial \mathbf{f}_2}{\partial \mathbf{x}_2} \right)^{(0)} & \dots & \left( \frac{\partial \mathbf{f}_2}{\partial \mathbf{x}_n} \right)^{(0)} \\ \vdots & \vdots & \vdots & \vdots \\ \left( \frac{\partial \mathbf{f}_n}{\partial \mathbf{x}_1} \right)^{(0)} & \left( \frac{\partial \mathbf{f}_n}{\partial \mathbf{x}_2} \right)^{(0)} & \dots & \left( \frac{\partial \mathbf{f}_n}{\partial \mathbf{x}_n} \right)^{(0)} \end{pmatrix} \cdot \begin{pmatrix} \Delta \mathbf{x}_1^{(0)} \\ \Delta \mathbf{x}_2^{(0)} \\ \vdots \\ \Delta \mathbf{x}_n^{(0)} \end{pmatrix}$$

in short

$$(\Delta \mathbf{C}^{(0)}) = (\mathbf{J}^{(0)}) \cdot (\Delta \mathbf{X}^{(0)})$$

Hence

$$\left(\Delta X^{(0)}\right) = \left(J^{(0)}\right)^{-1} \cdot \left(\Delta C^{(0)}\right)$$

The method algorithm:

$$\left(\Delta C^{(k)}\right) = \begin{pmatrix} c_1 - (f_1^{(k)}) \\ c_2 - (f_2^{(k)}) \\ \vdots \\ c_n - (f_n^{(k)}) \end{pmatrix}$$

$$\left(\Delta X^{(k)}\right) = \left(J^{(k)}\right)^{-1} \cdot \left(\Delta C^{(k)}\right)$$

$$\left(X^{(k+1)}\right) = \left(X^{(k)}\right) + \left(\Delta X^{(k)}\right)$$

$$\left( \Delta \mathbf{C}^{(k+1)} \right) = \begin{pmatrix} \mathbf{c}_1 - (\mathbf{f}_1^{(k+1)}) \\ \mathbf{c}_2 - (\mathbf{f}_2^{(k+1)}) \\ \vdots \\ \mathbf{c}_n - (\mathbf{f}_n^{(k+1)}) \end{pmatrix} \quad \text{where} \quad \left( \Delta \mathbf{X}^{(k)} \right) = \begin{pmatrix} \Delta \mathbf{x}_1^{(k)} \\ \Delta \mathbf{x}_2^{(k)} \\ \vdots \\ \Delta \mathbf{x}_n^{(k)} \end{pmatrix}$$

$$\left( \mathbf{J}^{(k)} \right) = \begin{pmatrix} \left( \frac{\partial \mathbf{f}_1}{\partial \mathbf{x}_1} \right)^{(k)} & \left( \frac{\partial \mathbf{f}_1}{\partial \mathbf{x}_2} \right)^{(k)} & \dots & \left( \frac{\partial \mathbf{f}_1}{\partial \mathbf{x}_n} \right)^{(k)} \\ \left( \frac{\partial \mathbf{f}_2}{\partial \mathbf{x}_1} \right)^{(k)} & \left( \frac{\partial \mathbf{f}_2}{\partial \mathbf{x}_2} \right)^{(k)} & \dots & \left( \frac{\partial \mathbf{f}_2}{\partial \mathbf{x}_n} \right)^{(k)} \\ \vdots & \vdots & \vdots & \vdots \\ \left( \frac{\partial \mathbf{f}_n}{\partial \mathbf{x}_1} \right)^{(k)} & \left( \frac{\partial \mathbf{f}_n}{\partial \mathbf{x}_2} \right)^{(k)} & \dots & \left( \frac{\partial \mathbf{f}_n}{\partial \mathbf{x}_n} \right)^{(k)} \end{pmatrix}$$

$(\mathbf{J}^{(k)})$  – Jakobi matrix, regularity assumption

## Load Flow solution

U-I equations system can be extended to voltage-power dependence

$$\hat{I}_k = \sum_{m=1}^n \hat{U}_{fm} \hat{Y}_{(k,m)}$$

$$\hat{S}_k = 3\hat{S}_{fk} = 3\hat{U}_{fk} \hat{I}_k^* = 3\hat{U}_{fk} \sum_{m=1}^n \hat{U}_{fm}^* \hat{Y}_{(k,m)}^*$$

$$\hat{S}_k = \hat{U}_k \sum_{m=1}^n \hat{U}_m^* \hat{Y}_{(k,m)}^*$$

$$\left(\hat{S}\right) = \left(\hat{U}_{\text{diag}}\right) \left(\hat{Y}^*\right) \left(\hat{U}^*\right)$$

$$\begin{pmatrix} \hat{S}_1 \\ \dots \\ \hat{S}_k \\ \dots \\ \hat{S}_n \end{pmatrix} = \begin{pmatrix} \hat{U}_1 & 0 & 0 & 0 & 0 \\ 0 & \dots & 0 & 0 & 0 \\ 0 & 0 & \hat{U}_k & 0 & 0 \\ 0 & 0 & 0 & \dots & 0 \\ 0 & 0 & 0 & 0 & \hat{U}_n \end{pmatrix} \cdot \begin{pmatrix} \hat{Y}_{(1,1)}^* & \dots & \dots & \dots & \hat{Y}_{(1,n)}^* \\ \dots & \dots & \dots & \dots & \dots \\ \hat{Y}_{(k,1)}^* & \dots & \hat{Y}_{(k,k)}^* & \dots & \hat{Y}_{(k,n)}^* \\ \dots & \dots & \dots & \dots & \dots \\ \hat{Y}_{(n,1)}^* & \dots & \dots & \dots & \hat{Y}_{(n,n)}^* \end{pmatrix} \cdot \begin{pmatrix} \hat{U}_1^* \\ \dots \\ \hat{U}_k^* \\ \dots \\ \hat{U}_n^* \end{pmatrix}$$

- powers defined  $\rightarrow$  nonlinearity

Aim: to calculate  $\mathbf{P}$ ,  $\mathbf{Q}$ ,  $\mathbf{U}$ ,  $\delta$  in nodes and branches

Note: Assumption of symmetrical system and its loading  $\rightarrow$  single phase models.

## Bus types

Bus power		Bus voltage phasor components	
defined	to be calculated	defined	to be calculated
–	$P, Q$	$U, \delta$	–
$P, Q$	–	–	$U, \delta$
$P$	$Q$	$U$	$\delta$
$Q$	$P$	$\delta$	$U$

slack (swing bus) – „balance bus“, balance P, Q for losses, as a huge system, large generation

PQ – loads

PU – generators, controlled voltage

### Quantities

- fixed – requirements (P, Q for loads; P for generators)
- state – independent variables (U,  $\delta$  for loads;  $\delta$  for generators)
- control – here no changes (U for slack and generators), they change in optimization procedures

## Calculations in relative values

### Denominated values

$$\hat{S} = 3\hat{U}_f\hat{I}^* = \sqrt{3}\hat{U}\hat{I}^* \quad \hat{U}_f = \hat{Z}\hat{I} \quad \hat{U} = \sqrt{3}\hat{Z}\hat{I}$$

### Base values

$$\hat{S}_v = \sqrt{3}\hat{U}_v\hat{I}_v^*$$
$$\hat{Z}_v = \frac{\hat{U}_v}{\sqrt{3}\hat{I}_v} = \frac{\hat{U}_v}{\sqrt{3}\left(\frac{\hat{S}_v}{\sqrt{3}\hat{U}_v}\right)^*} = \frac{U_v^2}{\hat{S}_v^*}$$

### Relative values

$$\hat{s} \cdot S_v = \sqrt{3} \cdot \hat{u} \cdot U_v \cdot \hat{i}^* \cdot I_v^*$$

$$\underline{\hat{s} = \hat{u} \cdot \hat{i}^*}$$

$$\hat{u} \cdot U_v = \sqrt{3} \cdot \hat{z} \cdot Z_v \cdot \hat{i} \cdot I_v$$

$$\underline{\hat{u} = \hat{z} \cdot \hat{i}}$$

## Bus current (single phase)

$$\hat{I}_k = \hat{U}_{fk} \left( \sum_{\substack{m=1 \\ m \neq k}}^n \hat{Y}_{km} + \hat{Y}_{k0} \right) - \sum_{\substack{m=1 \\ m \neq k}}^n \hat{U}_{fm} \hat{Y}_{km}$$

$$\hat{i}_i = \hat{u}_i \sum_{\substack{j=0 \\ j \neq i}}^n \hat{y}_{ij} - \sum_{\substack{j=1 \\ j \neq i}}^n \hat{y}_{ij} \hat{u}_j$$

## Bus power

$$p_i + jq_i = \hat{u}_i \cdot \hat{i}_i^* \qquad \hat{i}_i = \frac{p_i - jq_i}{\hat{u}_i^*}$$

hence

$$\frac{p_i - jq_i}{\hat{u}_i^*} = \hat{u}_i \sum_{\substack{j=0 \\ j \neq i}}^n \hat{y}_{ij} - \sum_{\substack{j=1 \\ j \neq i}}^n \hat{y}_{ij} \hat{u}_j$$



## Newton-Raphson Power Flow Solution

$$\hat{S}_i = \hat{U}_i \sum_{j=1}^n \hat{U}_j^* \hat{Y}_{(i,j)}^* = U_i^2 \hat{Y}_{(i,i)}^* + \hat{U}_i \sum_{\substack{j=1 \\ j \neq i}}^n \hat{U}_j^* \hat{Y}_{(i,j)}^*$$

$$\hat{S}_i = f_i(\hat{U})$$

### Exponential form

$$\hat{S}_i = P_i + jQ_i \quad \hat{U}_i = U_i e^{j\delta_i} \quad \hat{Y}_{(i,j)} = Y_{(i,j)} e^{j\theta_{(i,j)}}$$

$$\hat{S}_i = U_i e^{j\delta_i} \sum_{j=1}^n U_j Y_{(i,j)} e^{-j(\delta_j + \theta_{(i,j)})}$$

Power separated into the real and imaginary part

$$P_i = \sum_{j=1}^n U_i U_j Y_{(i,j)} \cos(\delta_i - \delta_j - \theta_{(i,j)})$$

$$Q_i = \sum_{j=1}^n U_i U_j Y_{(i,j)} \sin(\delta_i - \delta_j - \theta_{(i,j)})$$

→ 2 equations for each PQ bus, 1 equation for each PU bus

The power changes are expressed (linearization)

$$\Delta \hat{S}_i = \sum_{j=1}^n \left( \frac{\partial \hat{S}_i}{\partial \delta_j} \Delta \delta_j + \frac{\partial \hat{S}_i}{\partial U_j} \Delta U_j \right)$$

$$\Delta P_i = \sum_{j=1}^n \left( \frac{\partial P_i}{\partial \delta_j} \Delta \delta_j + \frac{\partial P_i}{\partial U_j} \Delta U_j \right)$$

$$\Delta Q_i = \sum_{j=1}^n \left( \frac{\partial Q_i}{\partial \delta_j} \Delta \delta_j + \frac{\partial Q_i}{\partial U_j} \Delta U_j \right)$$

## Complete equation description

$$\begin{pmatrix} \Delta P_2^{(k)} \\ \dots \\ \Delta P_n^{(k)} \\ \Delta Q_2^{(k)} \\ \dots \\ \Delta Q_n^{(k)} \end{pmatrix} = \begin{pmatrix} \frac{\partial P_2^{(k)}}{\partial \delta_2} & \dots & \frac{\partial P_2^{(k)}}{\partial \delta_n} & \frac{\partial P_2^{(k)}}{\partial U_2} & \dots & \frac{\partial P_2^{(k)}}{\partial U_n} \\ \vdots & \ddots & \vdots & \vdots & \ddots & \vdots \\ \frac{\partial P_n^{(k)}}{\partial \delta_2} & \dots & \frac{\partial P_n^{(k)}}{\partial \delta_n} & \frac{\partial P_n^{(k)}}{\partial U_2} & \dots & \frac{\partial P_n^{(k)}}{\partial U_n} \\ \frac{\partial Q_2^{(k)}}{\partial \delta_2} & \dots & \frac{\partial Q_2^{(k)}}{\partial \delta_n} & \frac{\partial Q_2^{(k)}}{\partial U_2} & \dots & \frac{\partial Q_2^{(k)}}{\partial U_n} \\ \vdots & \ddots & \vdots & \vdots & \ddots & \vdots \\ \frac{\partial Q_n^{(k)}}{\partial \delta_2} & \dots & \frac{\partial Q_n^{(k)}}{\partial \delta_n} & \frac{\partial Q_n^{(k)}}{\partial U_2} & \dots & \frac{\partial Q_n^{(k)}}{\partial U_n} \end{pmatrix} \cdot \begin{pmatrix} \Delta \delta_2^{(k)} \\ \dots \\ \Delta \delta_n^{(k)} \\ \Delta U_2^{(k)} \\ \dots \\ \Delta U_n^{(k)} \end{pmatrix}$$

More compact equations form

$$\begin{pmatrix} \Delta P \\ \Delta Q \end{pmatrix} = \begin{pmatrix} \frac{\partial P}{\partial \delta} & \frac{\partial P}{\partial U} \\ \frac{\partial Q}{\partial \delta} & \frac{\partial Q}{\partial U} \end{pmatrix} \begin{pmatrix} \Delta \delta \\ \Delta U \end{pmatrix}$$

$$(J) = \begin{pmatrix} \frac{\partial P}{\partial \delta} & \frac{\partial P}{\partial U} \\ \frac{\partial Q}{\partial \delta} & \frac{\partial Q}{\partial U} \end{pmatrix} = \begin{pmatrix} J_1 & J_2 \\ J_3 & J_4 \end{pmatrix}$$

Equations number for  $n$  buses,  $s$  slacks,  $m$  PU buses,  $p$  PQ buses ( $n = s + m + p$ ):

$\Delta P \times (n-s)$ ,  $\Delta Q \times (n-s-m)$

$$P_i = \sum_{j=1}^n U_i U_j Y_{(i,j)} \cos(\delta_i - \delta_j - \theta_{(i,j)})$$

$$\frac{\partial P_i}{\partial \delta_i} = \sum_{\substack{j=1 \\ j \neq i}}^n U_i U_j Y_{(i,j)} \sin(-\delta_i + \delta_j + \theta_{(i,j)})$$

$$\frac{\partial P_i}{\partial \delta_j} = U_i U_j Y_{(i,j)} \sin(\delta_i - \delta_j - \theta_{(i,j)}) \quad j \neq i$$

$$\frac{\partial P_i}{\partial U_i} = 2U_i Y_{(i,i)} \cos(\theta_{(i,i)}) + \sum_{\substack{j=1 \\ j \neq i}}^n U_j Y_{(i,j)} \cos(\delta_i - \delta_j - \theta_{(i,j)})$$

$$\frac{\partial P_i}{\partial U_j} = U_i Y_{(i,j)} \cos(\delta_i - \delta_j - \theta_{(i,j)}) \quad j \neq i$$

$$Q_i = \sum_{j=1}^n U_i U_j Y_{(i,j)} \sin(\delta_i - \delta_j - \theta_{(i,j)})$$

$$\frac{\partial Q_i}{\partial \delta_i} = \sum_{\substack{j=1 \\ j \neq i}}^n U_i U_j Y_{(i,j)} \cos(\delta_i - \delta_j - \theta_{(i,j)})$$

$$\frac{\partial Q_i}{\partial \delta_j} = -U_i U_j Y_{(i,j)} \cos(\delta_i - \delta_j - \theta_{(i,j)}) \quad j \neq i$$

$$\frac{\partial Q_i}{\partial U_i} = -2U_i Y_{(i,i)} \sin(\theta_{(i,i)}) + \sum_{\substack{j=1 \\ j \neq i}}^n U_j Y_{(i,j)} \sin(\delta_i - \delta_j - \theta_{(i,j)})$$

$$\frac{\partial Q_i}{\partial U_j} = U_i Y_{(i,j)} \sin(\delta_i - \delta_j - \theta_{(i,j)}) \quad j \neq i$$

## Iterative solution idea

$$\begin{pmatrix} \delta \\ \mathbf{U} \end{pmatrix}_k$$

$$\text{defect} \begin{pmatrix} \Delta \mathbf{P} \\ \Delta \mathbf{Q} \end{pmatrix}$$

$$\begin{pmatrix} \Delta \delta \\ \Delta \mathbf{U} \end{pmatrix} = (\mathbf{J})^{-1} \begin{pmatrix} \Delta \mathbf{P} \\ \Delta \mathbf{Q} \end{pmatrix}$$

$$\begin{pmatrix} \delta \\ \mathbf{U} \end{pmatrix}_{k+1} = \begin{pmatrix} \delta \\ \mathbf{U} \end{pmatrix}_k + \begin{pmatrix} \Delta \delta \\ \Delta \mathbf{U} \end{pmatrix}$$