

Task 8: Waves on Transmission Lines

(Laboratory G1-116)

Determine by measurement the voltage waveforms at the reflection of waves on different terminations of a transmission line.


- Verify the wave impedance of coaxial cable 198 meters long and determine the speed of electromagnetic wave propagation in the cable.
- Record the voltage waveforms in the showed measurement circuit for these different cable terminations:

- no-load
- short circuit
- resistance higher and lower than the wave impedance
- resistance equal to the wave impedance
- capacitance 10 nF
- inductance 31 μ H

Used equipment:

- G function generator
- OSC Digital oscilloscope LeCroy
- P voltage probe 1:10
- C coaxial cable 198 meters long
- Z terminating impedance (resistor, capacitor, inductor)

Measurement circuit:

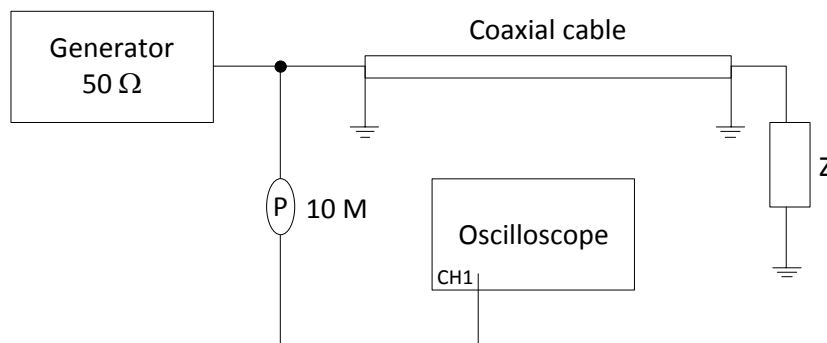

- The generator output is with impedance 50 Ω
- The coaxial cable is supplied by a square pulse signal with amplitude 4 V under 50 Ω output, measured voltage is led by voltage probe to oscilloscope input (the same time decay is chosen for all types of terminating \rightarrow 500 ns/div)
- The offset should be set at +2 V \rightarrow output is square pulses 0 - 4V - 0 - 4V
- Used terminating capacitance is $C = 10$ nF (decade) and inductance is $L = 31$ μ H (between top and bottom terminals of the small air coil)
- The wave resistance is 50 Ω , need time for a wave transmission to the end of the cable and back is about 1 μ s
- The comparison between waveforms should be a laboratory result (plots of waveforms in the XY plot for each type of terminations)