


## Three phase HV systems

Transmission lines, international connections.

Goal: relations between input and output ends, losses, efficiency. RLGC
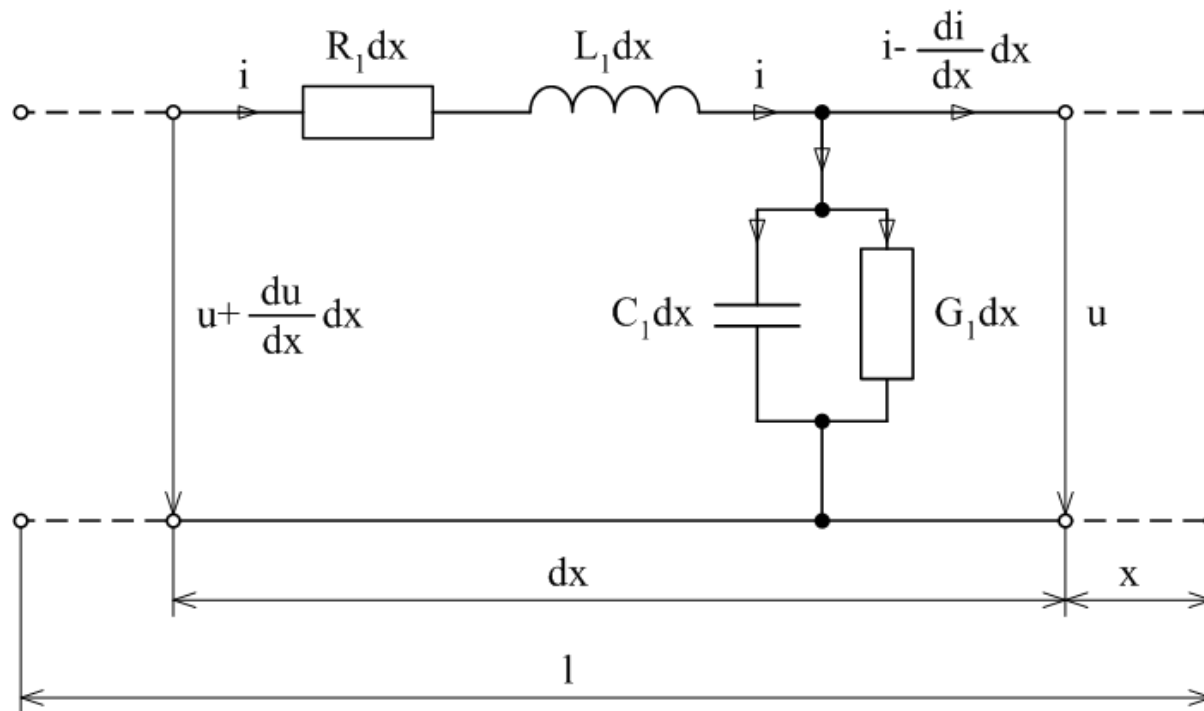
### Line with distributed parameters

Homogeneous line - parameters  $R_1$ ,  $L_1$ ,  $G_1$ ,  $C_1$  are equally distributed through all line length.



## 2nd Kirchhoff law

$$u + \frac{\partial u}{\partial x} dx - u - R_1 dx \cdot i - L_1 dx \frac{\partial i}{\partial t} = 0$$

$$\frac{\partial u}{\partial x} = R_1 i + L_1 \frac{\partial i}{\partial t}$$

## 1st Kirchhoff law

$$i - \frac{\partial i}{\partial x} dx - i + G_1 dx \cdot u + C_1 dx \frac{\partial u}{\partial t} = 0$$

$$\frac{\partial i}{\partial x} = G_1 u + C_1 \frac{\partial u}{\partial t}$$

For AC voltage (current):

$$u(t) = \text{Im} \left\{ \sqrt{2} \hat{U}_f e^{j\omega t} \right\}$$

$$\frac{\partial u(t)}{\partial x} = \sqrt{2} \text{Im} \left\{ \frac{d\hat{U}_f}{dx} e^{j\omega t} \right\}$$

$$\frac{\partial u(t)}{\partial t} = \sqrt{2} \text{Im} \left\{ j\omega \hat{U}_f e^{j\omega t} \right\}$$

After substitution:

$$\frac{d\hat{U}_f}{dx} = (\mathbf{R}_1 + j\omega\mathbf{L}_1)\hat{\mathbf{I}} = \hat{\mathbf{Z}}_{l_1} \hat{\mathbf{I}}$$

$$\frac{d\hat{\mathbf{I}}}{dx} = (\mathbf{G}_1 + j\omega\mathbf{C}_1)\hat{U}_f = \hat{\mathbf{Y}}_{q_1} \hat{U}_f$$

After derivation and substitution get wave equations:

$$\frac{d^2\hat{U}_f}{dx^2} = \hat{\mathbf{Z}}_{l_1} \frac{d\hat{\mathbf{I}}}{dx} = \hat{\mathbf{Z}}_{l_1} \hat{\mathbf{Y}}_{q_1} \hat{U}_f = \hat{\gamma}^2 \hat{U}_f$$

$$\frac{d^2\hat{\mathbf{I}}}{dx^2} = \hat{\mathbf{Y}}_{q_1} \frac{d\hat{U}_f}{dx} = \hat{\mathbf{Z}}_{l_1} \hat{\mathbf{Y}}_{q_1} \hat{\mathbf{I}} = \hat{\gamma}^2 \hat{\mathbf{I}}$$

Complex transmission constant:

$$\hat{\gamma} = \sqrt{\hat{\mathbf{Z}}_{l_1} \hat{\mathbf{Y}}_{q_1}} \quad (\text{km}^{-1}; \Omega \cdot \text{km}^{-1}, \text{S} \cdot \text{km}^{-1})$$

Note: For time area get telegrapher's equations (mathematically is wave equation for  $R = G = 0$ )

$$\frac{\partial^2 u(t, x)}{\partial x^2} = R_1 G_1 u(t, x) + (R_1 C_1 + L_1 G_1) \frac{\partial u(t, x)}{\partial t} + L_1 C_1 \frac{\partial^2 u(t, x)}{\partial t^2}$$

Ordinary wave equation is second-order linear ordinary differential equation (char. equation  $\hat{\lambda}^2 - \hat{\gamma}^2 = 0$ ) – forward-and-backward wave

$$\hat{U}_f = \hat{K}_1 e^{\hat{\gamma}x} + \hat{K}_2 e^{-\hat{\gamma}x}$$

$$\hat{I} = \frac{d\hat{U}_f}{dx} \frac{1}{\hat{Z}_{l_1}} = \frac{\hat{\gamma}}{\hat{Z}_{l_1}} (\hat{K}_1 e^{\hat{\gamma}x} - \hat{K}_2 e^{-\hat{\gamma}x}) = \sqrt{\frac{\hat{Y}_{q_1}}{\hat{Z}_{l_1}}} (\hat{K}_1 e^{\hat{\gamma}x} - \hat{K}_2 e^{-\hat{\gamma}x})$$

$$\hat{I} = \frac{1}{\hat{Z}_v} (\hat{K}_1 e^{\hat{\gamma}x} - \hat{K}_2 e^{-\hat{\gamma}x})$$

Characteristic impedance:

$$\hat{Z}_v = \sqrt{\frac{\hat{Z}_{l_1}}{\hat{Y}_{q_1}}} \quad (\Omega; \Omega \cdot \text{km}^{-1}, \text{S} \cdot \text{km}^{-1})$$

Integration constant  $\hat{K}_1, \hat{K}_2$  are evaluated from boundary value. At the end of line ( $x = 0$ ) index 2, beginning of the line ( $x = l$ ) index 1.

For  $x = 0$ :

$$\hat{U}_{f2} = \hat{K}_1 + \hat{K}_2$$
$$\hat{I}_2 = \frac{1}{\hat{Z}_v} (\hat{K}_1 - \hat{K}_2)$$

Hence:

$$\hat{K}_1 = \frac{1}{2} (\hat{U}_{f2} + \hat{Z}_v \hat{I}_2)$$
$$\hat{K}_2 = \frac{1}{2} (\hat{U}_{f2} - \hat{Z}_v \hat{I}_2)$$

For  $x = l$ :

$$\hat{U}_{f1} = \hat{U}_{f2} \frac{e^{\hat{\gamma}l} + e^{-\hat{\gamma}l}}{2} + \hat{Z}_v \hat{I}_2 \frac{e^{\hat{\gamma}l} - e^{-\hat{\gamma}l}}{2}$$

$$\hat{I}_1 = \frac{\hat{U}_{f2}}{\hat{Z}_v} \frac{e^{\hat{\gamma}l} - e^{-\hat{\gamma}l}}{2} + \hat{I}_2 \frac{e^{\hat{\gamma}l} + e^{-\hat{\gamma}l}}{2}$$

Definition of hyperbolic function:

$$\hat{U}_{f1} = \hat{U}_{f2} \cosh \hat{\gamma}l + \hat{Z}_v \hat{I}_2 \sinh \hat{\gamma}l$$

---

$$\hat{I}_1 = \frac{\hat{U}_{f2}}{\hat{Z}_v} \sinh \hat{\gamma}l + \hat{I}_2 \cosh \hat{\gamma}l$$

---

At matrix form:

$$\begin{pmatrix} \hat{U}_{f1} \\ \hat{I}_1 \end{pmatrix} = \begin{pmatrix} \hat{A} & \hat{B} \\ \hat{C} & \hat{D} \end{pmatrix} \begin{pmatrix} \hat{U}_{f2} \\ \hat{I}_2 \end{pmatrix}$$

where  $\hat{A}(-)$ ,  $\hat{B}(\Omega)$ ,  $\hat{C}(S)$ ,  $\hat{D}(-)$  are Blondel constant


valid  $\hat{A} = \hat{D}$ ,  $\hat{A}\hat{D} - \hat{B}\hat{C} = 1$

$$(\cosh \hat{\gamma}l)^2 - (\sinh \hat{\gamma}l)^2 = 1$$


(symmetrical, passive two-port connection)

Set values at the beginning of the line:
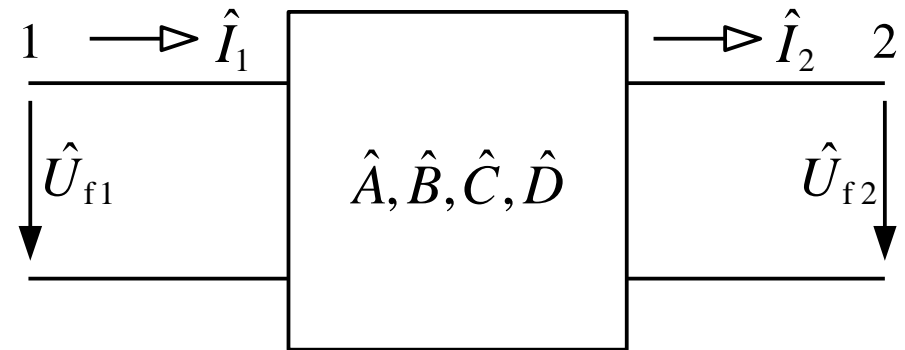
$$\begin{pmatrix} \hat{U}_{f2} \\ \hat{I}_2 \end{pmatrix} = \begin{pmatrix} \hat{D} & -\hat{B} \\ -\hat{C} & \hat{A} \end{pmatrix} \begin{pmatrix} \hat{U}_{f1} \\ \hat{I}_1 \end{pmatrix}$$



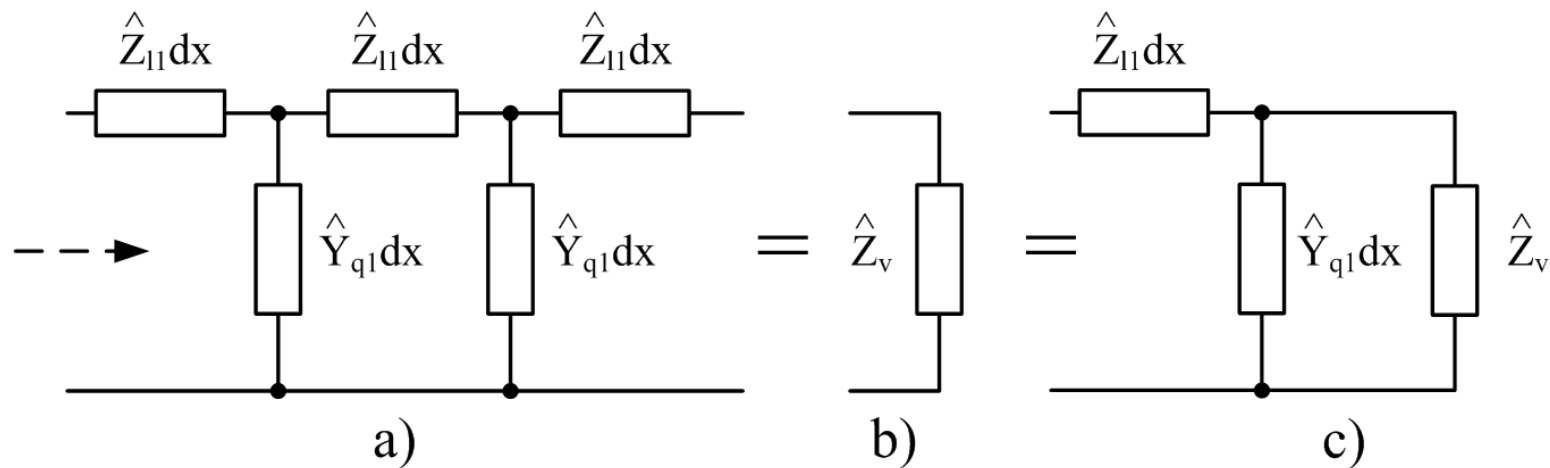Characteristic impedance = impedance of the infinite long line.



Input impedance:

$$\hat{Z}_v = \hat{Z}_{l1} dx + \frac{\hat{Z}_v \cdot (\hat{Y}_{q1} dx)^{-1}}{\hat{Z}_v + (\hat{Y}_{q1} dx)^{-1}}$$

$$\hat{Z}_v^2 - \hat{Z}_{l1} dx \cdot \hat{Z}_v - \hat{Z}_{l1} dx \cdot (\hat{Y}_{q1} dx)^{-1} = 0$$

$$\hat{Z}_v = \frac{\hat{Z}_{l1} dx \pm \sqrt{(\hat{Z}_{l1} dx)^2 + 4\hat{Z}_{l1} dx \cdot (\hat{Y}_{q1} dx)^{-1}}}{2}$$



Continues distribution of parameters for  $dx \rightarrow 0$ :

$$\hat{Z}_v = \sqrt{\frac{\hat{Z}_{l_1}}{\hat{Y}_{q_1}}}$$

Ideal line  $-R = 0$  and  $G = 0$ . For higher voltage levels model does not allow to calculate losses.

$$\hat{\gamma} = \sqrt{(R_1 + jX_1)(G_1 + jB_1)} = j\sqrt{X_1 B_1} = j\beta$$

$$\hat{Z}_v = \sqrt{\frac{R_1 + jX_1}{G_1 + jB_1}} = \sqrt{\frac{L_1}{C_1}} = Z_v$$

Change to trigonometric functions:

$$\cosh(j\beta l) = \frac{e^{j\beta l} + e^{-j\beta l}}{2} = \cos \beta l$$

$$\sinh(j\beta l) = \frac{e^{j\beta l} - e^{-j\beta l}}{2} = j \sin \beta l$$

Then

$$\hat{U}_{f1} = \hat{U}_{f2} \cos \beta l + jZ_v \hat{I}_2 \sin \beta l$$

$$\hat{I}_1 = j \frac{\hat{U}_{f2}}{Z_v} \sin \beta l + \hat{I}_2 \cos \beta l$$

$$(\cos \beta l)^2 - (j \cdot \sin \beta l)^2 = 1$$

Matched load – line at the end has load equal to characteristic impedance (for line's transmission capacity evaluation).

For imaginary infinite long line → power is transited just by forward wave, reflected is zero.

$$\hat{I}_2 = \frac{\hat{U}_{f2}}{\hat{Z}_v}$$

$$\hat{U}_{odr} = \frac{1}{2} (\hat{U}_{f2} - \hat{Z}_v \hat{I}_2) e^{-\hat{\gamma} l} = \hat{K}_2 e^{-\hat{\gamma} l} = 0$$

$$\hat{S}_{p2} = 3\hat{U}_{f2}\hat{I}_2^* = 3\hat{U}_{f2}\left(\frac{\hat{U}_{f2}}{\hat{Z}_v}\right)^* = \frac{U_2^2}{\hat{Z}_v^*}$$

(Active part is much bigger than imaginary → often in MW.)

$$\hat{U}_{f1} = \hat{U}_{f2}(\cosh \hat{\gamma}l + \sinh \hat{\gamma}l)$$

$$\hat{I}_1 = \hat{I}_2(\sinh \hat{\gamma}l + \cosh \hat{\gamma}l)$$

Phase between voltage and current does not change → reactive power at L and C are equal.

$$\frac{\hat{U}_{f(x)}}{\hat{I}_{(x)}} = \frac{\hat{U}_{f2}}{\hat{I}_2} = \hat{Z}_v$$

Along the line amplitude of voltage and current is declined (and active power).

$$\hat{U}_{f(x)} = \hat{U}_{f2}(\cosh \hat{\gamma}x + \sinh \hat{\gamma}x) = \hat{U}_{f2} \cdot e^{\hat{\gamma}x} = \hat{U}_{f2} \cdot e^{\alpha x} \cdot e^{j\beta x}$$

Overhead line:

$$Z_v = (250 \div 400) \Omega \quad \text{pro} \quad (400 \div 22) \text{ kV}$$

$$S_p = (1 \div 580) \text{ MW} \quad \text{pro} \quad (22 \div 400) \text{ kV}$$

For cable line is lower  $Z_v = (50 \div 70) \Omega \rightarrow$  higher  $S_p$

At ideal line voltage and current does not decline:

$$\hat{U}_{f1} = \hat{U}_{f2} \cos \beta l + j \hat{U}_{f2} \sin \beta l = \hat{U}_{f2} e^{j\beta l}$$

$$U_{f1} = U_{f2}$$

$$\hat{I}_1 = \hat{I}_2 e^{j\beta l}$$

## Open-circuit:

$$\hat{I}_2 = 0$$

$$\hat{U}_{f10} = \hat{U}_{f2} \cosh \hat{\gamma}l$$

$$\hat{I}_{10} = \frac{\hat{U}_{f2}}{\hat{Z}_v} \sinh \hat{\gamma}l$$

## For ideal line:

$$\hat{U}_{f10} = \hat{U}_{f2} \cos \beta l$$

$$\hat{I}_{10} = j \frac{\hat{U}_{f2}}{Z_v} \sin \beta l$$

Valid  $U_{f10} \leq U_{f2} \rightarrow$  Ferranti effect

Line is equal to capacity.

### Short-circuit:

$$\hat{U}_{f2} = 0$$

$$\hat{U}_{f1} = \hat{Z}_v \hat{I}_2 \sinh \hat{\gamma}l$$

$$\hat{I}_1 = \hat{I}_2 \cosh \hat{\gamma}l$$

### For ideal line:

$$\hat{U}_{f1} = jZ_v \hat{I}_2 \sin \beta l$$

$$\hat{I}_1 = \hat{I}_2 \cos \beta l$$

Voltage is declining from beginning to end.

Line is equal to induction.

Example:


Line 1 x 400kV with two ground wires

Phase conductor: 3x ACSR 450/52, ground wire: ACSR 185/31,  $l = 300$  km

$R_1 = 0,021 \Omega/\text{km}$ ;  $X_1 = 0,293 \Omega/\text{km}$ ;  $G_1 = 2 \cdot 10^{-8} \text{ S}/\text{km}$ ;  $B_1 = 3,9 \cdot 10^{-6} \text{ S}/\text{km}$


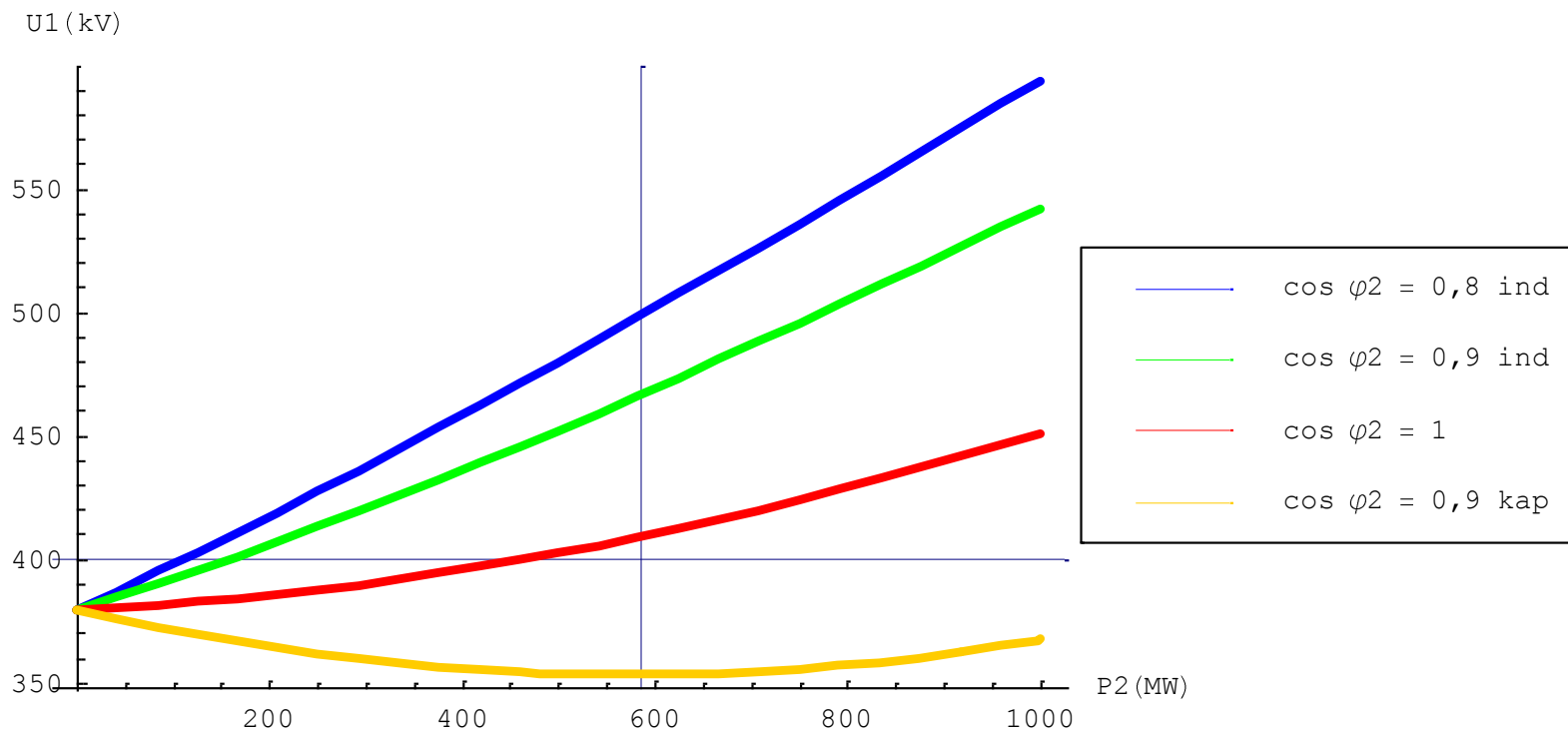
## Voltage level ( $U_2 = 400 \text{ kV}$ )




$U_1 < U_n$ : Ferranti effect

$U_1 \sim U_n$  for  $S_p$  area and  $\cos \varphi = 1$



## Transmission power factor


$$\cos \varphi_1 = \frac{P_1}{S_1}$$

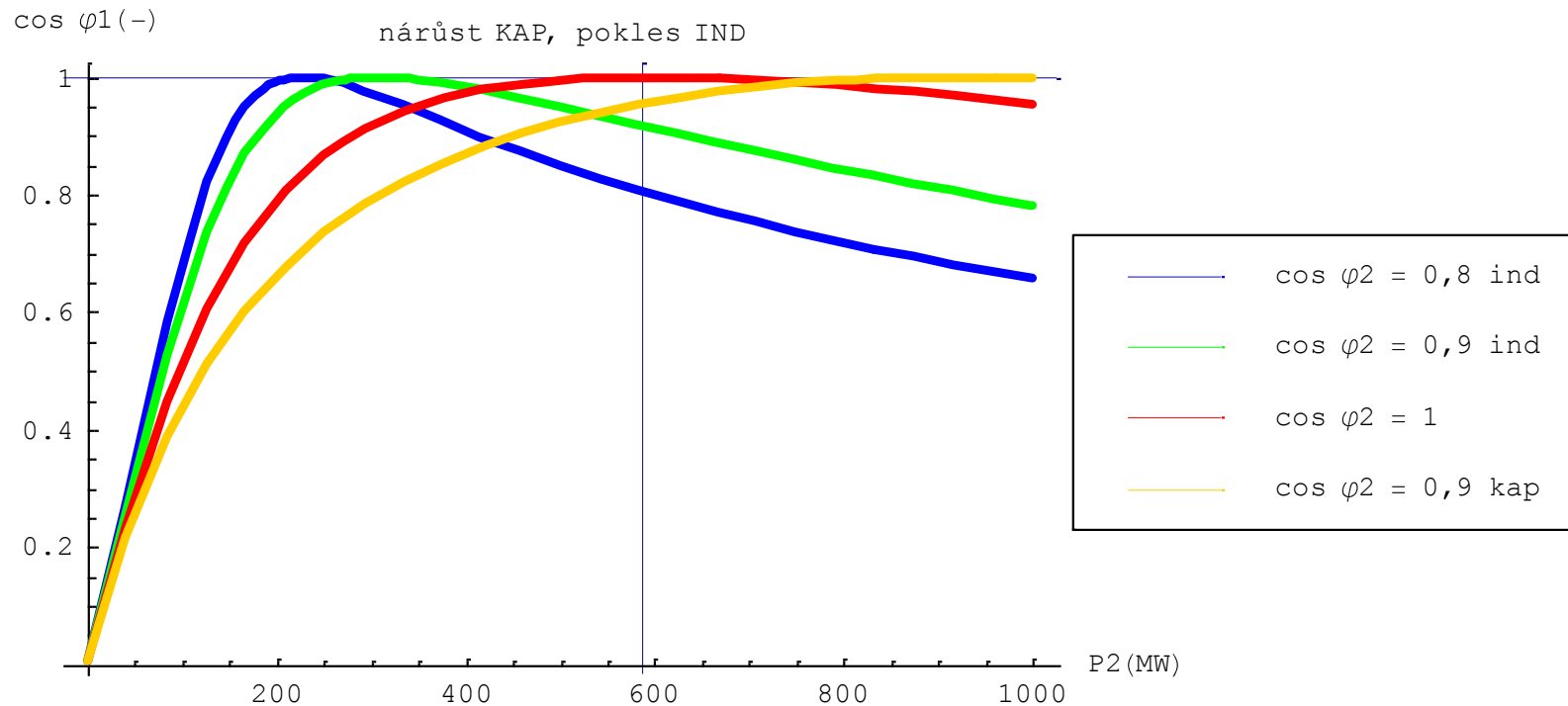


Open-circuit  $\rightarrow$  line is equal to capacity load  
Higher power  $\rightarrow$  „Self-compensating“ line
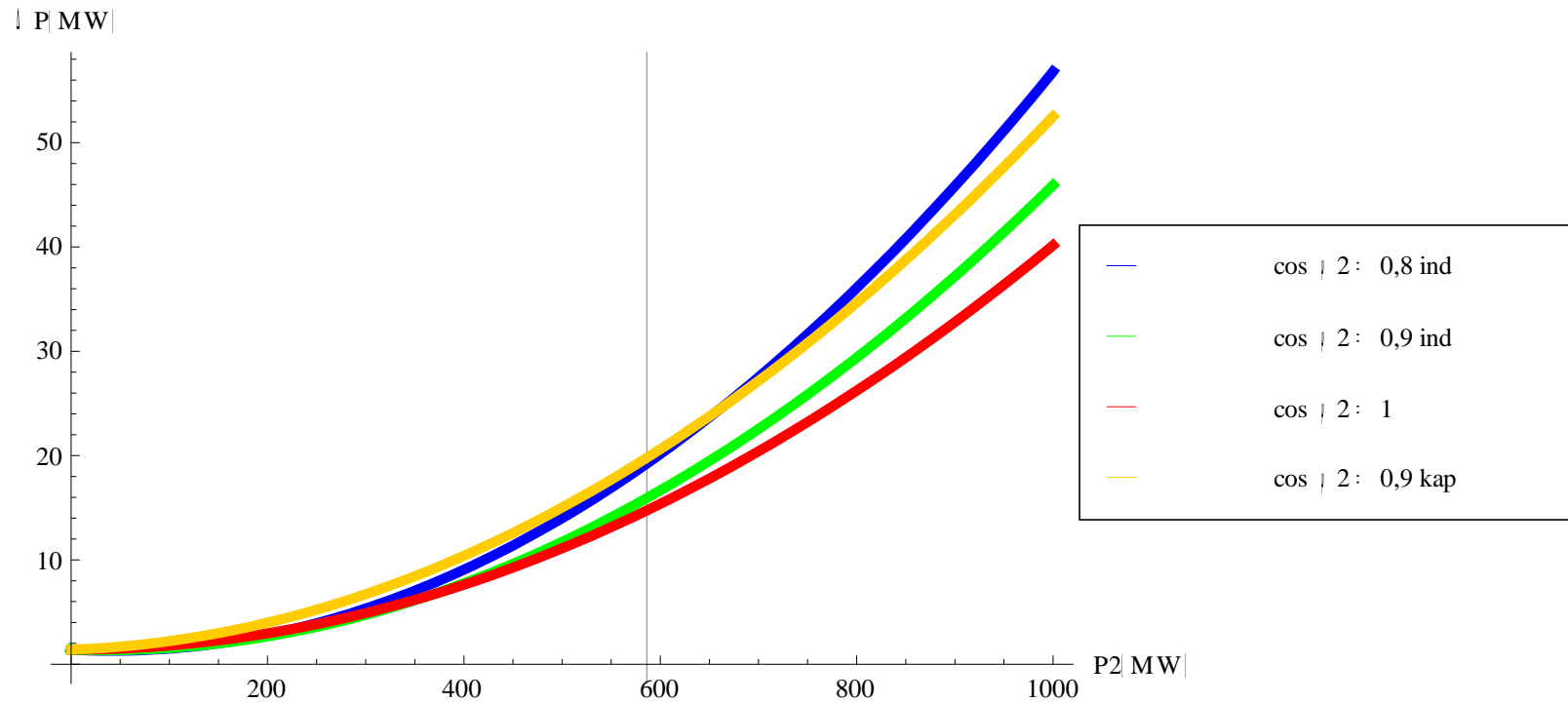
## Line losses


= open-circuit  $\sim U^2$  + load  $\sim I^2$



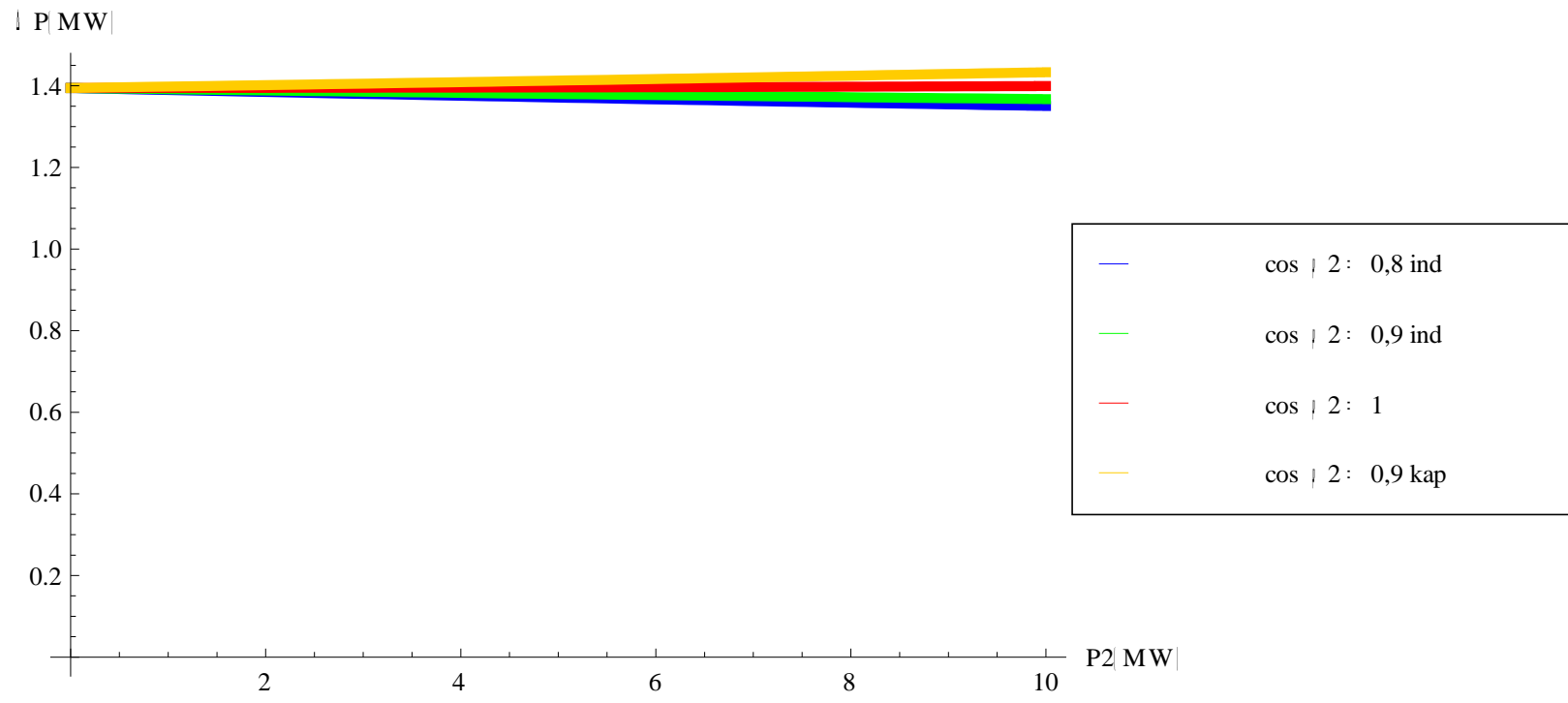

## Transmission power factor

$$\eta = \frac{P_2}{P_1}$$

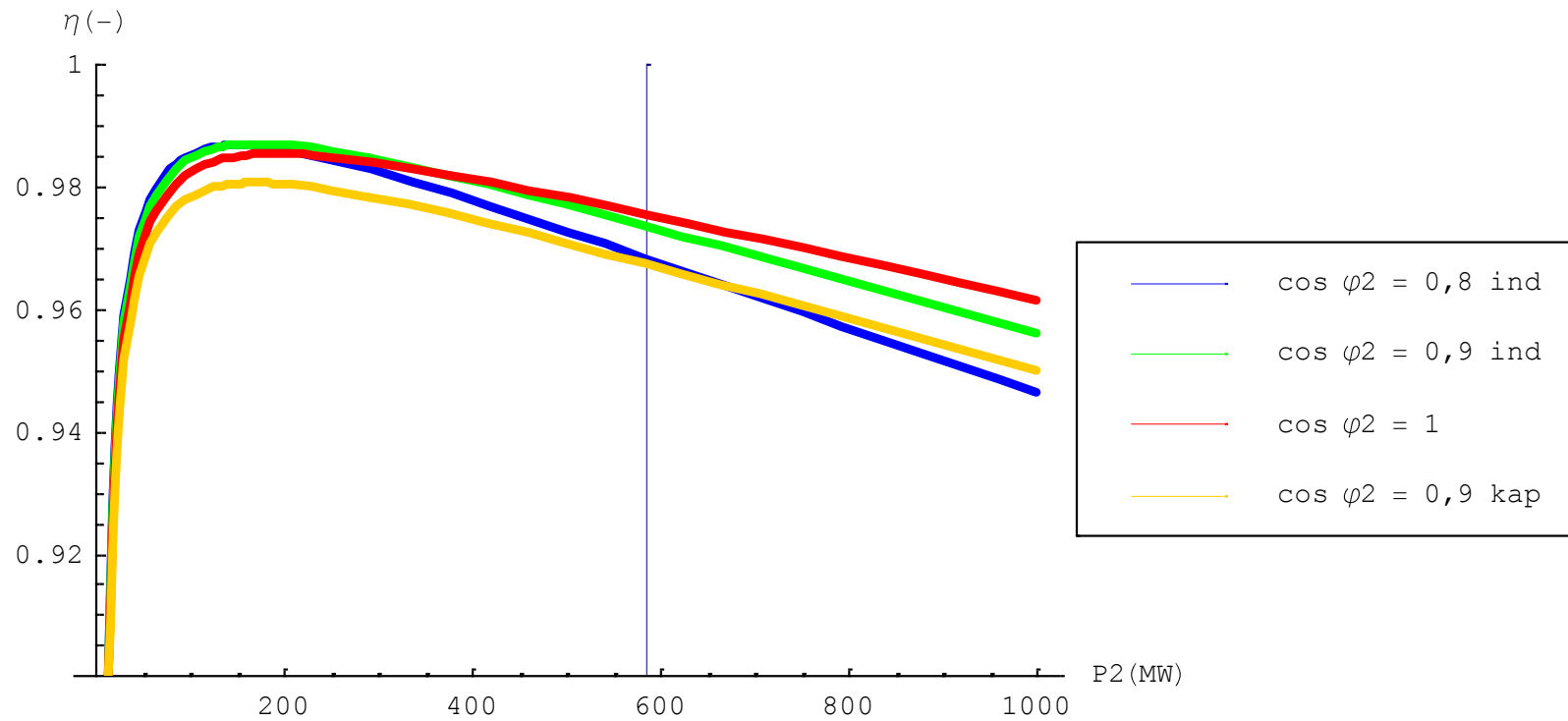

maximum for low powers  
for higher power curve is flat.

## Hyperbolic function series (Taylor series at $x = 0$ )

$$f(x)_{x_0} = \sum_{k=0}^{\infty} \frac{f^{(k)}(x_0)}{k!} (x - x_0)^k = f(x_0) + f'(x_0) \cdot (x - x_0) + \frac{f''(x_0)}{2} \cdot (x - x_0)^2 + \dots$$

$$\cosh \hat{y}l = 1 + \frac{(\hat{y}l)^2}{2} + \frac{(\hat{y}l)^4}{24} + \dots = 1 + \frac{\hat{Z}_{1_1} \hat{Y}_{q_1}}{2} l^2 + \dots$$

$$\sinh \hat{y}l = \hat{y}l + \frac{(\hat{y}l)^3}{6} + \dots = \sqrt{\hat{Z}_{1_1} \hat{Y}_{q_1}} l + \frac{(\hat{Z}_{1_1} \hat{Y}_{q_1})^{3/2}}{6} l^3 + \dots$$


$$\hat{Z}_v \sinh \hat{y}l = \sqrt{\frac{\hat{Z}_{1_1}}{\hat{Y}_{q_1}}} \sinh \hat{y}l = \hat{Z}_{1_1} l + \hat{Z}_{1_1} l \frac{\hat{Z}_{1_1} \hat{Y}_{q_1}}{6} l^2 + \dots$$

$$\frac{1}{\hat{Z}_v} \sinh \hat{y}l = \sqrt{\frac{\hat{Y}_{q_1}}{\hat{Z}_{1_1}}} \sinh \hat{y}l = \hat{Y}_{q_1} l + \hat{Y}_{q_1} l \frac{\hat{Z}_{1_1} \hat{Y}_{q_1}}{6} l^2 + \dots$$
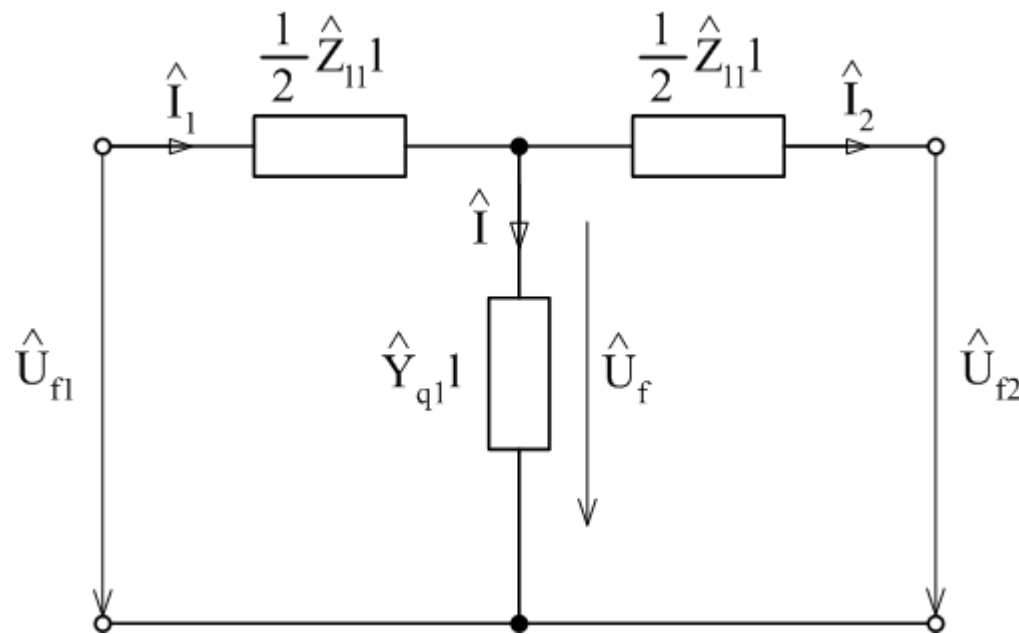
## Line with concentrated parameters

For ordinary calculation (nodal grids) is possible to replace by cell with good accuracy (by line length).

T-cell – short line, transformers; adding another node (replacement for overhead lines up to 200 km, cable up to 80 km)



Voltage and current at the beginning of the line:

$$\hat{U}_{f1} = \hat{U}_{f2} + \frac{1}{2} \hat{Z}_{l1} \mathbf{1} \cdot \hat{I}_2 + \frac{1}{2} \hat{Z}_{l1} \mathbf{1} \cdot \hat{I}_1 \quad \hat{I}_1 = \hat{I}_2 + \hat{I}$$

Voltage and current at shunt branch:

$$\hat{U}_f = \hat{U}_{f2} + \frac{1}{2} \hat{Z}_{l1} \mathbf{1} \cdot \hat{I}_2$$



$$\hat{I} = \hat{Y}_{q1} \mathbf{1} \cdot \hat{U}_f = \hat{U}_{f2} \hat{Y}_{q1} \mathbf{1} + \hat{I}_2 \frac{\hat{Z}_{l1} \hat{Y}_{q1} \mathbf{1}^2}{2}$$

Hence (using Blondel constants)

$$\hat{U}_{f1} = \hat{U}_{f2} \left( 1 + \frac{\hat{Z}_{l1} \hat{Y}_{q1} \mathbf{1}^2}{2} \right) + \hat{I}_2 \hat{Z}_{l1} \mathbf{1} \left( 1 + \frac{\hat{Z}_{l1} \hat{Y}_{q1} \mathbf{1}^2}{4} \right)$$


$$\hat{I}_1 = \hat{U}_{f2} \hat{Y}_{q1} \mathbf{1} + \hat{I}_2 \left( 1 + \frac{\hat{Z}_{l1} \hat{Y}_{q1} \mathbf{1}^2}{2} \right)$$

# Phasor diagram ( $G = 0$ )

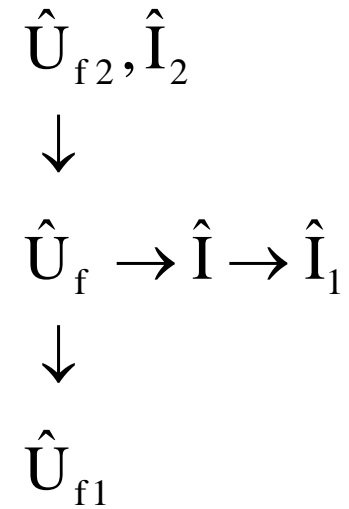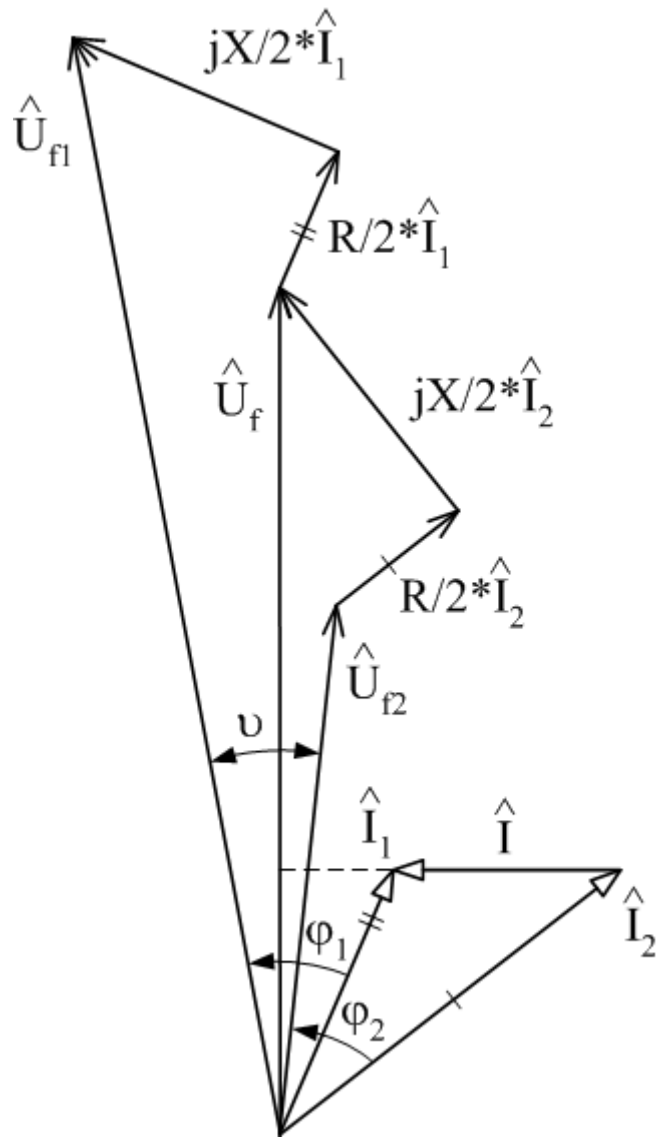



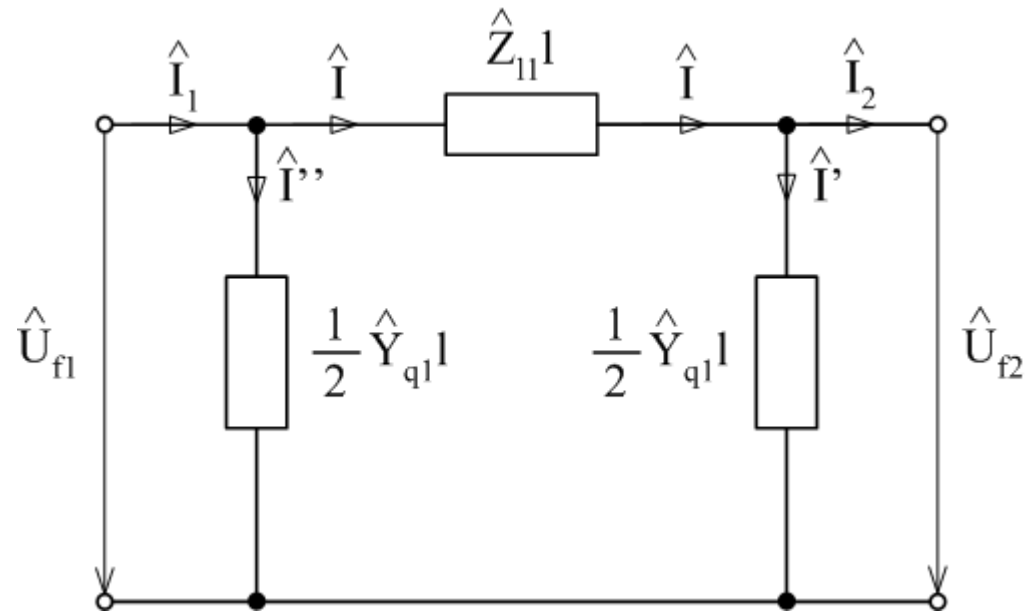$\pi$ -cell – longer line, more accurate (replacement for overhead lines up to 250 km, cable up to 100 km)



Voltage and current at the beginning of the line:

$$\hat{U}_{f1} = \hat{U}_{f2} + \hat{Z}_{11}l \cdot \hat{I} = \hat{U}_{f2} + \hat{Z}_{11}l \cdot (\hat{I}_2 + \hat{I}')$$

$$\hat{I}_1 = \hat{I}_2 + \hat{I}' + \hat{I}''$$

Current at series branch:

$$\hat{I}' = \frac{1}{2} \hat{Y}_{q_1} \mathbf{1} \hat{U}_{f2}$$



$$\hat{I}'' = \frac{1}{2} \hat{Y}_{q_1} \mathbf{1} \hat{U}_{f1}$$

After modification (using Blondel constants)



$$\hat{U}_{f1} = \hat{U}_{f2} \left( 1 + \frac{\hat{Z}_{l_1} \hat{Y}_{q_1}}{2} \mathbf{1}^2 \right) + \hat{I}_2 \hat{Z}_{l_1} \mathbf{1}$$

$$\hat{I}_1 = \hat{U}_{f2} \hat{Y}_{q_1} \mathbf{1} \left( 1 + \frac{\hat{Z}_{l_1} \hat{Y}_{q_1}}{4} \mathbf{1}^2 \right) + \hat{I}_2 \left( 1 + \frac{\hat{Z}_{l_1} \hat{Y}_{q_1}}{2} \mathbf{1}^2 \right)$$

# Phasor diagram ( $G = 0$ )

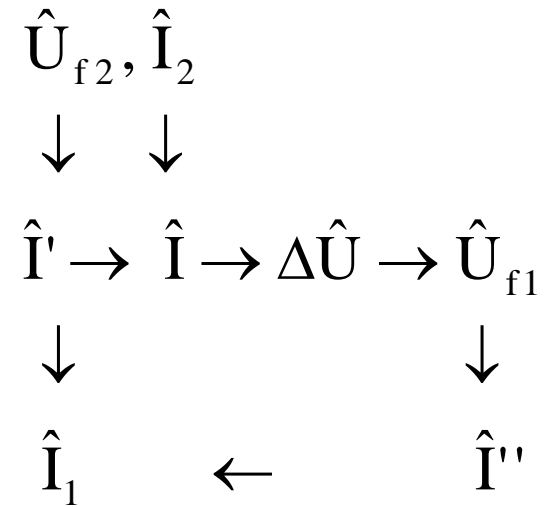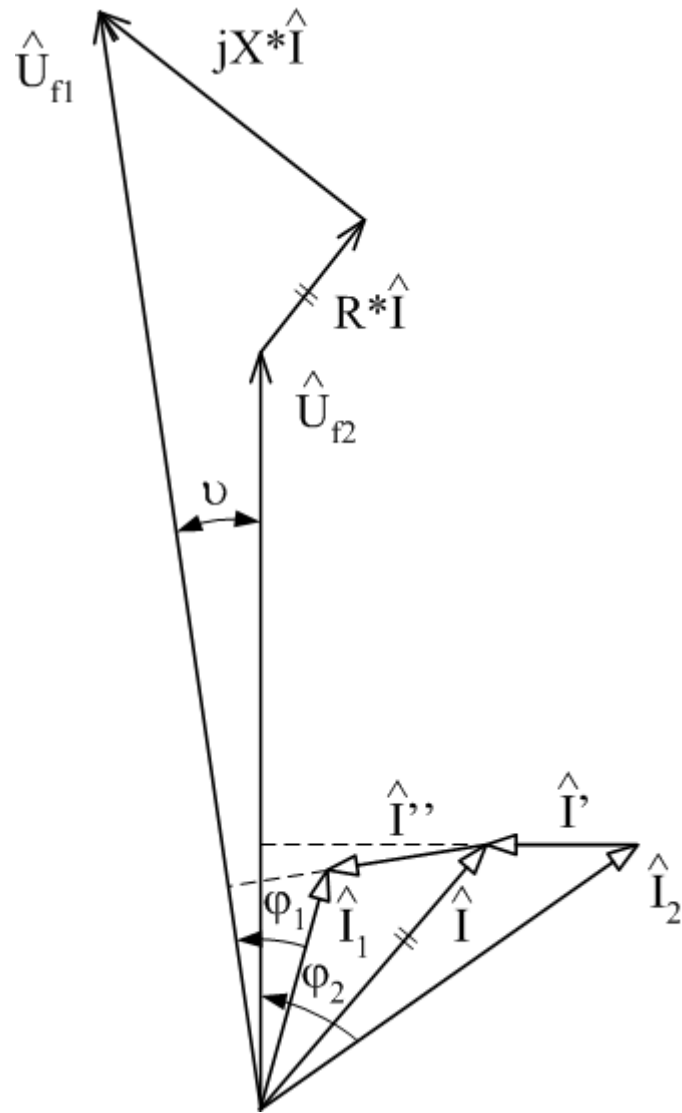

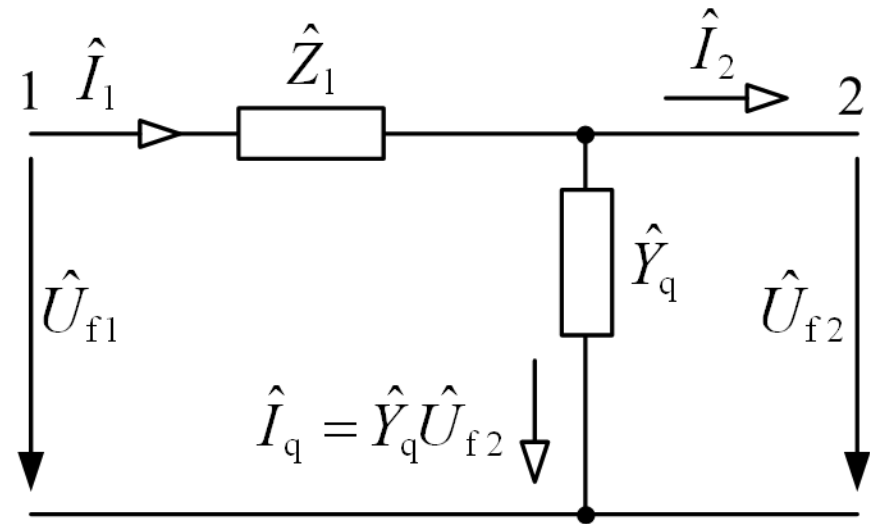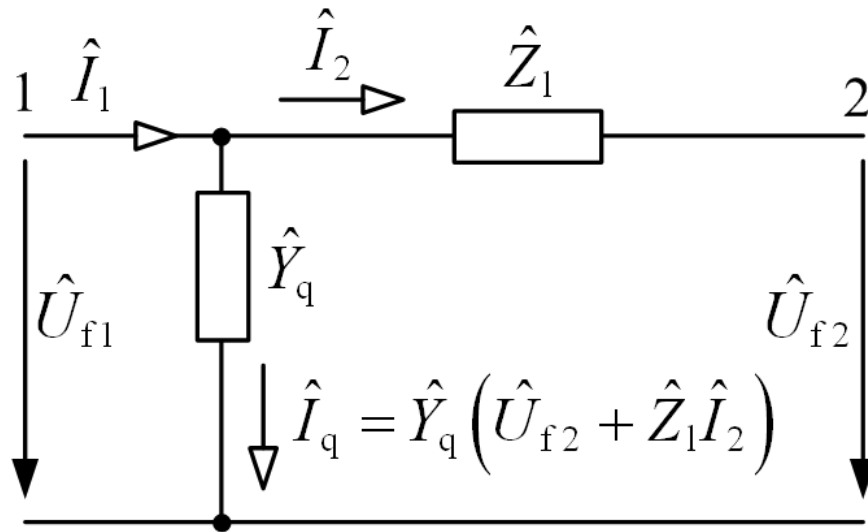$\Gamma$ -cell (gamma) – used rare, for shorter lines (overhead up to 80 km, cable up to 25 km), transformers.



$$\hat{U}_{f1} = \hat{U}_{f2} + \hat{I}_2 \hat{Z}_{1_1} 1$$


$$\hat{I}_1 = \hat{U}_{f2} \hat{Y}_{q_1} 1 + \hat{I}_2 (1 + \hat{Z}_{1_1} \hat{Y}_{q_1} 1^2)$$

$$\hat{U}_{f1} = \hat{U}_{f2} (1 + \hat{Z}_{1_1} \hat{Y}_{q_1} 1^2) + \hat{I}_2 \hat{Z}_{1_1} 1$$

$$\hat{I}_1 = \hat{U}_{f2} \hat{Y}_{q_1} 1 + \hat{I}_2$$

valid  $\hat{A} \neq \hat{D}$ ,  $\hat{A}\hat{D} - \hat{B}\hat{C} = 1$  (unsymmetrical, passive two-port)

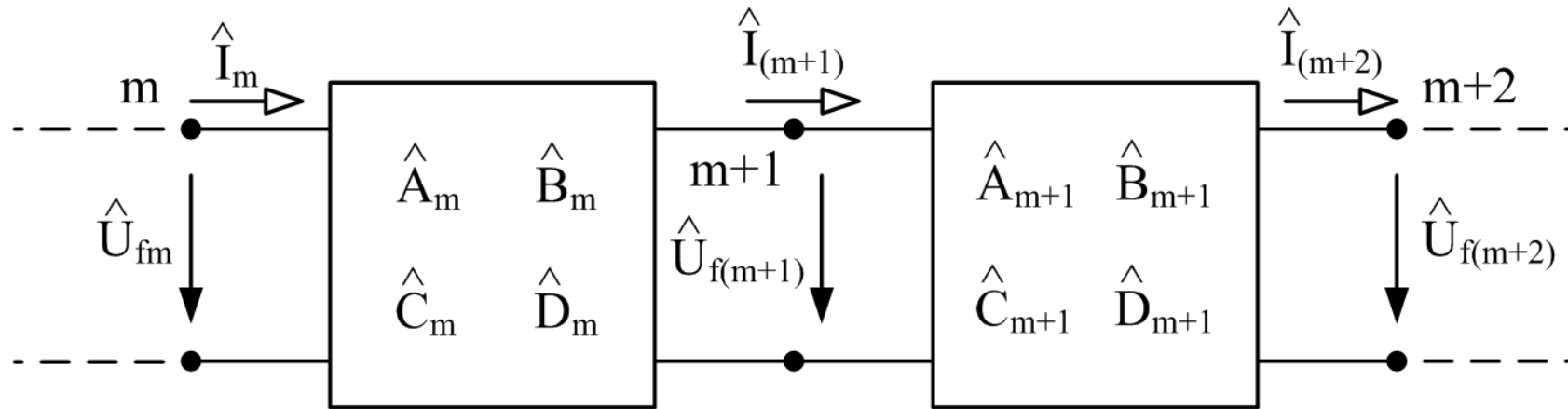Longer line  $\rightarrow$  cascade connection of cells for shorter sections (additional nodes)



$$\begin{pmatrix} \hat{U}_{fm} \\ \hat{I}_m \end{pmatrix} = \begin{pmatrix} \hat{A}_m & \hat{B}_m \\ \hat{C}_m & \hat{D}_m \end{pmatrix} \begin{pmatrix} \hat{U}_{f(m+1)} \\ \hat{I}_{(m+1)} \end{pmatrix}$$

$$\begin{pmatrix} \hat{A} & \hat{B} \\ \hat{C} & \hat{D} \end{pmatrix} = \prod_{m=1}^n \begin{pmatrix} \hat{A}_m & \hat{B}_m \\ \hat{C}_m & \hat{D}_m \end{pmatrix}$$