

## Short-circuits in ES

### Short-circuit:

- cross fault, quick emergency change in ES
- the most often fault in ES
- transient events occur during short-circuits

### Short-circuit formation:

- fault connection between phases or between phase(s) and the ground in the system with the grounded neutral point

### Main causes:

- insulation defect caused by overvoltage
- direct lightning strike
- insulation aging
- direct damage of overhead lines or cables

### Short-circuit impacts:

- total impedance of the network affected part decreases
- currents are increasing => so called short-circuit currents  $I_k$
- the voltage decreases near the short-circuit
- $I_k$  impacts causes device heating and power strain
- problems with  $I_k$  disconnecting, electrical arc and overvoltage occurred during the short-circuit
- synchronism disruption of ES working in parallel
- communication line disturbing => induced voltages

Note: In short-circuit places transient resistances arise.

- transient resistance is a sum of electrical arc resistance and resistance of other  $I_k$  way parts (determination of exact resistances is difficult)
- current and electrical arc length is changing during short-circuit => resistance of electrical arc is also changing

- transient resistances are neglected for  $I_k$  calculation (dimensioning of electrical devices) → perfect short-circuits





## Short-circuits types

### Symmetrical short-circuits:

- Three-phase short-circuit => all 3 phases are affected by short-circuit
  - little occurrence in the case of overhead lines
  - the most occurrences in the case of cable lines => other kinds of faults change to 3ph short-circuit due to electrical-arc impact

### Unbalanced (asymmetrical) short-circuits:

- phase-to-phase short-circuit
- double-phase-to-ground short-circuit
- single-phase-to-ground short-circuit:
  - in MV a different kind of fault => so called *ground fault*
  - in case of ground fault in MV (insulated or indirectly grounded neutral point) => no change in LV (grounded neutral point)
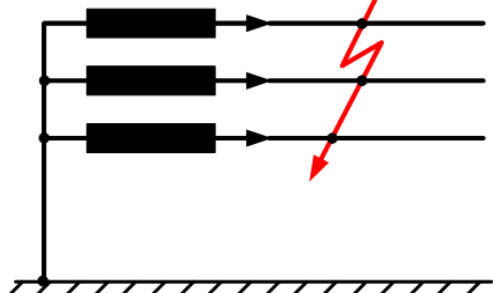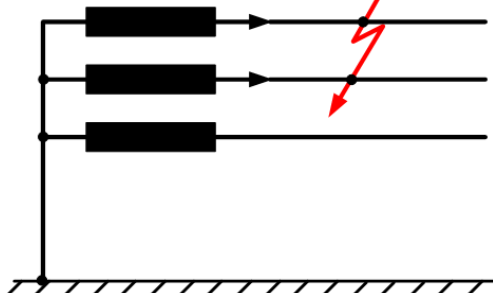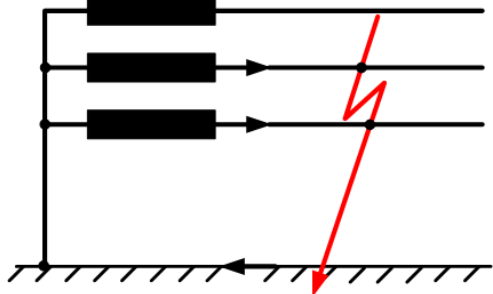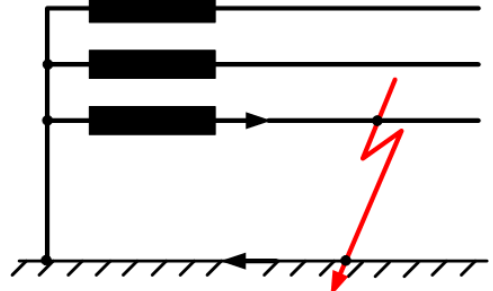
| Short-circuit type | Diagram   | Occurrence probability (%) |        |        |
|--------------------|---|----------------------------|--------|--------|
|                    |   | MV                         | 110 kV | 220 kV |
| 3ph                |    | 5                          | 0,6    | 0,9    |
| 2ph                |   | 10                         | 4,8    | 0,6    |
| 2ph to ground      |  | 20                         | 3,8    | 5,4    |
| 1ph                |  | *                          | 91     | 93,1   |

## Short-circuit current time behaviour

$$W_L = \frac{1}{2} Li^2$$


$$P = \frac{dW_L}{dt} < \infty \rightarrow \text{transient event}$$

Time behaviour: open-circuit, resistances neglected  
→ reactance, current of inductive character, higher  $I_k$  values

Impact of R on  $I_k$  attributes:

- finite R values decrease short-circuit impacts
- R neglecting results in time constants prolongation  $\tau = L/R$

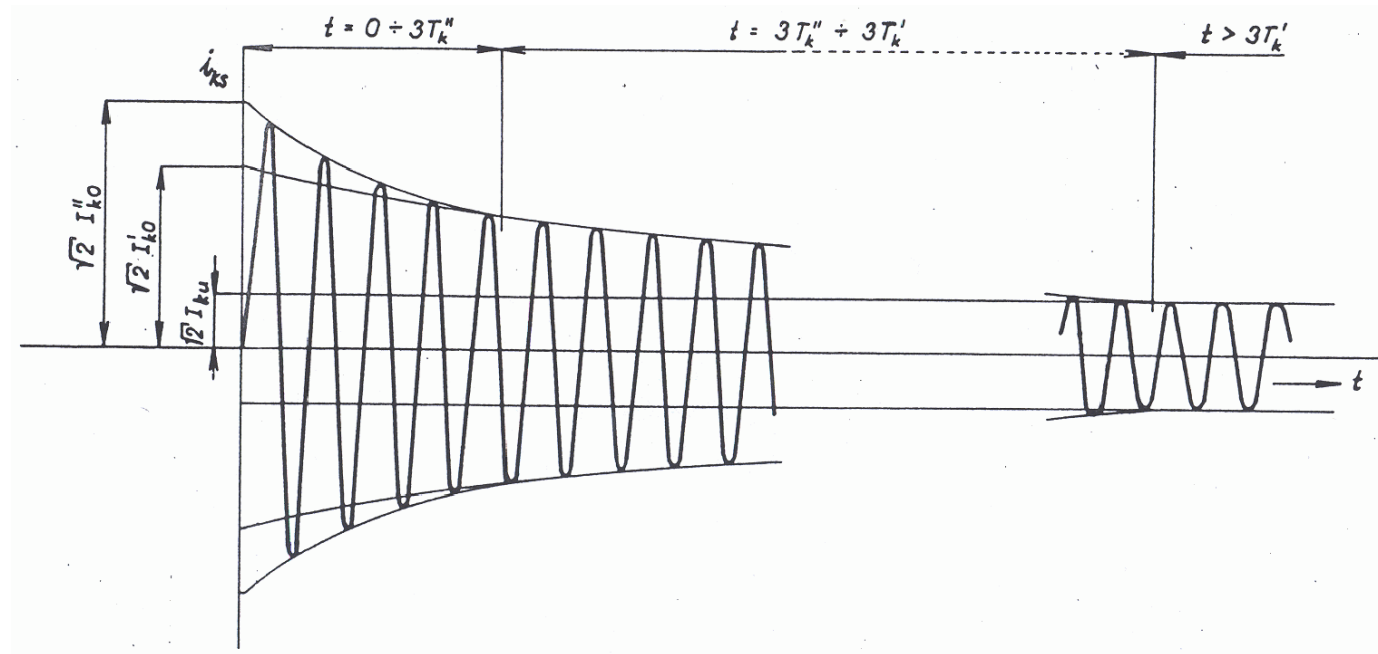$U = U_{\max}$  in the short-circuit moment  $\rightarrow I_k$  starts from zero (min. value)



Short-circuit components ( $f = 50$  Hz):


- sub-transient – exponential envelope,  $T_k''$
- transient – exponential envelope,  $T_k'$
- steady-state – constant magnitude

It is caused by synchronous machine behaviour during short-circuit  $\rightarrow$  more significant during short-circuits near the machine.
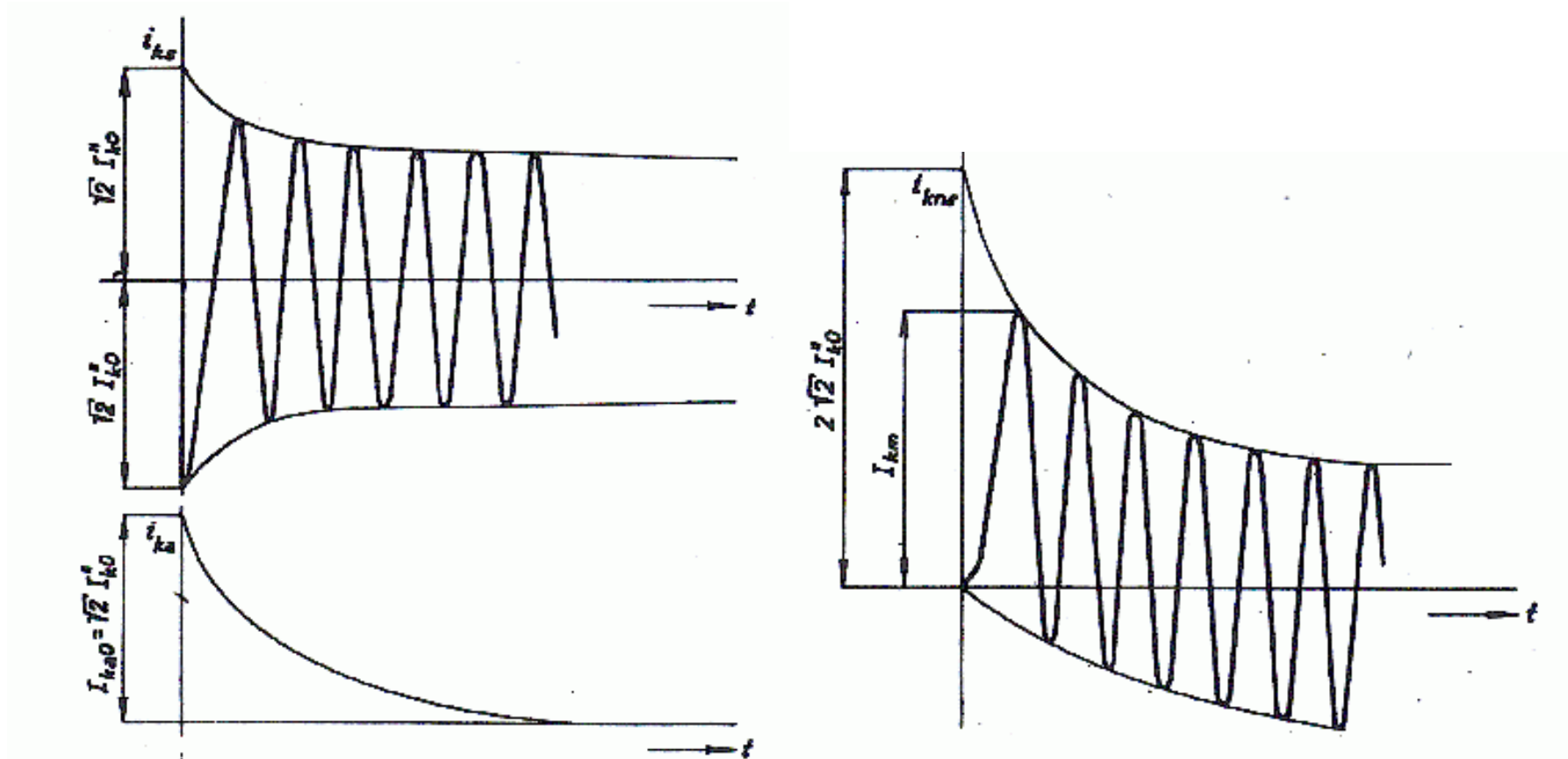
## Values

- symmetrical short-circuit current  $I_{ks}$  - steady-state, transient and sub-transient component sum, RMS value
- sub-transient short-circuit current  $I_k'' - I_{ks}$  RMS value in the period of sub-transient component  $t \doteq (0 \div 3T_k'')$
- initial sub-transient short-circuit current  $I_{k0}'' - I_k''$  value in the moment of short-circuit origin  $t = 0$
- transient short-circuit current  $I_k' - I_{ks}$  RMS value in the period from the sub-transient component end to the transient component end  $t \doteq (3T_k'' \div 3T_k')$
- initial transient short-circuit current  $I_{k0}' - I_{ks}$  - RMS value of the steady-state and transient component for  $t = 0$
- steady-state short-circuit current  $I_{ku} - I_{ks}$  after transient components end  $t > 3T_k'$

$U = 0$  in the short-circuit moment  $\rightarrow I_k$  starts from max. value






## Values

- DC component  $I_{ka}$  - disappears exponentially,  $T_{ka}$
- initial DC component  $I_{ka0}$  -  $I_{ka}$  in the moment  $t = 0$ , forced by the current continuous behaviour
- unbalanced short-circuit current  $I_{kns}$  - steady-state, transient, sub-transient and DC component sum, RMS value
- peak short-circuit current  $I_{km}$  - the first half-period magnitude during the maximal DC component

### Short-circuit current power factor

$$\varphi_k = \operatorname{arctg} \frac{X_{\text{tot}}}{R_{\text{tot}}}$$

| lines           | overhead |      |      |      |       |      | cable |      |       |
|-----------------|----------|------|------|------|-------|------|-------|------|-------|
| U (kV)          | 22       | 110  | 220  | 400  | 750   | 1150 | 10    | 35   | 110   |
| X : R           | 1/1      | 2/1  | 5/1  | 12/1 | 15/1  | 27/1 | 1/4   | 1/2  | 1/0,7 |
| Z  : X          | 1,41     | 1,12 | 1,02 | 1,01 | 1,005 | 1,00 | 4,1   | 2,24 | 1,22  |
| $\varphi_k$ (°) | 45       | 64   | 78,7 | 85,2 | 86,2  | 87,9 | 13    | 26   | 54    |

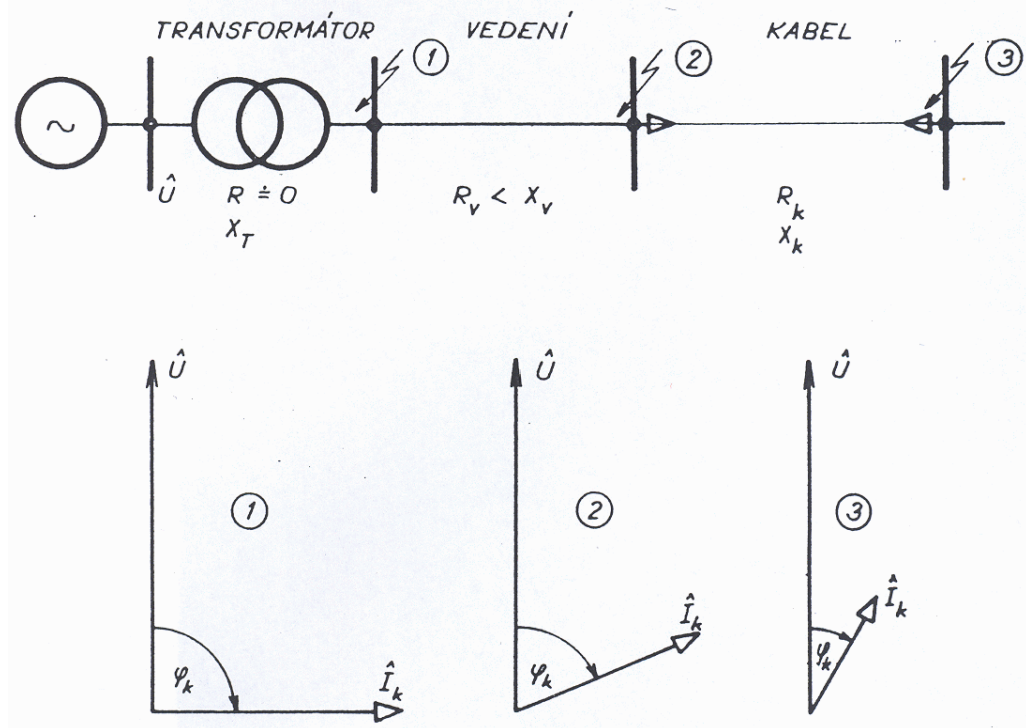

## Short-circuits in 3ph system

Conversion between phase values and symmetrical components


$$\begin{pmatrix} \mathbf{U}_{ABC} \end{pmatrix} = \begin{pmatrix} \hat{U}_A \\ \hat{U}_B \\ \hat{U}_C \end{pmatrix} = \begin{pmatrix} 1 & 1 & 1 \\ \hat{a}^2 & \hat{a} & 1 \\ \hat{a} & \hat{a}^2 & 1 \end{pmatrix} \begin{pmatrix} \hat{U}_1 \\ \hat{U}_2 \\ \hat{U}_0 \end{pmatrix} = (\mathbf{T})(\mathbf{U}_{120})$$

$$\begin{pmatrix} \mathbf{U}_{120} \end{pmatrix} = \begin{pmatrix} \hat{U}_1 \\ \hat{U}_2 \\ \hat{U}_0 \end{pmatrix} = \frac{1}{3} \begin{pmatrix} 1 & \hat{a} & \hat{a}^2 \\ 1 & \hat{a}^2 & \hat{a} \\ 1 & 1 & 1 \end{pmatrix} \begin{pmatrix} \hat{U}_A \\ \hat{U}_B \\ \hat{U}_C \end{pmatrix} = (\mathbf{T}^{-1})(\mathbf{U}_{ABC})$$

Impedance matrix in symmetrical components (for series sym. segment)

$$\begin{pmatrix} \mathbf{Z}_{120} \end{pmatrix} = \begin{pmatrix} \hat{Z}_1 & 0 & 0 \\ 0 & \hat{Z}_2 & 0 \\ 0 & 0 & \hat{Z}_0 \end{pmatrix} = \begin{pmatrix} \hat{Z} - \hat{Z}' & 0 & 0 \\ 0 & \hat{Z} - \hat{Z}' & 0 \\ 0 & 0 & \hat{Z} + 2\hat{Z}' \end{pmatrix}$$
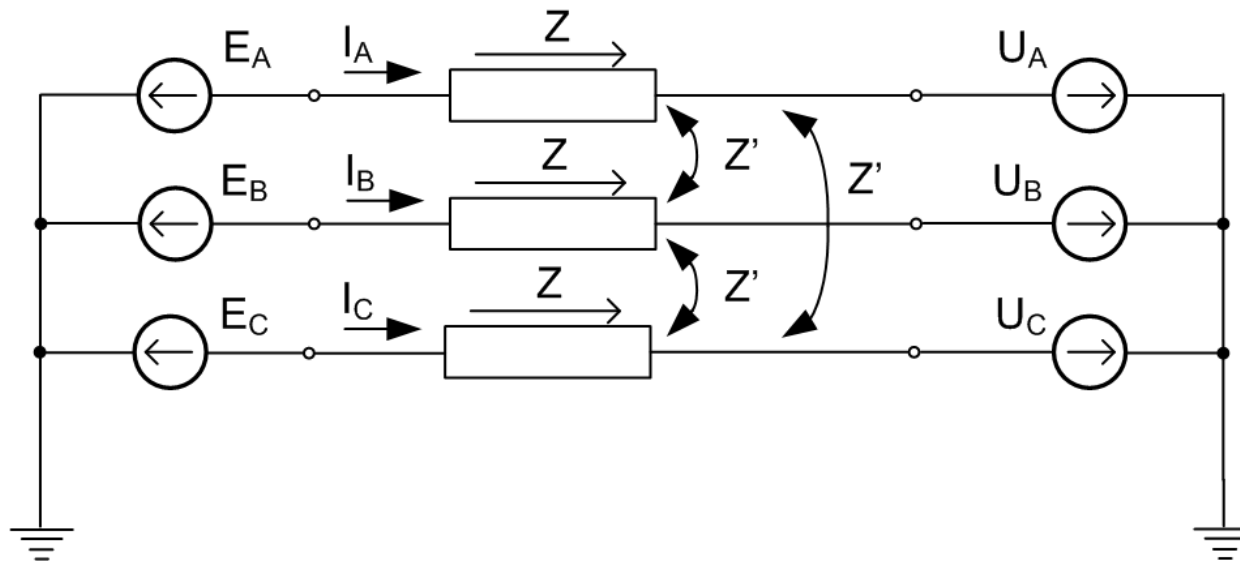
### 3ph system during short-circuit – internal generator voltage E (or $U_i$ )



$$\begin{pmatrix} E_{ABC} \end{pmatrix} = \begin{pmatrix} Z_{ABC} \end{pmatrix} \begin{pmatrix} I_{ABC} \end{pmatrix} + \begin{pmatrix} U_{ABC} \end{pmatrix}$$

### Symmetrical system (independent systems 1, 2, 0)

$$\begin{pmatrix} E_{120} \end{pmatrix} = \begin{pmatrix} Z_{120} \end{pmatrix} \begin{pmatrix} I_{120} \end{pmatrix} + \begin{pmatrix} U_{120} \end{pmatrix}$$

$$\hat{E}_1 = \hat{Z}_1 \hat{I}_1 + \hat{U}_1$$

$$\hat{E}_2 = \hat{Z}_2 \hat{I}_2 + \hat{U}_2$$

$$\hat{E}_0 = \hat{Z}_0 \hat{I}_0 + \hat{U}_0$$


Generator symmetrical voltage → only positive sequence component  
 Reference phase A:

$$\begin{pmatrix} \hat{E}_{120} \end{pmatrix} = \begin{pmatrix} T^{-1} \end{pmatrix} \begin{pmatrix} E_{ABC} \end{pmatrix} = \frac{1}{3} \begin{pmatrix} 1 & \hat{a} & \hat{a}^2 \\ 1 & \hat{a}^2 & \hat{a} \\ 1 & 1 & 1 \end{pmatrix} \begin{pmatrix} \hat{E}_A \\ \hat{a}^2 \hat{E}_A \\ \hat{a} \hat{E}_A \end{pmatrix} = \begin{pmatrix} \hat{E}_A \\ 0 \\ 0 \end{pmatrix} = \begin{pmatrix} \hat{E} \\ 0 \\ 0 \end{pmatrix}$$


$$\begin{pmatrix} \hat{E}_1 \\ \hat{E}_2 \\ \hat{E}_0 \end{pmatrix} = \begin{pmatrix} \hat{E} \\ 0 \\ 0 \end{pmatrix} = \begin{pmatrix} \hat{Z}_1 & 0 & 0 \\ 0 & \hat{Z}_2 & 0 \\ 0 & 0 & \hat{Z}_0 \end{pmatrix} \begin{pmatrix} \hat{I}_1 \\ \hat{I}_2 \\ \hat{I}_0 \end{pmatrix} + \begin{pmatrix} \hat{U}_1 \\ \hat{U}_2 \\ \hat{U}_0 \end{pmatrix}$$

Negative and zero sequence are caused by voltage unbalance in the faulted place.

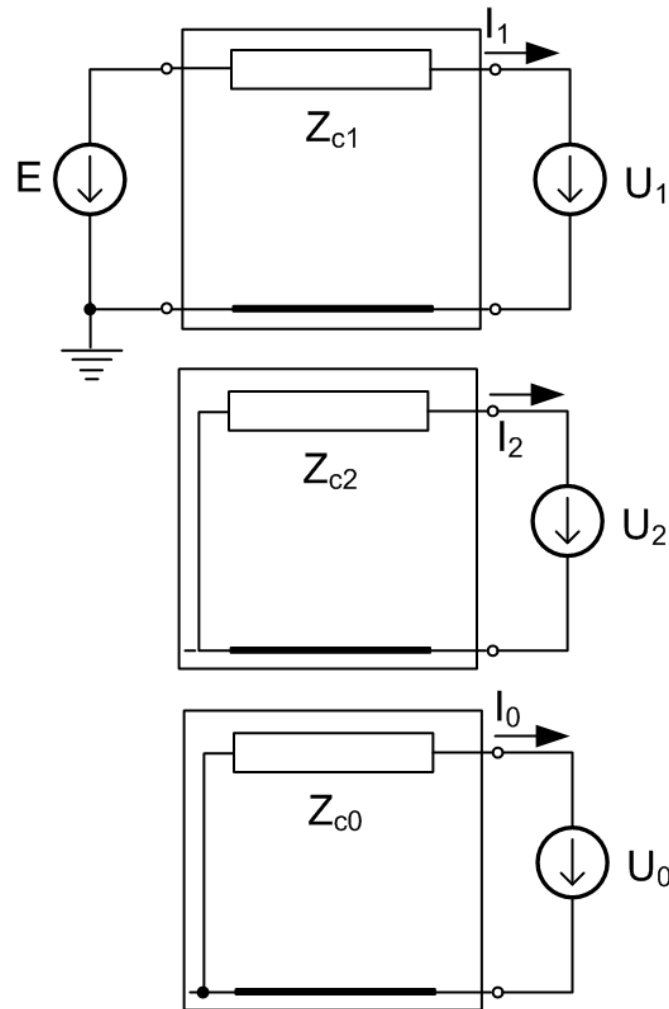In the fault point 6 quantities ( $U_{120}, I_{120}$ )  $\rightarrow$  3 equations necessary to be added by other 3 equations according to the short-circuit type (local unbalance description).



## Three-phase (to-ground) short-circuit

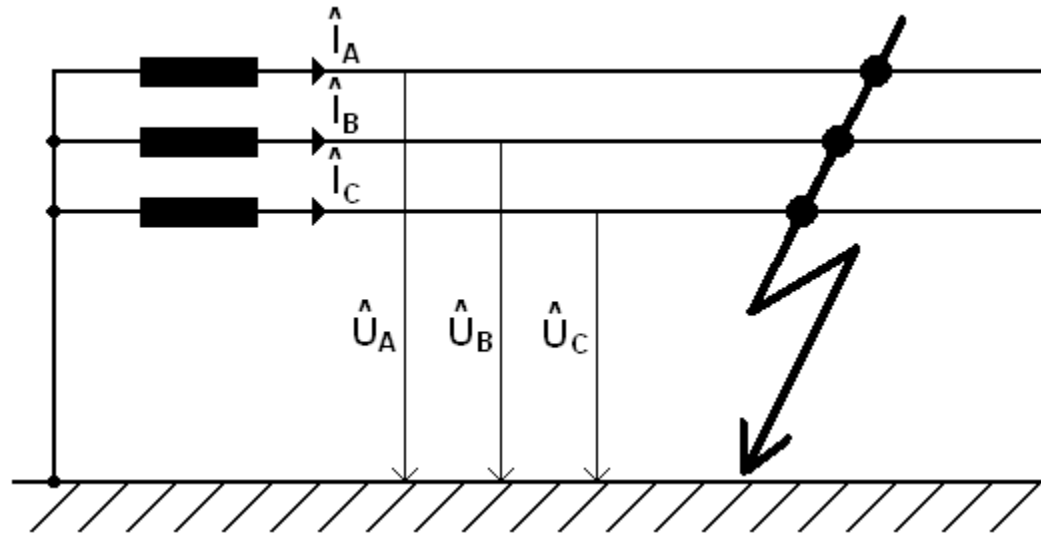

3 char. equations

$$\hat{U}_A = \hat{U}_B = \hat{U}_C = 0$$

Hence 6 equations for 6 unknowns

$$\begin{aligned} \hat{E} &= \hat{Z}_1 \hat{I}_1 + \hat{U}_1 & 0 &= \hat{U}_1 + \hat{U}_2 + \hat{U}_0 \\ 0 &= \hat{Z}_2 \hat{I}_2 + \hat{U}_2 & 0 &= \hat{a}^2 \hat{U}_1 + \hat{a} \hat{U}_2 + \hat{U}_0 \\ 0 &= \hat{Z}_0 \hat{I}_0 + \hat{U}_0 & 0 &= \hat{a} \hat{U}_1 + \hat{a}^2 \hat{U}_2 + \hat{U}_0 \end{aligned}$$

## Components

$$(\mathbf{U}_{120}) = (\mathbf{T}^{-1})(\mathbf{U}_{ABC}) = \frac{1}{3} \begin{pmatrix} 1 & \hat{a} & \hat{a}^2 \\ 1 & \hat{a}^2 & \hat{a} \\ 1 & 1 & 1 \end{pmatrix} \begin{pmatrix} 0 \\ 0 \\ 0 \end{pmatrix} = \begin{pmatrix} 0 \\ 0 \\ 0 \end{pmatrix}$$

$$\hat{U}_1 = \hat{U}_2 = \hat{U}_0 = 0$$


$$\hat{I}_1 = \frac{\hat{E}}{\hat{Z}_1}; \quad \hat{I}_2 = 0; \quad \hat{I}_0 = 0$$

## Phases

$$(\mathbf{I}_{ABC}) = (\mathbf{T})(\mathbf{I}_{120})$$



$$\hat{I}_A = \frac{\hat{E}}{\hat{Z}_1}; \quad \hat{I}_B = \hat{a}^2 \frac{\hat{E}}{\hat{Z}_1}; \quad \hat{I}_C = \hat{a} \frac{\hat{E}}{\hat{Z}_1}$$

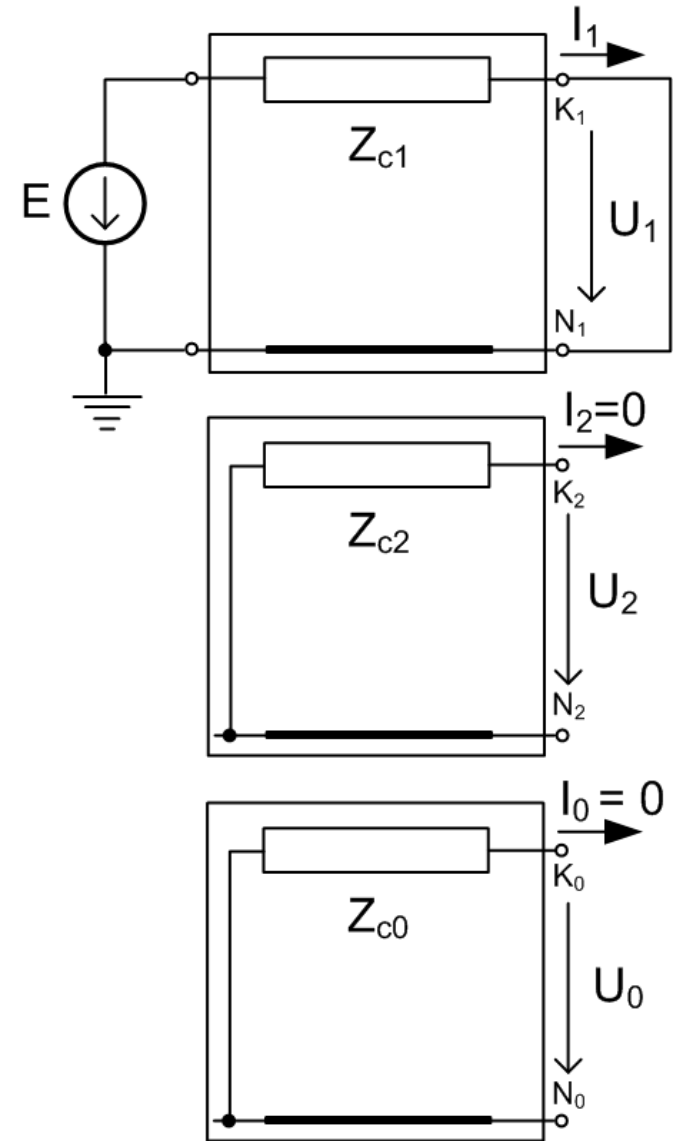Only the positive-sequence component included.





## Single-phase-to-ground short-circuit

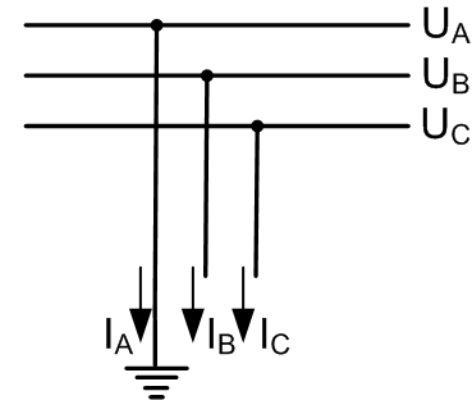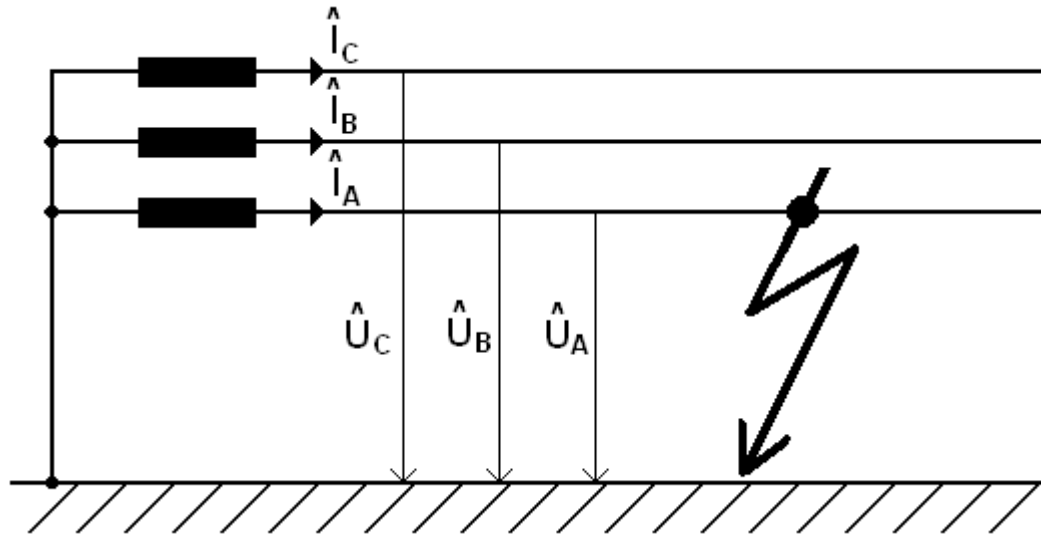

3 char. equations

$$\hat{U}_A = 0; \quad \hat{I}_B = \hat{I}_C = 0$$

Hence 6 equations for 6 unknowns

$$\hat{E} = \hat{Z}_1 \hat{I}_1 + \hat{U}_1 \quad 0 = \hat{U}_1 + \hat{U}_2 + \hat{U}_0$$

$$0 = \hat{Z}_2 \hat{I}_2 + \hat{U}_2 \quad 0 = \hat{a}^2 \hat{I}_1 + \hat{a} \hat{I}_2 + \hat{I}_0$$

$$0 = \hat{Z}_0 \hat{I}_0 + \hat{U}_0 \quad 0 = \hat{a} \hat{I}_1 + \hat{a}^2 \hat{I}_2 + \hat{I}_0$$

## Components

$$(\mathbf{I}_{120}) = (\mathbf{T}^{-1})(\mathbf{I}_{ABC}) = \frac{1}{3} \begin{pmatrix} 1 & \hat{a} & \hat{a}^2 \\ 1 & \hat{a}^2 & \hat{a} \\ 1 & 1 & 1 \end{pmatrix} \begin{pmatrix} \hat{I}_A \\ 0 \\ 0 \end{pmatrix} = \frac{1}{3} \begin{pmatrix} \hat{I}_A \\ \hat{I}_A \\ \hat{I}_A \end{pmatrix}$$


$$\hat{I}_1 = \hat{I}_2 = \hat{I}_0 = \frac{\hat{E}}{\hat{Z}_1 + \hat{Z}_2 + \hat{Z}_0}$$

$$\hat{U}_1 = (\hat{Z}_0 + \hat{Z}_2) \hat{I}_1$$

$$\hat{U}_2 = -\hat{Z}_2 \hat{I}_1$$

$$\hat{U}_0 = -\hat{Z}_0 \hat{I}_1$$

All three components are in series.

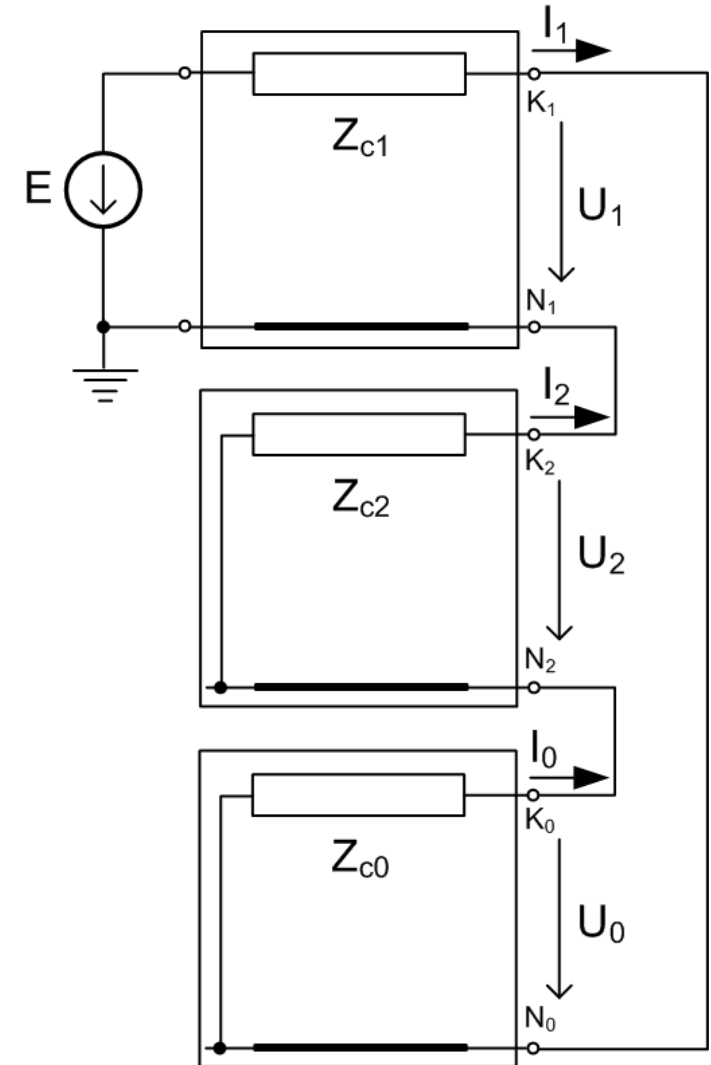



## Phases

$$(\mathbf{I}_{ABC}) = (\mathbf{T})(\mathbf{I}_{120}) = \begin{pmatrix} 1 & 1 & 1 \\ \hat{a}^2 & \hat{a} & 1 \\ \hat{a} & \hat{a}^2 & 1 \end{pmatrix} \begin{pmatrix} \hat{\mathbf{I}}_1 \\ \hat{\mathbf{I}}_1 \\ \hat{\mathbf{I}}_1 \end{pmatrix} = \begin{pmatrix} 3\hat{\mathbf{I}}_1 \\ 0 \\ 0 \end{pmatrix}$$



$$\hat{\mathbf{I}}_A = \frac{3\hat{\mathbf{E}}}{\hat{\mathbf{Z}}_1 + \hat{\mathbf{Z}}_2 + \hat{\mathbf{Z}}_0}; \quad \hat{\mathbf{I}}_B = 0; \quad \hat{\mathbf{I}}_C = 0$$

$$(\mathbf{U}_{ABC}) = (\mathbf{T})(\mathbf{U}_{120}) = \begin{pmatrix} 1 & 1 & 1 \\ \hat{a}^2 & \hat{a} & 1 \\ \hat{a} & \hat{a}^2 & 1 \end{pmatrix} \begin{pmatrix} (\hat{\mathbf{Z}}_0 + \hat{\mathbf{Z}}_2)\hat{\mathbf{I}}_1 \\ -\hat{\mathbf{Z}}_2\hat{\mathbf{I}}_1 \\ -\hat{\mathbf{Z}}_0\hat{\mathbf{I}}_1 \end{pmatrix} = \begin{pmatrix} 0 \\ (\hat{a}^2 - \hat{a})\hat{\mathbf{Z}}_2 + (\hat{a}^2 - 1)\hat{\mathbf{Z}}_0 \\ (\hat{a} - \hat{a}^2)\hat{\mathbf{Z}}_2 + (\hat{a} - 1)\hat{\mathbf{Z}}_0 \end{pmatrix} \hat{\mathbf{I}}_1$$



# Current phasor diagram

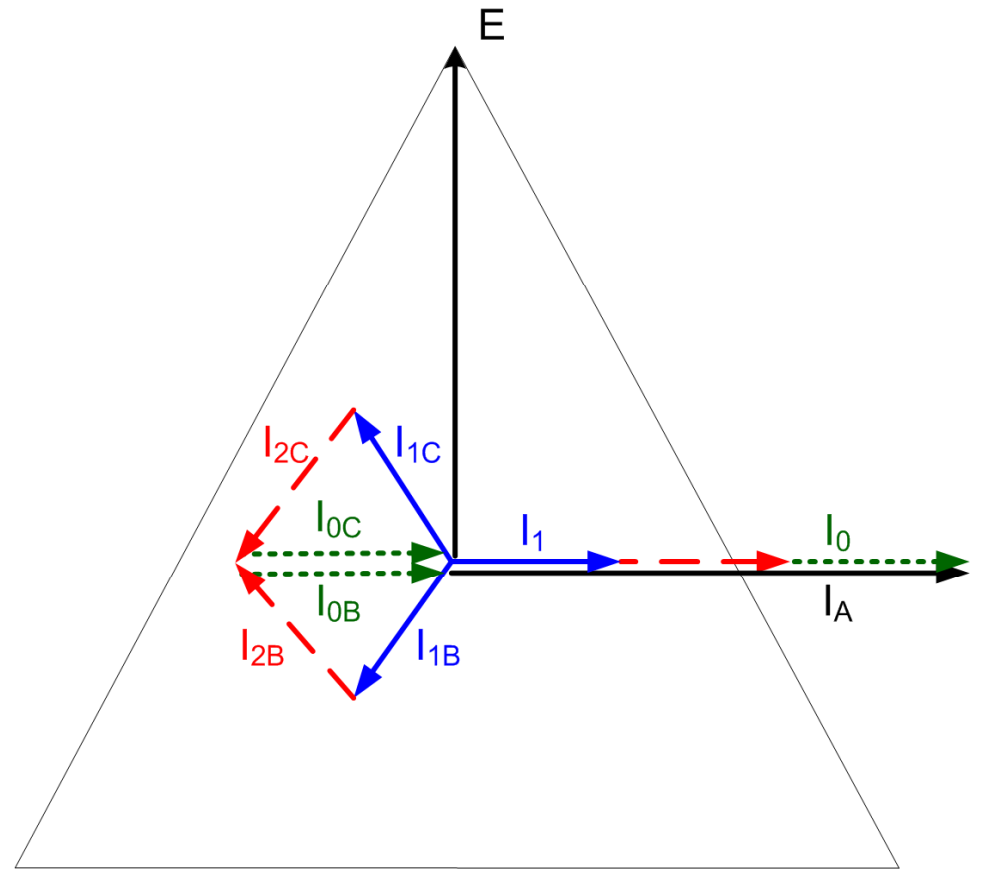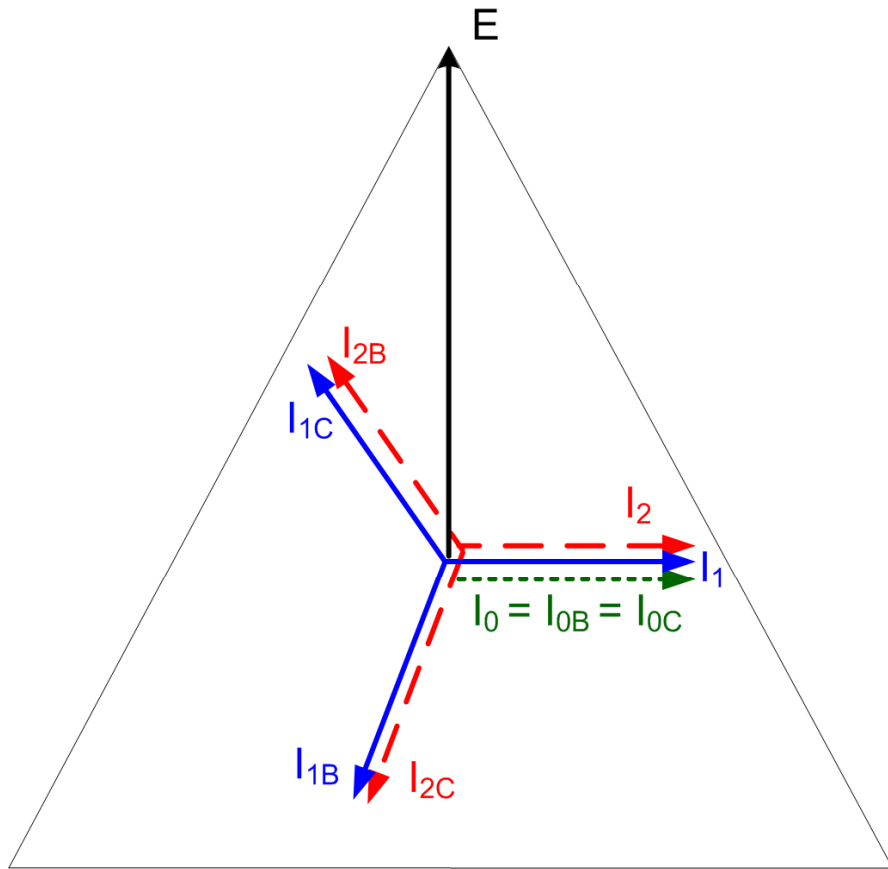

# Voltage phasor diagram

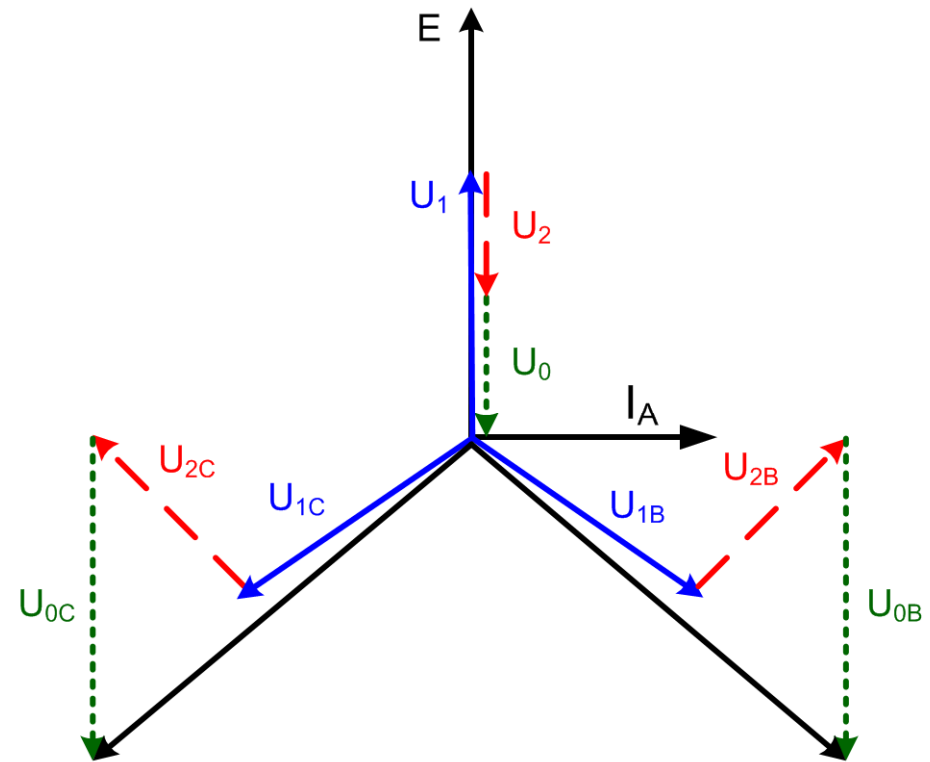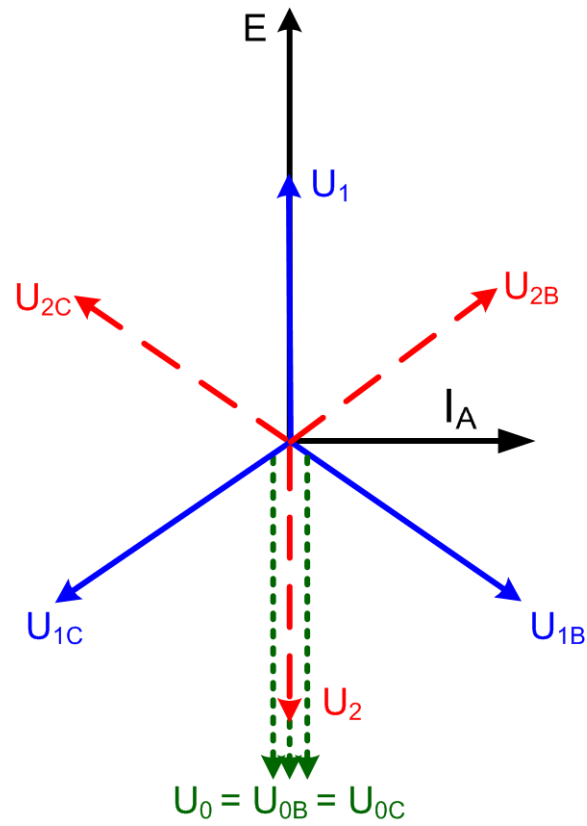

## Phase-to-phase short-circuit

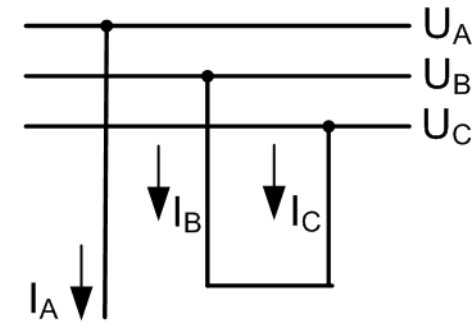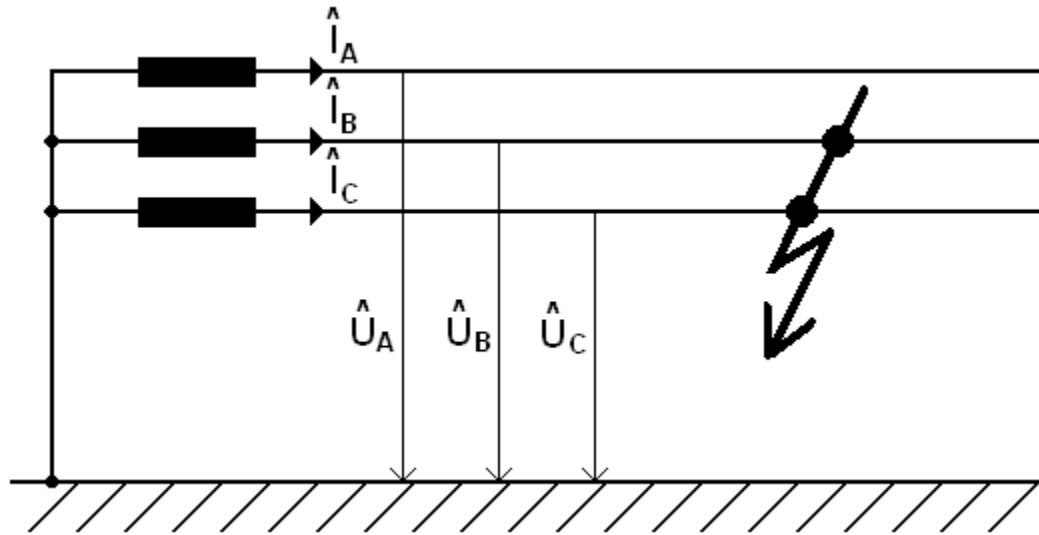

3 char. equations

$$\hat{U}_B = \hat{U}_C; \quad \hat{I}_B = -\hat{I}_C; \quad \hat{I}_A = 0$$

Hence 6 equations for 6 unknowns

$$\hat{E} = \hat{Z}_1 \hat{I}_1 + \hat{U}_1 \quad \hat{a}^2 \hat{U}_1 + \hat{a} \hat{U}_2 + \hat{U}_0 = \hat{a} \hat{U}_1 + \hat{a}^2 \hat{U}_2 + \hat{U}_0$$

$$0 = \hat{Z}_2 \hat{I}_2 + \hat{U}_2 \quad \hat{a}^2 \hat{I}_1 + \hat{a} \hat{I}_2 + \hat{I}_0 = -(\hat{a} \hat{I}_1 + \hat{a}^2 \hat{I}_2 + \hat{I}_0)$$

$$0 = \hat{Z}_0 \hat{I}_0 + \hat{U}_0 \quad \hat{I}_1 + \hat{I}_2 + \hat{I}_0 = 0$$

## Components


$$\begin{pmatrix} \mathbf{I}_{120} \end{pmatrix} = \frac{1}{3} \begin{pmatrix} 1 & \hat{a} & \hat{a}^2 \\ 1 & \hat{a}^2 & \hat{a} \\ 1 & 1 & 1 \end{pmatrix} \begin{pmatrix} 0 \\ \hat{\mathbf{I}}_B \\ -\hat{\mathbf{I}}_B \end{pmatrix} = \frac{1}{3} \begin{pmatrix} j\sqrt{3}\hat{\mathbf{I}}_B \\ -j\sqrt{3}\hat{\mathbf{I}}_B \\ 0 \end{pmatrix}$$

$$\hat{\mathbf{I}}_1 = \frac{\hat{\mathbf{E}}}{\hat{\mathbf{Z}}_1 + \hat{\mathbf{Z}}_2}; \quad \hat{\mathbf{I}}_2 = -\hat{\mathbf{I}}_1; \quad \hat{\mathbf{I}}_0 = 0$$

$$\hat{\mathbf{U}}_1 = \hat{\mathbf{U}}_2 = \frac{\hat{\mathbf{Z}}_2 \cdot \hat{\mathbf{E}}}{\hat{\mathbf{Z}}_1 + \hat{\mathbf{Z}}_2} = \hat{\mathbf{Z}}_2 \cdot \hat{\mathbf{I}}_1$$

$$\hat{\mathbf{U}}_0 = 0$$

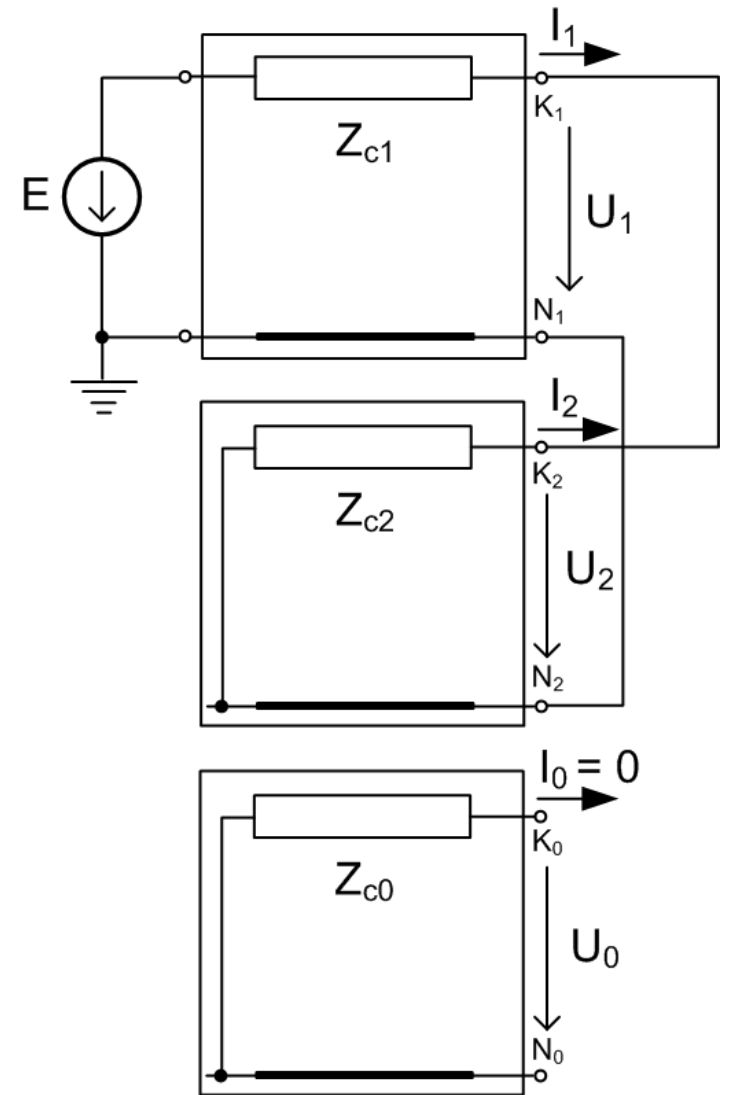Positive and negative components in parallel.



## Phases



$$(\mathbf{I}_{ABC}) = (\mathbf{T})(\mathbf{I}_{120}) = \begin{pmatrix} 1 & 1 & 1 \\ \hat{a}^2 & \hat{a} & 1 \\ \hat{a} & \hat{a}^2 & 1 \end{pmatrix} \begin{pmatrix} \hat{I}_1 \\ -\hat{I}_1 \\ 0 \end{pmatrix} = \begin{pmatrix} 0 \\ -j\sqrt{3}\hat{I}_1 \\ j\sqrt{3}\hat{I}_1 \end{pmatrix}$$

$$\hat{I}_A = 0; \quad \hat{I}_B = \frac{-j\sqrt{3}\hat{E}}{\hat{Z}_1 + \hat{Z}_2}; \quad \hat{I}_C = \frac{j\sqrt{3}\hat{E}}{\hat{Z}_1 + \hat{Z}_2}$$


$$(\mathbf{U}_{ABC}) = (\mathbf{T})(\mathbf{U}_{120}) = \begin{pmatrix} 1 & 1 & 1 \\ \hat{a}^2 & \hat{a} & 1 \\ \hat{a} & \hat{a}^2 & 1 \end{pmatrix} \begin{pmatrix} \hat{U}_1 \\ \hat{U}_1 \\ 0 \end{pmatrix} = \begin{pmatrix} 2\hat{U}_1 \\ -\hat{U}_1 \\ -\hat{U}_1 \end{pmatrix} = \begin{pmatrix} 2\hat{Z}_2 \cdot \hat{I}_1 \\ -\hat{Z}_2 \cdot \hat{I}_1 \\ -\hat{Z}_2 \cdot \hat{I}_1 \end{pmatrix}$$





# Current phasor diagram

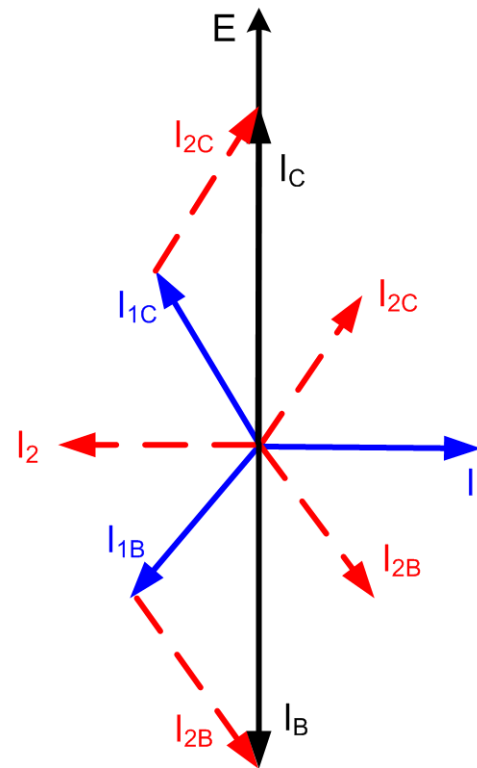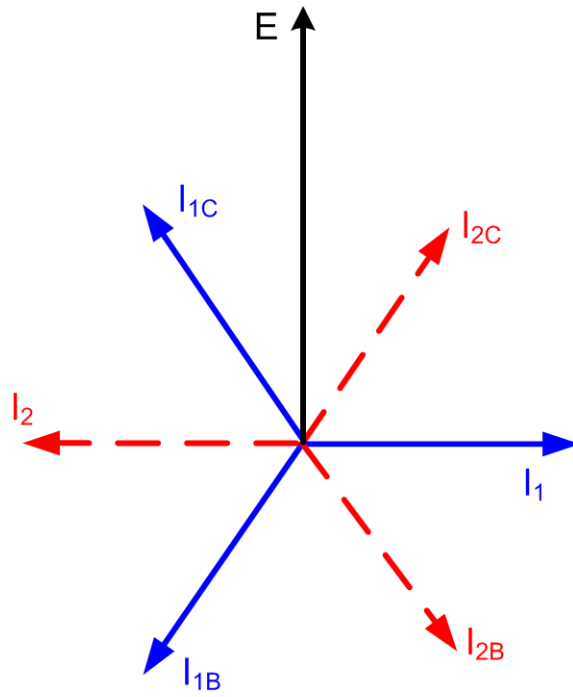

# Voltage phasor diagram

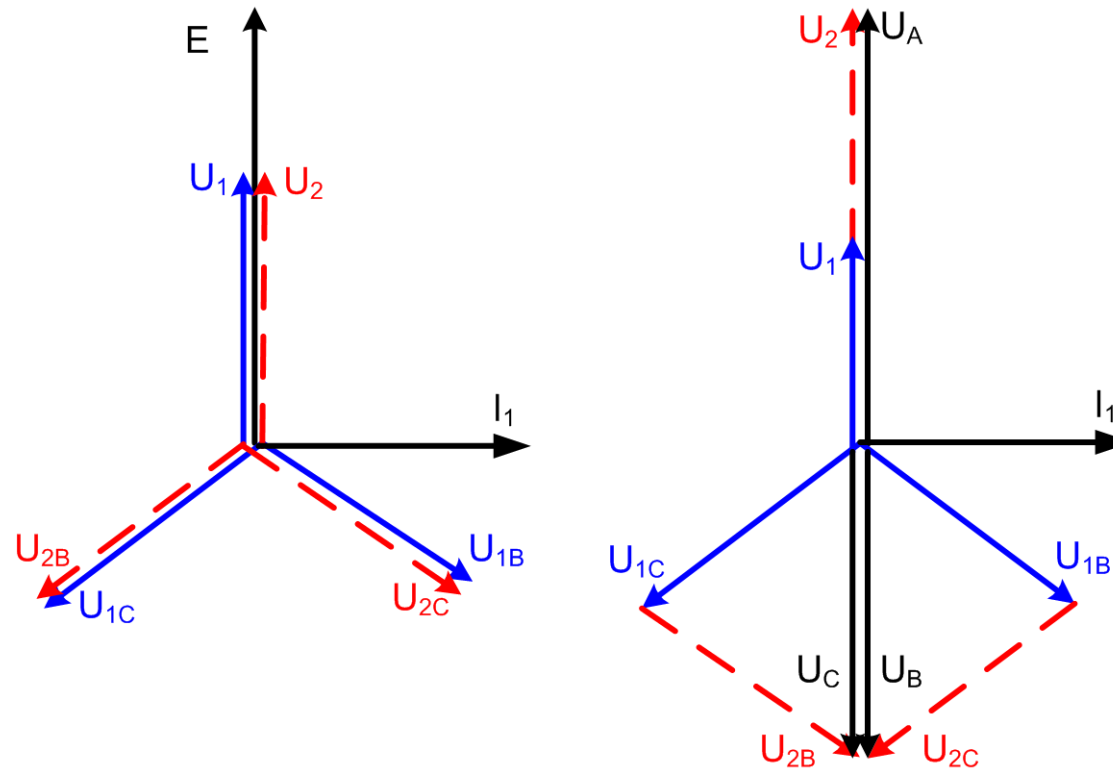

## Double-phase-to-ground short-circuit

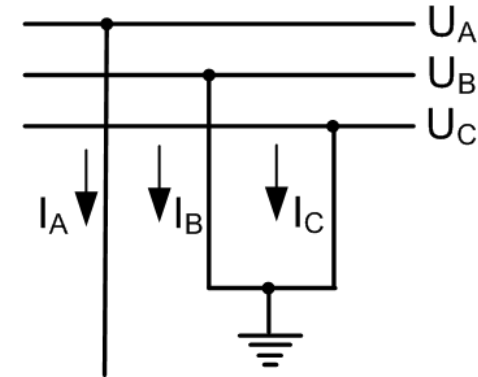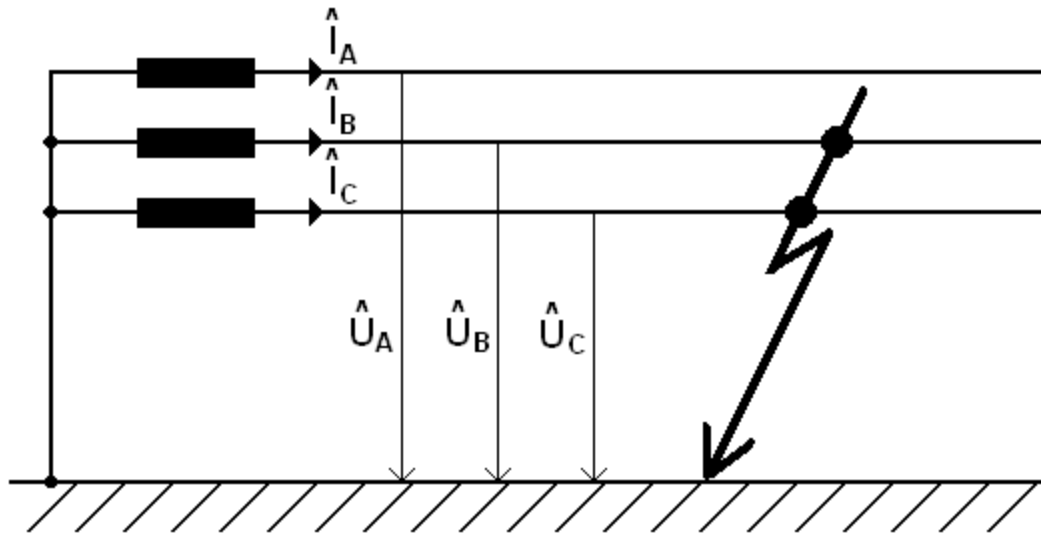

3 char. equations

$$\hat{U}_B = \hat{U}_C = 0; \hat{I}_A = 0$$

Hence 6 equations for 6 unknowns

$$\hat{E} = \hat{Z}_1 \hat{I}_1 + \hat{U}_1 \quad \hat{a}^2 \hat{U}_1 + \hat{a} \hat{U}_2 + \hat{U}_0 = 0$$

$$0 = \hat{Z}_2 \hat{I}_2 + \hat{U}_2 \quad \hat{a} \hat{U}_1 + \hat{a}^2 \hat{U}_2 + \hat{U}_0 = 0$$

$$0 = \hat{Z}_0 \hat{I}_0 + \hat{U}_0 \quad \hat{I}_1 + \hat{I}_2 + \hat{I}_0 = 0$$


## Components

$$(\mathbf{U}_{120}) = \frac{1}{3} \begin{pmatrix} 1 & \hat{a} & \hat{a}^2 \\ 1 & \hat{a}^2 & \hat{a} \\ 1 & 1 & 1 \end{pmatrix} \begin{pmatrix} \hat{U}_A \\ 0 \\ 0 \end{pmatrix} = \frac{1}{3} \begin{pmatrix} \hat{U}_A \\ \hat{U}_A \\ \hat{U}_A \end{pmatrix}$$

$$\hat{I}_1 = \frac{\hat{E}}{\hat{Z}_1 + \frac{\hat{Z}_0 \hat{Z}_2}{\hat{Z}_0 + \hat{Z}_2}}$$

$$\hat{I}_2 = -\frac{\hat{Z}_0}{\hat{Z}_0 + \hat{Z}_2} \hat{I}_1; \quad \hat{I}_0 = -\frac{\hat{Z}_2}{\hat{Z}_0 + \hat{Z}_2} \hat{I}_1$$
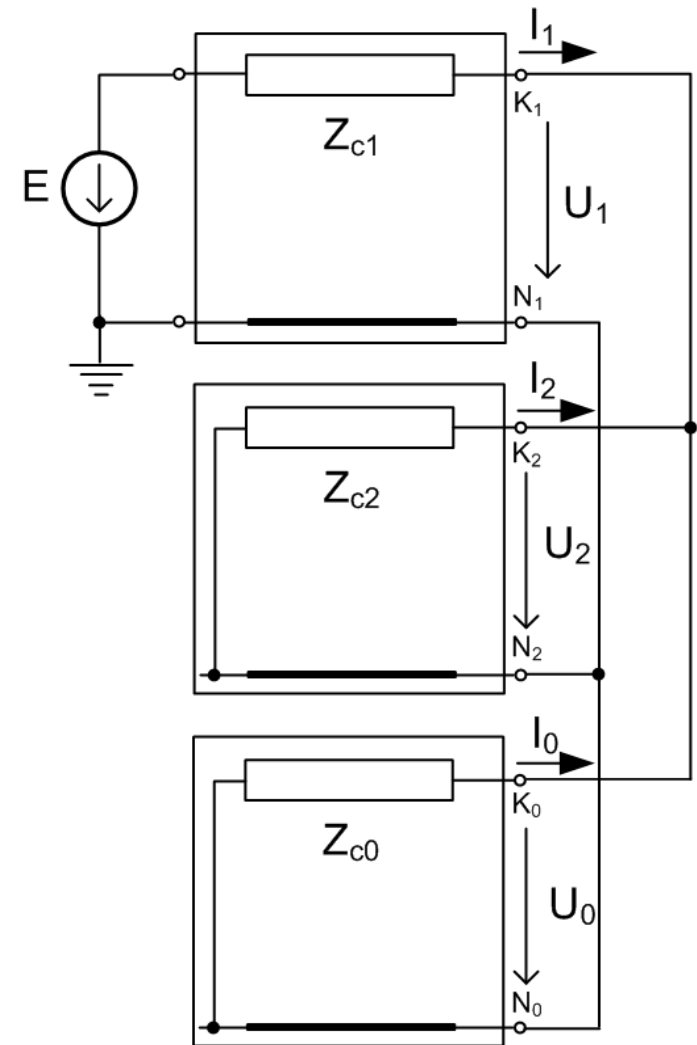
$$\hat{U}_1 = \hat{U}_2 = \hat{U}_0 = \frac{\hat{E} \frac{\hat{Z}_0 \hat{Z}_2}{\hat{Z}_0 + \hat{Z}_2}}{\hat{Z}_1 + \frac{\hat{Z}_0 \hat{Z}_2}{\hat{Z}_0 + \hat{Z}_2}}$$



All three components are in parallel.

Phases


$$(\mathbf{I}_{ABC}) = (\mathbf{T})(\mathbf{I}_{120})$$

$$\hat{I}_B = \frac{\hat{E}(\hat{Z}_0(\hat{a}^2 - \hat{a}) + \hat{Z}_2(\hat{a}^2 - 1))}{\hat{Z}_1\hat{Z}_2 + \hat{Z}_0\hat{Z}_1 + \hat{Z}_0\hat{Z}_2}$$

$$\hat{I}_C = \frac{\hat{E}(\hat{Z}_0(\hat{a} - \hat{a}^2) + \hat{Z}_2(\hat{a} - 1))}{\hat{Z}_1\hat{Z}_2 + \hat{Z}_0\hat{Z}_1 + \hat{Z}_0\hat{Z}_2}$$

$$(\mathbf{U}_{ABC}) = (\mathbf{T})(\mathbf{U}_{120}) = \begin{pmatrix} 1 & 1 & 1 \\ \hat{a}^2 & \hat{a} & 1 \\ \hat{a} & \hat{a}^2 & 1 \end{pmatrix} \begin{pmatrix} \hat{U}_1 \\ \hat{U}_1 \\ \hat{U}_1 \end{pmatrix} = \begin{pmatrix} 3\hat{U}_1 \\ 0 \\ 0 \end{pmatrix}$$

# Phasor diagrams

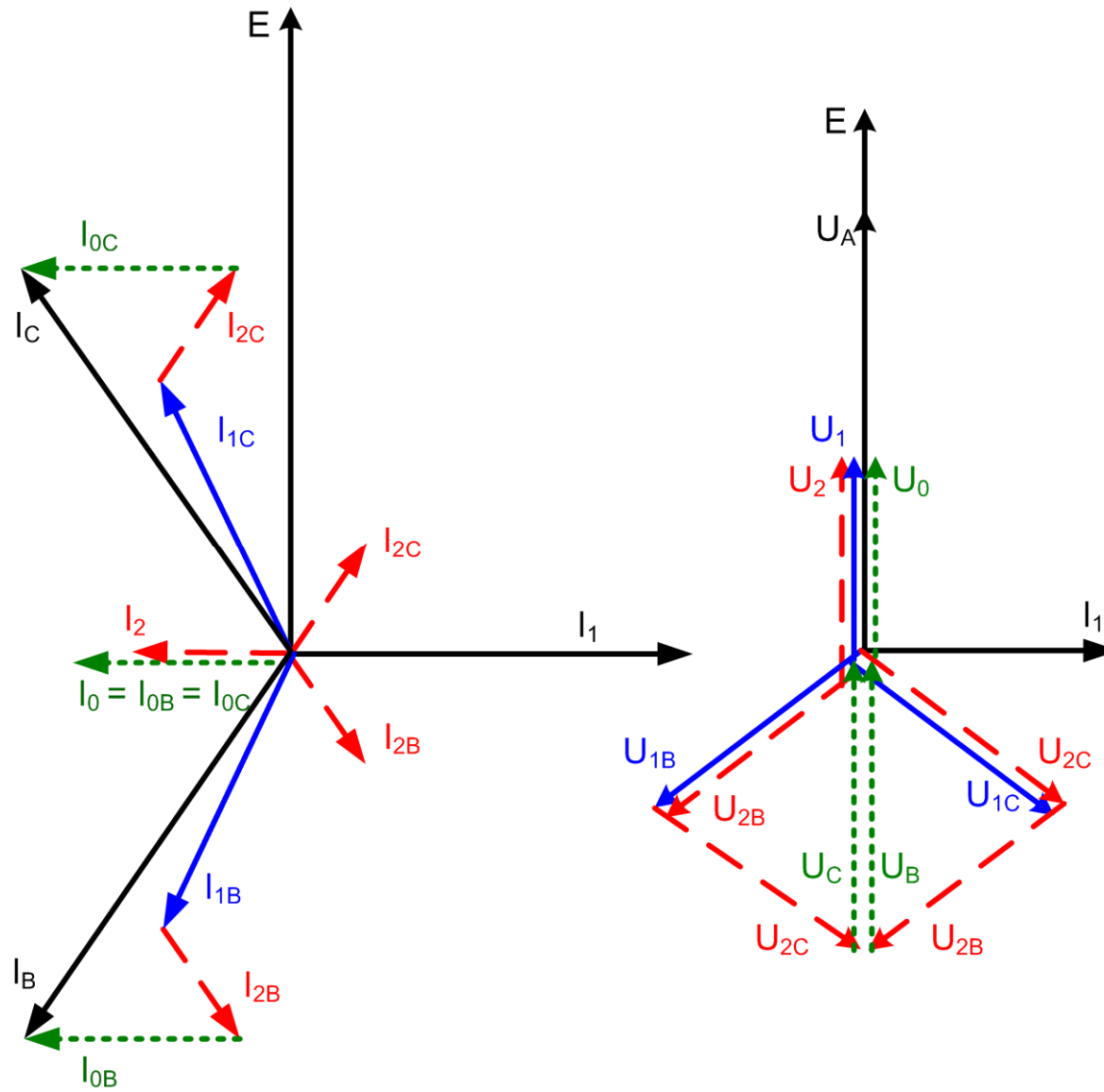

## Components during short-circuit:

|            |                          |
|------------|--------------------------|
| 3ph        | positive                 |
| 2ph        | positive, negative       |
| 2ph ground | positive, negative, zero |
| 1ph        | positive, negative, zero |

## Short-circuits calculation by means of relative values

Relative values – related to a defined base.

|                               |                    |
|-------------------------------|--------------------|
| base power (3ph)              | $S_v$ (VA)         |
| base voltage (phase-to-phase) | $U_v$ (V)          |
| base current                  | $I_v$ (A)          |
| base impedance                | $Z_v$ ( $\Omega$ ) |

$$S_v = \sqrt{3}U_v I_v$$

$$Z_v = \frac{U_{vf}}{I_v}$$

Relative impedance

$$z = \frac{Z}{Z_v} = \frac{Z}{\frac{U_{vf}}{I_v}} = Z \frac{I_v}{U_{vf}} \frac{3U_{vf}}{3U_{vf}} = Z \frac{S_v}{3U_{vf}^2} = Z \frac{S_v}{U_v^2}$$



## Initial sub-transient short-circuit current (3ph short-circuit)

$$I''_{k0} = |\hat{I}_A| = \frac{|\hat{U}_f|}{|\hat{Z}_1|}$$

$$Z_1 = z_1 \frac{U_v^2}{S_v}$$

$$I''_{k0} = \frac{\frac{U_v}{\sqrt{3}}}{z_1 \frac{U_v^2}{S_v}} = \frac{1}{z_1} \frac{S_v}{\sqrt{3}U_v} = \frac{1}{z_1} I_v$$

## Initial sub-transient short-circuit power

$$S''_{k0} = \sqrt{3}U_v I''_{k0} = \sqrt{3}U_v \frac{I_v}{z_1} = \frac{1}{z_1} S_v$$

Similarly for

1ph short-circuit

$$I_{k0}''^{(1)} = \frac{3}{Z_1 + Z_2 + Z_0} I_v$$

2ph short-circuit

$$I_{k0}''^{(2)} = \frac{\sqrt{3}}{Z_1 + Z_2} I_v$$

Note: Sometimes it is respected generator loading, more precisely higher internal generator voltage than nominal one.

$$I_{k0}'' = k \frac{1}{Z_1} I_v$$

$$k > 1$$