

## Ground fault in three-phase systems

MV grids without a directly grounded neutral point (distribution systems)  
→ single-phase ground fault has a different character than short-circuits  
(small capacitive current).

Fault current proportional to the system extent.

$I_p > 5 \text{ A}$  → arc formation → conductors, towers, insulators burning →  
→ 2ph, 3ph short-circuits (mainly at cables)

Interrupted GF → overvoltage up to  $4\div 5 U_{ph}$  on healthy phases

GF compensation → uninterrupted system operation (until the failure clearance, short supply break), arc self-extinguishing

Ground fault


- resistive ( $100x \Omega$ ), metal and arc ( $x \Omega$ )
- momentary (up to 0,5 s), short-term (up to 5 min), interrupted (repeating), permanent (x hours)

## Conditions in a system with insulated neutral point

Assumptions: considered only capacities to the ground, symmetrical source voltage, open-circuit system

Insulated neutral point – systems of a small extent,  $I_p < 10 \text{ A}$

### Before the fault

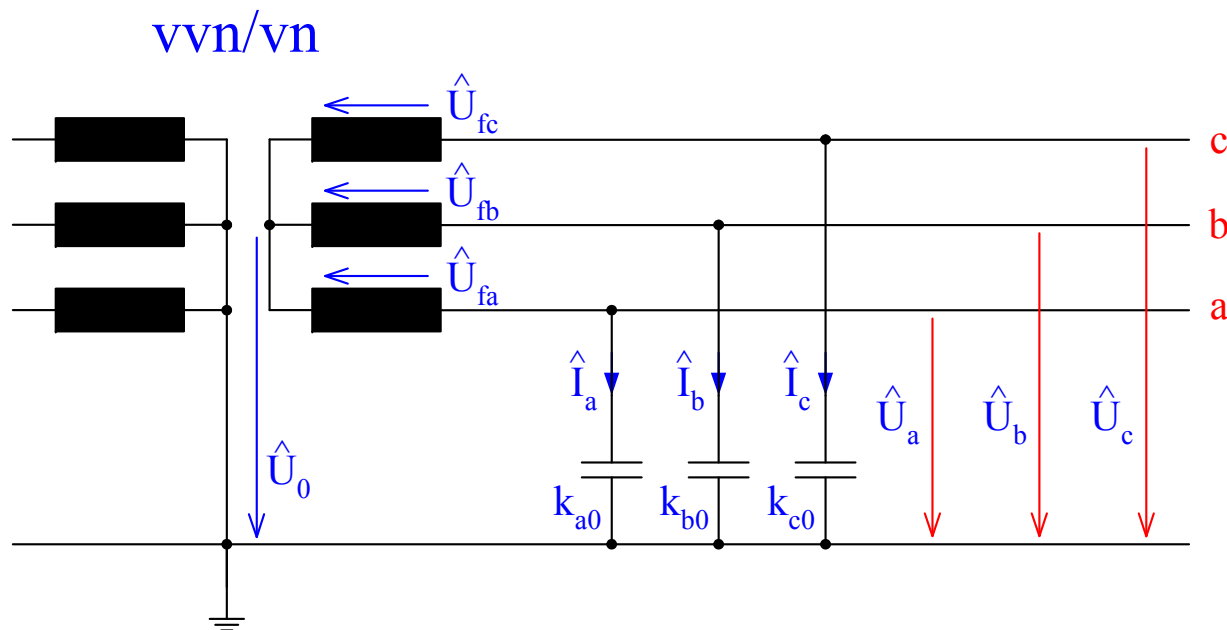

$$\hat{U}_a - \hat{U}_0 - \hat{U}_{fa} = 0$$

$$\hat{U}_b - \hat{U}_0 - \hat{U}_{fb} = 0$$

$$\hat{U}_c - \hat{U}_0 - \hat{U}_{fc} = 0$$

$$\hat{I}_a = j\omega k_{a0} \hat{U}_a$$

$$\hat{I}_b = j\omega k_{b0} \hat{U}_b$$

$$\hat{I}_c = j\omega k_{c0} \hat{U}_c$$

System with insulated neutral point

$$\hat{I}_a + \hat{I}_b + \hat{I}_c = 0$$

Symmetrical source

$$\hat{U}_{fb} = \hat{a}^2 \hat{U}_{fa}, \quad \hat{U}_{fc} = \hat{a} \hat{U}_{fa}$$

Neutral point voltage

$$\hat{U}_0 = -\frac{k_{a0} + \hat{a}^2 k_{b0} + \hat{a} k_{c0}}{k_{a0} + k_{b0} + k_{c0}} \hat{U}_{fa}$$

Unbalanced capacities


$$\hat{U}_0 \neq 0$$

## Symmetrical capacities

$$k_{a0} = k_{b0} = k_{c0} = k_0 \Rightarrow \hat{U}_0 = 0$$

Ex.: 2 tower terminals 22 kV,  $l = 50$  km


### “Talon”

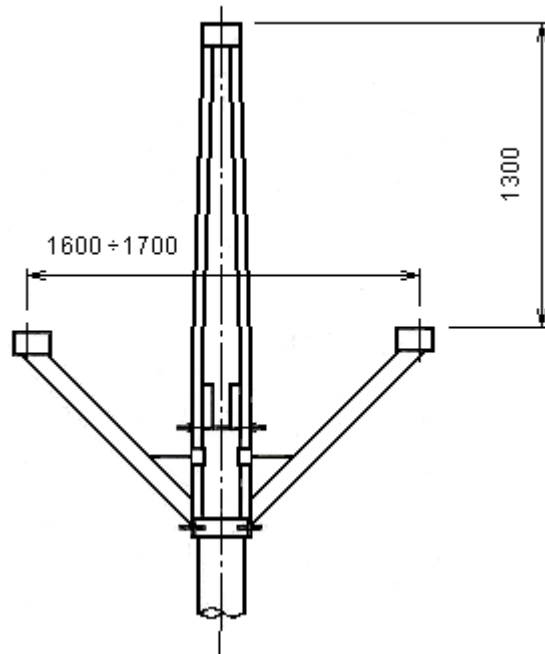

$$k_{a0} = k_{c0} = 4,16 \text{ nF / km}$$


$$k_{b0} = 4,00 \text{ nF / km} \quad (\Delta = 3,8 \%)$$

### Horizontal

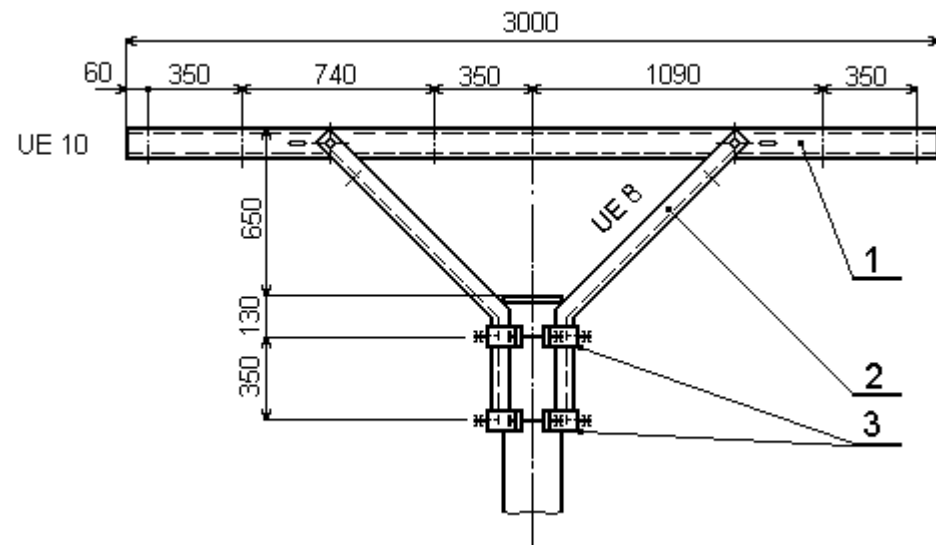

$$k_{a0} = k_{c0} = 4,48 \text{ nF / km}$$
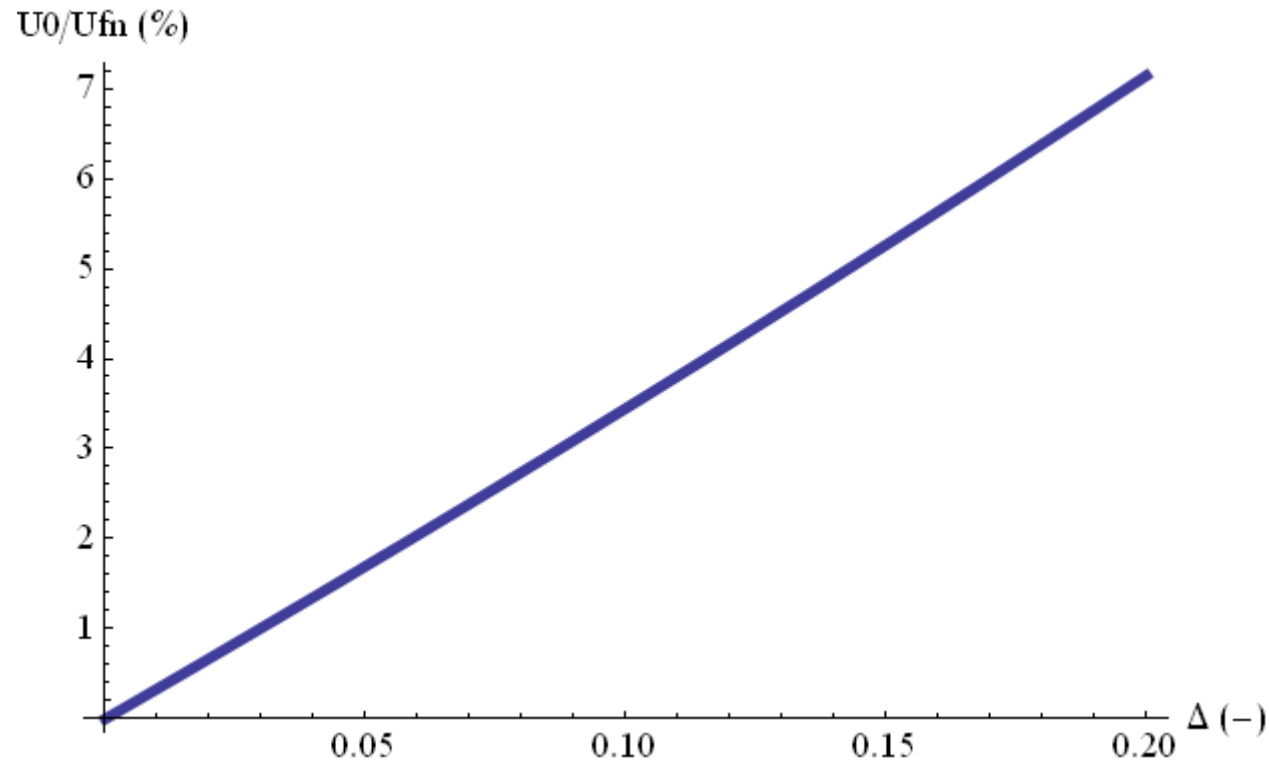
$$k_{b0} = 3,90 \text{ nF / km} \quad (\Delta = 12,9 \%)$$



### Talon

$$U_0 = 165 \text{ V (1,3 \%)}$$

$$U_a = U_c = 12620 \text{ V}$$

$$U_b = 12867 \text{ V}$$

$$U_{fn} = 12702 \text{ V}$$

### Horozontal


$$U_0 = 573 \text{ V (4,5 \%)}$$

$$U_a = U_c = 12425 \text{ V}$$

$$U_b = 13275 \text{ V}$$

## Perfect (metal) durable ground fault

### Symmetrical system

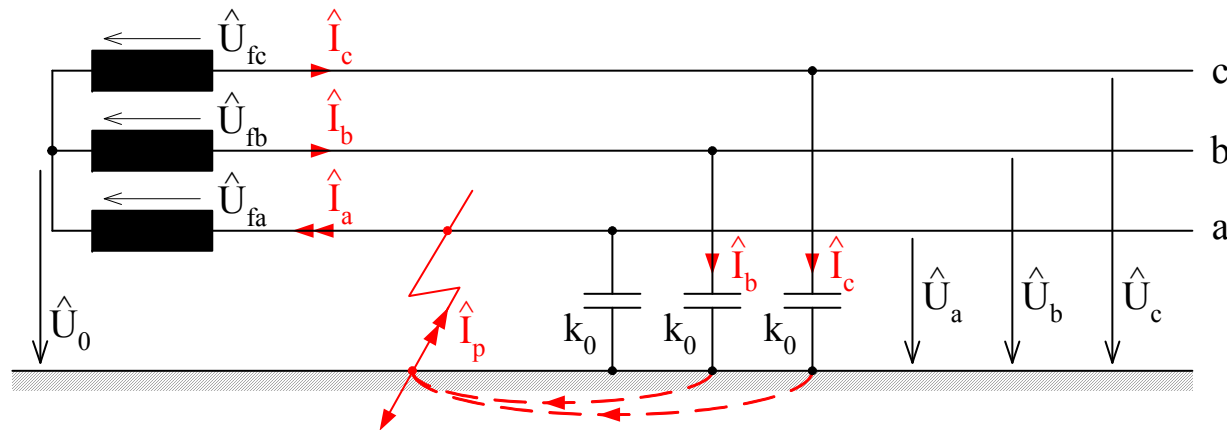

Fault current composed of 2 capacitive currents in the disaffected phases.

$$\hat{U}_a = 0$$

$$\hat{I}_p = \hat{I}_a = \hat{I}_b + \hat{I}_c$$

$$\hat{I}_b = j\omega k_0 \hat{U}_b \quad \hat{I}_c = j\omega k_0 \hat{U}_c$$

$$\hat{U}_a - \hat{U}_0 - \hat{U}_{fa} = 0 \quad \Rightarrow \quad \hat{U}_0 = -\hat{U}_{fa} !$$

$$\hat{U}_b - \hat{U}_0 - \hat{U}_{fb} = 0 \quad \Rightarrow \quad \hat{U}_b = \hat{U}_0 + \hat{U}_{fb} = (-1 + \hat{a}^2)\hat{U}_{fa} = -\sqrt{3}e^{j30^\circ}\hat{U}_{fa} !$$

$$\hat{U}_c - \hat{U}_0 - \hat{U}_{fc} = 0 \quad \Rightarrow \quad \hat{U}_c = \hat{U}_0 + \hat{U}_{fc} = (-1 + \hat{a})\hat{U}_{fa} = -\sqrt{3}e^{-j30^\circ}\hat{U}_{fa} !$$

→ affected phase voltage – zero

neutral point voltage – phase-to-ground value


disaffected phases voltage – phase-to-phase value

Ground fault current

$$\begin{aligned} \hat{I}_p &= \hat{I}_b + \hat{I}_c = j\omega k_0 (\hat{U}_b + \hat{U}_c) \\ &= j\omega k_0 [(-1 + \hat{a}^2) + (-1 + \hat{a})]\hat{U}_{fa} \\ &= j\omega k_0 (-2 + \hat{a}^2 + \hat{a} + 1 - 1)\hat{U}_{fa} \\ \hat{I}_p &= -3j\omega k_0 \hat{U}_{fa} = 3j\omega k_0 \hat{U}_0 \quad (\text{A}; \text{s}^{-1}, \text{F}, \text{V}) \end{aligned}$$


---


# Voltage and current conditions

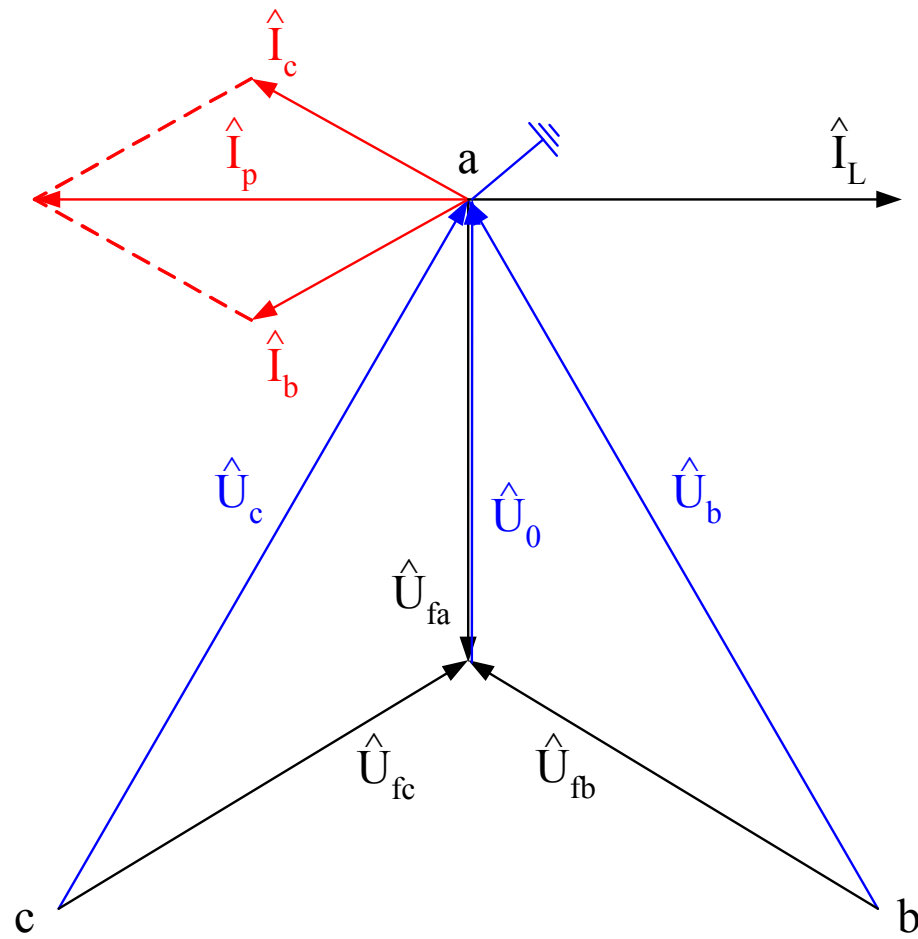



Fault current depends on the total system extent and almost doesn't depend on the fault point distance from the transformer.

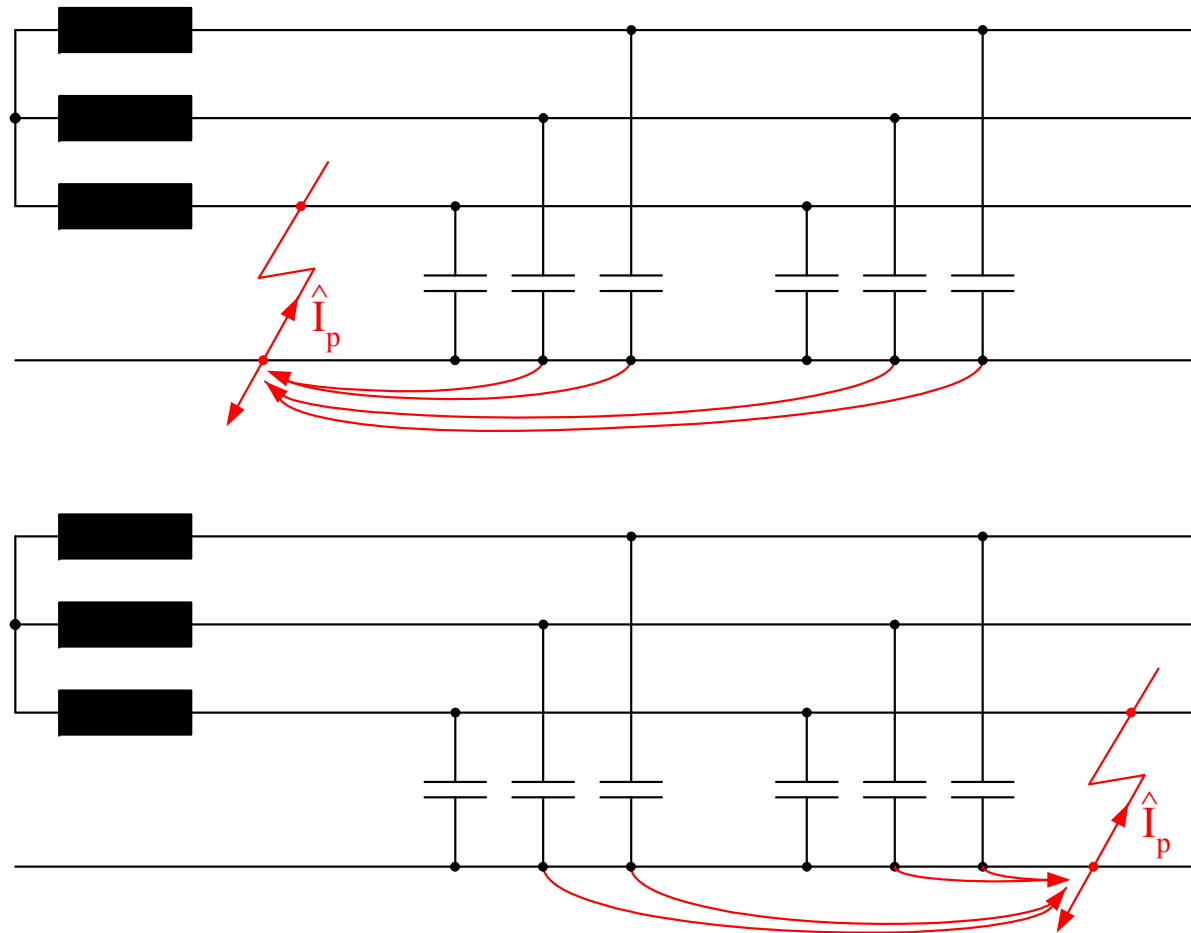
$$I_p = 3\omega k_{01} l U_f \quad (\text{A}; \text{s}^{-1}, \text{F} / \text{km}, \text{km}, \text{V})$$



Note: overhead 22 kV – current c. 0,06 A/km  
cables 22 kV – current c. 4 A/km

Note: MV system can be operated also with GF, on LV level again 3-phase supplying due to transformers MV/LV D/yn (Y/zn)

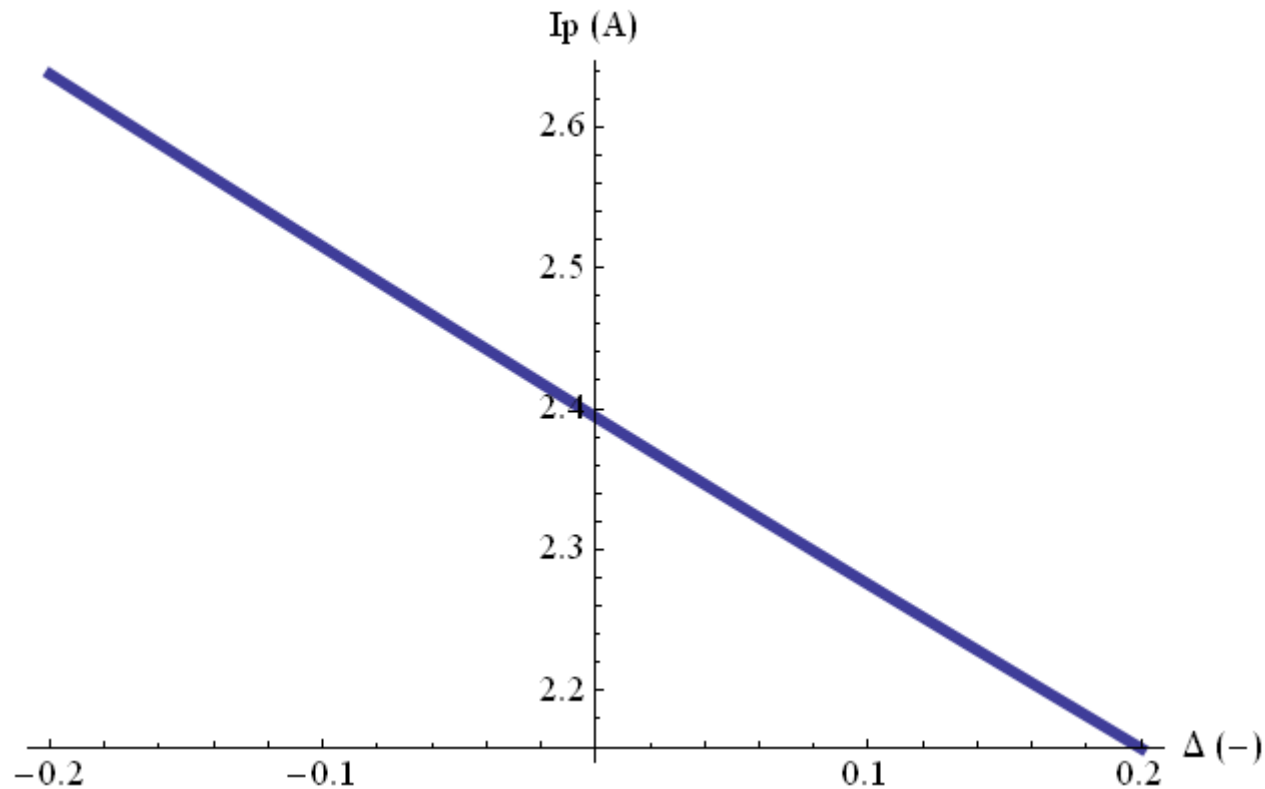Unbalanced system ( $k_{b0} = (1 - \Delta)k_{c0}$ ;  $k_{c0} = 4 \text{ nF / km} \cdot 50 \text{ km}$ )



## Talon

$$I_{pa} = I_{pc} = 2,44 \text{ A}$$


$$I_{pb} = 2,49 \text{ A}$$

## Horizontal

$$I_{pa} = I_{pc} = 2,51 \text{ A}$$

$$I_{pb} = 2,68 \text{ A}$$

## Resistive ground fault

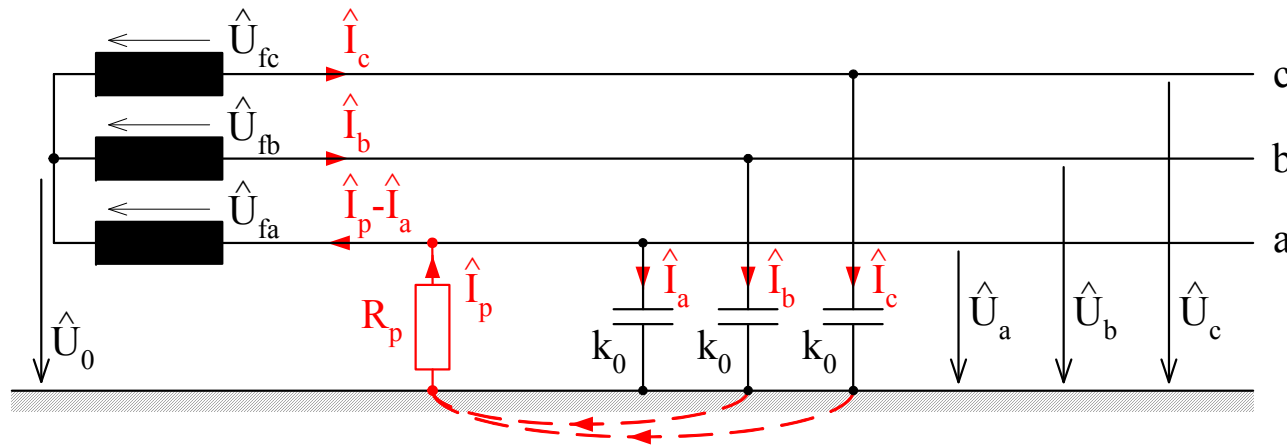

## Affected phase voltage non-zero

$$\hat{I}_p = -\hat{U}_a / R_p = \hat{I}_a + \hat{I}_b + \hat{I}_c$$

## Neutral point voltage

$$\hat{U}_0 = -\frac{j\omega(k_{a0} + \hat{a}^2 k_{b0} + \hat{a} k_{c0}) + R_p^{-1}}{j\omega(k_{a0} + k_{b0} + k_{c0}) + R_p^{-1}} \hat{U}_{fa}$$

## Circle equation in the Gauss plane


$$\hat{U}_0 = -\frac{\hat{A} + R_p^{-1}}{\hat{B} + R_p^{-1}} \hat{U}_{fa}$$

$$R_p = 0$$

$$\hat{U}_0 = -\hat{U}_{fa}$$



$$R_p = \infty$$
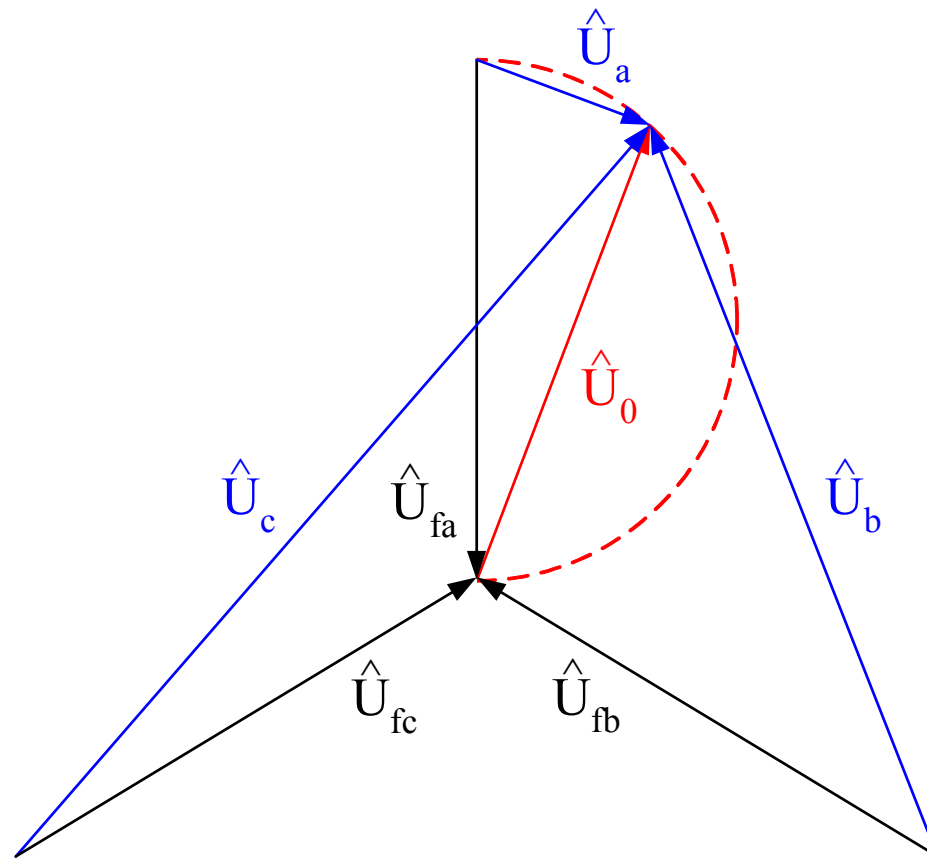
$$\hat{U}_0 = 0 \text{ (for symmetrical capacities)}$$





Disaffected phase voltage can be higher than the phase-to-phase value.

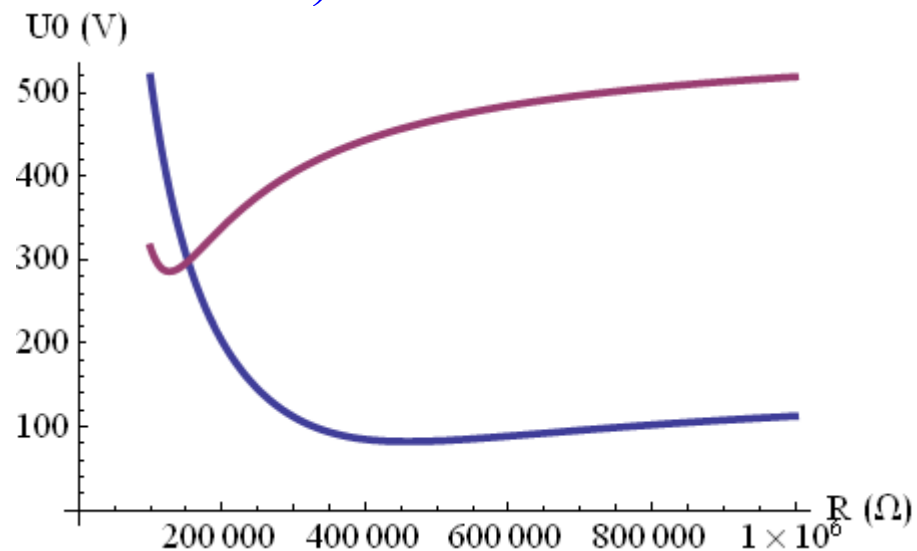
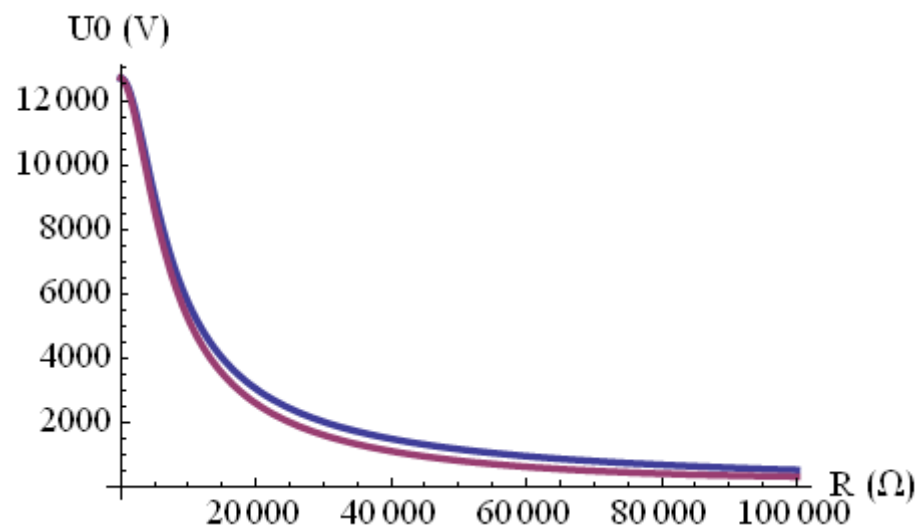
## Neutral point voltage (talon blue, horizontal violet)


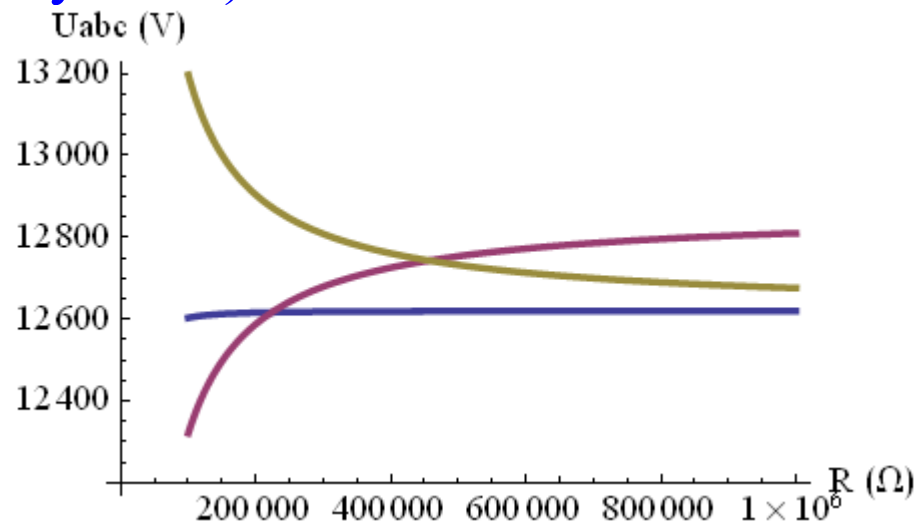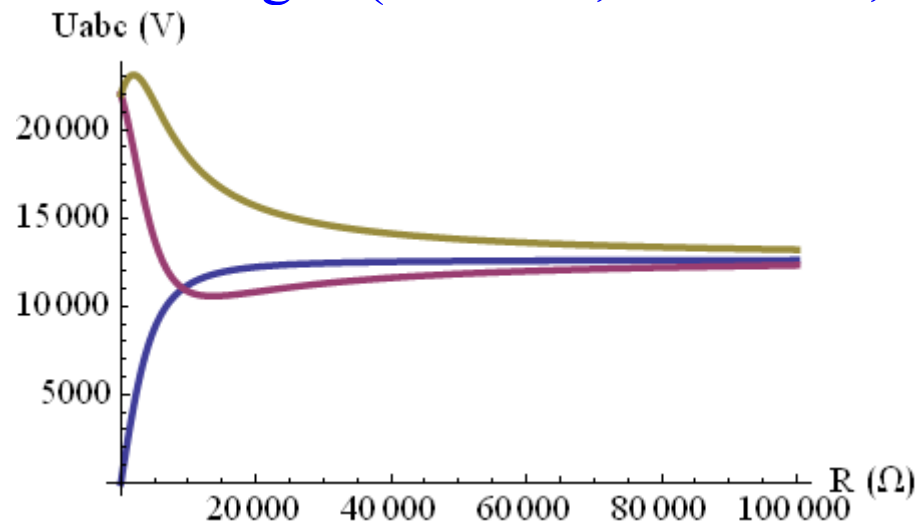
## Phase voltages (A - blue, B - violet, C - yellow) - talon



## Fault current – talon, phase A

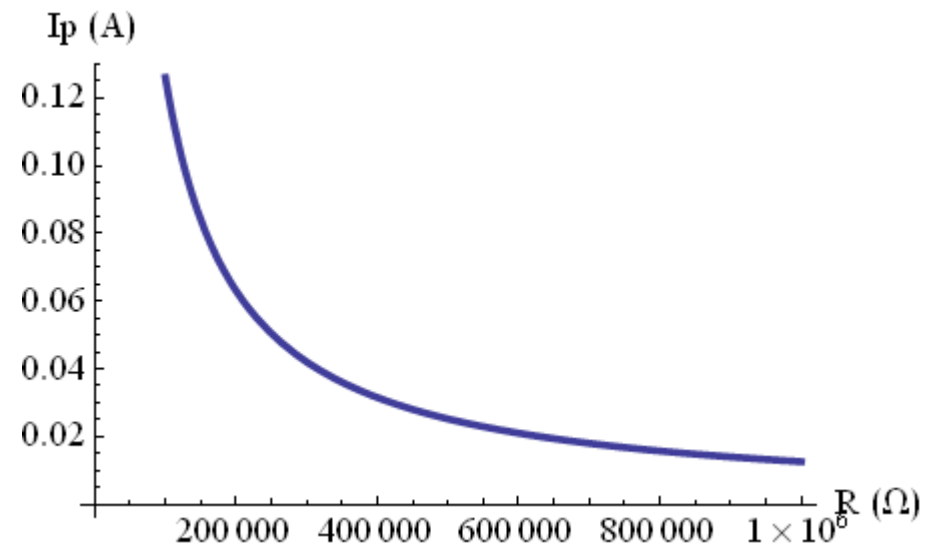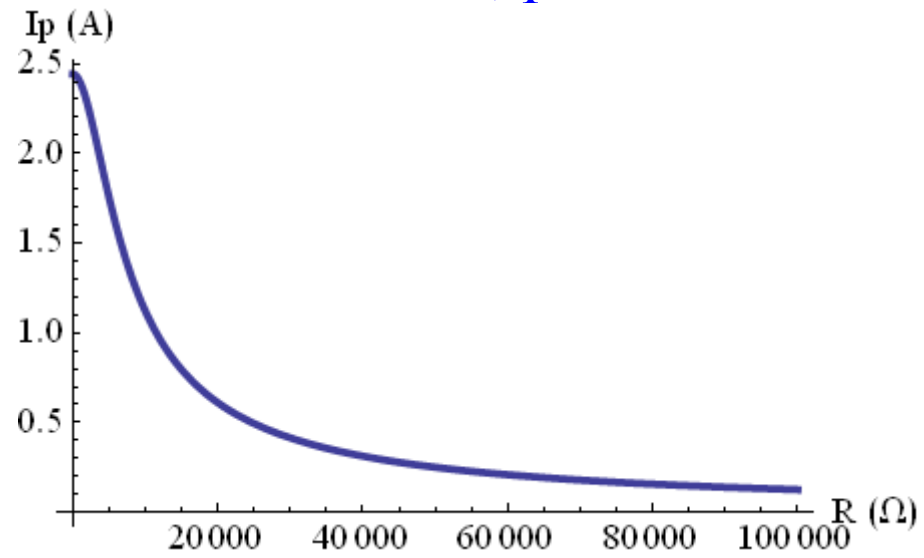


## Ground fault current compensation

Compensation in systems where  $I_p > 5A$  - suitable

$I_p > 10A$  - necessary

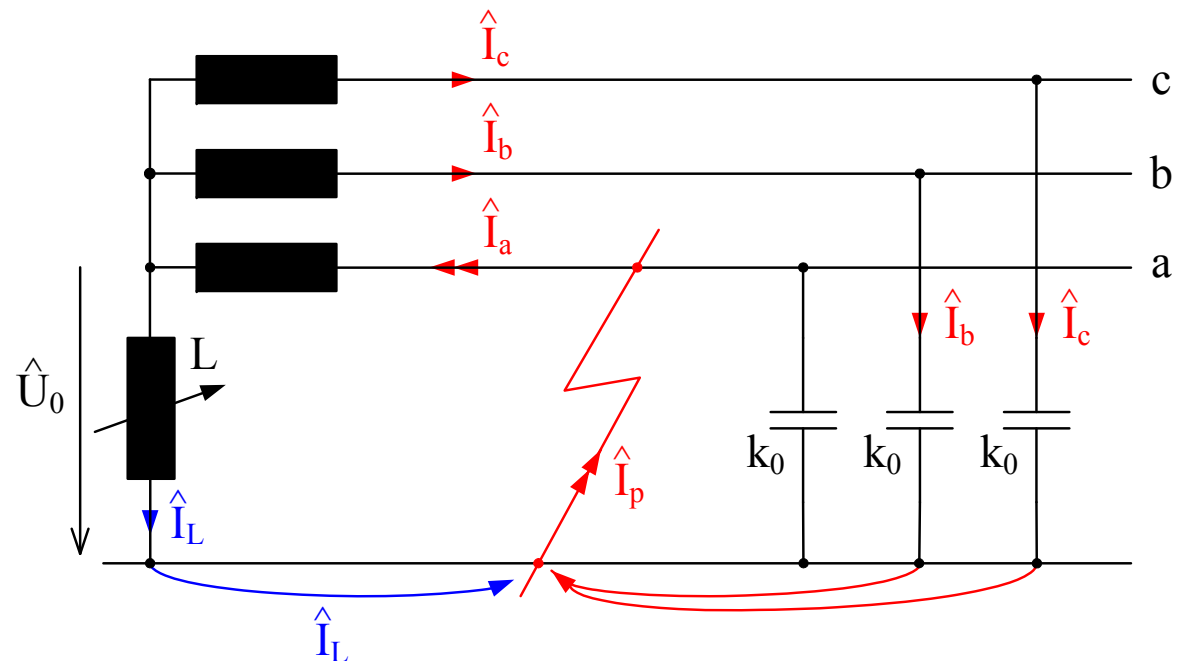Method: continuously controlled arc-suppression coil (Petersen coil) between the transformer neutral point and the ground (in case of transformers with D winding by means of grounding transformer with Zn, Yn – artificial neutral point)





## Faultless state

$$U_0 = 0 \quad - \text{symmetrical capacities}$$

$$U_0 \approx x \cdot 0,01 U_f \quad - \text{usual unbalance}$$

## Perfect ground fault

$$\hat{U}_0 = -\hat{U}_{fa}$$

## Arc-suppression coil current

$$\hat{I}_L = -j \frac{\hat{U}_0}{\omega L}$$

## Total compensation

$$\hat{I}_L = -\hat{I}_p$$

$$-j \frac{\hat{U}_0}{\omega L} = -3j\omega k_0 \hat{U}_0$$

Hence

$$\underline{L = \frac{1}{3\omega^2 k_0} \quad (\text{H; s}^{-1}, \text{F})}$$

Coil power (reactive inductive)


$$\hat{S} = \hat{U}_0 \hat{I}_L^* = 3j\omega k_0 \hat{U}_0 \hat{U}_0^* = j\omega k_0 U^2 = Q_L$$

Ideal compensation:  $I_p = 0$  in the fault point

Real situation: residual current (small active)

- inaccurate inductance setting (error or intention)
- uncompensatable active component (power line conductance, coil R)
- higher harmonics

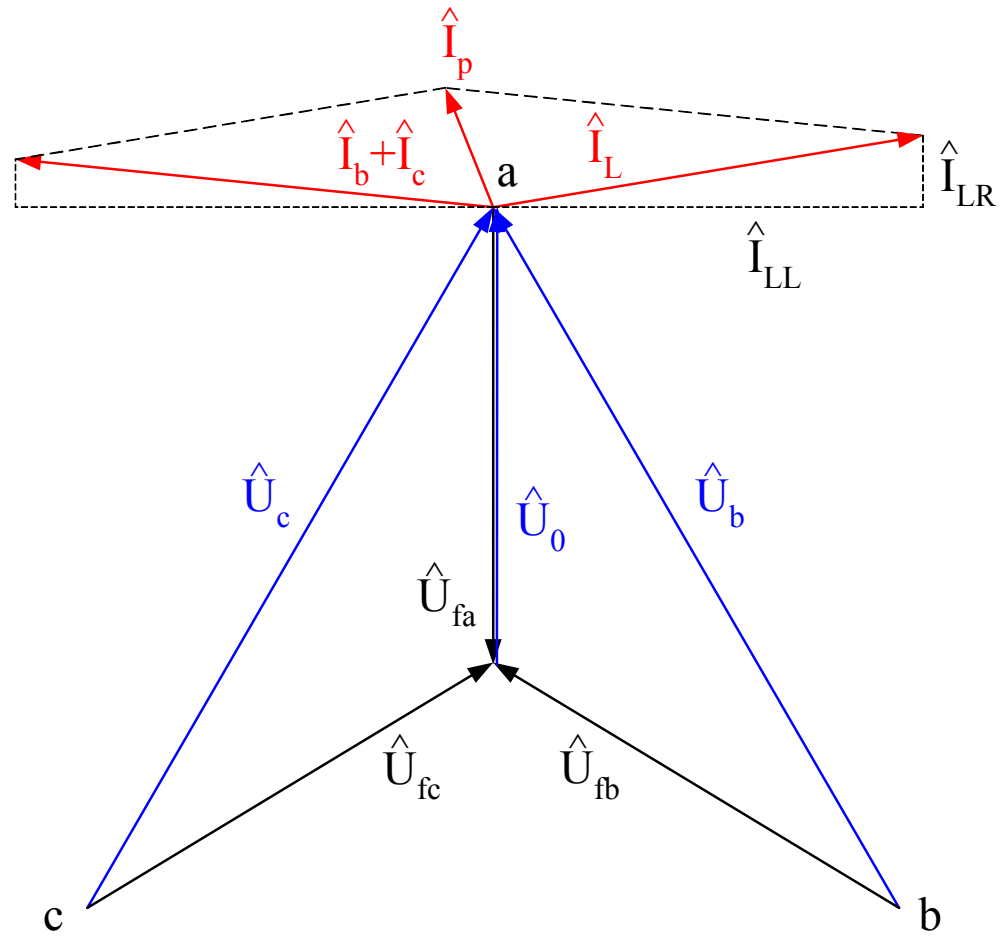
$$\hat{I}_p = \left[ \frac{1}{R_L} + 3G_0 + j \left( 3\omega k_0 - \frac{1}{\omega L} \right) \right] \hat{U}_0$$


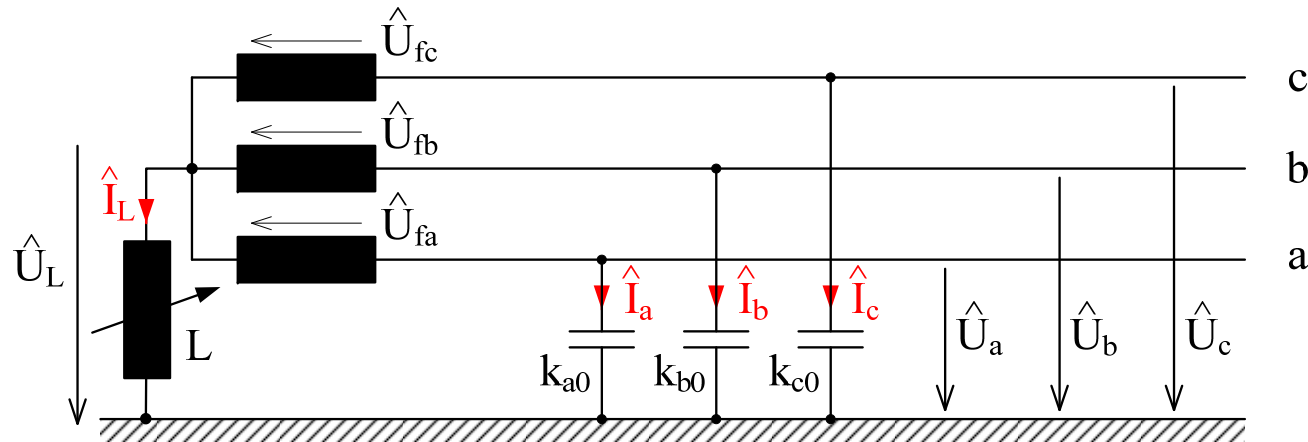
## Arc-suppression coil tuning

L dimensioning by calculation, setting in the faultless state (for given system configuration).

Tuning is done by magnetic circuit change by means of motor (air gap).




Coil voltage

$$\hat{U}_L = \frac{-\omega^2 L (k_{a0} + \hat{a}^2 k_{b0} + \hat{a} k_{c0})}{\omega^2 L (k_{a0} + k_{b0} + k_{c0}) - 1} \hat{U}_{fa}$$

## Resonance dependence

$$\left| \frac{U_L}{U_{fa}} \right| = f(L)$$
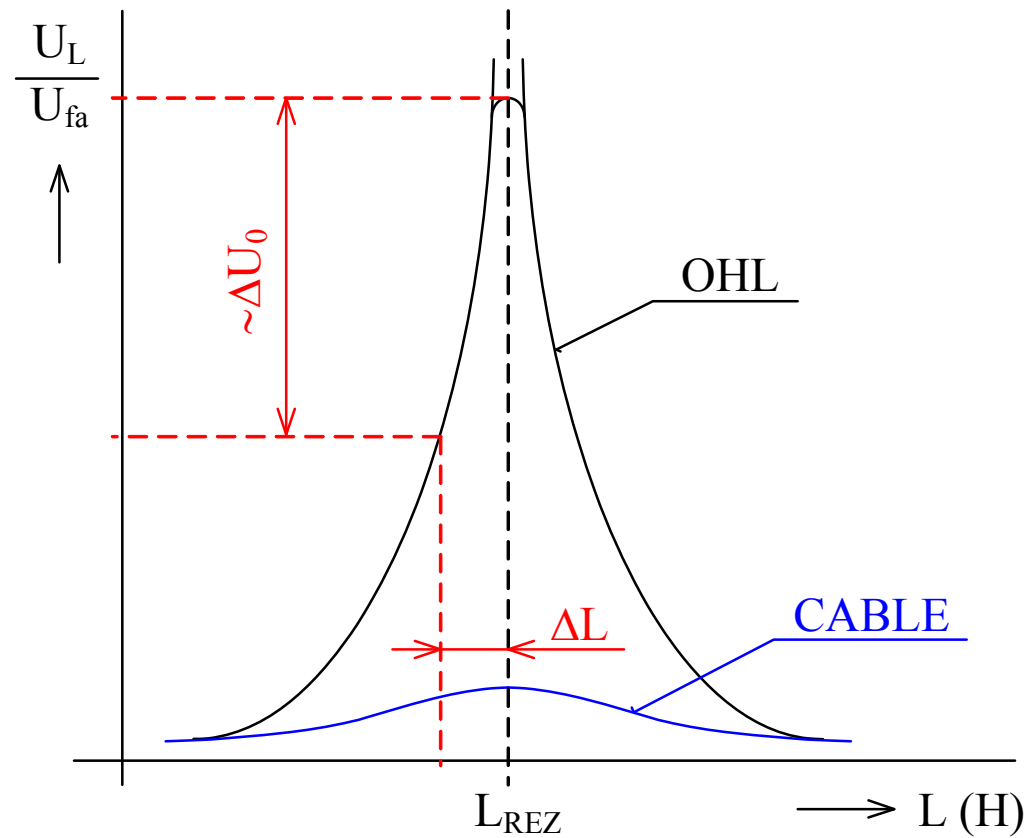
$$L_{\text{REZ}} = \frac{1}{\omega^2 (k_{a0} + k_{b0} + k_{c0})}$$



## Overhead power lines


- higher capacitive unbalance
- maximum limited by resistances
- $L_{\text{REZ}}$  compensates GF totally  $\rightarrow$  resonance coil
- setting by  $U_L$  measurement
- with small R the transformer neutral point is strained too much in resonance  $\rightarrow$  intended (small) detuning  $\rightarrow$  dissonance coil

## Cable power lines

- small capacitive unbalance  $\rightarrow$  flat curve  $\rightarrow$  difficult tuning


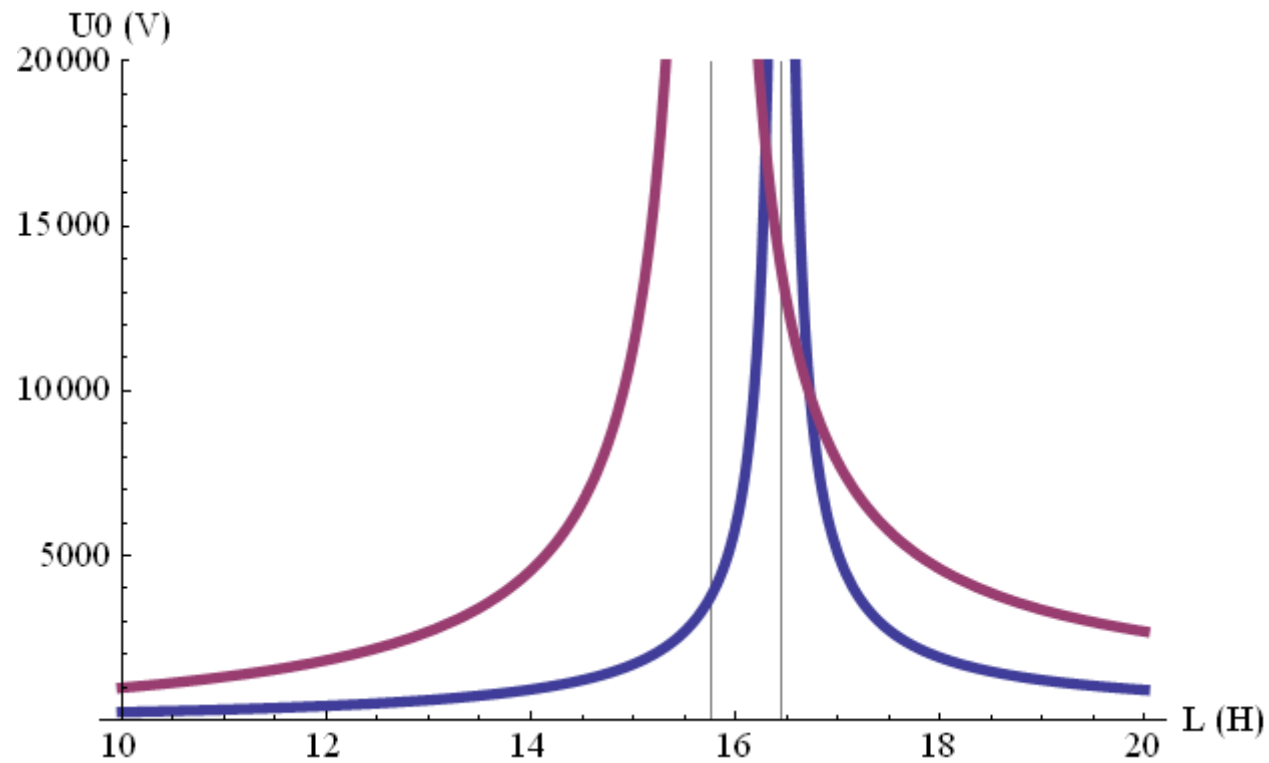
## Neutral point voltage (talon blue, horizontal violet)



talon

$$L_{REZ} = 16,45 \text{ H}$$

horizontal


$$L_{REZ} = 15,76 \text{ H}$$




# Fault current for coil detuning (talon blue, horizontal violet)

phase A

phase B

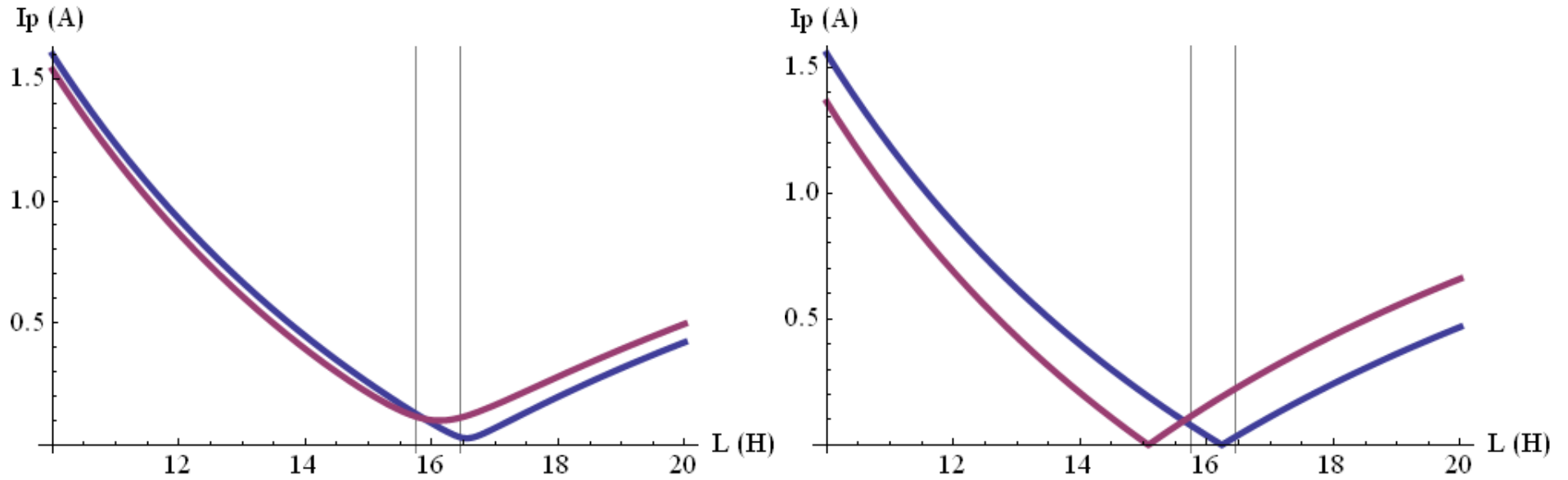

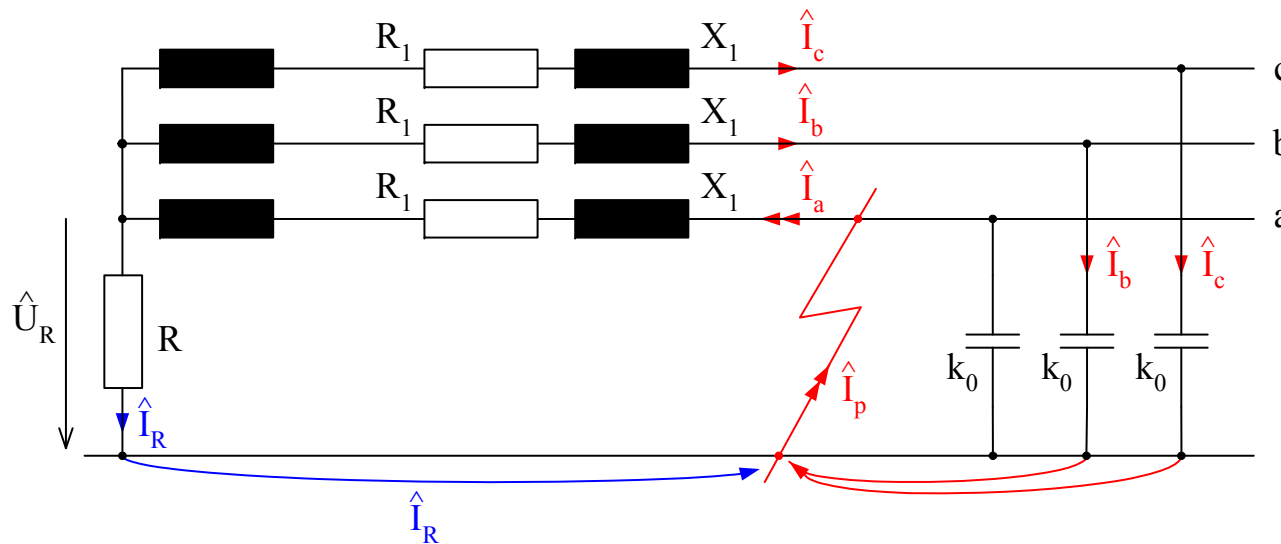
## Cable systems grounded with the resistance



During the fault

- neutral point voltage almost phase-to-ground value
- $I_p$  uncompensated
- $I_p$  depends on the system extent  $x$  decreases with the distance from the transformer (short-circuit character)
- $R$  value choice can influence  $I_p$  size and character


$$\hat{I}_p = -(1/R + j3\omega k_0)U_f$$

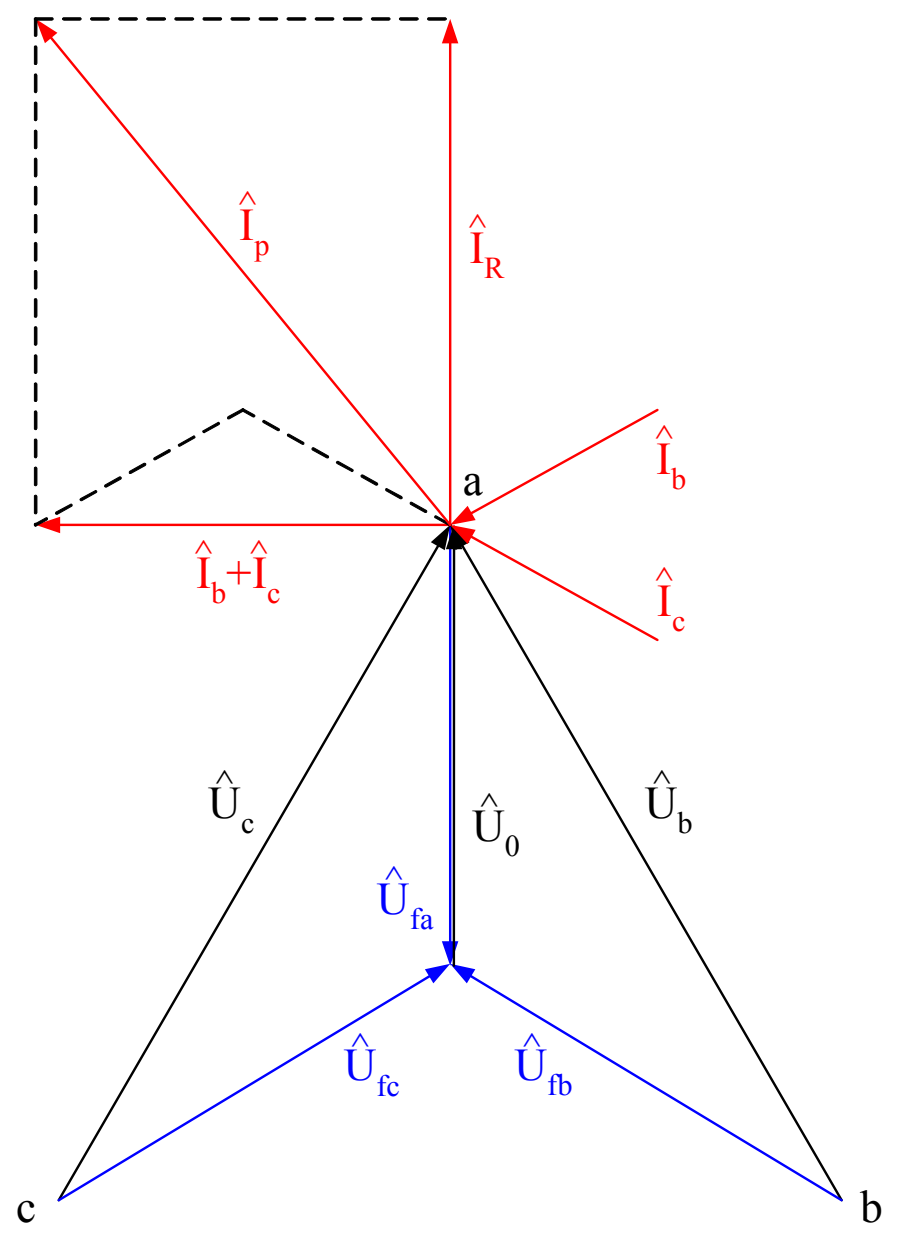


## Neutral point voltage in a faultless state

( $k_{b0} = (1 - \Delta)k_{c0}$ ;  $k_{a0} = k_{c0} = 4 \text{ nF / km} \cdot 50 \text{ km}$ )


$$R_{uz} = 20 \Omega$$

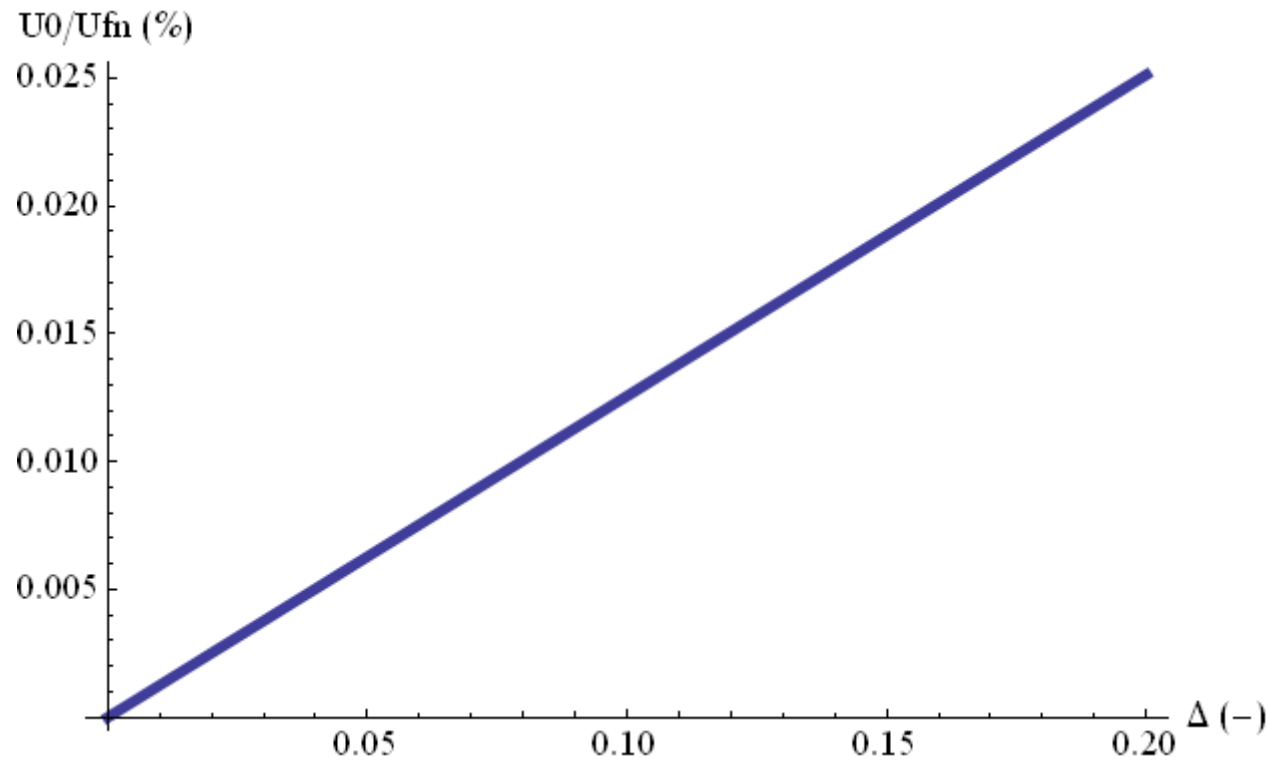

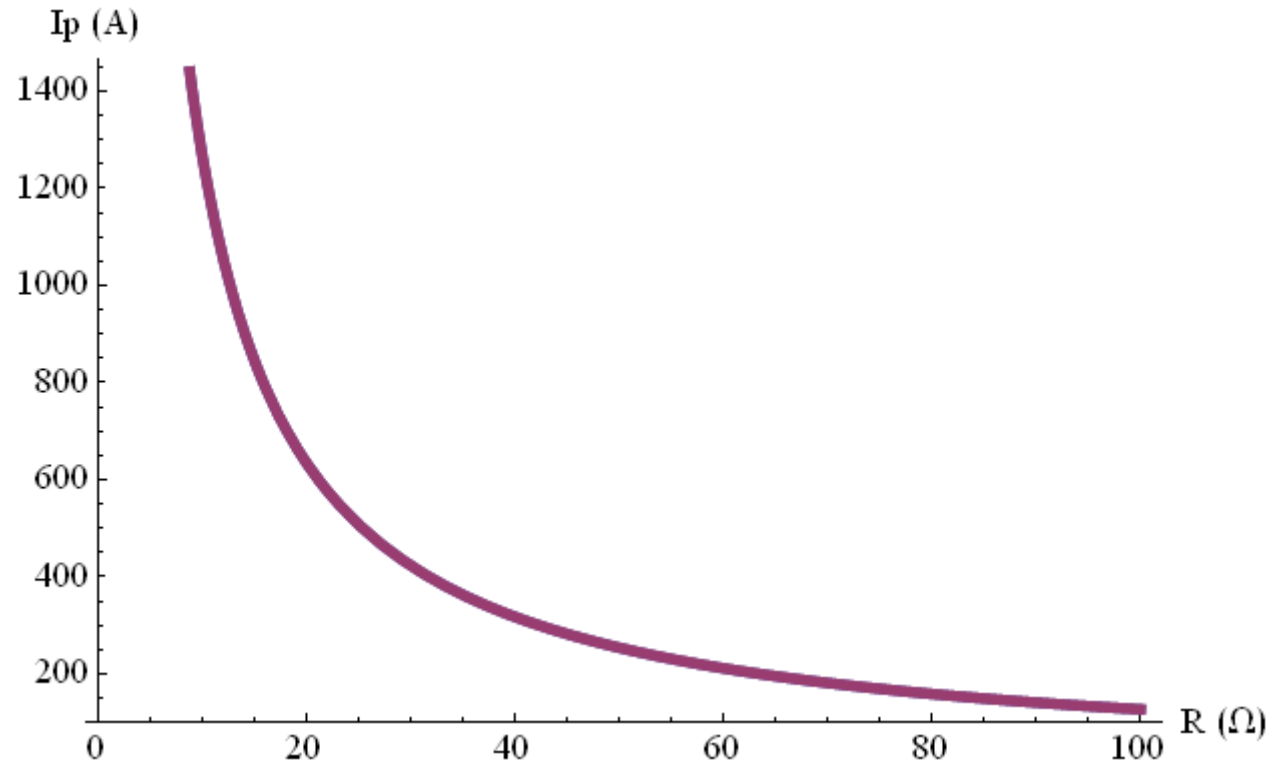
Fault current – talon, 50 km  
fault at the line beginning, i.e. without series parameters considering


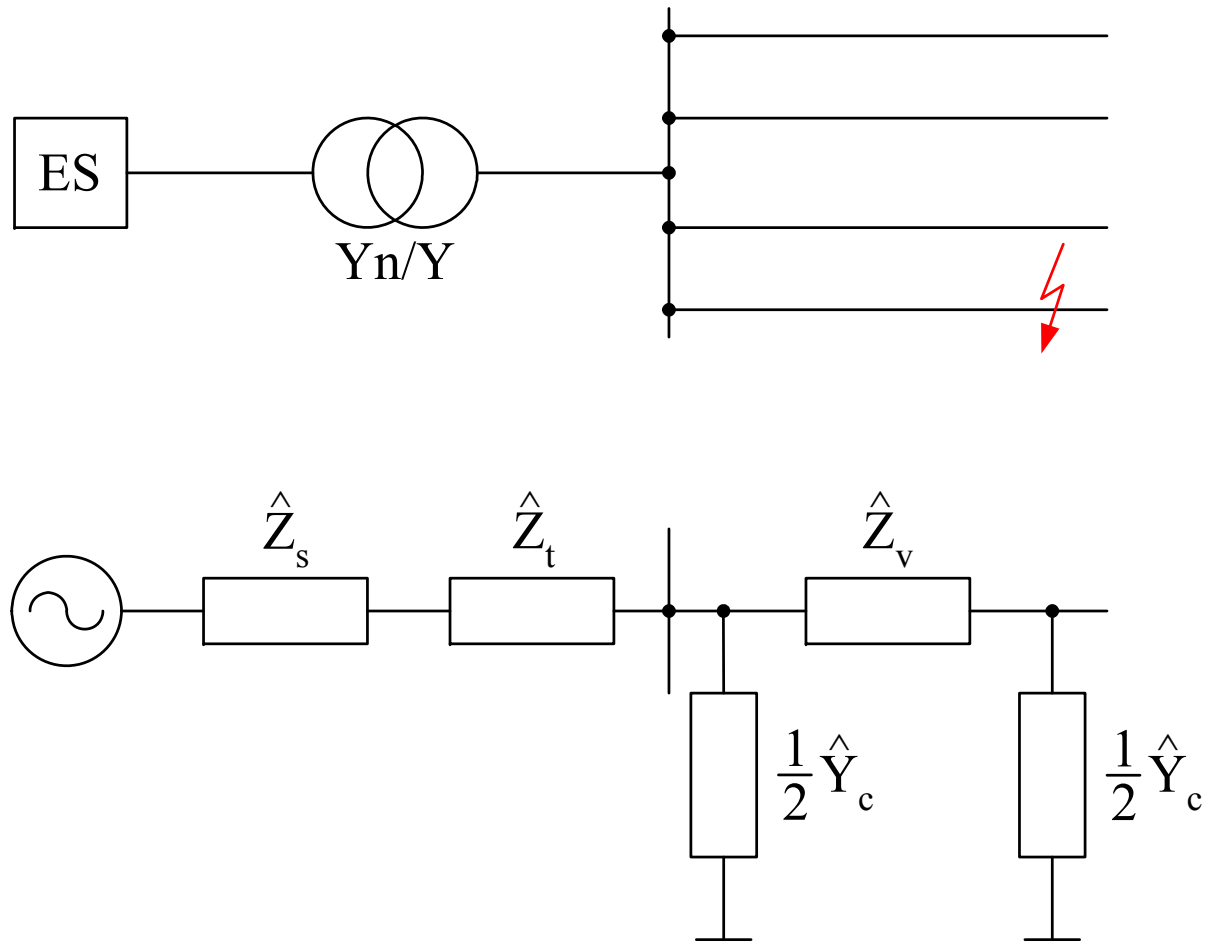
## Permanent ground fault – in symmetrical components




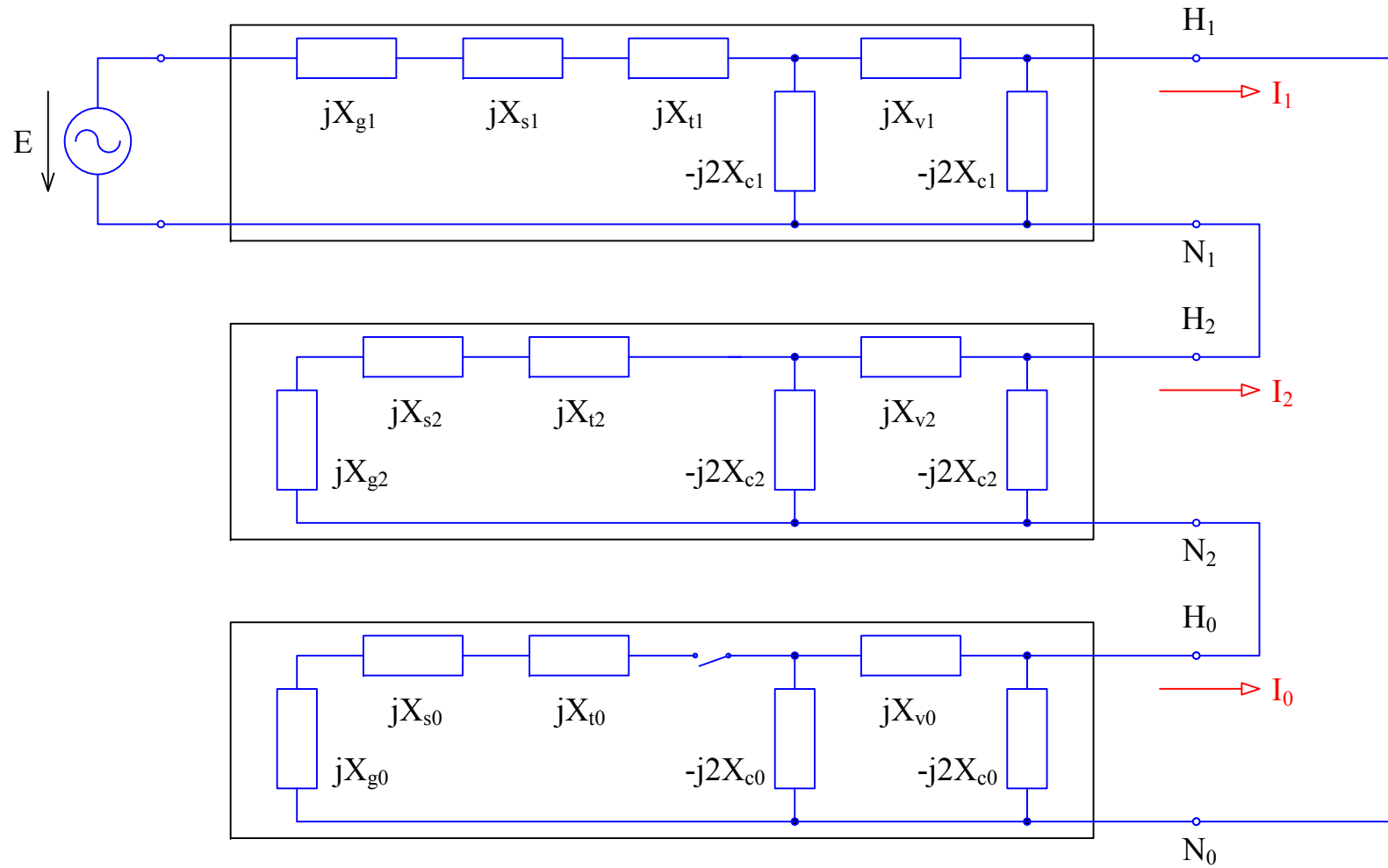Char. equations:  $U_a = 0, I_b = 0, I_c = 0$



$$\hat{Y}_c^{-1} = \hat{Z}_c = -jX_c \gg |\hat{Z}_v|, |\hat{Z}_t|, |\hat{Z}_s|$$
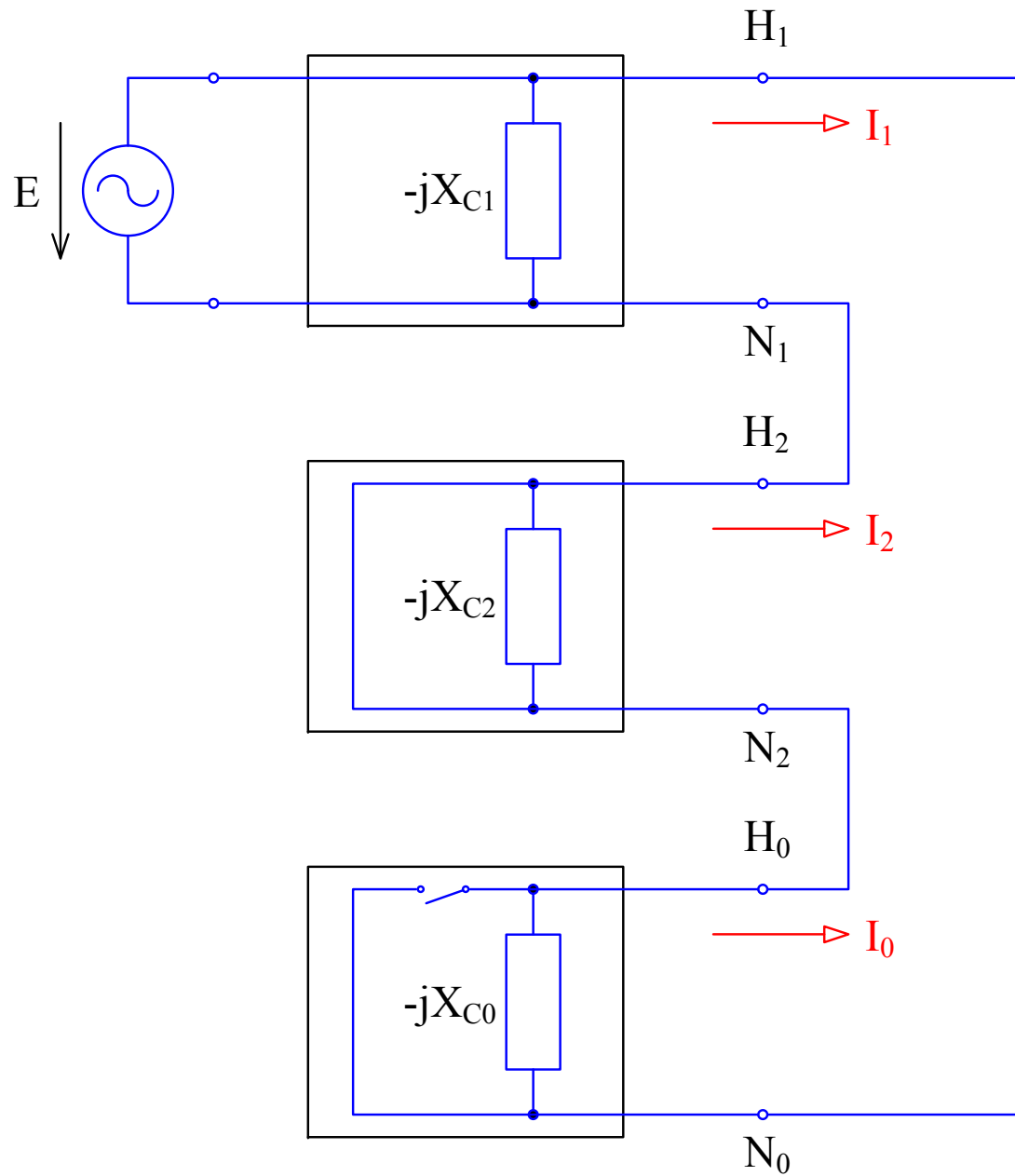
$$\begin{aligned} X_{c1} &= 0 \\ X_{c2} &= 0 \\ X_{c0} &= X_C \end{aligned}$$





$$(\mathbf{I}_{120}) = (\mathbf{T}^{-1})(\mathbf{I}_{ABC}) = \frac{1}{3} \begin{pmatrix} 1 & \hat{a} & \hat{a}^2 \\ 1 & \hat{a}^2 & \hat{a} \\ 1 & 1 & 1 \end{pmatrix} \begin{pmatrix} \hat{I}_A \\ 0 \\ 0 \end{pmatrix} = \frac{1}{3} \begin{pmatrix} \hat{I}_A \\ \hat{I}_A \\ \hat{I}_A \end{pmatrix}$$

$$\hat{I}_1 = \hat{I}_2 = \hat{I}_0 = \frac{1}{3} \hat{I}_A = \frac{\hat{E}}{-jX_C}$$

$$\hat{U}_1 = \hat{E} \qquad \hat{U}_2 = 0 \qquad \hat{U}_0 = -\hat{E}$$

- phase currents

$$\hat{I}_A = 3\hat{I}_1 \qquad \hat{I}_B = 0 \qquad \hat{I}_C = 0$$

$$\hat{I}_p = -\hat{I}_A = -3j \frac{\hat{E}}{X_C}$$

$$\underline{\hat{I}_p = -3j\omega k_0 \hat{E}}$$

- phase voltages

$$\hat{U}_A = 0$$


$$\hat{U}_B = \hat{a}^2 \hat{U}_1 + \hat{a} \hat{U}_2 + \hat{U}_0 = \hat{a}^2 \hat{E} - \hat{E} = (\hat{a}^2 - 1) \hat{E}$$


$$\hat{U}_C = \hat{a} \hat{U}_1 + \hat{a}^2 \hat{U}_2 + \hat{U}_0 = \hat{a} \hat{E} - \hat{E} = (\hat{a} - 1) \hat{E}$$


- neutral point voltage

$$\hat{U}_N = \frac{1}{3} (\hat{U}_A + \hat{U}_B + \hat{U}_C) = \frac{1}{3} (\hat{a}^2 - 1 + \hat{a} - 1) \hat{E}$$

$$\underline{\hat{U}_N = -\hat{E}}$$

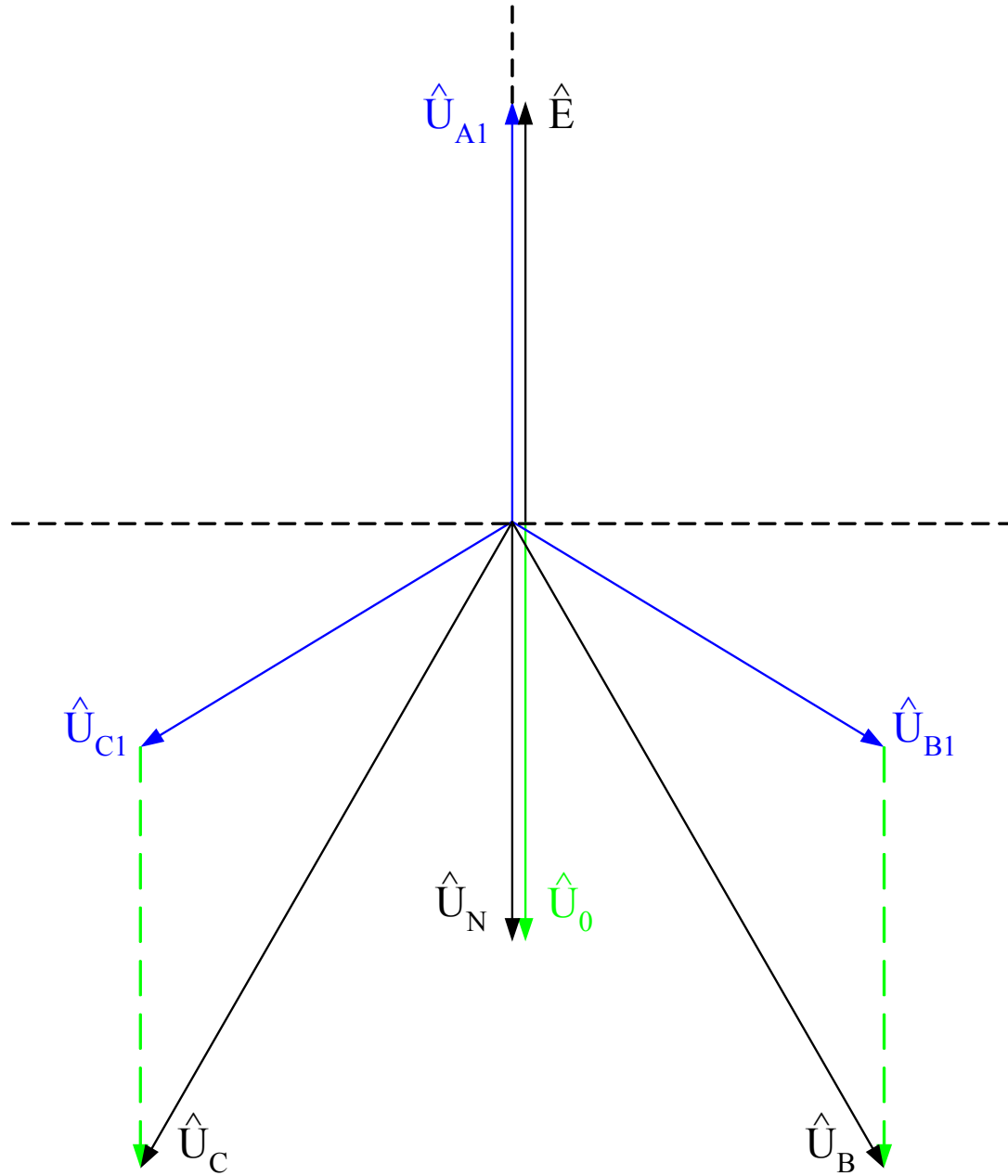

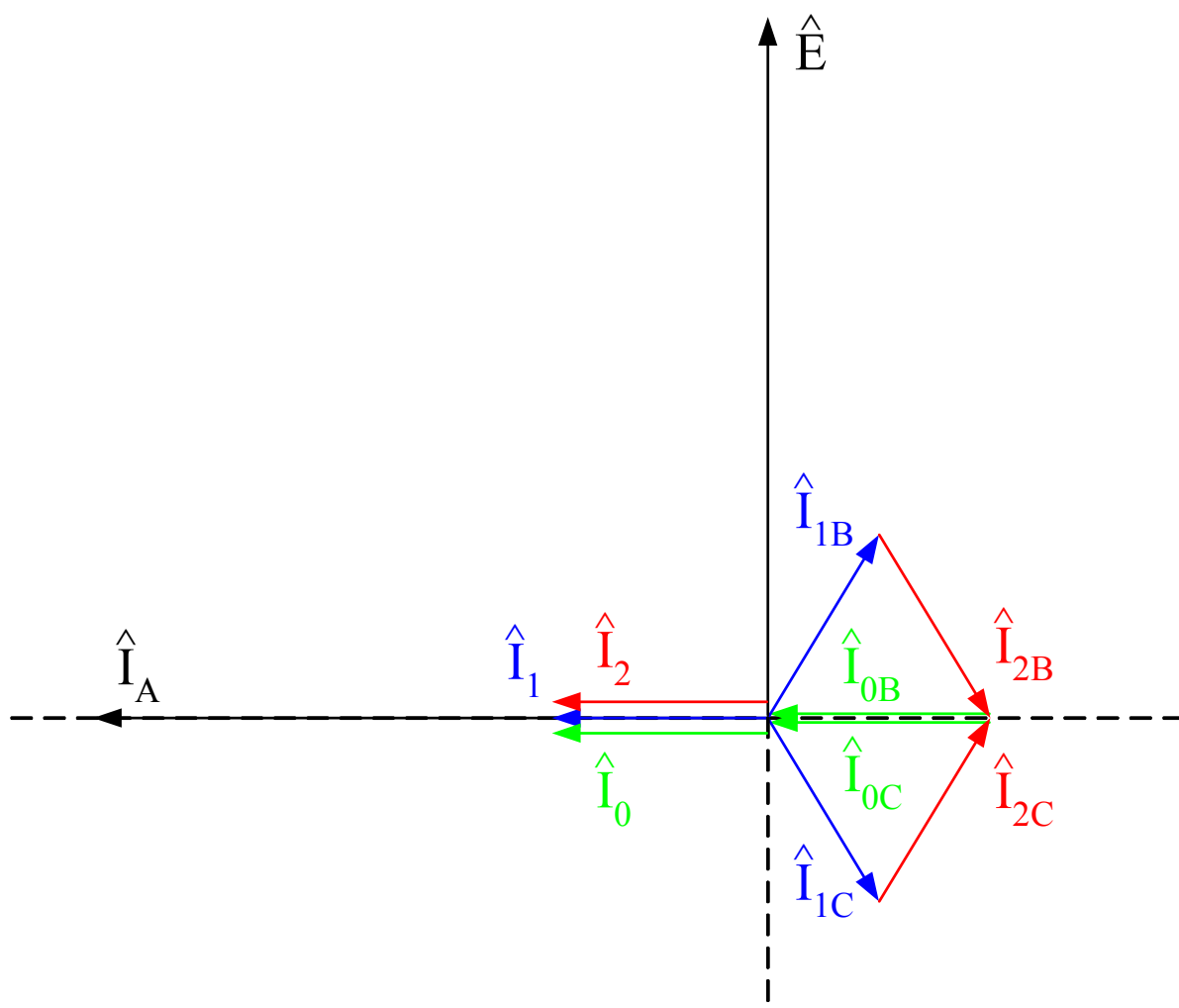

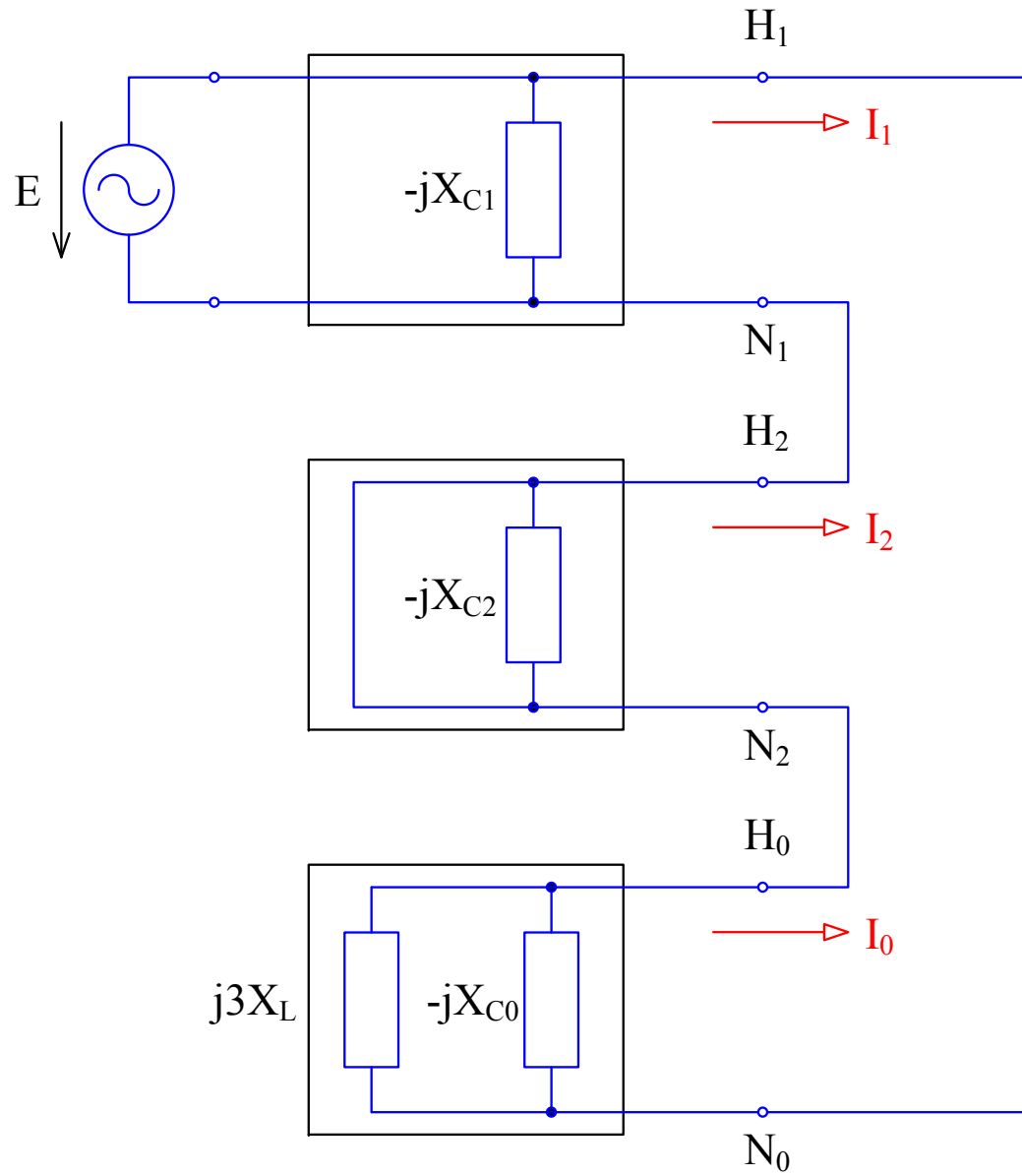

$$X_0 = (j3X_L) // (-jX_C) = j \frac{3X_L X_C}{X_C - 3X_L}$$

$$\hat{I}_1 = \frac{\hat{E}}{j \frac{3X_L X_C}{X_C - 3X_L}} = -j \frac{X_C - 3X_L}{3X_L X_C} \hat{E}$$

$$\hat{I}_p = -\hat{I}_A = -3\hat{I}_1 = j \frac{X_C - 3X_L}{3X_L X_C} \hat{E}$$

$$\hat{I}_p = 0$$

$$X_{c0} - 3X_L = 0$$

$$X_L = \frac{1}{3} X_{c0} = \frac{1}{3\omega k_0}$$

---