

Ground fault in three-phase systems

MV systems without the directly grounded neutral point (distribution systems) → single-phase fault of a different character than short-circuits (small capacitive current).

Fault current proportional to the system extent.

$I_p > 5 \text{ A}$ → arc formation → conductors, towers, insulators burning →
→ 2ph, 3ph short-circuits (mainly at cables)

Interrupted GF → overvoltage up to $4\div 5 U_{ph}$

GF compensation → uninterrupted system operation (to the failure clearance, short supply break), arc self-extinguishing

Ground fault


- resistive ($100 \times \Omega$), metal and arc ($x \Omega$)
- momentary (up to 0,5 s), short-term (up to 5 min), interrupted (repeating), durable (x hours)

Conditions in a system with insulated neutral point

Presumptions: considered only capacities, symmetrical source voltage, open-circuit system

Systems of a small extent, $I_p < 10 \text{ A}$.

Before the fault

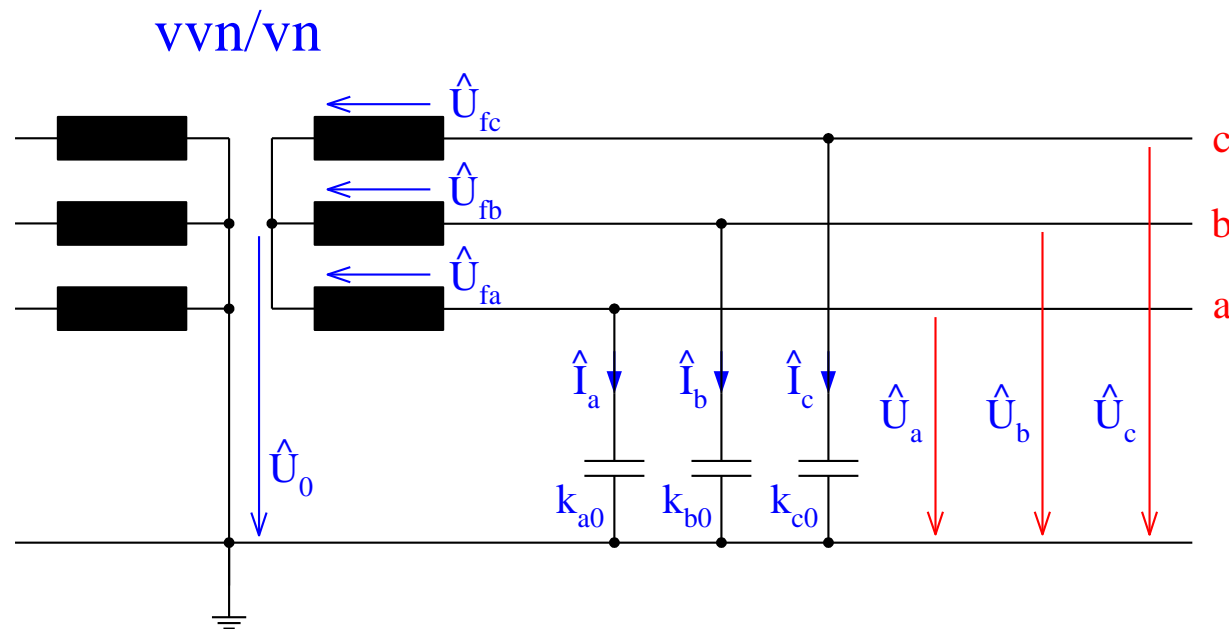

$$\hat{U}_a - \hat{U}_0 - \hat{U}_{fa} = 0$$

$$\hat{U}_b - \hat{U}_0 - \hat{U}_{fb} = 0$$

$$\hat{U}_c - \hat{U}_0 - \hat{U}_{fc} = 0$$

$$\hat{I}_a = j\omega k_{a0} \hat{U}_a$$

$$\hat{I}_b = j\omega k_{b0} \hat{U}_b$$

$$\hat{I}_c = j\omega k_{c0} \hat{U}_c$$

System with insulated neutral point

$$\hat{I}_a + \hat{I}_b + \hat{I}_c = 0$$

Symmetrical source

$$\hat{U}_{fb} = \hat{a}^2 \hat{U}_{fa}, \quad \hat{U}_{fc} = \hat{a} \hat{U}_{fa}$$

Neutral point voltage

$$\hat{U}_0 = -\frac{k_{a0} + \hat{a}^2 k_{b0} + \hat{a} k_{c0}}{k_{a0} + k_{b0} + k_{c0}} \hat{U}_{fa}$$

Unbalanced capacities


$$\hat{U}_0 \neq 0$$

Symmetrical capacities

$$k_{a0} = k_{b0} = k_{c0} = k_0 \Rightarrow \hat{U}_0 = 0$$

Perfect (metal) durable ground fault

Symmetrical system

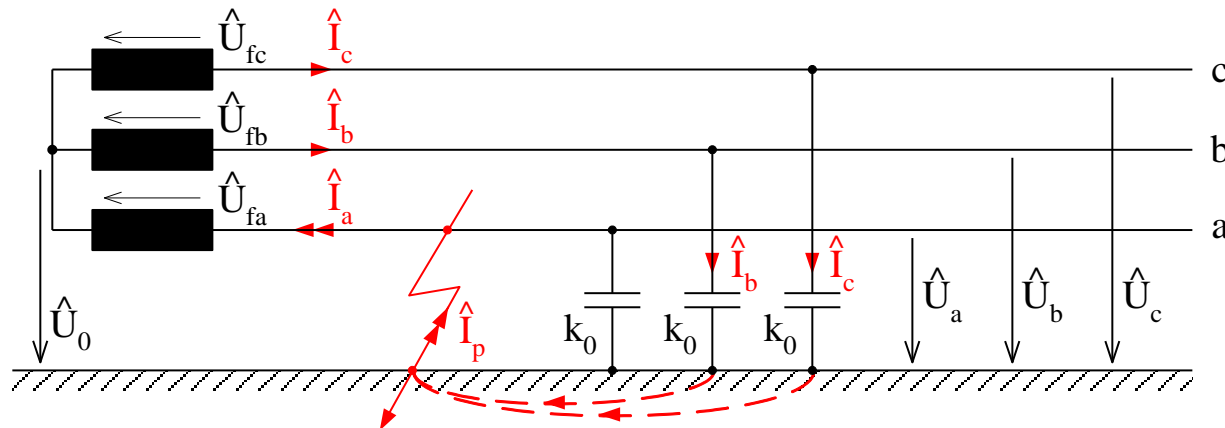

Fault current composed of 2 capacitive currents in the disaffected phases.

$$\hat{U}_a = 0$$

$$\hat{I}_p = \hat{I}_a = \hat{I}_b + \hat{I}_c$$

$$\hat{I}_b = j\omega k_0 \hat{U}_b \quad \hat{I}_c = j\omega k_0 \hat{U}_c$$

$$\hat{U}_a - \hat{U}_0 - \hat{U}_{fa} = 0 \Rightarrow \hat{U}_0 = -\hat{U}_{fa} !$$

$$\hat{U}_b - \hat{U}_0 - \hat{U}_{fb} = 0 \Rightarrow \hat{U}_b = \hat{U}_0 + \hat{U}_{fb} = (-1 + \hat{a}^2) \hat{U}_{fa} = -\sqrt{3}e^{j30^\circ} \hat{U}_{fa} !$$


$$\hat{U}_c - \hat{U}_0 - \hat{U}_{fc} = 0 \Rightarrow \hat{U}_c = \hat{U}_0 + \hat{U}_{fc} = (-1 + \hat{a}) \hat{U}_{fa} = -\sqrt{3}e^{-j30^\circ} \hat{U}_{fa} !$$

→ affected phase voltage - zero
 neutral point voltage - phase
 disaffected phases voltage - line-to-line

Fault ground current


$$\begin{aligned} \hat{I}_p &= \hat{I}_b + \hat{I}_c = j\omega k_0 (\hat{U}_b + \hat{U}_c) \\ &= j\omega k_0 [(-1 + \hat{a}^2) + (-1 + \hat{a})] \hat{U}_{fa} \\ &= j\omega k_0 (-2 + \hat{a}^2 + \hat{a} + 1 - 1) \hat{U}_{fa} \\ \hat{I}_p &= -3j\omega k_0 \hat{U}_{fa} = 3j\omega k_0 \hat{U}_0 \quad (\text{A}; \text{s}^{-1}, \text{F}, \text{V}) \end{aligned}$$

Voltage and current conditions

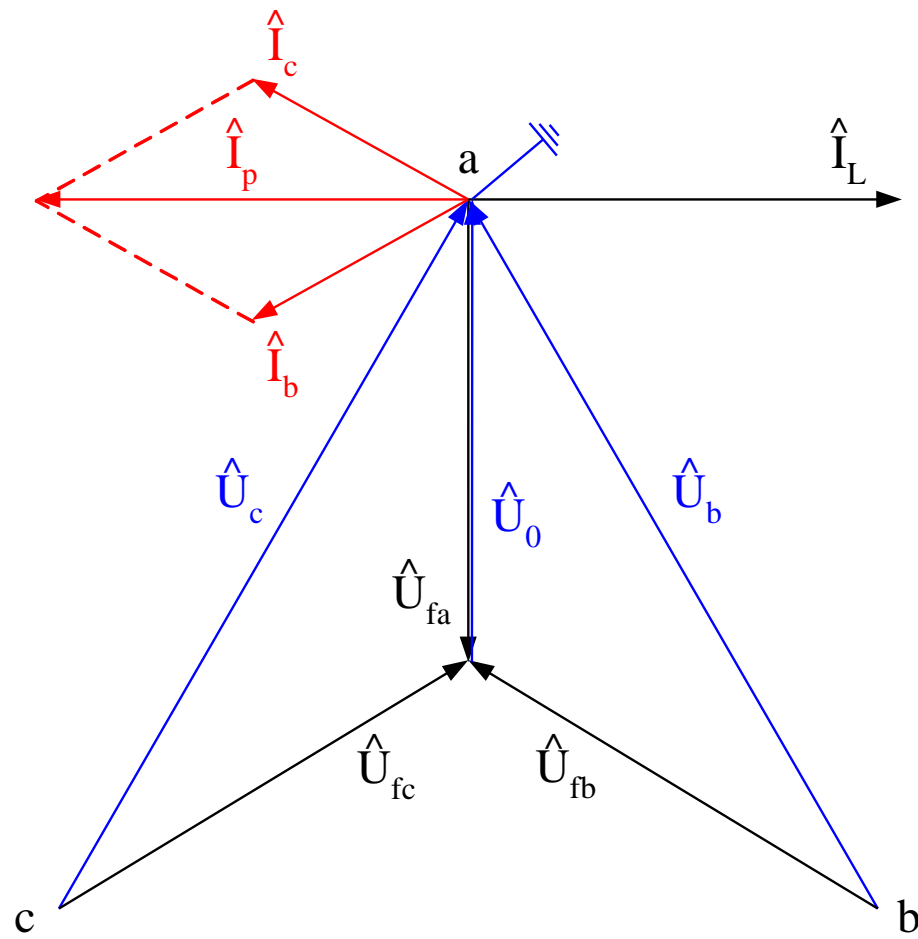

Fault current depends on the total system extent and almost doesn't depend on the failure point distance from the transformer.

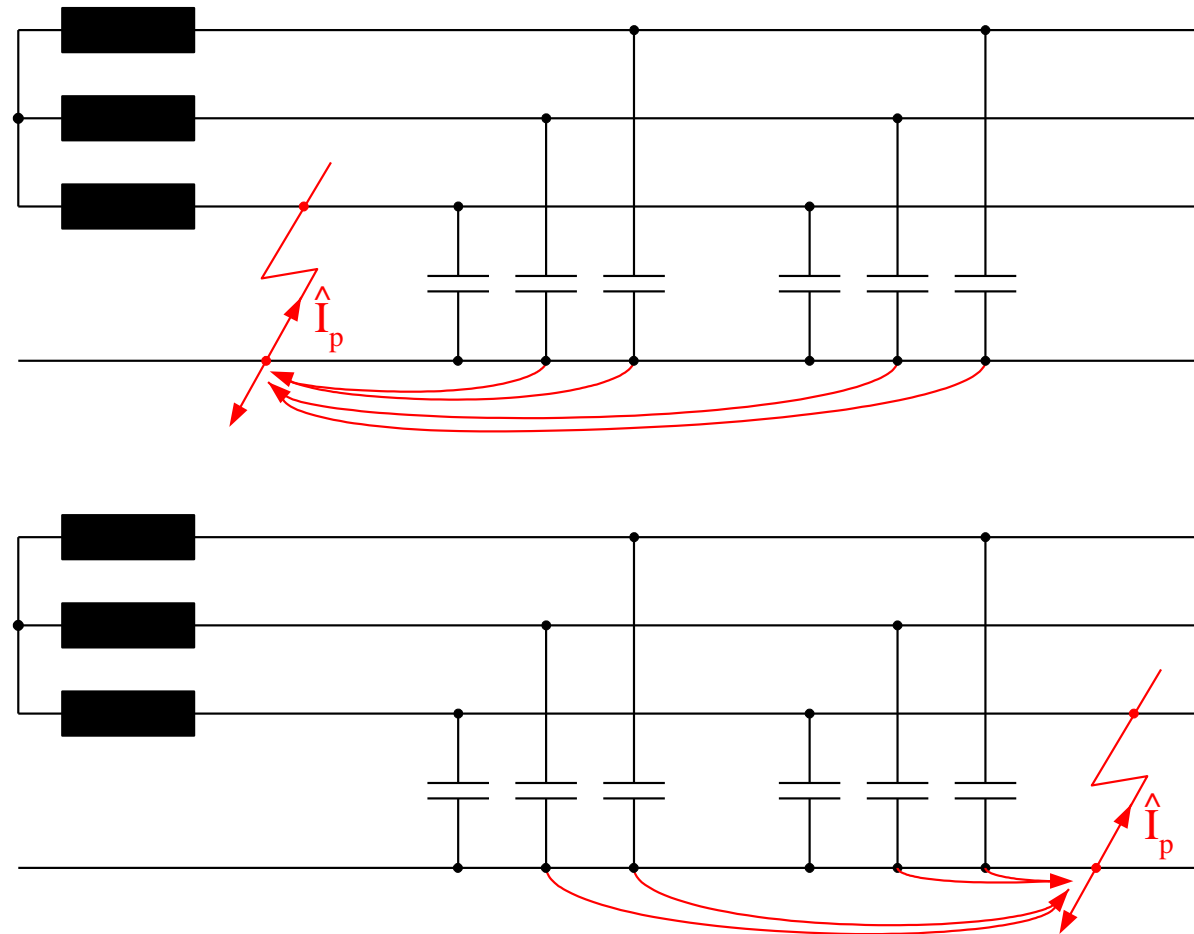
$$I_p = 3\omega k_{01} l U_f \quad (\text{A}; \text{s}^{-1}, \text{F/km}, \text{km}, \text{V})$$



Note: overhead 22kV – current ca. 0,06 A/km
 cables 22kV – current ca. 4 A/km

Note: MV system can be operated also with GF, on LV level again 3-phase supplying due to transformers Y/D/yn

Resistive ground fault

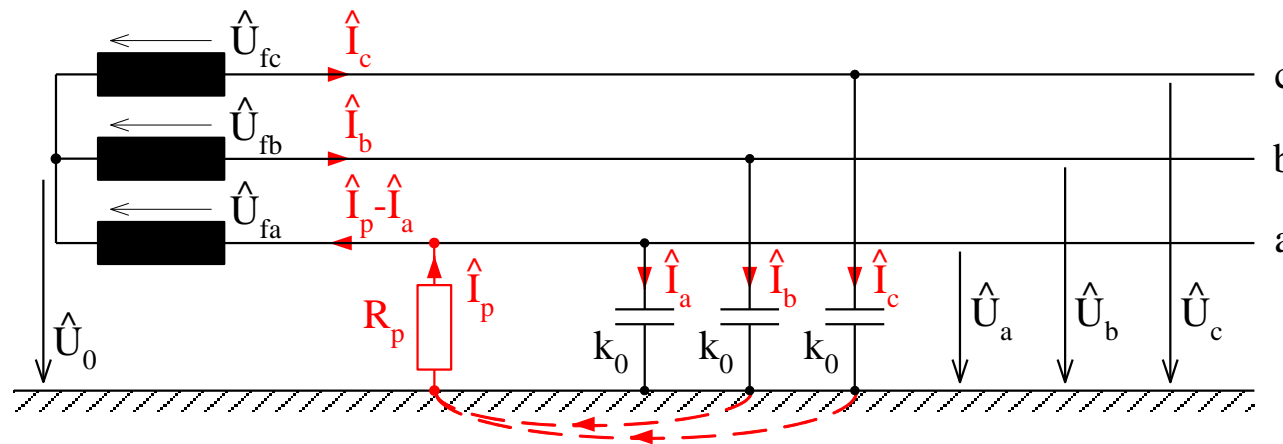

Affected phase voltage non-zero

$$\hat{I}_p = -\hat{U}_a / R_p = \hat{I}_a + \hat{I}_b + \hat{I}_c$$

Neutral point voltage

$$\hat{U}_0 = -\frac{j\omega(k_{a0} + \hat{a}^2 k_{b0} + \hat{a} k_{c0}) + R_p^{-1}}{j\omega(k_{a0} + k_{b0} + k_{c0}) + R_p^{-1}} \hat{U}_{fa}$$

Circle equation in the Gauss plane


$$\hat{U}_0 = -\frac{\hat{A} + R_p^{-1}}{\hat{B} + R_p^{-1}} \hat{U}_{fa}$$

$$R_p = 0$$

$$\hat{U}_0 = -\hat{U}_{fa}$$

$$R_p = \infty$$
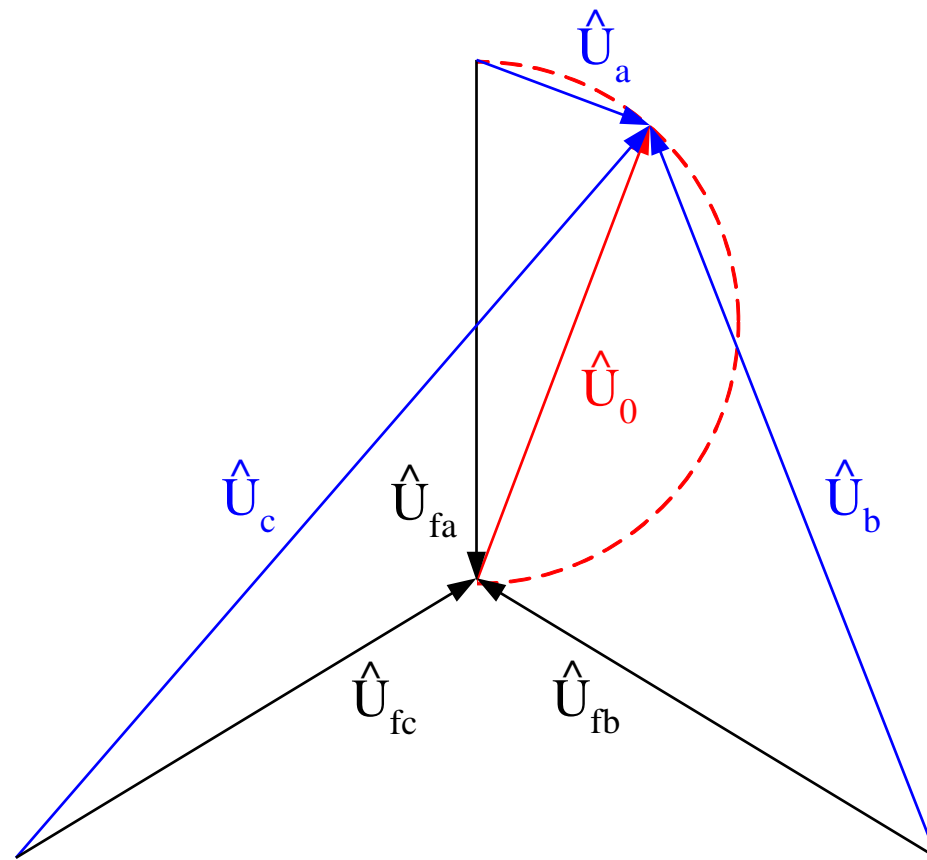
$$\hat{U}_0 = 0 \text{ (for symmetrical capacities)}$$




Disaffected voltage can be higher than line-to-line value.

Ground current compensation

Compensation in system where $I_p > 5A$ - suitable

$I_p > 10A$ - necessary

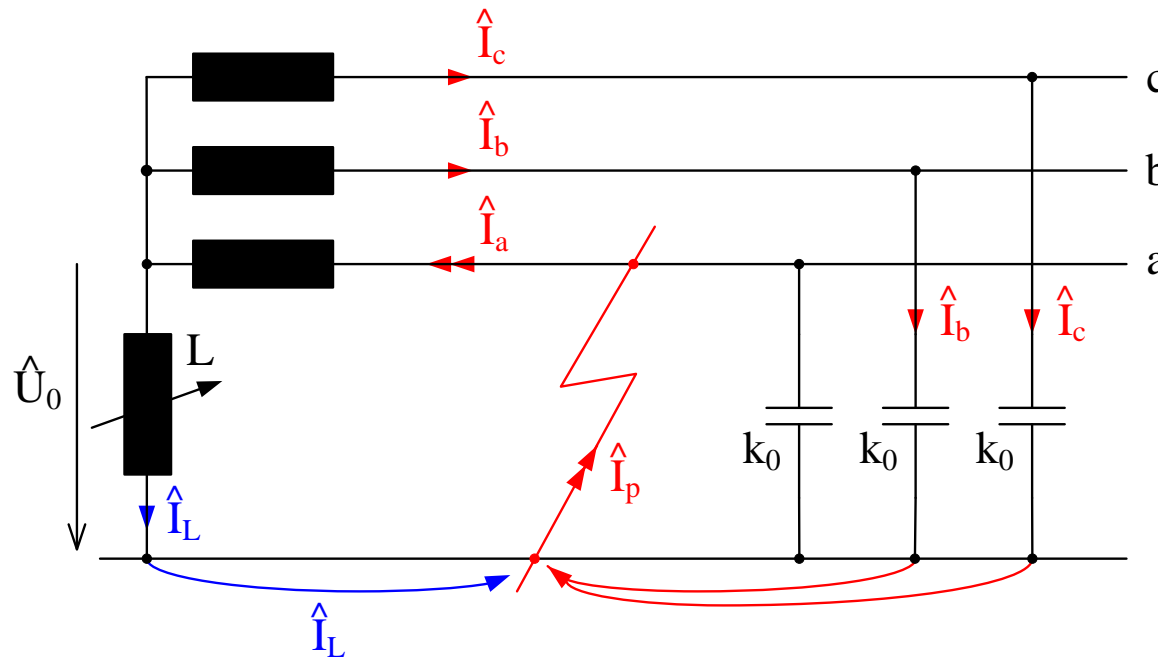Method: Continuously controlled arc-suppression coil between the transformer neutral point and the ground (at transformers with D winding by means of neutral coil with Y)



Faultless state

$$U_0 = 0 \quad - \text{symmetrical capacities}$$

$$U_0 < 0,01 U_f \quad - \text{usual unbalance}$$

Perfect ground fault

$$\hat{U}_0 = -\hat{U}_{fa}$$

Arc-suppression coil current

$$\hat{I}_L = -j \frac{\hat{U}_0}{\omega L}$$

Total compensation

$$\hat{I}_L = -\hat{I}_p$$

$$-j \frac{\hat{U}_0}{\omega L} = -3j\omega k_0 \hat{U}_0$$

Hence

$$\underline{L = \frac{1}{3\omega^2 k_0} \quad (\text{H; s}^{-1}, \text{F})}$$

Coil power (reactive inductive)


$$\hat{S} = \hat{U}_0 \hat{I}_L^* = 3j\omega k_0 \hat{U}_0 \hat{U}_0^* = j\omega k_0 U^2 = Q_L$$

Ideal compensation: $I_p = 0$ in the fault point

Real situation: residual current (small active)

- inaccurate inductance setting
- uncompensatable active component (power line conductance, coil R)
- higher harmonics

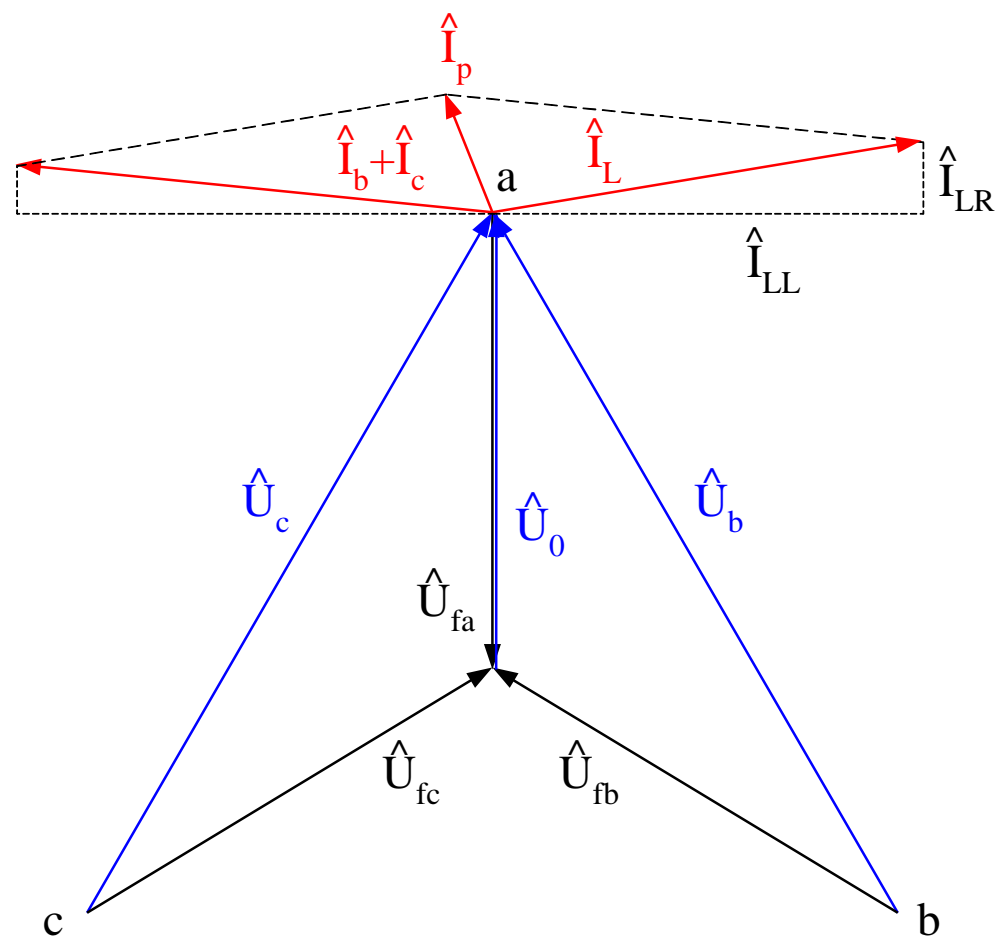
$$\hat{I}_p = \left[\frac{1}{R_L} + 3G_0 + j \left(3\omega k_0 - \frac{1}{\omega L} \right) \right] \hat{U}_0$$



Arc-suppression coil tuning

L dimensioning by calculation, setting in the faultless state (for given system configuration).

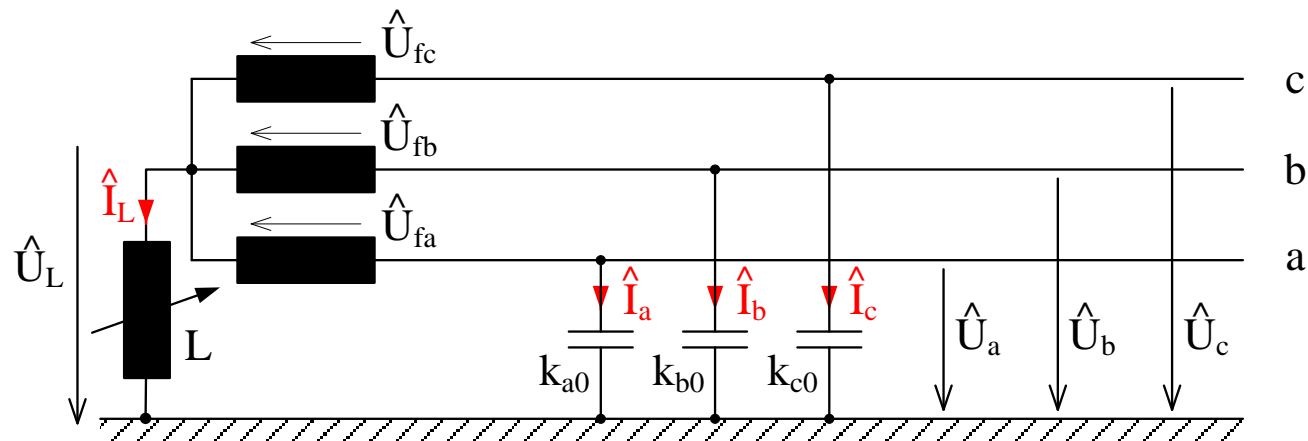Tuning is done by magnetic circuit change by means of motor (air gap).




Coil voltage

$$\hat{U}_L = \frac{-\omega^2 L (k_{a0} + \hat{a}^2 k_{b0} + \hat{a} k_{c0})}{\omega^2 L (k_{a0} + k_{b0} + k_{c0}) - 1} \hat{U}_{fa}$$

Resonance dependence

$$\left| \frac{U_L}{U_{fa}} \right| = f(L)$$
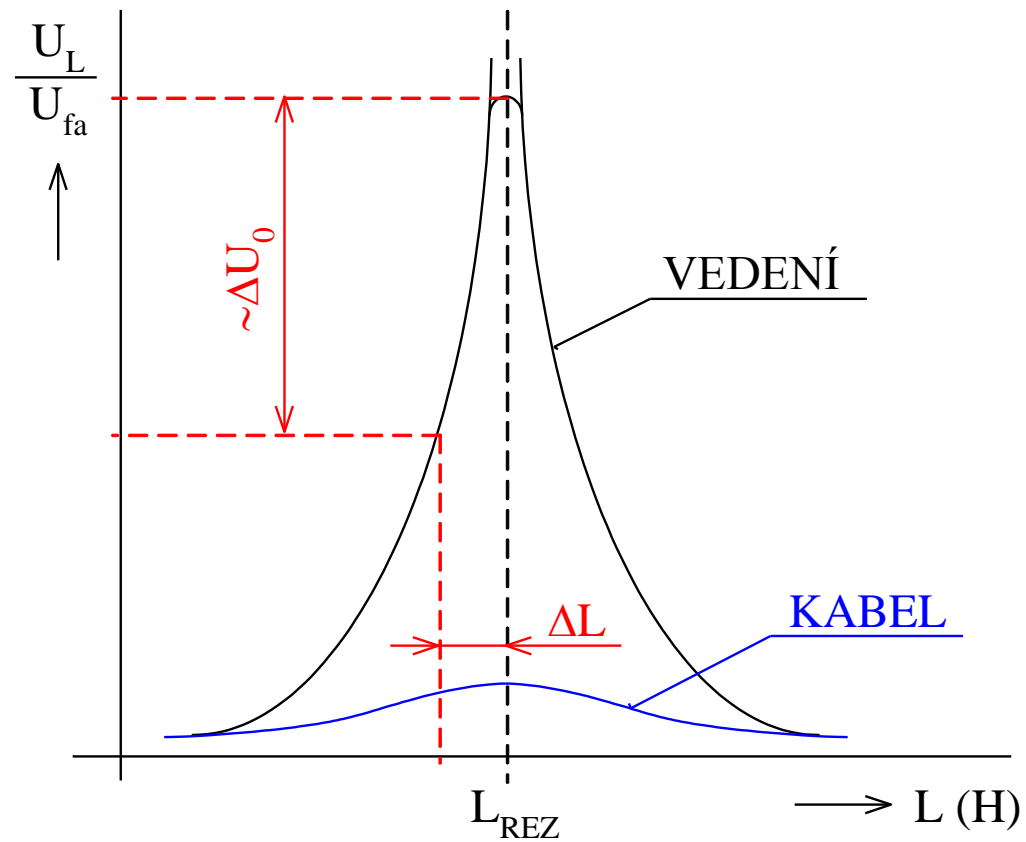
$$L_{\text{REZ}} = \frac{1}{\omega^2 (k_{a0} + k_{b0} + k_{c0})}$$




Overhead power lines


- higher capacitive unbalance
- maximum limited by resistances
- L_{REZ} compensates GF totally \rightarrow resonance coil
- setting by U_L measuring
- with small R the transformer neutral point strained too much in resonance \rightarrow intended (small) detuning \rightarrow dissonance coil

Cable power lines

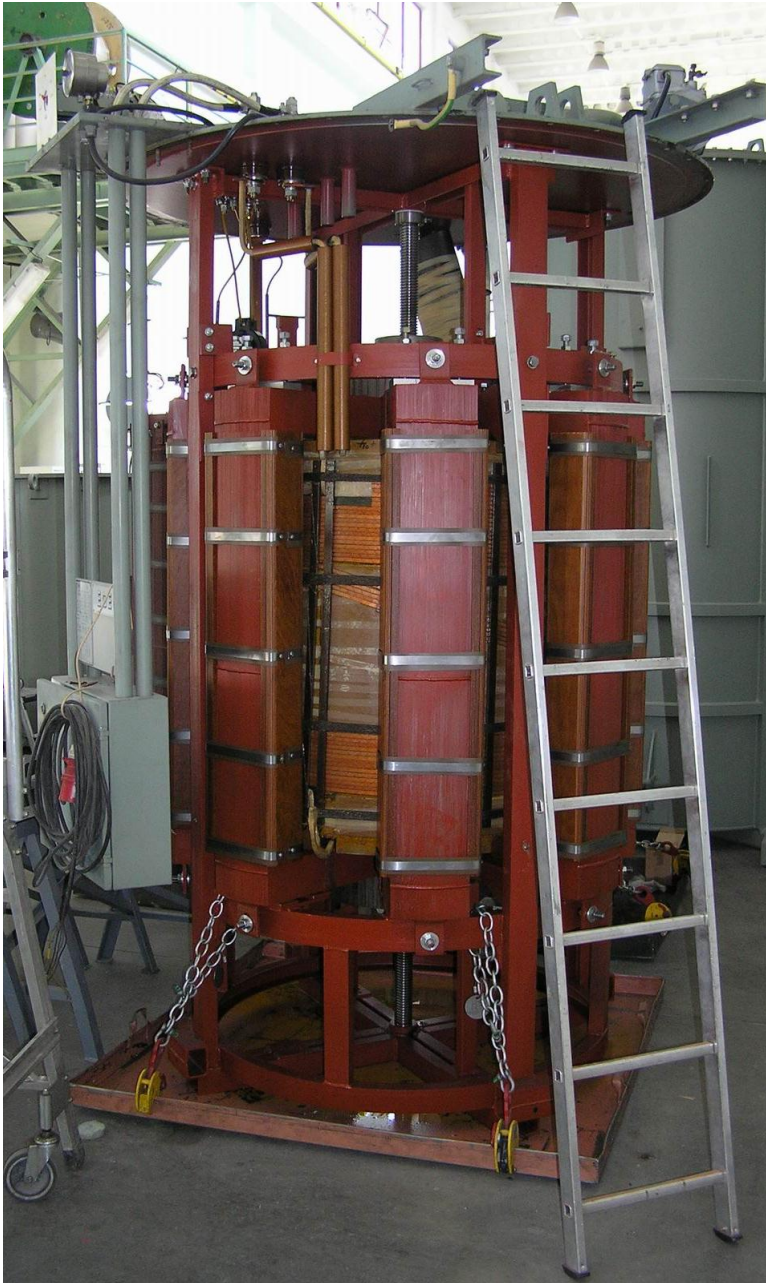- small capacitive unbalance \rightarrow flat curve \rightarrow difficult tuning



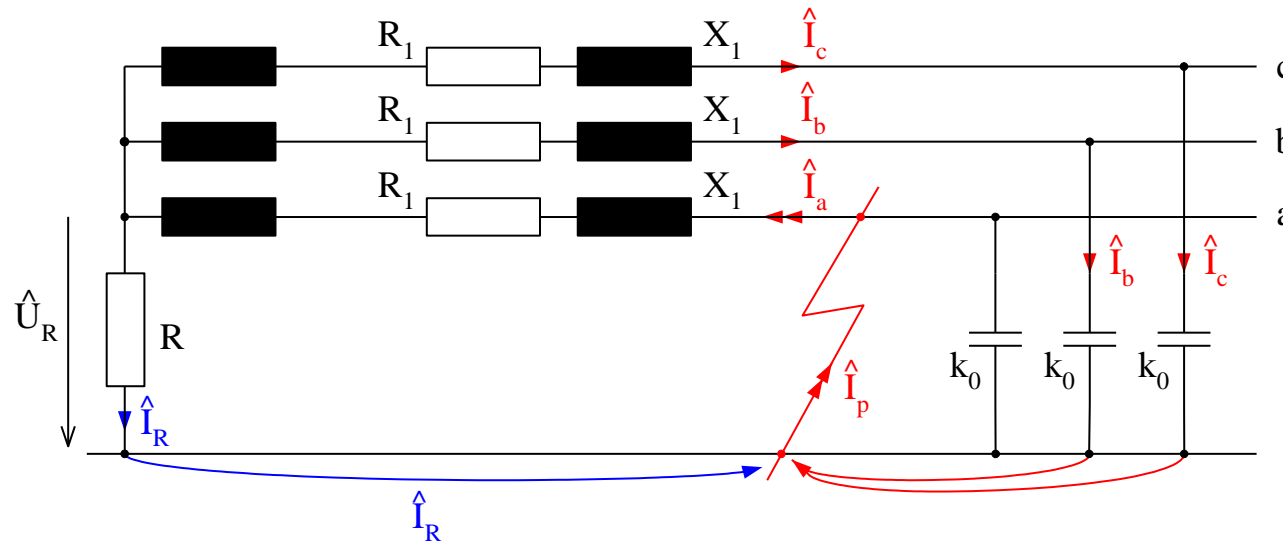
Cable systems grounded with the resistance





During the fault

- neutral point voltage almost phase value
- I_p uncompensated
- I_p depend on the system extent x decreases with the distance from transformer (short-circuit character)
- R value can influence I_p size and character


$$\hat{I}_p = -(1/R + j3\omega k_0)U_f$$

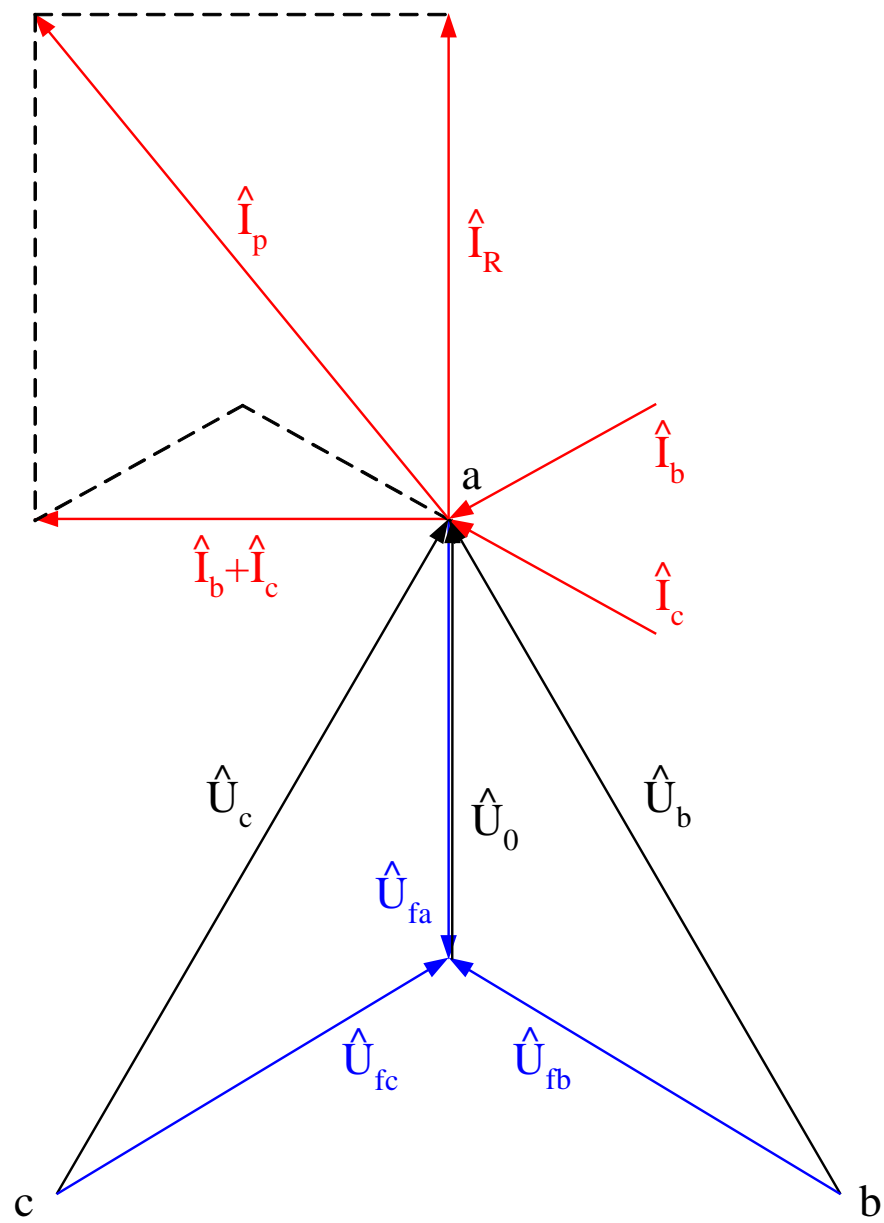

Permanent ground connection – components

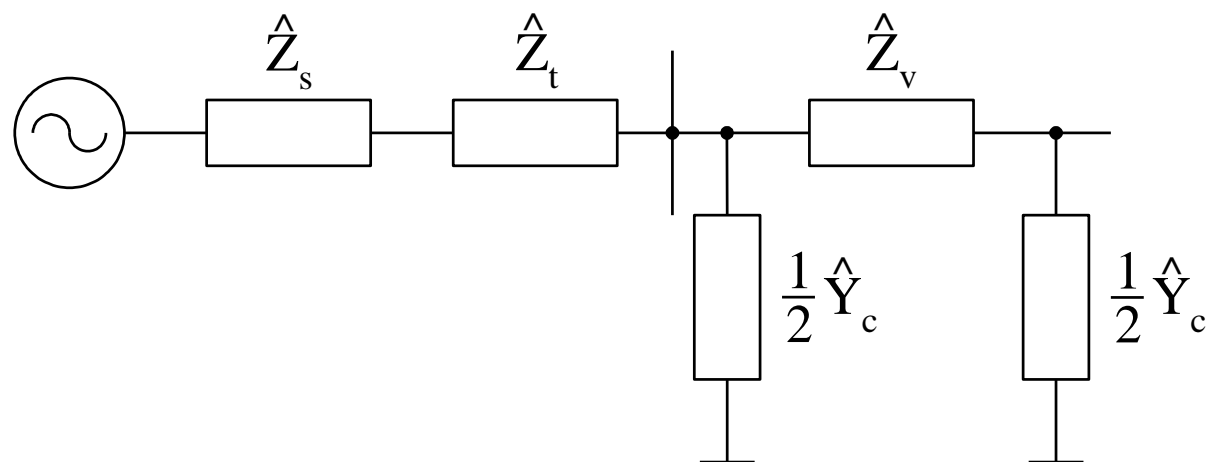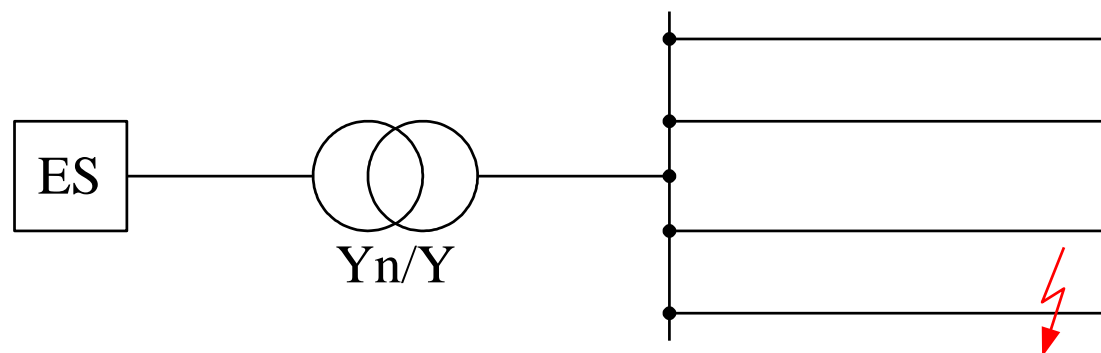

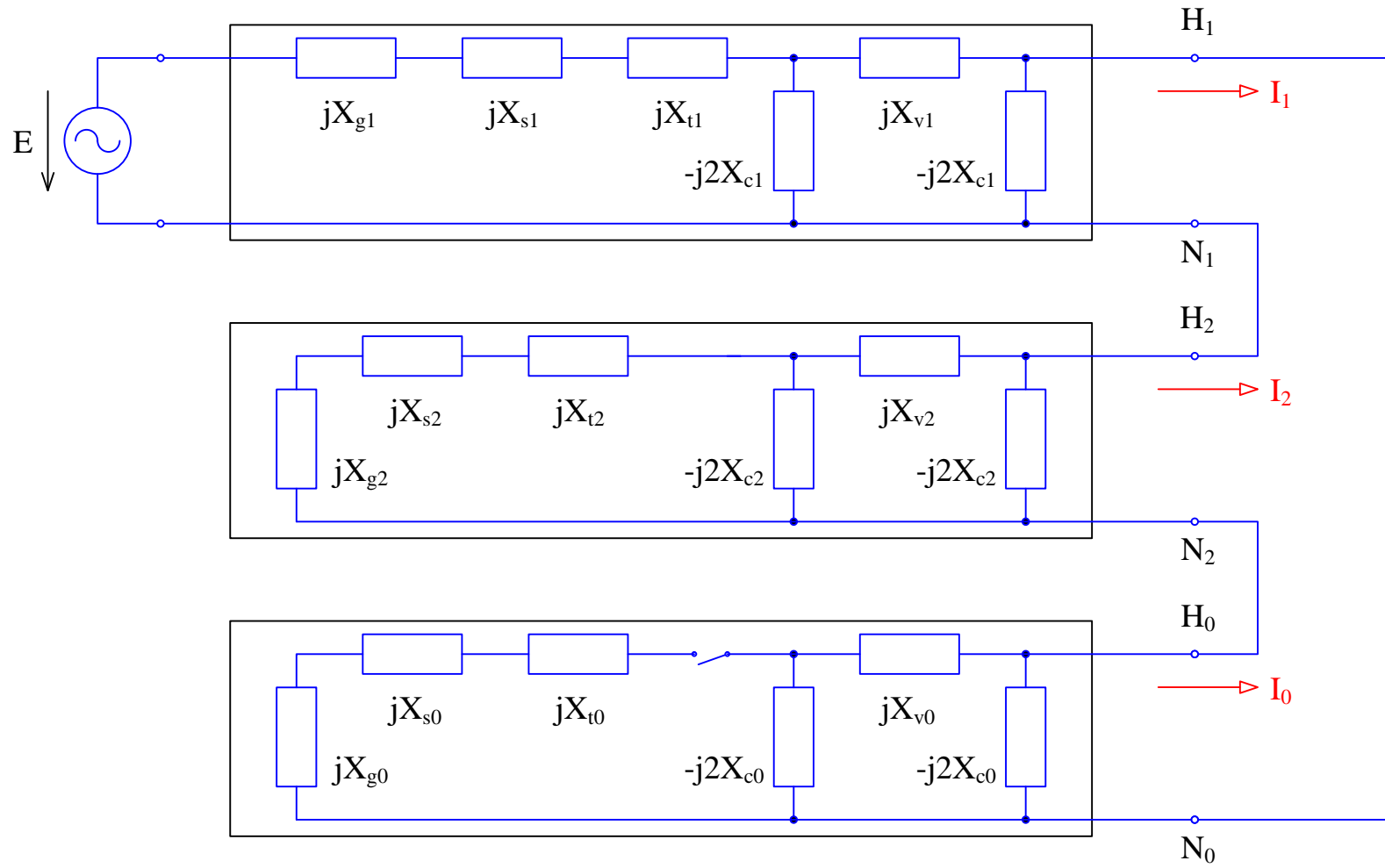Char. equations: $U_a = 0, I_b = 0, I_c = 0$




$$\hat{Y}_c^{-1} = \hat{Z}_c = -jX_c \gg |\hat{Z}_v|, |\hat{Z}_t|, |\hat{Z}_s|$$

$$X_{c1} = 0$$

$$X_{c2} = 0$$

$$X_{c0} = X_C$$

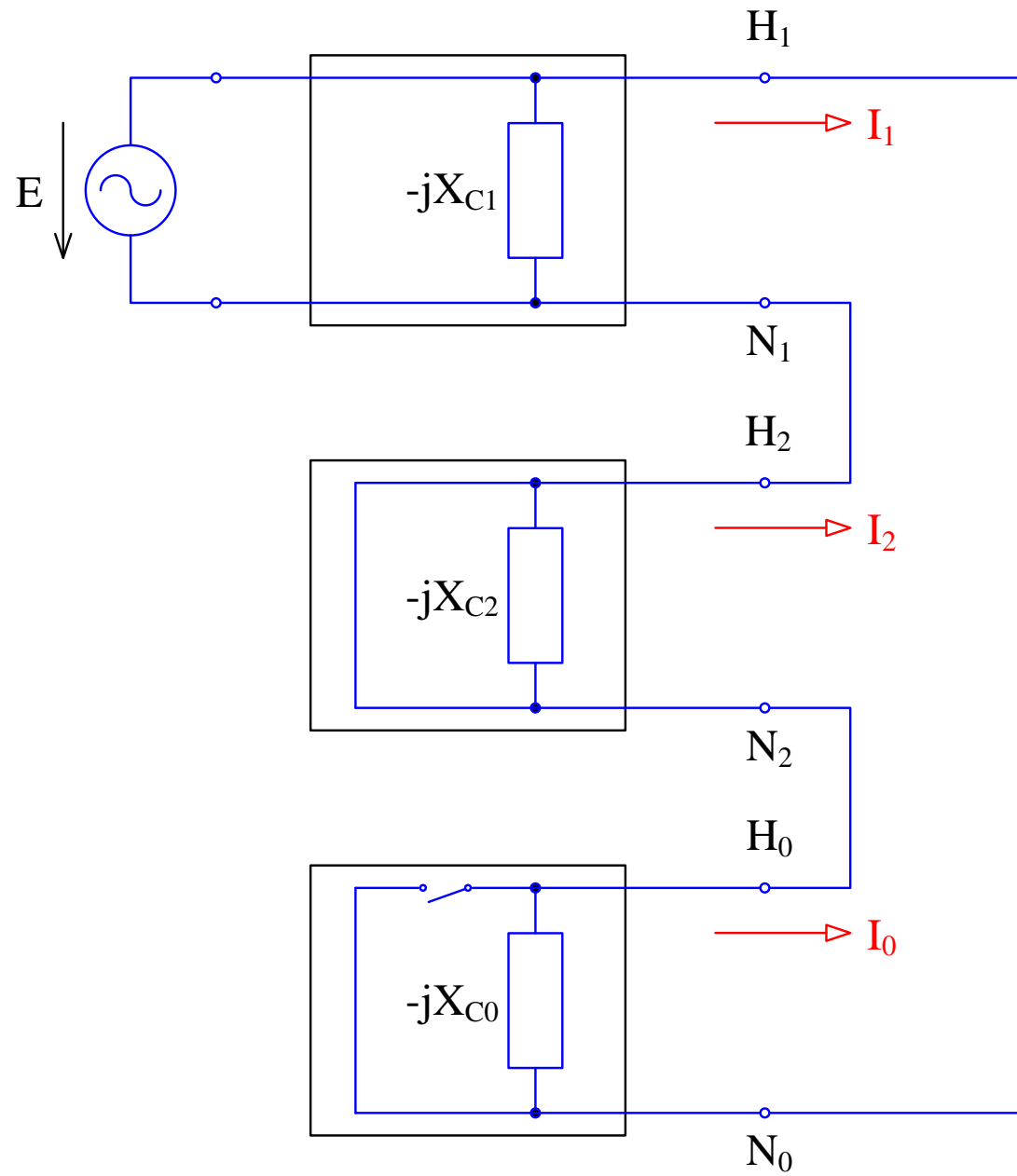

$$(\mathbf{I}_{120}) = (\mathbf{T}^{-1})(\mathbf{I}_{ABC}) = \frac{1}{3} \begin{pmatrix} 1 & \hat{a} & \hat{a}^2 \\ 1 & \hat{a}^2 & \hat{a} \\ 1 & 1 & 1 \end{pmatrix} \begin{pmatrix} \hat{\mathbf{I}}_A \\ 0 \\ 0 \end{pmatrix} = \frac{1}{3} \begin{pmatrix} \hat{\mathbf{I}}_A \\ \hat{\mathbf{I}}_A \\ \hat{\mathbf{I}}_A \end{pmatrix}$$

$$\hat{\mathbf{I}}_1 = \hat{\mathbf{I}}_2 = \hat{\mathbf{I}}_0 = \frac{1}{3} \hat{\mathbf{I}}_A = \frac{\hat{\mathbf{E}}}{-\mathbf{jX}_C}$$

$$\hat{\mathbf{U}}_1 = \hat{\mathbf{E}} \qquad \hat{\mathbf{U}}_2 = 0 \qquad \hat{\mathbf{U}}_0 = -\hat{\mathbf{E}}$$

- phase currents

$$\hat{\mathbf{I}}_A = 3\hat{\mathbf{I}}_1 \qquad \hat{\mathbf{I}}_B = 0 \qquad \hat{\mathbf{I}}_C = 0$$

$$\hat{\mathbf{I}}_p = -\hat{\mathbf{I}}_A = -3\mathbf{j} \frac{\hat{\mathbf{E}}}{\mathbf{X}_C}$$

$$\underline{\hat{I}_p = -3j\omega k_0 \hat{E}}$$

- phase voltage

$$\hat{U}_A = 0$$


$$\hat{U}_B = \hat{a}^2 \hat{U}_1 + \hat{a} \hat{U}_2 + \hat{U}_0 = \hat{a}^2 \hat{E} - \hat{E} = (\hat{a}^2 - 1) \hat{E}$$


$$\hat{U}_C = \hat{a} \hat{U}_1 + \hat{a}^2 \hat{U}_2 + \hat{U}_0 = \hat{a} \hat{E} - \hat{E} = (\hat{a} - 1) \hat{E}$$


- neutral point voltage

$$\hat{U}_N = \frac{1}{3} (\hat{U}_A + \hat{U}_B + \hat{U}_C) = \frac{1}{3} (\hat{a}^2 - 1 + \hat{a} - 1) \hat{E}$$

$$\underline{\hat{U}_N = -\hat{E}}$$

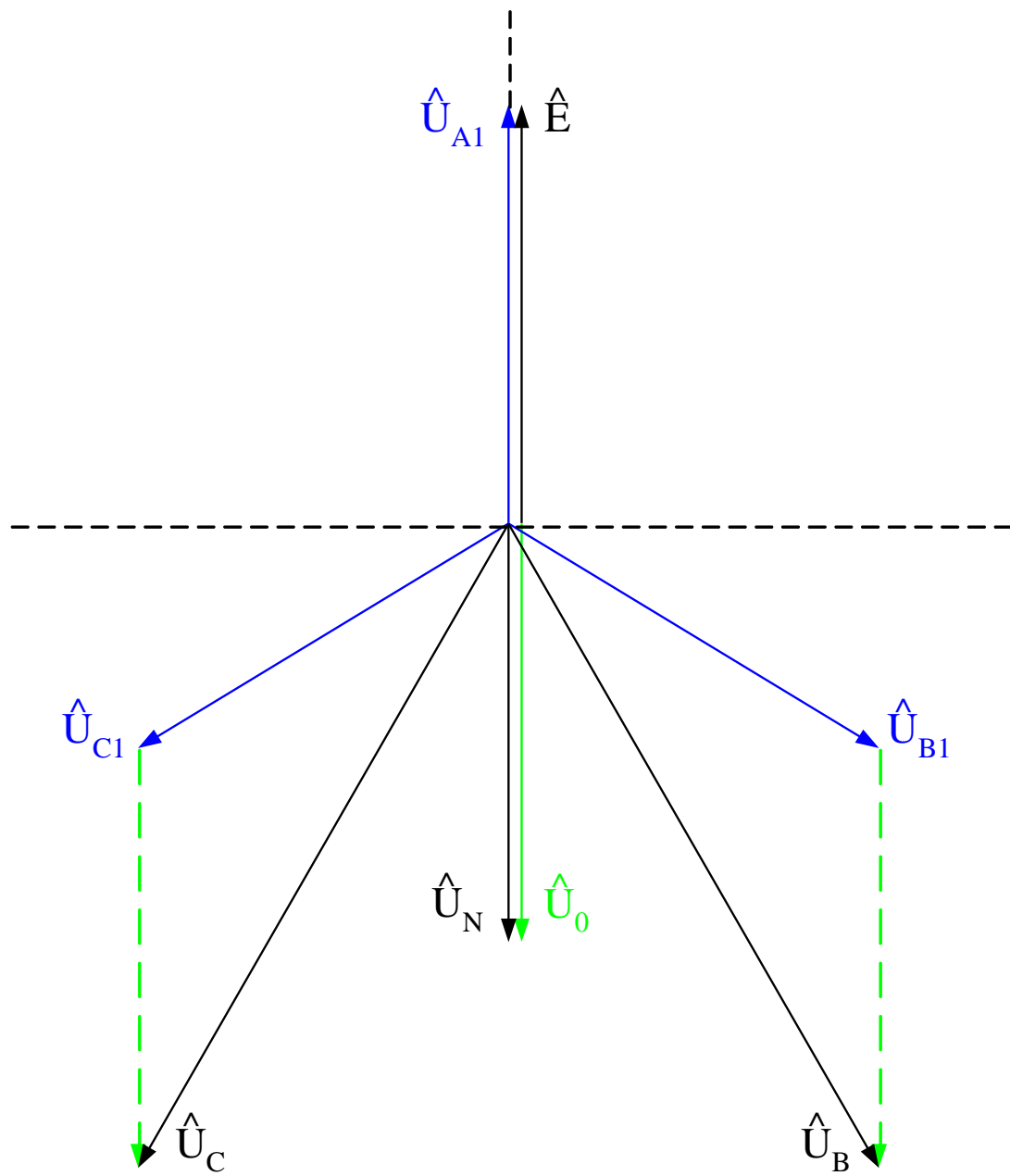

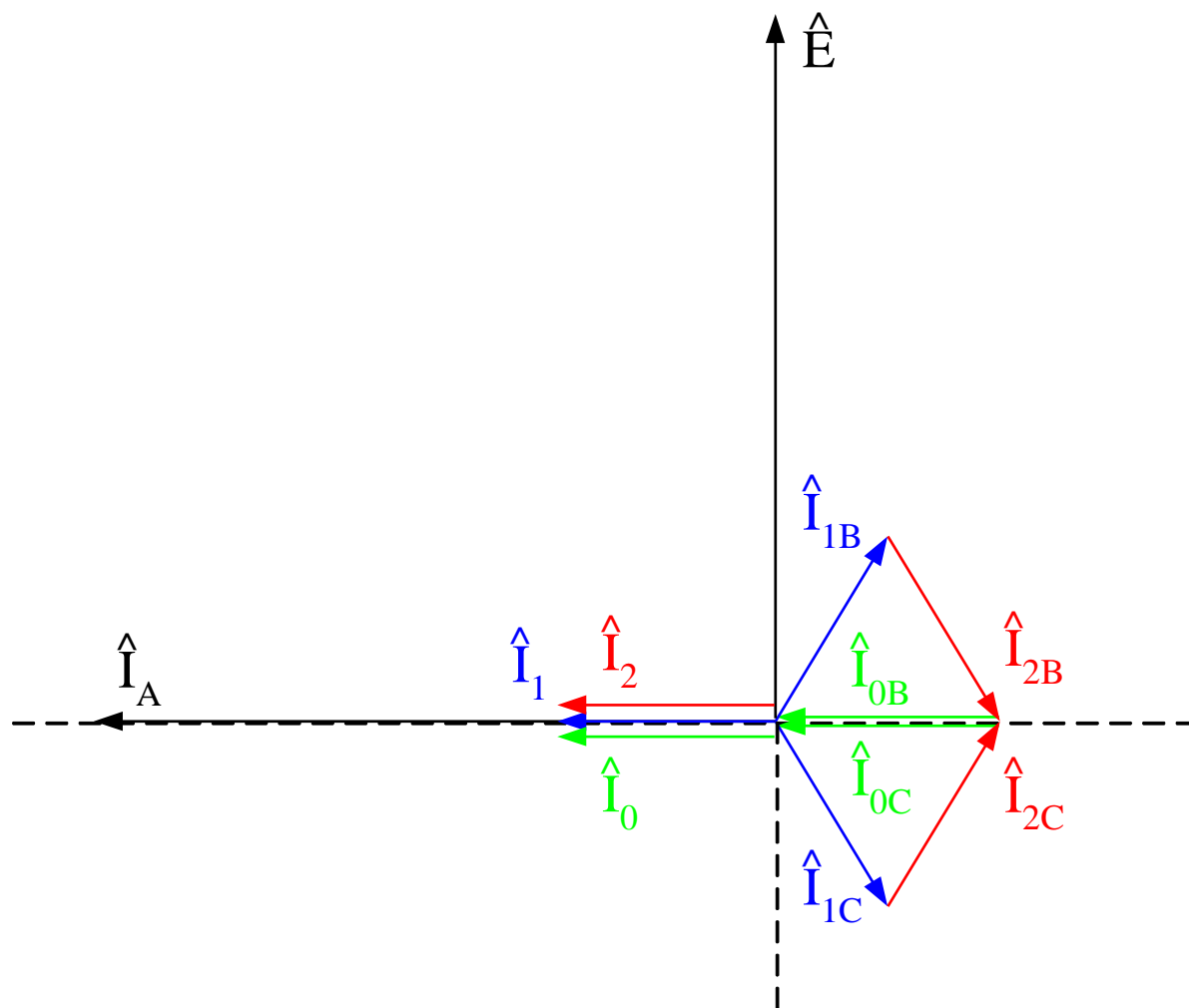

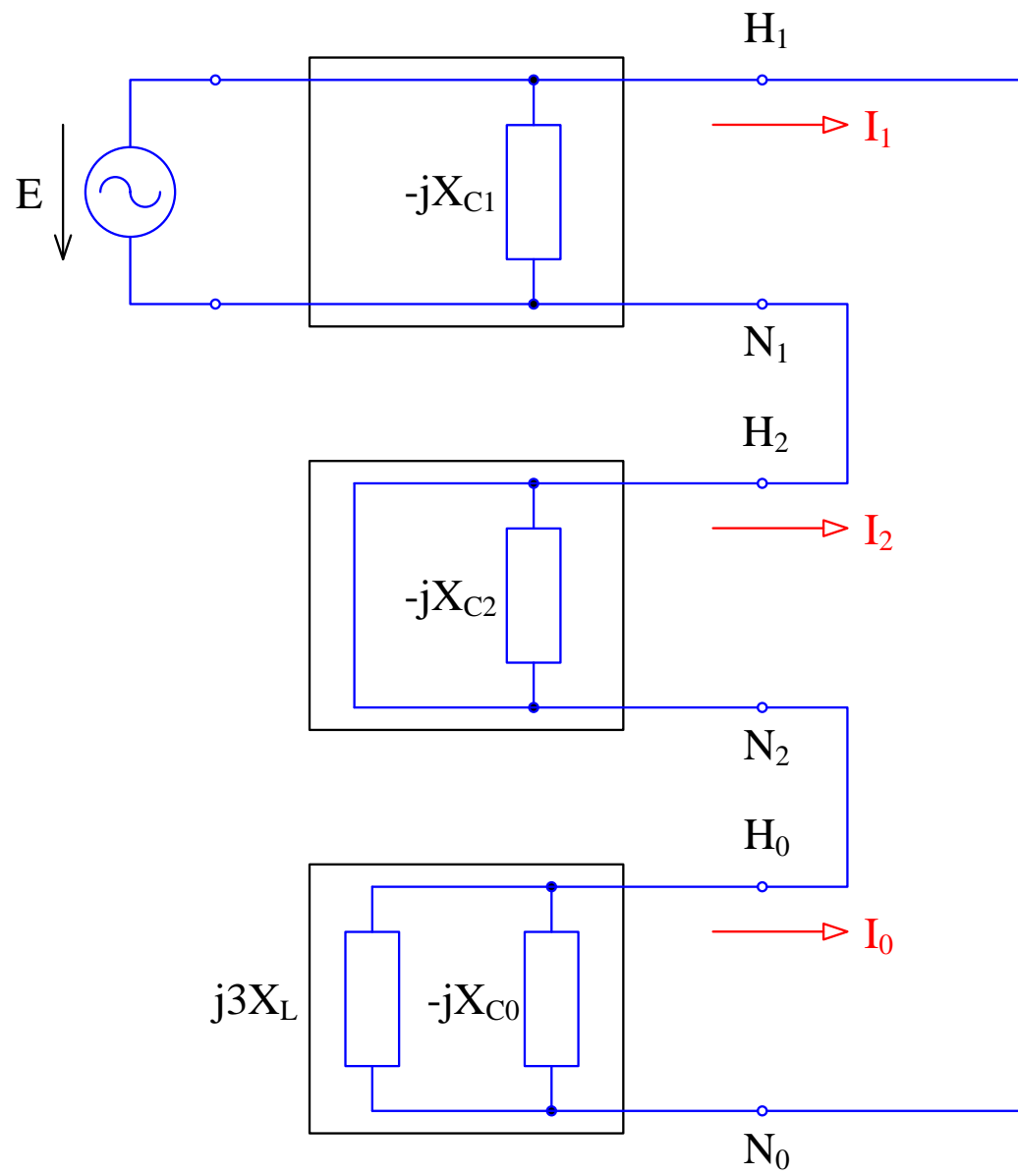

$$X_0 = (j3X_L) // (-jX_C) = j \frac{3X_L X_C}{X_C - 3X_L}$$

$$\hat{I}_1 = \frac{\hat{E}}{j \frac{3X_L X_C}{X_C - 3X_L}} = -j \frac{X_C - 3X_L}{3X_L X_C} \hat{E}$$

$$\hat{I}_p = -\hat{I}_A = -3\hat{I}_1 = j \frac{X_C - 3X_L}{3X_L X_C} \hat{E}$$

$$\hat{I}_p \stackrel{!}{=} 0$$

$$X_{c0} - 3X_L = 0$$

$$X_L = \frac{1}{3} X_{c0} = \frac{1}{3\omega k_0}$$
