

Calculation of voltage in a small electrical network

Electrical DC network is shown (Fig. 1). Calculate the voltage in the nodes 2, 3 and 4. Calculate the node current in the balance node 1. The loads in the nodes, the balance node voltage and resistances of each branch are shown in Fig. 1.

- Calculate it: 1) with node voltage method NVM
2) with gradual simplification method

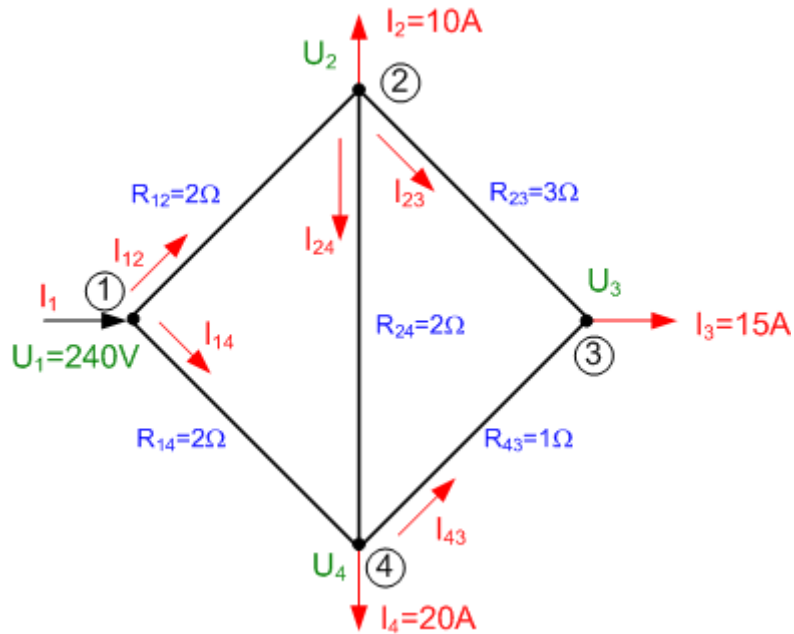


Fig. 1

1. Node voltage method (NVM)

First admittance matrix elements can be calculated based on the knowledge of each element parameters and the system topology. The principle is following:

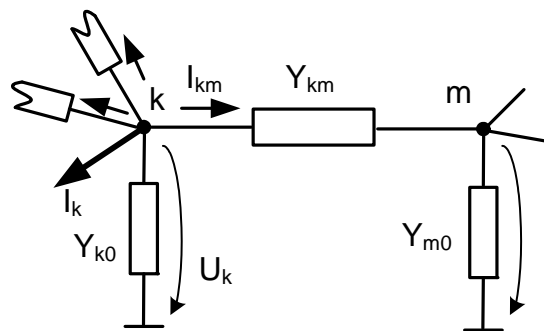


Fig. 2: Model of a system branch

Node current in node k :

$$\hat{I}_k + \sum_{m \neq k} \hat{I}_{km} = 0 \quad (1)$$

$$\hat{I}_k = -\sum_{m \neq k} \hat{I}_{km} = -\sum_{m \neq k} \hat{Y}_{km} \cdot (\hat{U}_k - \hat{U}_m) = -\sum_{m \neq k} \hat{Y}_{km} \cdot \hat{U}_k + \sum_{m \neq k} \hat{Y}_{km} \cdot \hat{U}_m \quad (2)$$

Previous equations are matrix multiplications where $\hat{Y}_{(k,k)}$ is nodal self-admittance (diagonal element) and $\hat{Y}_{(k,m)}$ is between nodes admittance (non-diagonal elements).

$$\hat{I}_k = -\hat{U}_k \cdot \hat{Y}_{(k,k)} + \sum_{m \neq k} \hat{U}_m \cdot \hat{Y}_{(k,m)} \quad (3)$$

where $\hat{Y}_{(k,k)}$, $\hat{Y}_{(k,m)}$ are the system admittance matrix elements.

Diagonal elements are negative and non-diagonal elements are positive.

Because of 4 nodes – admittance matrix type is 4 x 4.

The first element Y_{11} is calculated as the negative sum of all admittances connected to the node 1.

$$Y_{11} = -(Y_{12} + Y_{14}) = -\left(\frac{1}{2} + \frac{1}{2}\right) = -1 \quad (4)$$

The second element Y_{12} is the same as Y_{21} and it is calculated as the sum of admittances between the nodes 1 and 2:

$$Y_{12} = Y_{21} = \frac{1}{2} \quad (5)$$

The next element Y_{13} is the same as Y_{31} and since the nodes 1 and 3 are not connected, the admittance is equal to 0. And further:

$$Y_{22} = -(Y_{12} + Y_{14} + Y_{24}) = -\frac{4}{3} \quad (6)$$

$$Y_{33} = -(Y_{23} + Y_{34}) = -\frac{4}{3} \quad (7)$$

$$Y_{44} = -(Y_{14} + Y_{24} + Y_{34}) = -2 \quad (8)$$

$$Y_{14} = Y_{41} = \frac{1}{2} \quad (9)$$

$$Y_{23} = Y_{32} = \frac{1}{3} \quad (10)$$

$$Y_{24} = Y_{42} = \frac{1}{2} \quad (11)$$

$$Y_{34} = Y_{43} = 1 \quad (12)$$

Admittance matrix Y looks like:

$$[Y] = \begin{pmatrix} Y_{11} & Y_{12} & Y_{13} & Y_{14} \\ Y_{21} & Y_{22} & Y_{23} & Y_{24} \\ Y_{31} & Y_{32} & Y_{33} & Y_{34} \\ Y_{41} & Y_{42} & Y_{43} & Y_{44} \end{pmatrix} = \begin{pmatrix} -1 & \frac{1}{2} & 0 & \frac{1}{2} \\ \frac{1}{2} & -\frac{4}{3} & \frac{1}{3} & \frac{1}{2} \\ 0 & \frac{1}{3} & -\frac{4}{3} & 1 \\ \frac{1}{2} & \frac{1}{2} & 1 & -2 \end{pmatrix} \quad (13)$$

First we do the general derivation for the specified network. The matrix equation is: (current is equal to product of admittance and voltage)

$$[I] = [Y] \cdot [U] \quad (14)$$

To calculate voltage it is necessary to multiply currents by the inverse matrix $[Y]^{-1}$ from the left. This is not possible because $[Y]$ is a singular matrix ($\det Y = 0$). Therefore the matrix and column vectors are divided to sub-matrices for known and unknown quantities:

$$\begin{matrix} [I_1] & [Y_1] & [Y_2] & [U_1] \\ \begin{pmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{pmatrix} & = & \begin{pmatrix} Y_{11} & Y_{12} & Y_{13} & Y_{14} \\ Y_{21} & Y_{22} & Y_{23} & Y_{24} \\ Y_{31} & Y_{32} & Y_{33} & Y_{34} \\ Y_{41} & Y_{42} & Y_{43} & Y_{44} \end{pmatrix} & \cdot & \begin{pmatrix} U_1 \\ U_2 \\ U_3 \\ U_4 \end{pmatrix} \\ [I_{odb}] & [Y_3] & [Y_4] & [U_{odb}] \end{matrix} \quad (15)$$

$$\begin{bmatrix} [I_1] \\ [I_{odb}] \end{bmatrix} = \begin{bmatrix} [Y_1] & [Y_2] \\ [Y_3] & [Y_4] \end{bmatrix} \cdot \begin{bmatrix} [U_1] \\ [U_{odb}] \end{bmatrix} \quad (16)$$

where:

$[I_1]$ unknown current value in the node 1

$[U_1]$ known voltage value in the node 1

$[I_{odb}]$ known load current values in calculated nodes

$[U_{odb}]$ unknown voltage values in calculated nodes

Dimensions of matrixes:

$$[I_1] \in R^{1 \times 1}, [U_1] \in R^{1 \times 1}, [I_{odb}] \in R^{3 \times 1}, [U_{odb}] \in R^{3 \times 1}$$

$$[Y_1] \in R^{1 \times 1}, [Y_2] \in R^{1 \times 3}, [Y_3] \in R^{3 \times 1}, [Y_4] \in R^{3 \times 3}$$

After few modifications and particular multiplications:

$$[\mathbf{I}_1] = [\mathbf{Y}_1] \cdot [\mathbf{U}_1] + [\mathbf{Y}_2] \cdot [\mathbf{U}_{\text{odb}}] \quad (17)$$

$$[\mathbf{I}_{\text{odb}}] = [\mathbf{Y}_3] \cdot [\mathbf{U}_1] + [\mathbf{Y}_4] \cdot [\mathbf{U}_{\text{odb}}] \quad / \cdot [\mathbf{Y}_4]^{-1} \quad (18)$$

$$[\mathbf{Y}_4]^{-1} \cdot [\mathbf{I}_{\text{odb}}] = [\mathbf{Y}_4]^{-1} \cdot [\mathbf{Y}_3] \cdot [\mathbf{U}_1] + [\mathbf{U}_{\text{odb}}] \quad (19)$$

$$[\mathbf{U}_{\text{odb}}] = [\mathbf{Y}_4]^{-1} \cdot [\mathbf{I}_{\text{odb}}] - [\mathbf{Y}_4]^{-1} \cdot [\mathbf{Y}_3] \cdot [\mathbf{U}_1] \quad (20)$$

First there are calculated unknown voltage values from matrix equation (20) and then there is calculated the current value from matrix equation (17)

The final voltages in nodes 2, 3 and 4:

$$[\mathbf{U}_{\text{odb}}] = \begin{bmatrix} U_2 \\ U_3 \\ U_4 \end{bmatrix} = \begin{bmatrix} 199,375 \\ 181,563 \\ 190,625 \end{bmatrix} \text{ (V)} \quad (21)$$

The current I_1 is (based on equation 17):

$$I_1 = -45 \text{ A} \quad (22)$$

A negative value is for delivery (if all node currents have the same orientation). Currents between individual nodes are:

$$I_{12} = (U_1 - U_2) \cdot Y_{12} = 20,31 \text{ A} \quad (23)$$

$$I_{14} = (U_1 - U_4) \cdot Y_{14} = 24,69 \text{ A} \quad (24)$$

$$I_{24} = (U_2 - U_4) \cdot Y_{24} = 4,38 \text{ A} \quad (25)$$

$$I_{23} = (U_2 - U_3) \cdot Y_{23} = 5,94 \text{ A} \quad (26)$$

$$I_{43} = (U_4 - U_3) \cdot Y_{34} = 9,06 \text{ A} \quad (27)$$

2. Gradual simplification method

For further simplifications it is needed to remove Δ between the nodes 1, 2 and 4 (by transfiguration $D \rightarrow Y$):

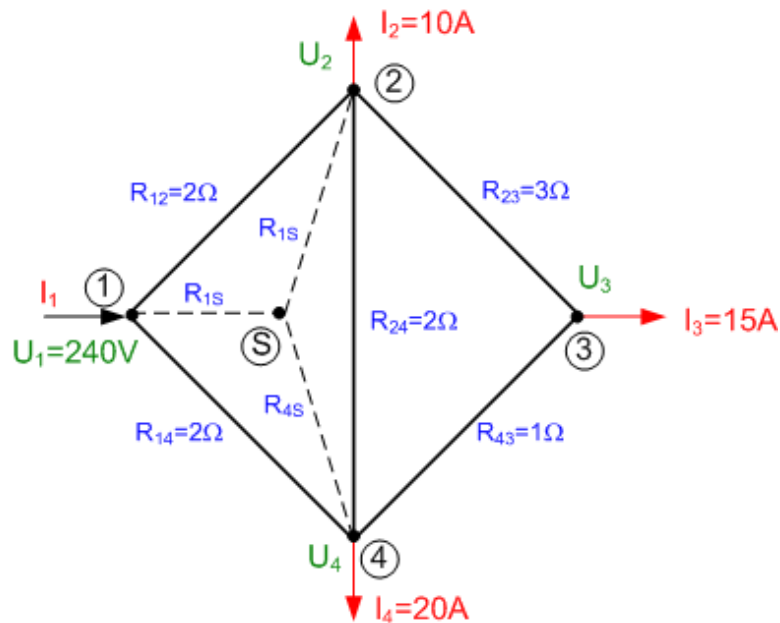


Fig. 3: Power system with transfiguration

The resistances recalculations:

$$R_{1S} = \frac{R_{12} \cdot R_{14}}{R_{12} + R_{14} + R_{24}} = \frac{2}{3} \Omega \quad (28)$$

$$R_{2S} = \frac{R_{12} \cdot R_{24}}{R_{12} + R_{14} + R_{24}} = \frac{2}{3} \Omega \quad (29)$$

$$R_{4S} = \frac{R_{14} \cdot R_{24}}{R_{12} + R_{14} + R_{24}} = \frac{2}{3} \Omega \quad (30)$$

The power network can be redrawn:

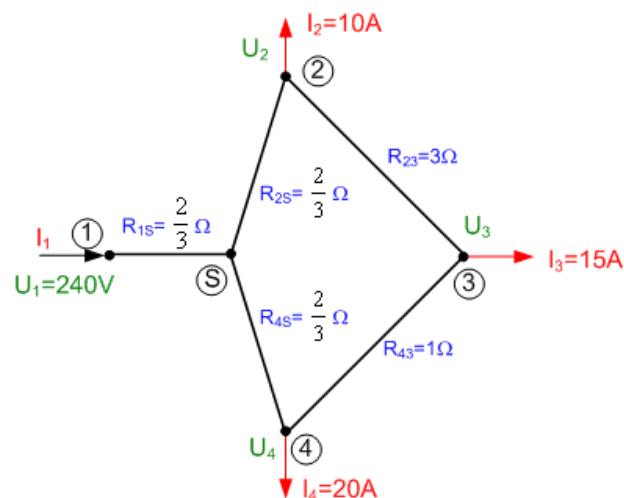


Fig. 4: Redrawn power network

The current reduction from nodes 2 and 4 is made further. This is done by distribution of loads to neighbouring nodes based on current divider principle. Currents I_2 and I_4 are distributed to the nodes S and 3 as follows:

$$I_{23} = \frac{R_{2S}}{R_{2S} + R_{23}} \cdot I_2 = \frac{20}{11} \text{ A} \quad (31)$$

$$I_{2S} = \frac{R_{23}}{R_{2S} + R_{23}} \cdot I_2 = \frac{90}{11} \text{ A} \quad (32)$$

$$I_{43} = \frac{R_{4S}}{R_{4S} + R_{34}} \cdot I_4 = 8 \text{ A} \quad (33)$$

$$I_{4S} = \frac{R_{34}}{R_{4S} + R_{34}} \cdot I_4 = 12 \text{ A} \quad (34)$$

The resulting nodal currents in the nodes S and 3 are:

$$I_S = I_{2S} + I_{4S} = \frac{222}{11} \text{ A} \quad (35)$$

$$I_3 = I_{23} + I_{43} + I_3 = \frac{273}{11} \text{ A} \quad (35)$$

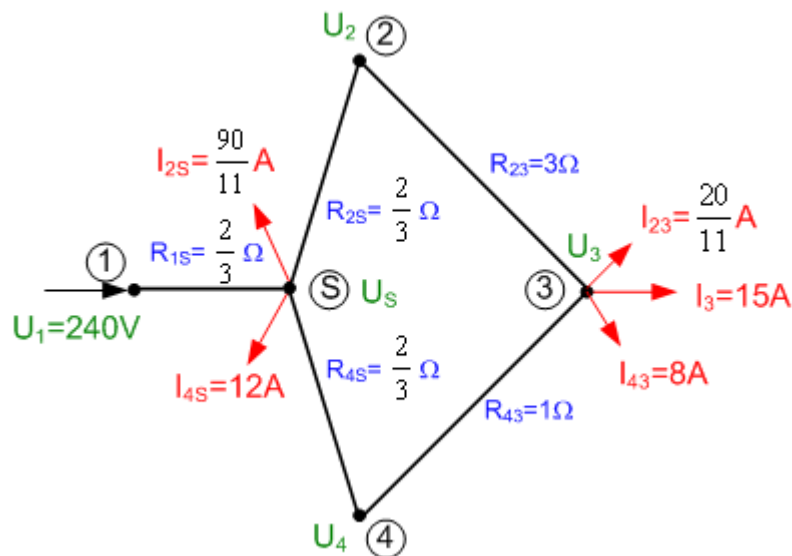


Fig. 5: Network after reducing the loads in the nodes 2 and 4

Simplifying of parts S – 2 – 3 and S – 4 – 3 (this parts are serial summed) and then a parallel combination:

$$R_{S3a} = R_{2S} + R_{23} \quad \text{and} \quad R_{S3b} = R_{4S} + R_{43} \quad (36)$$

$$R_{S3} = \frac{R_{S3a} \cdot R_{S3b}}{R_{S3a} + R_{S3b}} = \frac{55}{48} \Omega \quad (37)$$

Current I_1 :

$$I_1 = I_2 + I_3 + I_4 = 10 + 15 + 20 = 45 \text{ A} \quad (38)$$

The whole network is simplified now as a radial network supplied from one side (Fig.6). The voltages in the nodes S and 3 are:

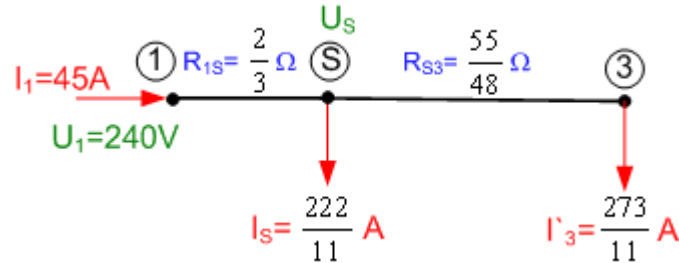


Fig. 6: Radial network supplied from one side

$$U_S = U_1 - I_1 \cdot R_{1S} = 240 - 45 \cdot \frac{2}{3} = 210 \text{ V} \quad (39)$$

$$U_3 = U_S - I_{S3} \cdot R_{S3} = 210 - \frac{273}{11} \cdot \frac{55}{48} = 181,56 \text{ V} \quad (39)$$

The voltages in the nodes 2, 3 and 4 are calculated now. The calculation is made for the same voltages of both feeders U_S (see Fig.4). First we calculate the currents I_{S1} and I_{S2} by means of the current moments and then voltages are calculated based on these currents.

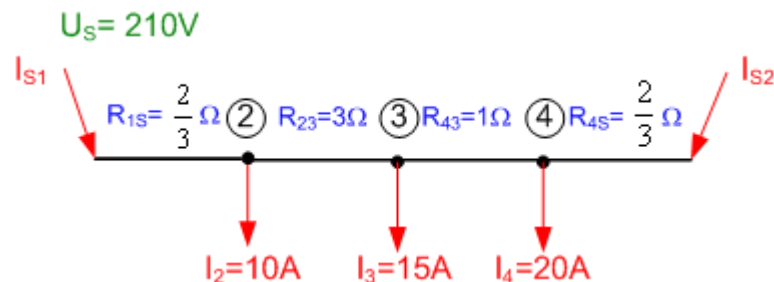


Fig. 7: The power network supplied from both sides

$$I_{S1} = \frac{R_{4S} \cdot I_4 + (R_{4S} + R_{43}) \cdot I_3 + (R_{4S} + R_{43} + R_{23}) \cdot I_2}{R_{4S} + R_{43} + R_{23} + R_{1S}} = 15,94 \text{ A} \quad (40)$$

$$I_{S2} = \frac{R_{1S} \cdot I_2 + (R_{1S} + R_{23}) \cdot I_3 + (R_{1S} + R_{23} + R_{43}) \cdot I_4}{R_{4S} + R_{43} + R_{23} + R_{1S}} = 29,06 \text{ A} \quad (41)$$

$$U_2 = U_S - I_{S1} \cdot R_{1S} = 210 - 15,94 \cdot \frac{2}{3} = 199,37 \text{ V} \quad (42)$$

$$U_4 = U_S - I_{S2} \cdot R_{4S} = 210 - 29,06 \cdot \frac{2}{3} = 190,63 \text{ V} \quad (42)$$