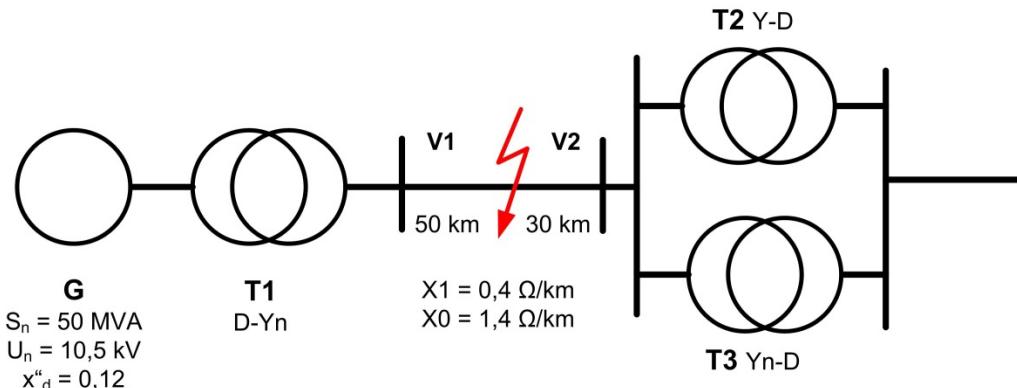


Calculate initial sub-transient short-circuit current in case of single-phase-to-ground, phase-to-phase and three-phase short-circuit.

Parameters T1, T2, T3: 31,5 MVA; 10,5/110 kV;  $u_k = 10,5\%$ ;

T2 has different winding connection than T1 and T3. G voltage is 10,5 kV.



1) base power  $S_v = 31,5 \text{ MVA}$

2) reactances recalculation to  $S_v$  a and voltage in the short-circuit place (110 kV) for sequences **positive (1)**, **negative (2)** and **zero (0)**.

$$\text{G: } X_{1G} = X_d'' \cdot \frac{S_v}{S_{nG1}} = 12 \cdot \frac{31,5}{50} = 7,56\% = X_{2G}$$

$$\text{T1, T2, T3: } X_{1T} = U_k \cdot \frac{S_v}{S_{nT}} = 10,5 \cdot \frac{31,5}{31,5} = 10,5\% = X_{2T}$$

$$X_{0T1} = X_{0T3} = X_{1T} = 10,5\%$$

$$X_{0T2} = \text{Infinity for T2}$$


$$\text{V1: } X_{1V1} = X_1 \cdot l \cdot \frac{S_v}{U_{nV1}^2} \cdot 100 = 0,4 \cdot 50 \cdot \frac{31,5}{110^2} \cdot 100 = 5,2\% = X_{2V1}$$

$$X_{0V1} = X_0 \cdot l \cdot \frac{S_v}{U_{nV1}^2} \cdot 100 = 1,4 \cdot 50 \cdot \frac{31,5}{110^2} \cdot 100 = 18,22\%$$

$$\text{V2: } X_{1V2} = X_1 \cdot l \cdot \frac{S_v}{U_{nV2}^2} \cdot 100 = 0,4 \cdot 30 \cdot \frac{31,5}{110^2} \cdot 100 = 3,13\% = X_{2V1}$$


$$X_{0V2} = X_0 \cdot l \cdot \frac{S_v}{U_{nV2}^2} \cdot 100 = 1,4 \cdot 30 \cdot \frac{31,5}{110^2} \cdot 100 = 10,9\%$$

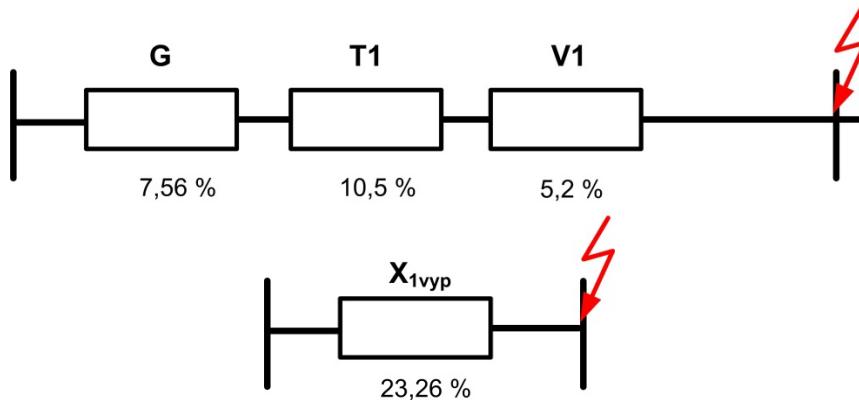3) substitute diagram for **positive** and **negative** sequences and their calculational reactances:



$$X_{1vyp} = X_{2vyp} = 23,26 \%$$

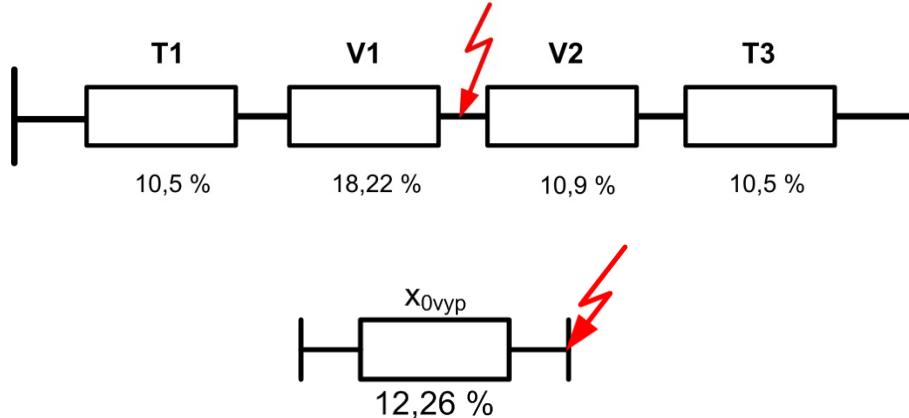4) substitute diagram for **zero** sequence and its calculational reactance:



5) base current

$$I_v = \frac{S_v}{\sqrt{3} \cdot U_v} = \frac{31,5}{\sqrt{3} \cdot 110} = 0,165 \text{ kA}$$

6) three-phase short-circuit

$$I_{k0}^{(3)} = k \cdot \frac{I_v}{X_{1vyp}} = 1,1 \cdot \frac{0,165}{23,26} \cdot 100 = 0,78 \text{ kA}$$

7) phase-to-phase short-circuit

$$I_{k0}^{(2)} = k \cdot \frac{\sqrt{3} \cdot I_v}{X_{1vyp} + X_{2vyp}} = 1,1 \cdot \frac{\sqrt{3} \cdot 0,165}{23,26 + 23,26} \cdot 100 = 0,614 \text{ kA}$$

8) single-phase-to-ground short-circuit

$$I_{k0}^{(1)} = k \cdot \frac{3 \cdot I_v}{X_{1vyp} + X_{2vyp} + X_{0vyp}} = 1,1 \cdot \frac{3 \cdot 0,165}{23,26 + 23,26 + 12,26} \cdot 100 = 0,926 \text{ kA}$$