

Example for solving a non-symmetrical fault – the phase interruption

The generator non-symmetrical load may occur during operation because of failure of a switch pole in the three phase system, interruption of one or two phases, etc.

The negative current sequence is formed in the generator stator when loaded non-symmetrically. It results in the negative magnetic field that causes double frequency currents in the rotor which heat up the rotor.

In this example the phase A is interrupted (see Fig. 1).

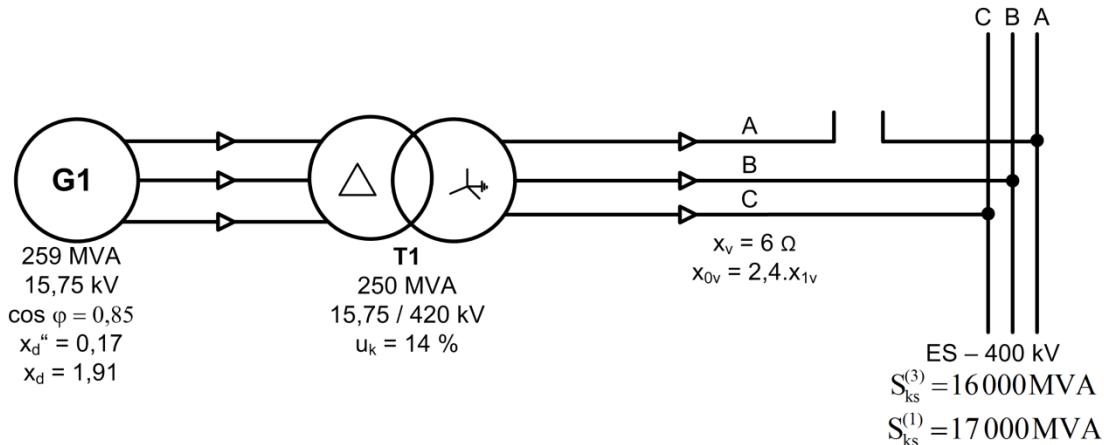


Fig. 1

The base values:

$$S_v = 259 \text{ MVA}; U_v = 15,75 \text{ kV} \rightarrow I_v = 9,494 \text{ kA}$$

Generator:

$$x_{1g} = x_{2g} = x_d'' \cdot \frac{S_v}{S_g} = 0,17 \cdot \frac{259}{259} = 0,17$$

Transformer:

$$x_{1t} = x_{2t} = x_{0t} = u_k \cdot \frac{S_v}{S_t} = 0,14 \cdot \frac{259}{250} = 0,145$$

Network:

$$x_{1s} = x_{2s} = \frac{U_s^2}{S_{ks}} \cdot \frac{S_v}{U_v^2} \cdot p_T^2 = \frac{400^2}{16000} \cdot \frac{259}{15,75^2} \cdot \left(\frac{15,75}{420}\right)^2 = 0,0146$$

$$\frac{S_{ks}^{(3)}}{S_{ks}^{(1)}} = \frac{x_{1s} + x_{2s} + x_{0s}}{3 \cdot x_{1s}} \rightarrow x_{0s}$$

$$x_{0s} = 0,0121$$

Power line:

$$x_{1v} = x_{2v} = x_v \cdot \frac{S_v}{U_v^2} \cdot p_T^2 = 6 \cdot \frac{259}{15,75^2} \cdot \left(\frac{15,75}{420} \right)^2 = 0,0088$$

$$x_{0v} = 2,4 \cdot x_{1v} = 0,021$$


The generator voltage:

$$e_g'' = 1,099 \cdot e^{j \cdot 58,5714^\circ}$$

The network voltage:

$$e_s'' = 0,9303 \cdot e^{j \cdot 43,2159^\circ}$$

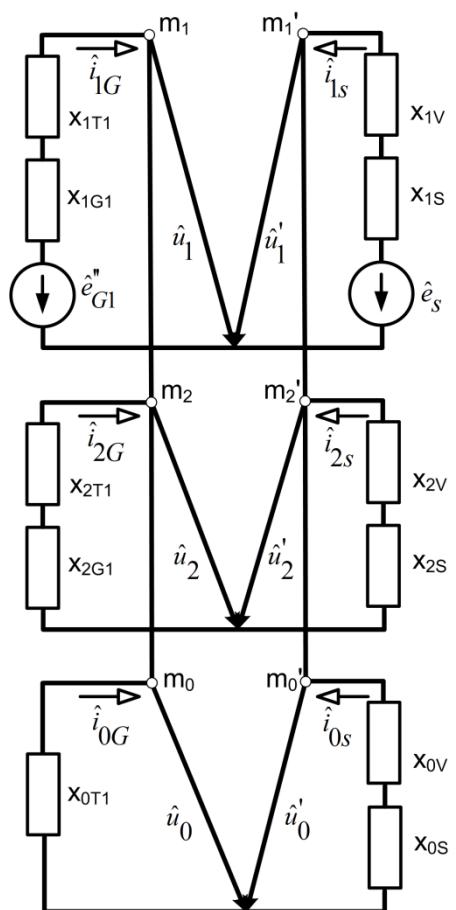The diagram of sequence systems connection is shown in Fig. 2. All sequence systems are connected in parallel in the points of interruption.



The Fig. 2 is simplified and redrawn in Fig. 3. The negative and zero sequences are replaced with reactances x_2 and x_0 , finally with the reactance $x_{20\Sigma} = x_2 // x_0$.

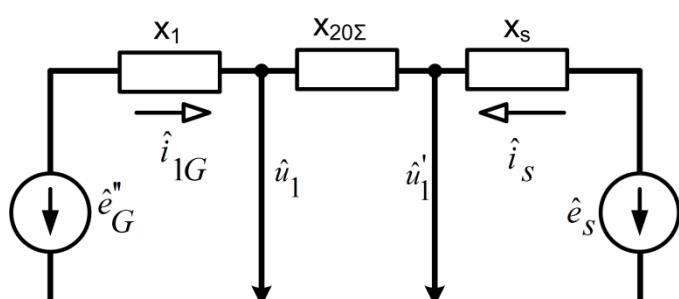


Fig. 3

Fig. 2

After interruption of one phase:

$$\hat{u}_1 - \hat{u}'_1 = \hat{u}_2 - \hat{u}'_2 = \hat{u}_0 - \hat{u}'_0$$

$$\hat{i}_{1g} = -\hat{i}_{1s} \quad \hat{i}_{1g} + \hat{i}_{2g} + \hat{i}_{0g} = 0$$

$$\hat{i}_{2g} = -\hat{i}_{2s} \quad \hat{i}_{1s} + \hat{i}_{2s} + \hat{i}_{0s} = 0$$

$$\hat{i}_{0g} = -\hat{i}_{0s}$$

Further:

$$x_1 = x_{1g} + x_{1t} = 0,315$$

$$x_s = x_{1s} + x_{1v} = 0,0235$$

$$x_{2\Sigma} = x_{2t} + x_{2g} + x_{2v} + x_{2s} = 0,3385$$

$$x_{0\Sigma} = x_{0t} + x_{0s} + x_{0v} = 0,1783$$

$$x_{20\Sigma} = x_{2\Sigma} / x_{0\Sigma} = 0,117$$

$$\hat{i}_{1g} = -\hat{i}_{1s} = \frac{\hat{e}_g'' - \hat{e}_s}{j \cdot (x_1 + x_{20\Sigma} + x_s)} = 0,6996 \cdot e^{j \cdot 19,2331^\circ}$$

$$\hat{u}_1 = \hat{e}_g'' - j \cdot x_1 \cdot \hat{i}_{1g} = 0,9743 \cdot e^{j \cdot 48,4957^\circ}$$

$$\hat{u}'_1 = \hat{e}_s - j \cdot x_s \cdot \hat{i}_{1s} = \hat{e}_s + j \cdot x_s \cdot \hat{i}_{1g} = 0,9371 \cdot e^{j \cdot 44,134^\circ}$$

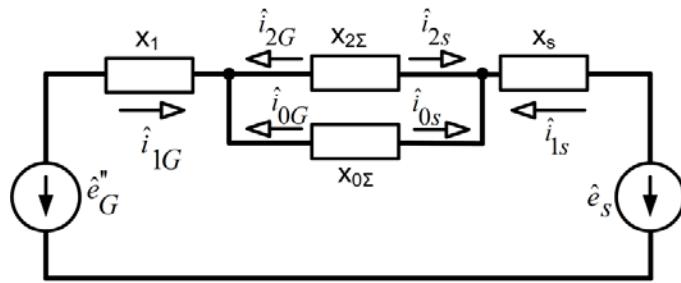


Fig. 4

Further (as shown in fig. 4):

$$\hat{i}_{2g} x_{2\Sigma} = \hat{i}_{0g} \cdot x_{02\Sigma} = -\hat{i}_{1g} \cdot \frac{x_{2\Sigma} \cdot x_{0\Sigma}}{x_{2\Sigma} + x_{0\Sigma}}$$

$$\hat{i}_{2g} = -\hat{i}_{1g} \cdot \frac{x_{0\Sigma}}{x_{2\Sigma} + x_{0\Sigma}} = 0,2413 \cdot e^{-j \cdot 160,767^\circ} = -\hat{i}_{2s}$$

$$\hat{i}_{0g} = -\hat{i}_{1g} \cdot \frac{x_{2\Sigma}}{x_{2\Sigma} + x_{0\Sigma}} = 0,4583 \cdot e^{-j \cdot 160,767^\circ} = -\hat{i}_{0s}$$

Further:

$$\hat{u}_2 = -\hat{i}_{2g} \cdot j \cdot (x_{2t} + x_{2g}) = 0,0761 \cdot e^{j \cdot 109,233^\circ}$$

$$\hat{u}'_2 = -\hat{i}_{2s} \cdot j \cdot (x_{2s} + x_{2v}) = 0,0057 \cdot e^{-j \cdot 70,7669^\circ}$$

$$\hat{u}_0 = -\hat{i}_{0g} \cdot j \cdot x_{0t} = 0,0665 \cdot e^{j \cdot 109,233^\circ}$$

$$\hat{u}'_0 = -\hat{i}_{0s} \cdot j \cdot (x_{0s} + x_{0v}) = 0,0153 \cdot e^{-j \cdot 70,7669^\circ}$$

The voltage in the fault point on the HV network side:

$$\begin{bmatrix} \hat{u}_A \\ \hat{u}_B \\ \hat{u}_C \end{bmatrix}_{ES} = [T] \begin{bmatrix} \hat{u}'_1 \\ \hat{u}'_2 \\ \hat{u}'_0 \end{bmatrix} = \begin{bmatrix} 0,9285 \cdot e^{j \cdot 42,964^\circ} \\ 0,9490 \cdot e^{-j \cdot 75,504^\circ} \\ 0,9341 \cdot e^{j \cdot 164,929^\circ} \end{bmatrix} [p.u.]$$

Where T^{-1} is transformation matrix between the sequence system and phase system:

$$[T] = \begin{bmatrix} 1 & 1 & 1 \\ a^2 & a & 1 \\ a & a^2 & 1 \end{bmatrix}, a = e^{j \frac{2\pi}{3}}$$

The voltage on the transformer side:

$$\begin{bmatrix} \hat{u}_A \\ \hat{u}_B \\ \hat{u}_C \end{bmatrix}_{T1} = [T] \begin{bmatrix} \hat{u}_1 \\ \hat{u}_2 \\ \hat{u}_0 \end{bmatrix} = \begin{bmatrix} 1,0514 \cdot e^{j \cdot 55,286^\circ} \\ 0,9490 \cdot e^{-j \cdot 75,504^\circ} \\ 0,9341 \cdot e^{j \cdot 164,929^\circ} \end{bmatrix} [p.u.]$$

Note: The voltage of non-affected phases must be equal.

The currents flowing from the transformer to HV network:

$$\begin{bmatrix} \hat{i}_A \\ \hat{i}_B \\ \hat{i}_C \end{bmatrix} = [T] \begin{bmatrix} \hat{i}_{1g} \\ \hat{i}_{2g} \\ \hat{i}_{0g} \end{bmatrix} = \begin{bmatrix} 0 \\ 1,066 \cdot e^{-j \cdot 110,917^\circ} \\ 1,066 \cdot e^{j \cdot 149,383^\circ} \end{bmatrix} [p.u.]$$

The generator currents:

The zero sequence is closed in the triangle (delta) winding, the positive sequence is turned by the angle -30° , the negative sequence is turned by the angle $+30^\circ$.

$$\hat{i}_{1g\Delta} = 0,6996 \cdot e^{j \cdot (19,2331 - 30)^\circ} = 0,6996 \cdot e^{-j \cdot 10,7669^\circ}$$

$$\hat{i}_{2g\Delta} = 0,2413 \cdot e^{j \cdot (160,767 + 30)^\circ} = 0,2413 \cdot e^{-j \cdot 130,767^\circ}$$

$$\hat{i}_{0g\Delta} = 0$$

$$\begin{bmatrix} \hat{i}_A \\ \hat{i}_B \\ \hat{i}_C \end{bmatrix}_G = [T] \begin{bmatrix} \hat{i}_{1g\Delta} \\ \hat{i}_{2g\Delta} \\ \hat{i}_{0g\Delta} \end{bmatrix} = \begin{bmatrix} 0,6155 \cdot e^{-j \cdot 30,617^\circ} \\ 0,6155 \cdot e^{-j \cdot 110,917^\circ} \\ 0,9409 \cdot e^{j \cdot 109,233^\circ} \end{bmatrix} [p.u.]$$

$$\begin{bmatrix} \hat{i}_A \\ \hat{i}_B \\ \hat{i}_C \end{bmatrix} = \begin{bmatrix} 5,844 \cdot e^{-j \cdot 30,617^\circ} \\ 5,844 \cdot e^{-j \cdot 110,917^\circ} \\ 8,933 \cdot e^{j \cdot 109,233^\circ} \end{bmatrix} [kA]$$

The ground current: $\hat{i}_z = 3 \cdot \hat{i}_{0g} = 1,375 \cdot e^{j \cdot 19,227^\circ}$ [p.u.]

$$\hat{i}_z = 0,489 \cdot e^{j \cdot 19,2^\circ}$$
 [kA]

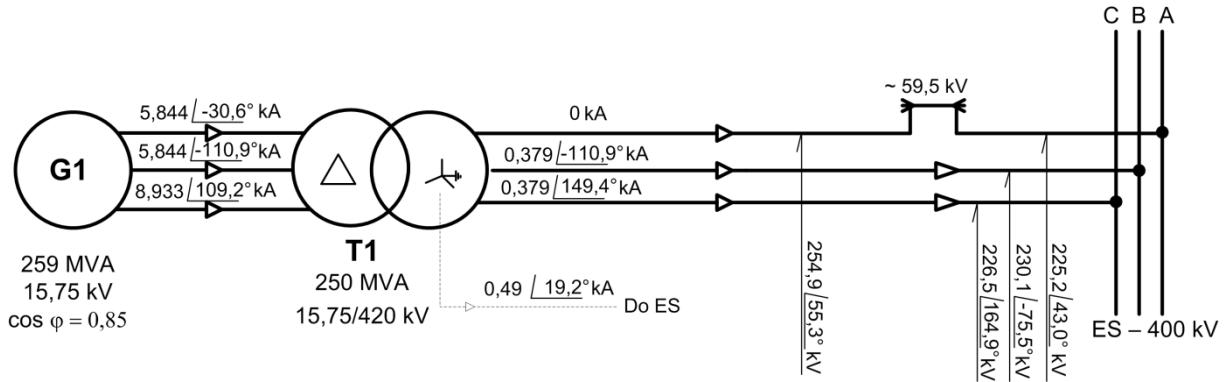


Fig. 5

The calculation shows that interruption of one phase causes non-symmetry – it can be calculated as the ratio of the negative and positive sequence:

$$\frac{i_{2g\Delta}}{i_{1g\Delta}} = \frac{0,2413}{0,6996} \cong 34,5\%$$

The currents and voltages are shown in Fig. 5. These values are for the beginning of fault. For the steady state (the next calculation with subscript u) we assume: the calculation are for the same generator exciting current as before the phase interruption – so the generator can be modelled as the internal voltage behind the synchronous reactance:

$$\hat{u}_f = 2,581 \cdot e^{j \cdot 90^\circ} \text{ behind the synchronous reactance } x_d = 1,91.$$

The transformer negative reactance is unchanged. The generator negative reactance equals to the subtransient reactance for the steady state.

Substitute generator positive reactance for the steady state is:

$$x_{1gu} = x_d \cdot \frac{S_v}{S_g} = 1,91$$

Assumed that internal network voltage is:

$$\hat{u}_s = 0,9303 \cdot e^{j \cdot 43,2159^\circ}$$

$$x_{1u} = x_{1gu} + x_{1t} = 1,91 + 0,145 = 2,055$$

According to Fig. 1 or Fig. 2, analogically as above:

$$\hat{i}_{1gu} = -\hat{i}_{1su} = \frac{\hat{u}_f - \hat{u}_s}{j \cdot (x_{1u} + x_{20\Sigma} + x_s)} = 0,938 \cdot e^{j \cdot 19,227^\circ}, \text{ where}$$

$$x_{1u} + x_{20\Sigma} + x_s = 2,055 + 0,117 + 0,0235 = 2,195$$

$$\hat{i}_{2gu} = -\hat{i}_{1gu} \cdot \frac{x_{0\Sigma}}{x_{2\Sigma} + x_{0\Sigma}} = -\hat{i}_{2su} = 0,324 \cdot e^{-j \cdot 160,773^\circ}$$

$$\hat{i}_{0gu} = -\hat{i}_{1gu} \cdot \frac{x_{2\Sigma}}{x_{2\Sigma} + x_{0\Sigma}} = -\hat{i}_{0su} = 0,614 \cdot e^{-j \cdot 160,773^\circ}$$

$$\hat{i}_{1gu} = 0,938 \cdot e^{j \cdot 19,227^\circ} = -\hat{i}_{1su}$$

$$\hat{i}_{2gu} = 0,324 \cdot e^{-j \cdot 160,773^\circ} = -\hat{i}_{2su} \quad [p.u.]$$

$$\hat{i}_{0gu} = 0,614 \cdot e^{-j \cdot 160,773^\circ} = -\hat{i}_{0su}$$

The phase currents of transformer T on the HV side:

$$\begin{bmatrix} \hat{i}_A \\ \hat{i}_B \\ \hat{i}_C \end{bmatrix}_{T_u} = \begin{bmatrix} 0 \\ 1,429 \cdot e^{-j \cdot 110,923^\circ} \\ 1,429 \cdot e^{j \cdot 149,377^\circ} \end{bmatrix} \quad [p.u.]$$

$$\begin{bmatrix} \hat{i}_A \\ \hat{i}_B \\ \hat{i}_C \end{bmatrix}_{T_u} = \begin{bmatrix} 0 \\ 0,509 \cdot e^{-j \cdot 110,923^\circ} \\ 0,509 \cdot e^{j \cdot 149,377^\circ} \end{bmatrix} \quad [kA]$$

The ground current: $\hat{i}_z = 3 \cdot \hat{i}_{0gu} = 1,843 \cdot e^{j \cdot 19,227^\circ} [p.u.]$

$$\hat{I}_{zu} = 0,656 \cdot e^{-j \cdot 19,227^\circ} [kA]$$

The generator current:

$$\hat{i}_{1gu\Delta} = 0,938 \cdot e^{-j \cdot 10,773^\circ}$$

$$\hat{i}_{2gu\Delta} = 0,324 \cdot e^{-j \cdot 130,773^\circ}$$

$$\hat{i}_{ogu\Delta} = 0 \quad \text{because it is closed in the transformer } \Delta \text{ winding}$$

$$\begin{bmatrix} \hat{i}_A \\ \hat{i}_B \\ \hat{i}_C \end{bmatrix}_{G_u} = \begin{bmatrix} 0,825 \cdot e^{-j \cdot 30,623^\circ} \\ 0,825 \cdot e^{-j \cdot 110,923^\circ} \\ 1,261 \cdot e^{j \cdot 109,227^\circ} \end{bmatrix} \quad [p.u.]$$

$$\begin{bmatrix} \hat{I}_A \\ \hat{I}_B \\ \hat{I}_C \end{bmatrix}_{G_u} = \begin{bmatrix} 7,834 \cdot e^{-j \cdot 30,623^\circ} \\ 7,834 \cdot e^{-j \cdot 110,923^\circ} \\ 11,975 \cdot e^{j \cdot 109,227^\circ} \end{bmatrix} \quad [kA]$$