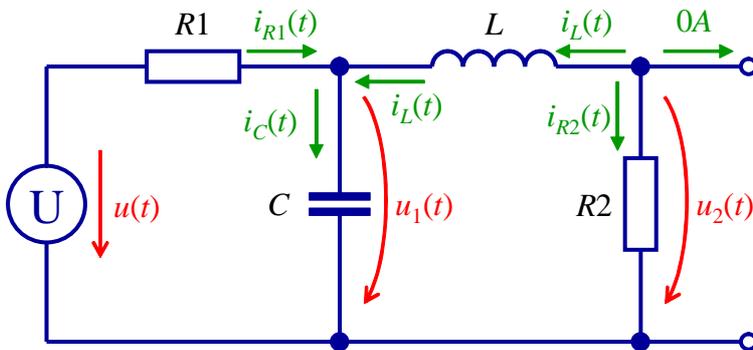



Metoda uzlových napětí - ukázka

Zadání



```
In[29]:= ClearAll["Global`*"];
```
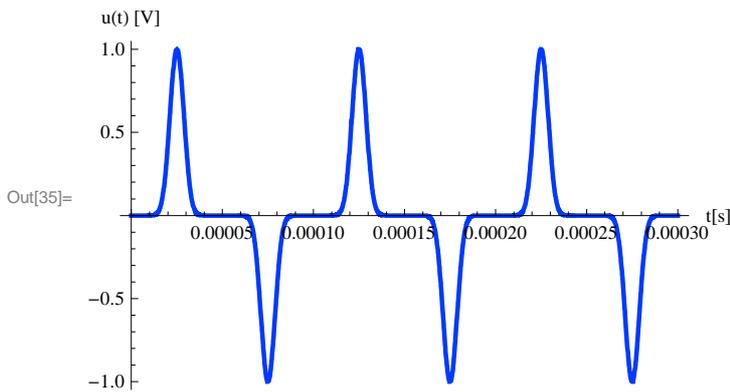
```
In[30]:= f0 = 104;  
vstup = Sin[2 * Pi * f0 * t]17;  
tau = 1 / f0;  
tmax = 3 tau;  
pl[co_, popis_, barva_] := Plot[Evaluate[co], {t, 0, tmax},  
  AxesOrigin -> {0, 0}, PlotRange -> {Automatic, {-1.05, 1.05}}, PlotStyle ->  
  Evaluate[{Hue[#], Thickness[0.008]} & /@ barva], AxesLabel -> {"t[s]", popis}];  
p11 = pl[vstup, "u(t) [V]", {0.63}]
```



```
In[36]:= dos = {R1 -> 1 kΩ, c -> 1 μF, R2 -> 10 kΩ, L -> 50 mH, mH -> 10-3, μF -> 10-6, kΩ -> 103, u[t] -> vstup};
```

Popis obvodu

```
In[37]:= uzel1 = {  $\frac{u[t] - u1[t]}{R1} + iL[t] == c * u1'[t], u1[0] == 0, u2[t] - u1[t] == L * iL'[t], iL[0] == 0$  };
uzel2 = {  $iL[t] + \frac{u2[t]}{R2} == 0$  };
vse = Union[uzel1, uzel2] //. dos;
```

Řešení

```
In[40]:= nezname = {u1[t], u2[t], iL[t]};
res = NDSolve[vse, nezname, {t, 0, tmax}][[1]];
```

Zobrazení výsledků

```
In[42]:= pl[{100 * u2[t] /. res, vstup}, "u(t) , 100u2(t) [V]", {0, 0.63}]
```

